

Constructive Computer Architecture

Combinational circuits

Arvind

Computer Science & Artificial Intelligence Lab.
Massachusetts Institute of Technology

Content


- ◆ Design of a combinational ALU starting with primitive gates And, Or and Not
- ◆ Combinational circuits as acyclic wiring diagrams of primitive gates
- ◆ Introduction to BSV
 - Intro to types – enum, typedefs, numeric types, int#(32) vs integer, bool vs bit#(1), vectors
 - Simple operations: concatenation, conditionals, loops
 - Functions
 - Static elaboration and a structural interpretation of the textual code

Combinational circuits

Combinational circuits are acyclic interconnections of gates

- ◆ And, Or, Not
- ◆ Nand, Nor, Xor
- ◆ ...

Arithmetic-Logic Unit (ALU)

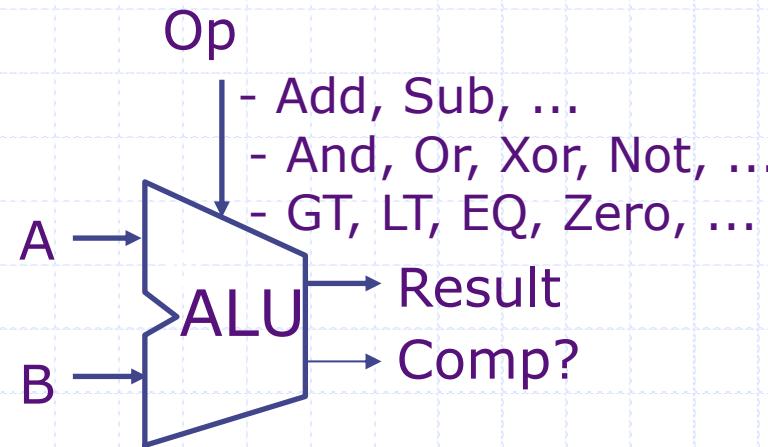


ALU performs all the arithmetic
and logical functions

Each individual function can be described
as a combinational circuit

Half Adder

| A | B | S | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

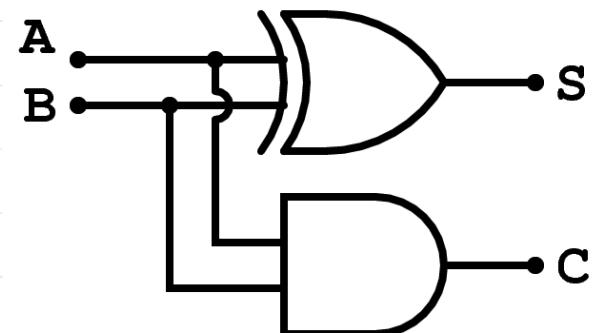

Boolean equations

$$S = (\sim a \cdot b) + (a \cdot \sim b)$$


$$C = a \cdot b$$

“Optimized”

$$S = a \oplus b$$

Full Adder

| A | B | C _{in} | S | C _{out} |
|---|---|-----------------|---|------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

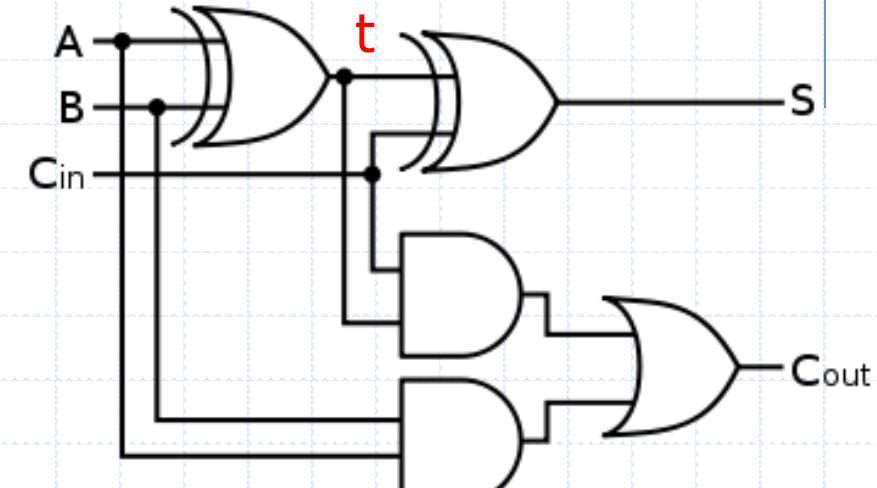

Boolean equations

$$S = (\sim a \cdot \sim b \cdot c_{in}) + (\sim a \cdot b \cdot \sim c_{in}) + (a \cdot \sim b \cdot \sim c_{in}) + (a \cdot b \cdot c_{in})$$

$$C_{out} = (\sim a \cdot b \cdot c_{in}) + (a \cdot \sim b \cdot c_{in}) + (a \cdot b \cdot \sim c_{in}) + (a \cdot b \cdot c_{in})$$

“Optimized”

$$t = a \oplus b$$

$$S = t \oplus c_{in}$$


$$C_{out} = a \cdot b + c_{in} \cdot t$$

Full Adder: A one-bit adder

```
function fa(a, b, c_in);  
    t = (a ^ b);  
    s = t ^ c_in;  
    c_out = (a & b) | (c_in & t);  
    return {c_out,s};  
endfunction
```

Structural code –
only specifies
interconnection
between boxes

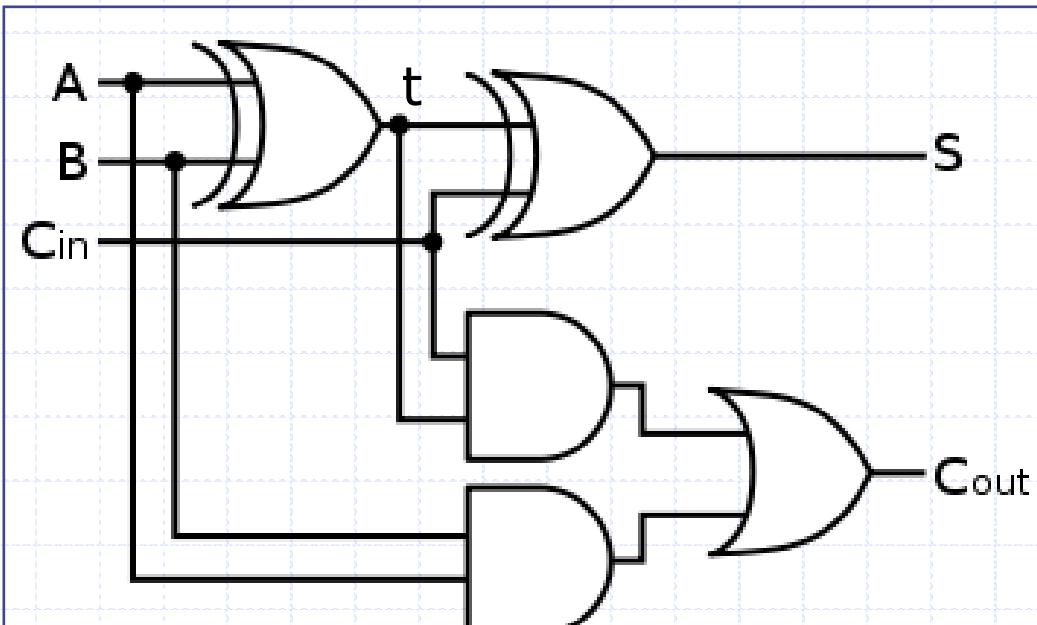Not quite correct –
needs type annotations




Full Adder: A one-bit adder *corrected*

```
function Bit#(2) fa(Bit#(1) a, Bit#(1) b,  
                      Bit#(1) c_in);  
    Bit#(1) t = a ^ b;  
    Bit#(1) s = t ^ c_in;  
    Bit#(1) c_out = (a & b) | (c_in & t);  
    return {c_out,s};  
endfunction
```

“Bit#(1) a” type declaration says that a is one bit wide

{c_out, s} represents bit concatenation

How big is {c_out, s}?
2 bits

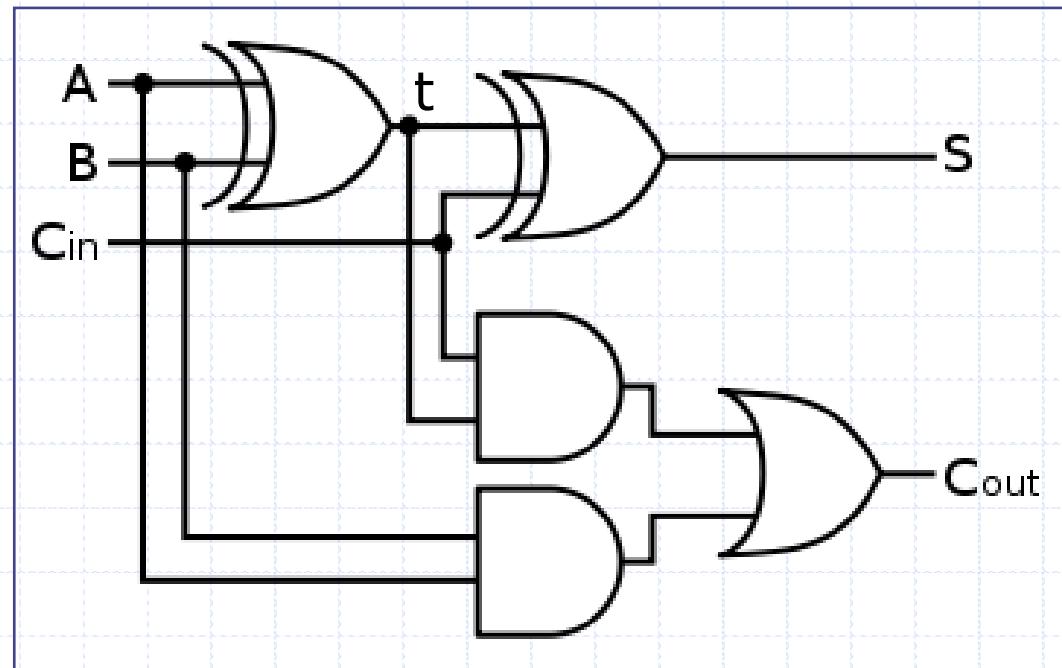

Types

- ◆ A type is a grouping of values:
 - Integer: 1, 2, 3, ...
 - Bool: True, False
 - Bit: 0, 1
 - A pair of Integers: Tuple2#(Integer, Integer)
 - A function `fname` from Integers to Integers:
`function` Integer `fname` (Integer arg)
- ◆ Every expression in a BSV program has a type; sometimes it is specified explicitly and sometimes it is deduced by the compiler
- ◆ Thus we say an expression has a type or belongs to a type

The type of each expression is unique

Parameterized types:

- ◆ A type declaration itself can be parameterized by other types
- ◆ Parameters are indicated by using the syntax '#'
 - For example Bit#(n) represents n bits and can be instantiated by specifying a value of n
Bit#(1), Bit#(32), Bit#(8), ...

Type synonyms

```
typedef bit [7:0] Byte;
```

The same

```
typedef Bit#(8) Byte;
```

```
typedef Bit#(32) Word;
```

```
typedef Tuple2#(a,a) Pair#(type a);
```

```
typedef Int#(n) MyInt#(type n);
```

The same

```
typedef Int#(n) MyInt#(numeric type n);
```


Type declaration versus deduction

- ◆ The programmer writes down types of some expressions in a program and the compiler deduces the types of the rest of expressions
- ◆ If the type deduction cannot be performed or the type declarations are inconsistent then the compiler complains

```
function Bit#(2) fa(Bit#(1) a, Bit#(1) b,  
                      Bit#(1) c_in);  
    Bit#(1) t = a ^ b;  
    Bit#(1) s = t ^ c_in;  
    Bit#(2) c_out = (a & b) | (c_in & t);  
    return {c_out,s};  
endfunction  
                                         type error
```

Type checking prevents lots of silly mistakes

2-bit Ripple-Carry Adder

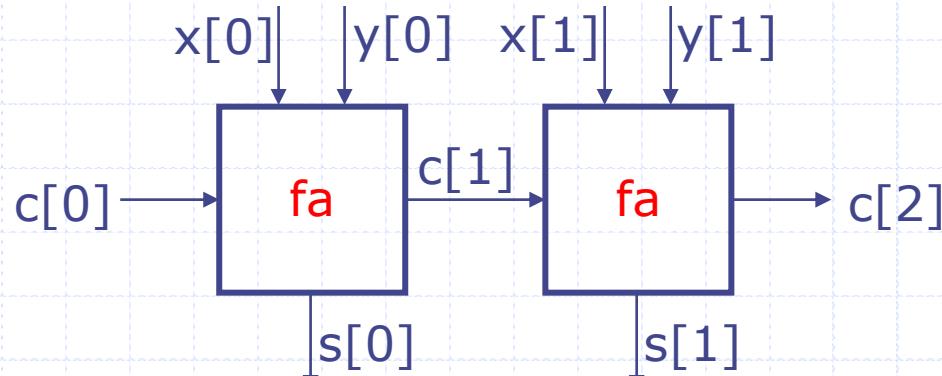

`fa` can be used as a black-box as long as we understand its type signature

```
function Bit#(3) add(Bit#(2) x, Bit#(2) y,  
                      Bit#(1) c0);  
  
    Bit#(2) s = 0;           Bit#(3) c=0; c[0] = c0;  
    let cs0 = fa(x[0], y[0], c[0]);  
    c[1] = cs0[1]; s[0] = cs0[0];  
    let cs1 = fa(x[1], y[1], c[1]);  
    c[2] = cs1[1]; s[1] = cs1[0];  
  
    return {c[2],s};  
endfunction
```

The “let” syntax avoids having to write down types explicitly

“let” syntax

- ◆ The “let” syntax: avoids having to write down types explicitly

- `let cs0 = fa(x[0], y[0], c[0]);`



- `Bits#(2) cs0 = fa(x[0], y[0], c[0]);`

The same

Selecting a wire: $x[i]$



assume x is 4 bits wide

- Constant Selector: e.g., $x[2]$

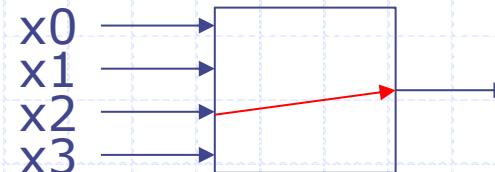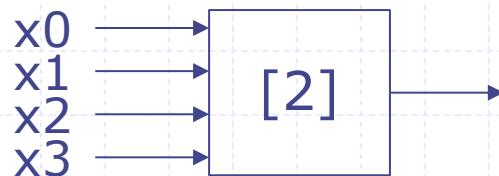


no hardware;
 $x[2]$ is just
the name of
a wire

- Dynamic selector: $x[i]$

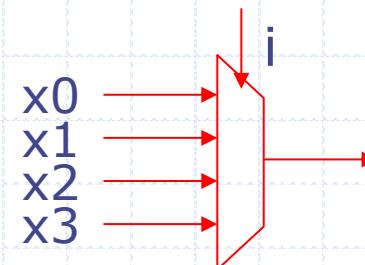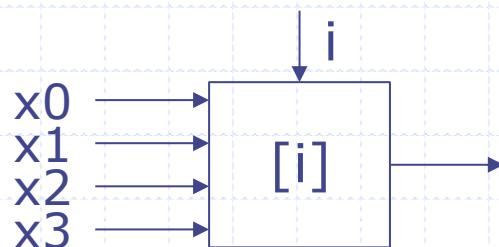


4-way mux

A 2-way multiplexer

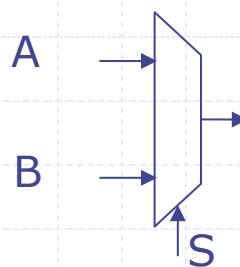

$(s==0) ? A : B$

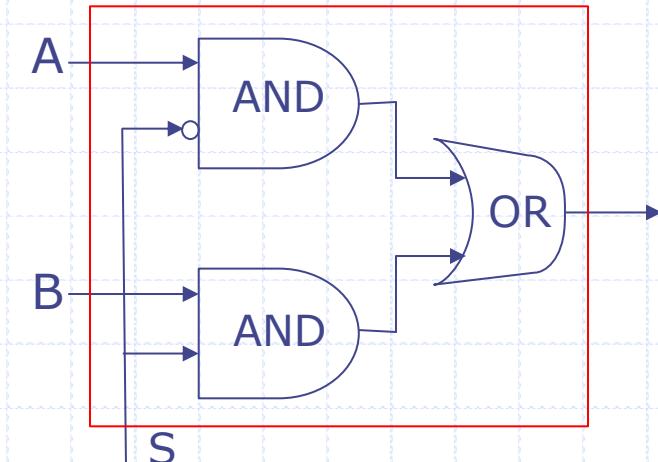
Conditional expressions are also synthesized
using muxes



Gate-level implementation

A 4-way multiplexer
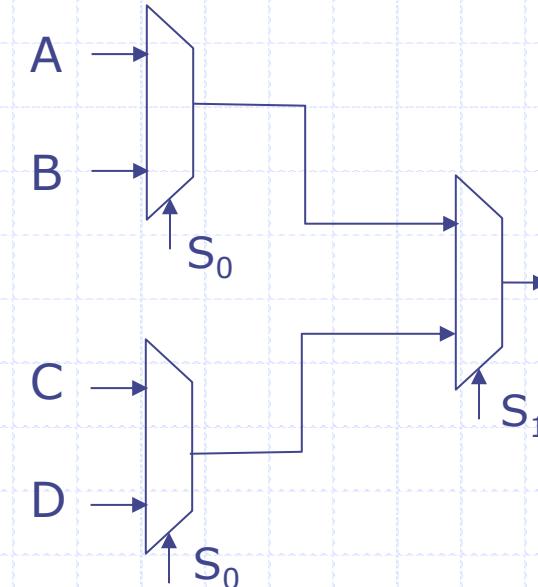
```
case {s1,s0} matches
  0: A;
  1: B;
  2: C;
  3: D;
endcase
```




An w-bit Ripple-Carry Adder

```
function Bit#(w+1) addN(Bit#(w) x, Bit#(w) y,  
                         Bit#(1) c0);  
    Bit#(w) s; Bit#(w+1) c=0; c[0] = c0;  
    for(Integer i=0; i<w; i=i+1)  
    begin  
        let cs = fa(x[i],y[i],c[i]);  
        c[i+1] = cs[1]; s[i] = cs[0];  
    end  
    return {c[w],s};  
endfunction
```

Not quite correct

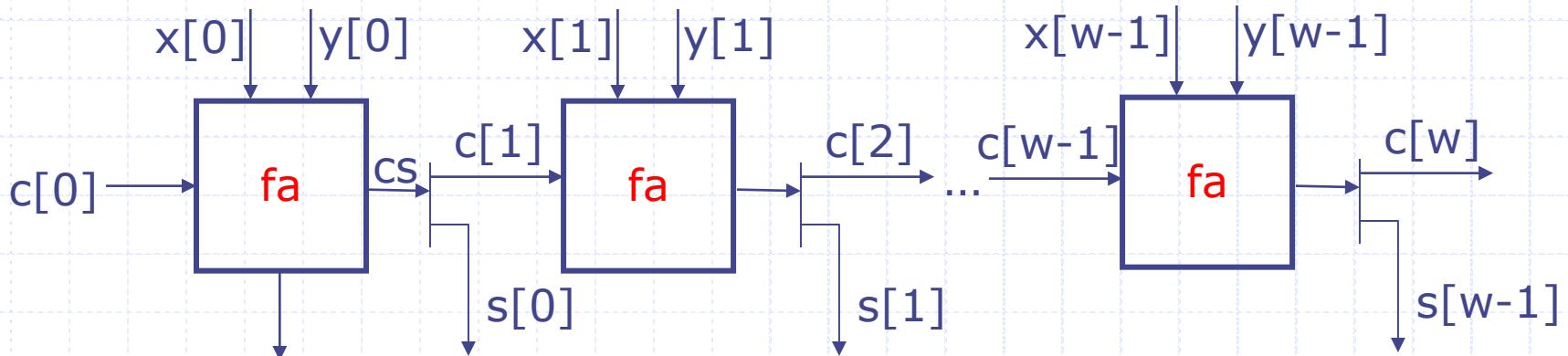Unfold the loop to get
the wiring diagram



Instantiating the parametric Adder

```
function Bit#(w+1) addN(Bit#(w) x, Bit#(w) y,  
Bit#(1) c0);
```

Define add32, add3 ... using addN

// concrete instances of addN!

```
function Bit#(33) add32(Bit#(32) x, Bit#(32) y,  
Bit#(1) c0) = addN(x,y,c0);
```

```
function Bit#(4) add3(Bit#(3) x, Bit#(3) y,  
Bit#(1) c0) = addN(x,y,c0);
```

valueOf (w) versus w

- ◆ Each expression has a type and a value and these come from two entirely disjoint worlds
- ◆ w in $\text{Bit\#}(w)$ resides in the types world
- ◆ Sometimes we need to use values from the types world into actual computation. The function `valueOf` allows us to do that
 - Thus
 - $i < w$ is not type correct
 - $i < \text{valueOf}(w)$ is type correct

TAdd#(w, 1) versus w+1

- ◆ Sometimes we need to perform operations in the types world that are very similar to the operations in the value world
 - Examples: Add, Mul, Log
- ◆ We define a few special operators in the types world for such operations
 - Examples: TAdd#(m, n), TMul#(m, n), ...

A w-bit Ripple-Carry Adder

corrected

```
function Bit#(TAdd#(w, 1)) addN(Bit#(w) x, Bit#(w) y,  
Bit#(1) c0);  
Bit#(w) s; Bit#(TAdd#(w, 1)) c; c[0] = c0;  
let valw = valueOf(w);  
for(Integer i=0; i<valw; i=i+1)  
begin  
let cs = fa(x[i], y[i], c[i]);  
c[i+1] = cs[1]; s[i] = cs[0];  
end  
return {c[valw], s};  
endfunction
```

types world
equivalent of $w+1$

Lifting a type
into the value
world

Structural interpretation of a loop – unfold it to
generate an acyclic graph

Static Elaboration phase

- When BSV programs are compiled, first type checking is done and then the compiler gets rid of many constructs which have no direct hardware meaning, like Integers, loops

```
for(Integer i=0; i<valw; i=i+1) begin  
    let cs = fa(x[i],y[i],c[i]);  
    c[i+1] = cs[1]; s[i] = cs[0];  
end
```

```
cs0 = fa(x[0], y[0], c[0]); c[1]=cs0[1]; s[0]=cs0[0];  
cs1 = fa(x[1], y[1], c[1]); c[2]=cs1[1]; s[1]=cs1[0];  
...  
csw = fa(x[valw-1], y[valw-1], c[valw-1]);  
c[valw] = cs w[1]; s[valw-1] = cs w[0];
```


Integer versus Int#(32)

- ◆ In mathematics integers are unbounded but in computer systems integers always have a fixed size
- ◆ BSV allows us to express both types of integers, though unbounded integers are used only as a programming convenience

```
for(Integer i=0; i<valw; i=i+1)
begin
    let cs = fa(x[i],y[i],c[i]);
    c[i+1] = cs[1]; s[i] = cs[0];
end
```


Shift operators

Logical right shift by 2

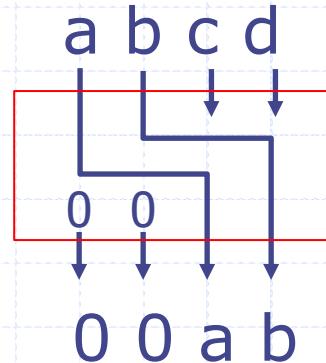

- ◆ Fixed size shift operation is cheap in hardware – just wire the circuit appropriately
- ◆ Rotate, sign-extended shifts – all are equally easy

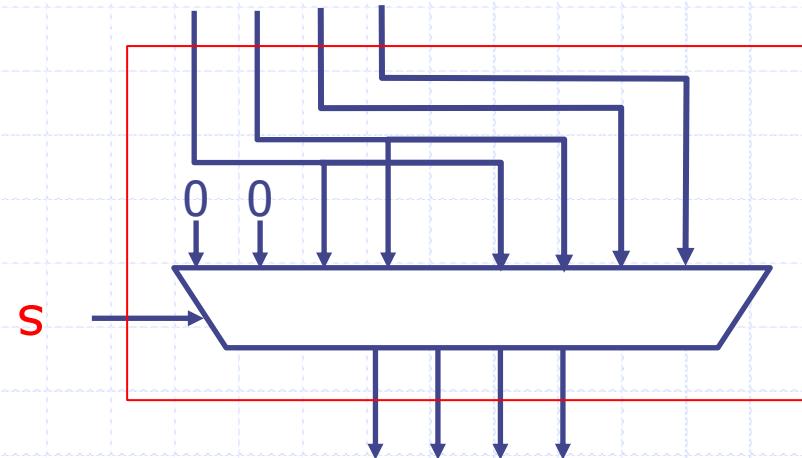Conditional operation: shift versus no-shift




- ◆ We need a mux to select the appropriate wires: if **s** is one the mux will select the wires on the left otherwise it would select wires on the right

```
(s==0) ? {a,b,c,d} : {0,0,a,b};
```

Logical right shift by n

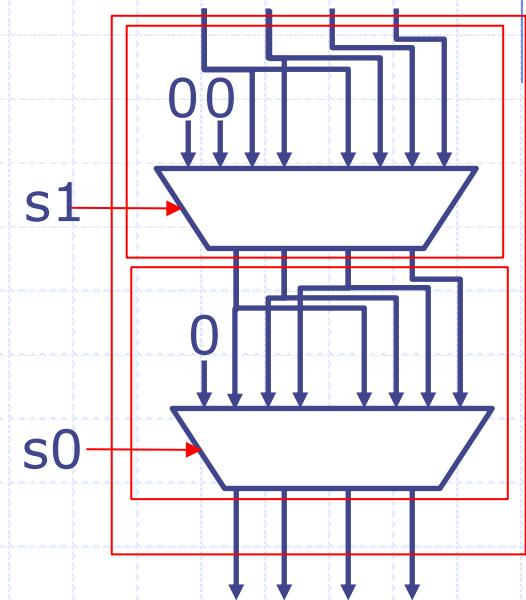- ◆ Shift n can be broken down in $\log n$ steps of fixed-length shifts of size 1, 2, 4, ...
 - Shift 3 can be performed by doing a shift 2 and shift 1
- ◆ We need a mux to omit a particular size shift
- ◆ Shift circuit can be expressed as $\log n$ nested conditional expressions



A digression on types

- ◆ Suppose we have a variable c whose values can represent three different colors
 - We can declare the type of c to be Bit#(2) and say that 00 represents Red, 01 Blue and 10 Green
- ◆ A better way is to create a new type called Color as follows:

```
typedef enum {Red, Blue, Green}  
Color deriving(Bits, Eq);
```

Types prevent us from mixing bits that represent color from raw bits

The compiler will automatically assign some bit representation to the three colors and also provide a function to test if the two colors are equal. If you do not use "deriving" then you will have to specify the representation and equality

Enumerated types

```
typedef enum {Red, Blue, Green}  
Color deriving(Bits, Eq);
```

```
typedef enum {Eq, Neq, Le, Lt, Ge, Gt, AT, NT}  
BrFunc deriving(Bits, Eq);
```

```
typedef enum {Add, Sub, And, Or, Xor, Nor, Slt, Sltu,  
LShift, RShift, Sra}  
AluFunc deriving(Bits, Eq);
```

Each enumerated type defines a new type

Combinational ALU

```
function Data alu(Data a, Data b, AluFunc func);  
    Data res = case(func)  
        Add      : (a + b);  
        Sub      : (a - b);  
        And      : (a & b);  
        Or       : (a | b);  
        Xor      : (a ^ b);  
        Nor      : ~(a | b);  
        Slt      : zeroExtend( pack( signedLT(a, b) ) );  
        Sltu     : zeroExtend( pack( a < b ) );  
        LShift   : (a << b[4:0]);  
        RShift   : (a >> b[4:0]);  
        Sra      : signedShiftRight(a, b[4:0]);  
    endcase;  
    return res;  
endfunction
```

Given an implementation of the primitive operations like addN, Shift, etc. the ALU can be implemented simply by introducing a mux controlled by `op` to select the appropriate circuit

Comparison operators

```
function Bool aluBr(Data a, Data b, BrFunc brFunc);  
    Bool brTaken = case (brFunc)  
        Eq : (a == b);  
        Neq : (a != b);  
        Le : signedLE(a, 0);  
        Lt : signedLT(a, 0);  
        Ge : signedGE(a, 0);  
        Gt : signedGT(a, 0);  
        AT : True;  
        NT : False;  
    endcase;  
    return brTaken;  
endfunction
```

ALU including Comparison operators

