
 
 
 


# Sequential Circuits

Arvind  
Computer Science & Artificial Intelligence Lab.  
Massachusetts Institute of Technology


# Combinational circuits

 

Such circuits have no cycles (feedback) or state elements

# Flip flop: The basic building block of Sequential Circuits





## Edge-Triggered Flip-flop

 

Metastability


*Data is sampled at the rising edge of the clock*

# Flip-flops with Write Enables

    

Data is captured only if EN is on

# Registers

 


*Register:* A group of flip-flops with a common clock and enable

*Register file:* A group of registers with a common clock, input and output port(s)

An example

# Modulo-4 counter


Prev State q1q0	NextState	
	inc = 0	inc = 1
00	00	01
01	01	10
10	10	11
11	11	00

 

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$

$$q1^{t+1} = \sim inc \cdot q1^t + inc \cdot \sim q1^t \cdot q0^t + inc \cdot q1^t \cdot \sim q0^t$$

## Modulo-4 counter circuit

 

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$
$$q1^{t+1} = \sim inc \cdot q1^t + inc \cdot \sim q1^t \cdot q0^t + inc \cdot q1^t \cdot \sim q0^t$$

"Optimized" logic

$$q0^{t+1} = inc \oplus q0^t$$
$$q1^{t+1} = (inc == 1) ? q0^t \oplus q1^t : q1^t$$


## Finite State Machines (Sequential Ckts)

- ◆ A computer (in fact all digital hardware) is an FSM
- ◆ Neither State tables nor diagrams are suitable for describing very large digital designs
  - large circuits must be described in a modular fashion -- as a collection of cooperating FSMs
- ◆ BSV is a modern programming language to describe cooperating FSMs
  - We will give various examples of FSMs in BSV

## modulo4 counter in BSV

```
module moduloCounter(Counter);  
  Reg#(Bit#(2)) cnt <- mkReg(0);  
  method Action inc;  
    cnt <= {~cnt[1]&cnt[0] | cnt[1]&~cnt[0],  
           ~cnt[0]};  
  endmethod  
  method Bit#(2) read;  
    return cnt;  
  endmethod  
endmodule
```

Can be  
replaced by  
cnt+1

 

September 14, 2016

<http://csg.csail.mit.edu/6.175>

L04-9

## Interface

- ◆ Modulo counter has the following interface, i.e., type

```
interface Counter;  
  method Action inc;  
  method Bit#(2) read;  
endinterface
```

- ◆ An interface can have many different implementations
  - For example, the numbers may be represented as Gray code

September 14, 2016

<http://csg.csail.mit.edu/6.175>


L04-10

# FIFO Interface

```

interface Fifo#(numeric type size, type t);
  method Bool notFull;
  method Bool notEmpty;
  method Action enq(t x);
  method Action deq;
  method t first;
endinterface
  
```

 - enq should be called only if notFull returns True;
- deq and first should be called only if notEmpty returns True



September 14, 2016


<http://csg.csail.mit.edu/6.175>

L04-11
 
# One-Element FIFO Implementation

```

module mkCFifo (Fifo#(1, t));
  Reg#(t) d <- mkRegU;
  Reg#(Bool) v <- mkReg(False);
  method Bool notFull;
    return !v;
  endmethod
  method Bool notEmpty;
    return v;
  endmethod
  method Action enq(t x);
    v <= True; d <= x;
  endmethod
  method Action deq;
    v <= False;
  endmethod
  method t first;
    return d;
  endmethod
endmodule
  
```



September 14, 2016

<http://csg.csail.mit.edu/6.175>

L04-12

# Two-Element FIFO



```


module mkCFifo (Fifo#(2, t));
  Reg#(t)    da <- mkRegU();
  Reg#(Bool) va <- mkReg(False);
  Reg#(t)    db <- mkRegU();
  Reg#(Bool) vb <- mkReg(False);
  method Bool notFull; return !vb; endmethod
  method Bool notEmpty; return va; endmethod
  method Action enq(t x);
    if (va) begin db <= x; vb <= True; end
    else begin da <= x; va <= True; end
  endmethod
  method Action deq;
    if (vb) begin da <= db; vb <= False; end
    else begin va <= False; end
  endmethod
  method t first; return da; endmethod
endmodule
  
```

Assume, if there is only one element in the FIFO it resides in da

parallel composition of actions

no change in fifo interface

# Switch

 

```

if (inQ.first.color == Red) begin
  redQ.enq(inQ.first.value); inQ.deq;
end else begin
  greenQ.enq(inQ.first.value); inQ.deq;
end
  
```


parallel composition of actions. Effect of inQ.deq is not visible to inQ.first

```

let x = inQ.first;
if (x.color == Red) redQ.enq(x.value);
else greenQ.enq(x.value);
inQ.deq;
  
```

The code does not test for empty inQ or full redQ or full greenQ conditions!

# Switch with empty/full tests on queues

 

```
if (inQ.notEmpty) begin
  if (inQ.first.color == Red) begin
    if (redQ.notFull) begin
      redQ.enq(inQ.first.value); inQ.deq;
    end
  end else begin
    if (greenQ.notFull) begin
      greenQ.enq(inQ.first.value); inQ.deq;
    end
  end
  inQ.deq;
end
```

What's wrong if the deq is moved here?


*Atomicity violation!*

September 14, 2016

<http://csg.csail.mit.edu/6.175>

L04-15

# Switch with counters

 

```
if (inQ.first.color == Red) begin
  redQ.enq(inQ.first.value); inQ.deq;
  redC <= redC+1;
end else begin
  greenQ.enq(inQ.first.value); inQ.deq;
  greenC <= greenC+1;
end
```

Ignoring full/empty conditions

September 14, 2016

<http://csg.csail.mit.edu/6.175>


L04-16



# Shared counters

```
if (inQA.first.color == Red) begin
  redQA.enq(inQA.first.value);
  inQA.deq; redC <= redC+1;
end else begin
  greenQA.enq(inQA.first.value);
  inQA.deq; greenC <= greenC+1;
end;
if (inQB.first.color == Red) begin
  redQB.enq(inQB.first.value);
  inQB.deq; redC <= redC+1;
end else begin
  greenQB.enq(inQB.first.value);
  inQB.deq; greenC <= greenC+1;
end
```

Ignoring full/empty conditions

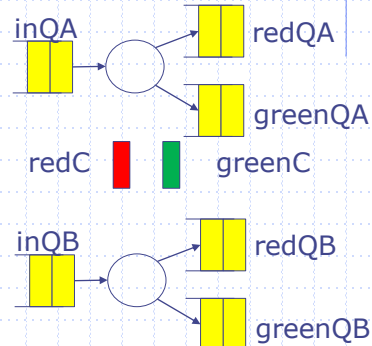

What is wrong with this code?

Double write error

September 14, 2016

<http://csg.csail.mit.edu/6.175>

L04-17

# Double-write problem

- ◆ Parallel composition is illegal if a double-write possibility exists
- ◆ If the BSV compiler cannot prove that the predicates for writes into a register or a method call are mutually exclusive, it rejects the program

September 14, 2016

<http://csg.csail.mit.edu/6.175>

L04-18

# Observations

- ◆ These programs are not very complex and yet it would have been tedious to express these programs in a state table or as a circuit directly
- ◆ BSV method calls are not available in Verilog/VHDL, and thus such programs sometimes require tedious programming
- ◆ Even the meaning of double-write errors is not standardized across tool implementations in Verilog