

Constructive Computer Architecture

Sequential Circuits - 2

Arvind
Computer Science & Artificial Intelligence Lab.
Massachusetts Institute of Technology

September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-1

Content

- ◆ So far we have seen modules with methods which are called by rules outside the body
- ◆ Now we will see examples where a module may also contain rules
 - gcd
- ◆ A common way to implement large combinational circuits is by *folding* where registers hold the state from one iteration to the next
 - Implementing imperative loops
 - Multiplication

September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-2

Programming with rules: A simple example

Euclid's algorithm for computing the Greatest Common Divisor (GCD):

15	6	
9	6	<i>subtract</i>
3	6	<i>subtract</i>
6	3	<i>swap</i>
3	3	<i>subtract</i>
0	<i>answer:</i> 3	<i>subtract</i>

September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-3

GCD module

Euclidean Algorithm

```
Reg#(Bit#(32)) x <- mkReg(0);
Reg#(Bit#(32)) y <- mkReg(0);
rule gcd;
  if (x >= y) begin
    x <= x - y;
  end else if (x != 0) begin
    x <= y; y <= x;
  end
endrule
method Action start(Bit#(32) a, Bit#(32) b);
  x <= a; y <= b; endmethod
method Bit#(32) result; return y; endmethod
method Bool resultRdy; return x == 0; endmethod
method Bool busy; return x != 0; endmethod
```

A rule inside a module
may execute anytime

If x is 0 then the rule
has no effect


- ◆ Start method should be called only if busy is False.
- ◆ The result is available only when resultRdy is True.

September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-4

Circuits for GCD

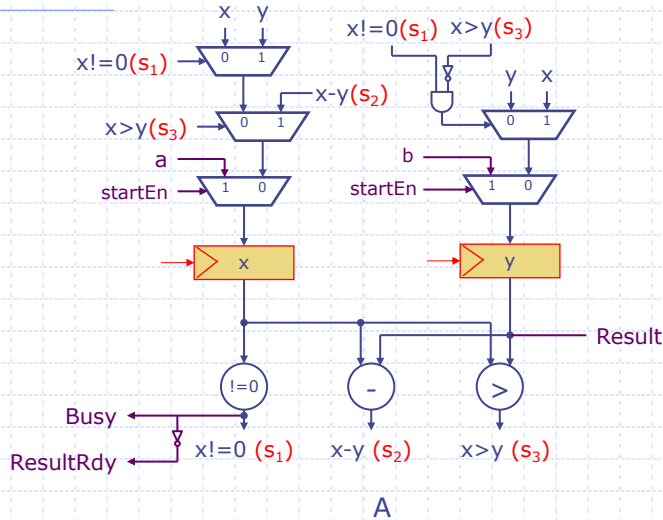

September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-5


Expressing a loop using registers

```
int s = s0;
for (int i = 0; i < 32; i = i+1) {
    s = f(s);
}
return s;
```

C-code

We need two registers to hold s and i values from one iteration to the next.

 These registers are initialized when the computation starts and updated every cycle until the computation terminates



$sel = start$
 $en = start \mid notDone$

September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-6


Expressing a loop in BSV

◆ When a rule executes:

- all the registers are read at the beginning of a clock cycle
- computations to evaluate the next value of the registers are performed
- Registers that need to be updated are updated at the end of the clock cycle

◆ Muxes are need to initialize the registers
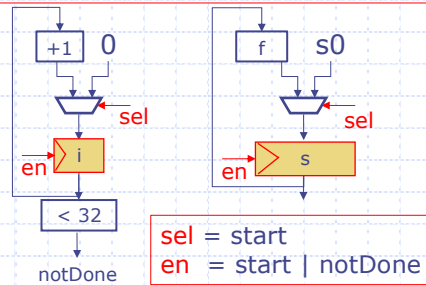
```
Reg#(Bit#(32)) s <- mkRegU();
Reg#(Bit#(6)) i <- mkReg(32);
rule step;
  if (i < 32) begin
    s <= f(s); i <= i+1;
  end
endrule
```



Combinational 32-bit multiply

```
function Bit#(64) mul32(Bit#(32) a, Bit#(32) b);
  Bit#(32) tp = 0;
  Bit#(32) prod = 0;
  for(Integer i = 0; i < 32; i = i+1)
  begin
    Bit#(32) m = (a[i]==0)? 0 : b;
    Bit#(33) sum = add32(m, tp, 0);
    prod[i:i] = sum[0];
    tp = sum[32:1];
  end
  return {tp, prod};
endfunction
```

Combinational circuit uses 31 add32 circuits

We can reuse the same add32 circuit if we store the partial results in a register

Multiply using registers

```
function Bit#(64) mul32(Bit#(32) a, Bit#(32) b);
  Bit#(32) prod = 0;
  Bit#(32) tp = 0;
  for(Integer i = 0; i < 32; i = i+1)
  begin
    Bit#(32) m = (a[i]==0)? 0 : b;
    Bit#(33) sum = add32(m,tp,0);
    prod[i:i] = sum[0];
    tp = sum[32:1];
  end
  return {tp,prod};
endfunction
```

Combinational
version

Need registers to hold a, b, tp, prod and i

Update the registers every cycle until we are done

September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-9

Sequential Circuit for Multiply

```
Reg#(Bit#(32)) a <- mkRegU();
Reg#(Bit#(32)) b <- mkRegU();
Reg#(Bit#(32)) prod <-mkRegU();
Reg#(Bit#(32)) tp <- mkReg(0);
Reg#(Bit#(6)) i <- mkReg(32);

rule mulStep;
  if (i < 32) begin
    Bit#(32) m = (a[i]==0)? 0 : b;
    Bit#(33) sum = add32(m,tp,0);
    prod[i] <= sum[0];
    tp <= sum[32:1];
    i <= i+1;
  end
endrule
```

state
elements

a rule to
describe
the
dynamic
behavior

similar to the
loop body in the
combinational
version


So that the rule has
no effect until i is set
to some other value

September 16, 2016


<http://csg.csail.mit.edu/6.175>

L05-10

Dynamic selection requires a mux

 

 when the selection indices are regular then it is better to use a shift operator (no gates!)



September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-11

Replacing repeated selections by shifts

```
Reg#(Bit#(32)) a <- mkRegU();
Reg#(Bit#(32)) b <- mkRegU();
Reg#(Bit#(32)) prod <-mkRegU();
Reg#(Bit#(32)) tp <- mkReg(0);
Reg#(Bit#(6)) i <- mkReg(32);


rule mulStep if (i < 32);
  Bit#(32) m = (a[0]==0)? 0 : b;
  a <= a >> 1;
  Bit#(33) sum = add32(m,tp,0);
  prod <= {sum[0], prod[31:1]};
  tp <= sum[32:1];
  i <= i+1;
endrule
```

September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-12

Circuit for Sequential Multiply

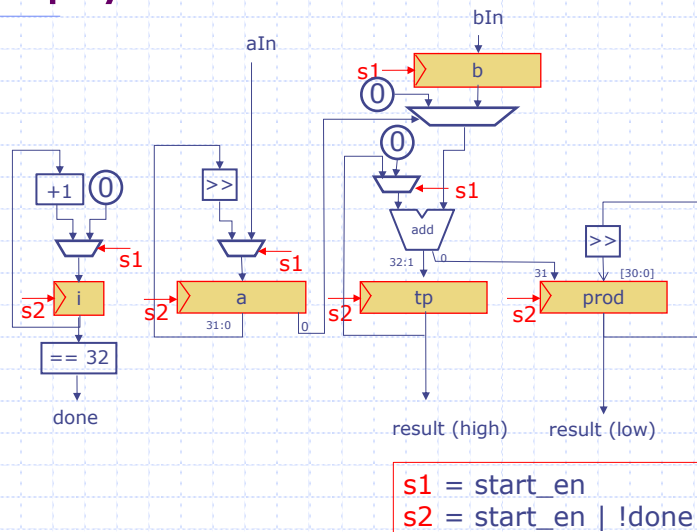

September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-13

Circuit analysis


- ◆ Number of add32 circuits has been reduced from 31 to one, though some registers and muxes have been added
- ◆ The longest combinational path has been reduced from 62 FAs to one add32 plus a few muxes
- ◆ The sequential circuit will take 31 clock cycles to compute an answer

September 16, 2016

<http://csg.csail.mit.edu/6.175>

L05-14

A subtle problem

 


```

let x = workQ.first;
workQ.deq;
if (isDone(x)) begin
    doneQ.enq(x);
end else begin
    workQ.enq(doStep(x));
end
    
```

Double write problem for previously shown FIFOs

Later we will design FIFOs to permit simultaneous enq and deq


Pipelining Combinational Functions

 


3 different datasets in the pipeline

- ◆ Lot of area and long combinational delay
- ◆ Folded or multi-cycle version can save area and reduce the combinational delay but throughput per clock cycle gets worse
- ◆ Pipelining: a method to increase the circuit throughput by evaluating multiple inputs

Inelastic vs Elastic pipeline

 

 Inelastic: all pipeline stages move synchronously



Elastic: A pipeline stage can process data if its input FIFO is not empty and output FIFO is not Full

Most complex processor pipelines are a combination of the two styles