

Constructive Computer Architecture

Combinational circuits

Arvind

Computer Science & Artificial Intelligence Lab.
Massachusetts Institute of Technology


Combinational circuit

◆ A combinational circuit is a pure function; given the same input, it produces the same output

◆ It can be described using a Truth Table though it is not practical to do so for large number of inputs

- Size of truth table for a 32-bit adder? 2^{32+32} rows

 
We will use a programming language called Bluespec System Verilog (BSV) to express all ckts



a	b	c	s1	s2
0	0	0	1	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	0

Half Adder

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

```
function ha(a, b); XOR
  s = a ^ b;
  c = a & b;
  return {c, s}; AND
endfunction
```

Boolean equations

$$s = a \oplus b$$

$$c = a \cdot b$$

Not quite correct –
needs type annotations

Half Adder *corrected*

```
function Bit#(2) ha(Bit#(1) a, Bit#(1) b);  
  Bit#(1) s = a ^ b;  
  Bit#(1) c = a & b;  
  return {c, s};  
endfunction
```

“Bit#(1) a” type declaration says that a is one bit wide

{c, s} represents bit concatenation

How big is {c, s}?

2 bits

BSV notes

```
function Bit#(2) ha(Bit#(1) a, Bit#(1) b);  
  Bit#(1) s = a ^ b;  
  Bit#(1) c = a & b;  
  return {c, s};  
endfunction
```


ha can be used as a black-box as long as we understand its type signature

- ◆ Suppose we write $t = \text{ha}(a, b)$ then t is a two bit quantity representing c and s values
- ◆ We can recover c and s values from t by writing $t[1]$ and $t[0]$, respectively



Full Adder

1-bit adder with a carry-in input

 


```
function Bit#(2) fa(Bit#(1) a, Bit#(1) b,  
                    Bit#(1) c_in);  
    Bit#(2) ab = ha(a, b);  
    Bit#(2) abc = ha(ab[0], c_in);  
    Bit#(1) c_out = ab[1] | abc[1];  
    return {c_out, abc[0]};  
endfunction
```

Extracts the sum bit

Extracts the carry bit

ha is being used as a black-box; fa code is simply a wiring diagram

The “let” syntax

 

```
function Bit#(2) fa(Bit#(1) a, Bit#(1) b,  
                  Bit#(1) c_in);  
  
  let ab = ha(a, b);  
  let abc = ha(ab[0], c_in);  
  let c_out = ab[1] | abc[1];  
  return {c_out, abc[0]};  
endfunction
```

No need to
write the type
if the compiler
can deduce it

Types

◆ A type is a grouping of values:

- Integer: 1, 2, 3, ...
- Bool: True, False
- Bit: 0, 1
- A pair of Integers: `Tuple2#(Integer, Integer)`
- A function `fname` from Integers to Integers:

```
function Integer fname (Integer arg)
```

◆ Every expression in a BSV program has a type; sometimes it is specified explicitly and sometimes it is deduced by the compiler

◆ Thus, we say an expression has a type or belongs to a type

The type of each expression is unique

Parameterized types:

- ◆ A type declaration itself can be parameterized by other types
- ◆ Parameters are indicated by using the syntax `#`
 - For example `Bit#(n)` represents `n` bits and can be instantiated by specifying a value of `n`
`Bit#(1)`, `Bit#(32)`, `Bit#(8)`, ...

Type synonyms

```
typedef bit [7:0] Byte;
```

```
typedef Bit#(8) Byte;
```

```
typedef Bit#(32) Word;
```

```
typedef Tuple2#(a, a) Pair#(type a);
```

```
typedef Int#(n) MyInt#(numeric type n);
```

In some special cases one can just write:

```
typedef Int#(n) MyInt#(type n);
```



The same

Type declaration versus deduction

- ◆ The programmer writes down types of some expressions in a program and the compiler deduces the types of the rest of expressions
- ◆ If the type deduction cannot be performed or the type declarations are inconsistent then the compiler complains


```
function Bit#(2) fa(Bit#(1) a, Bit#(1) b,  
                  Bit#(1) c_in);  
    Bit#(2) ab = ha(a, b);  
    Bit#(2) abc = ha(ab[0], c_in);  
    Bit#(2) c_out = ab[1] | abc[1];  
    return {c_out, abc[0]};  
endfunction
```

type error?

Type checking prevents
lots of silly mistakes

2-bit Ripple-Carry Adder

cascading full adders

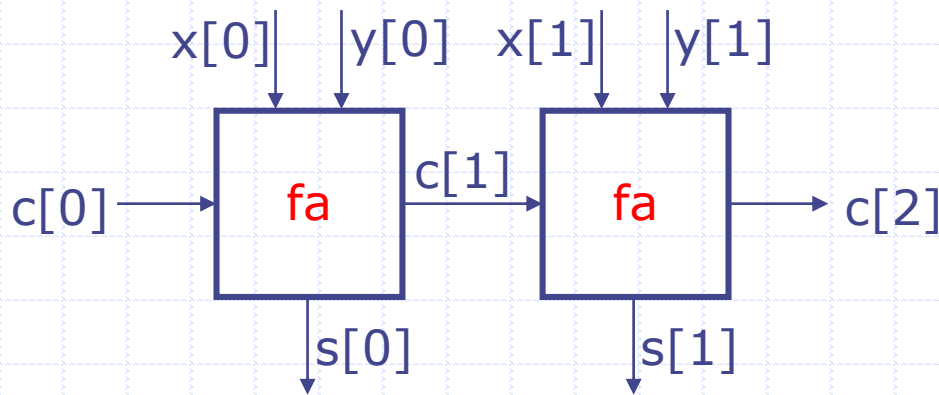

Use `fa` as a black-box

```
function Bit#(3) add(Bit#(2) x, Bit#(2) y, Bit#(1) c0);
```

Initially
s wires
are zero

```
Bit#(2) s = 0; Bit#(3) c=0; c[0] = c0;
```

```
let cs0 = fa(x[0], y[0], c[0]);
```

```
c[1] = cs0[1]; s[0] = cs0[0];
```

wire `s[0]` is updated

```
let cs1 = fa(x[1], y[1], c[1]);
```

```
c[2] = cs1[1]; s[1] = cs1[0];
```

wire `s[1]` is updated

```
return {c[2], s};
```

```
endfunction
```

Assigning to Vector elements

```
Bit# (3)  c=0;
```

- ◆ Means c is three bits wide and each element is set to zero

```
c[0] = c0;
```

- ◆ Element 0 of c is connected to c_0 but the value of the rest of the elements is not affected
- ◆ Initial value of a vector must be set; we use "?" if we don't know the initial value

An w -bit Ripple-Carry Adder

- ◆ For a w -bit adder, unless we know the value of w , we cannot write a straight-line program as we did for 2-bit adder
- ◆ Use loops!

```
function Bit#(w+1) addN(Bit#(w) x, Bit#(w) y,  
                        Bit#(1) c0);  
  
  Bit#(w) s; Bit#(w+1) c=0; c[0] = c0;  
  for(Integer i=0; i<w; i=i+1)  
  begin  
    let cs = fa(x[i],y[i],c[i]);  
    c[i+1] = cs[1]; s[i] = cs[0];  
  end  
  return {c[w],s};  
endfunction
```

There are some subtle type errors in this program but before we fix them, you may wonder what is the meaning of a loop in terms of gates?


All loops are unfolded by the compiler!

```
for(Integer i=0; i<w; i=i+1)
  begin
    let cs = fa(x[i],y[i],c[i]);
    c[i+1] = cs[1]; s[i] = cs[0];
  end
```

Can be done only when the value of w is known

```
cs0 = fa(x[0], y[0], c[0]); c[1]=cs0[1]; s[0]=cs0[0];
cs1 = fa(x[1], y[1], c[1]); c[2]=cs1[1]; s[1]=cs1[0];
...
csw = fa(x[valw-1], y[valw-1], c[valw-1]);
c[valw] = csw[1]; s[valw-1] = csw[0];
```

Loops to gates

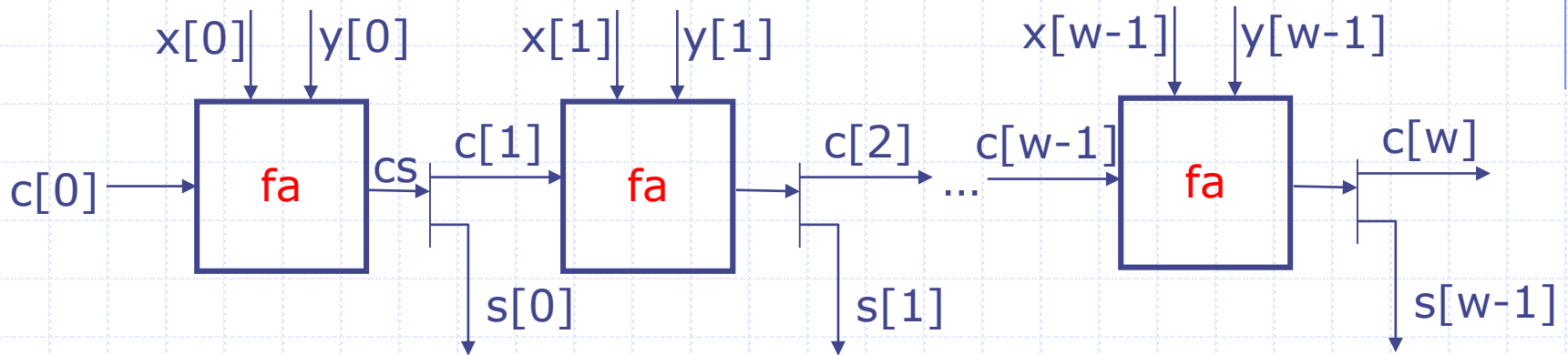

```
cs0 = fa(x[0], y[0], c[0]); c[1]=cs0[1]; s[0]=cs0[0];  
cs1 = fa(x[1], y[1], c[1]); c[2]=cs1[1]; s[1]=cs1[0];  
...  
csw = fa(x[valw-1], y[valw-1], c[valw-1]);  
c[valw] = csw[1]; s[valw-1] = csw[0];
```

Unfolded loop defines an acyclic wiring diagram

Instantiating the parametric Adder

```
function Bit#(w+1) addN(Bit#(w) x, Bit#(w) y,  
                        Bit#(1) c0);
```

How do we define a `add32`, `add3` ... using `addN` ?

```
// concrete instances of addN!
```

```
function Bit#(33) add32(Bit#(32) x, Bit#(32) y,  
                       Bit#(1) c0) = addN(x, y, c0);
```

The numeric type `w` on the RHS implicitly gets instantiated to 32 because of the LHS declaration

```
function Bit#(4) add3(Bit#(3) x, Bit#(3) y,  
                     Bit#(1) c0) = addN(x, y, c0);
```

Fixing the type errors

`valueOf (w)` versus `w`

- ◆ Each expression has a type and a value, and these two come from entirely disjoint worlds
- ◆ `w` in `Bit# (w)` resides in the types world
- ◆ Sometimes we need to use values from the types world into actual computation. The function `valueOf` allows us to do that
 - Thus
 - `i < w` is not type correct
 - `i < valueOf (w)` is type correct

Fixing the type errors

TAdd# (w, 1) versus w+1

- ◆ Sometimes we need to perform operations in the types world that are very similar to the operations in the value world
 - Examples: Add, Mul, Log
- ◆ We define a few special operators in the types world for such operations
 - Examples: TAdd# (m, n), TMul# (m, n), ...

Fixing the type errors

Integer **versus** Int# (32)

- ◆ In mathematics integers are unbounded but in computer systems integers always have a fixed size
- ◆ BSV allows us to express both types of integers, though unbounded integers are used only as a programming convenience

```
integer for(Integer i=0; i<valw; i=i+1)  
  begin  
    let cs = fa(x[i],y[i],c[i]);  
    c[i+1] = cs[1]; s[i] = cs[0];  
  end
```

A w -bit Ripple-Carry Adder

corrected

```
function Bit#(TAdd#(w, 1)) addN(Bit#(w) x, Bit#(w) y,  
                                Bit#(1) c0);  
  Bit#(w) s; Bit#(TAdd#(w, 1)) c; c[0] = c0;  
  let valw = valueOf(w);  
  for (Integer i=0; i<valw; i=i+1)  
  begin  
    let cs = fa(x[i], y[i], c[i]);  
    c[i+1] = cs[1]; s[i] = cs[0];  
  end  
  return {c[valw], s};  
endfunction
```

types world
equivalent of $w+1$

Lifting a type
into the value
world

Structural interpretation of a loop – unfold it to generate an acyclic graph

BSV Compiling phases

- ◆ Type checking: Ensures that type of each expression can be determined uniquely; Otherwise the program is rejected
- ◆ Static elaboration: Compiler eliminates all constructs which have no direct hardware meaning
 - Loops are unfolded
 - Functions are in-lined; even recursive functions can be used as long as all the recursion can be gotten rid of at compile time
 - After this stage the program does not contain any Integers because Integers are unbounded in BSV
- ◆ Gates are generated (actually Verilog)

Takeaway

- ◆ Once we define a combinational ckt, we can use it repeatedly to build larger ckts
- ◆ The BSV compiler, because of the type signatures of functions, prevents us from connecting them in obviously illegal ways
- ◆ We can write parameterized ckts in BSV, for example an n-bit adder. Once n is specified, the correct ckt is automatically generated
- ◆ Even though we use loop constructs and functions to express combinational ckts, all loops are unfolded and functions are inlined during the compilation phase