

Constructive Computer Architecture

Combinational ALU

Arvind
Computer Science & Artificial Intelligence Lab.
Massachusetts Institute of Technology

September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-1

Outline

- ◆ Building complex combinational circuits in pieces
- ◆ Parameterization that goes beyond data path widths


September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-2

Arithmetic-Logic Unit (ALU)

 ALU performs all the arithmetic and logical functions



```
function Data alu(Data a, Data b,
                  AluFunc func);
```

Each individual function can be described as a combinational circuit and these can be combined together to produce a combinational ALU


September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-3

ALU for comparison operators

Like ALU but returns a Bool

 

```
function Bool aluBr(Data a, Data b,
                   BrFunc func);
    what does func look like?
```

September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-4

Enumerated types

- ◆ Suppose we have a variable `c` whose values can represent three different colors
 - Declare the type of `c` to be `Bit#(2)` and adopt the convention that 00 represents Red, 01 Blue and 10 Green
- ◆ A better way is to create a new type called `Color`:

```
typedef enum {Red, Blue, Green}
Color deriving(Bits, Eq);
```

BSV compiler automatically assigns a bit representation to the three colors and provides a function to test if the two colors are equal

If you do not use “`deriving`” then you will have to specify your own encoding and equality function

Enumerated types

```
typedef enum {Red, Blue, Green}
Color deriving(Bits, Eq);
```

```
typedef enum {Add, Sub, And, Or, Xor, Nor, Slt, Sltu,
LShift, RShift, Sra} AluFunc deriving(Bits, Eq);
```

```
typedef enum {Eq, Neq, Le, Lt, Ge, Gt, AT, NT}
BrFunc deriving(Bits, Eq);
```

Combinational ALU

```
function Data alu(Data a, Data b, AluFunc func);
  Data res = case(func)
    Add   : addN(a,b);
    Sub   : subN(a,b);
    And   : andN(a,b);
    Or    : orN(a,b);
    Xor   : xorN(a,b);
    Nor   : norN(a,b);
    Slt   : zeroExtend(pack(signedLT(a,b)));
    Sltu  : zeroExtend(pack(lt(a,b)));
    LShift: shiftLeft(a,b[4:0]);
    RShift: shiftRight(a,b[4:0]);
    Sra   : signedShiftRight(a,b[4:0]);
  endcase;
  return res;
endfunction
```

September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-7

Comparison operators


```
function Bool aluBr(Data a, Data b, BrFunc brFunc);
  Bool brTaken = case(brFunc)
    Eq   : (a == b);
    Neq  : (a != b);
    Le   : signedLE(a,b);
    Lt   : signedLT(a,b);
    Ge   : signedGE(a,b);
    Gt   : signedGT(a,b);
    AT   : True;
    NT   : False;
  endcase;
  return brTaken;
endfunction
```

September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-8

ALU including Comparison operators

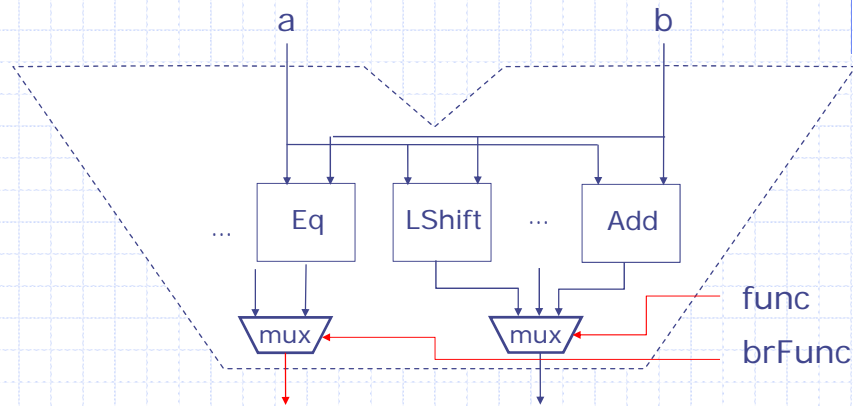

September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-9

Selectors and Multiplexers

September 11, 2017



<http://csg.csail.mit.edu/6.175>

L03-10

Selecting a wire: $x[i]$



assume x is 4 bits wide

- ◆ Constant Selector: e.g., $x[2]$

  



no hardware;
 $x[2]$ is just
the name of
a wire

- ◆ Dynamic selector: $x[i]$

  

4-way mux

A 2-way multiplexer

  


$(s==0) ? A : B ;$

Gate-level implementation


A 4-way multiplexer
 
```
case ({s1,s0}) matches
  0: A;
  1: B;
  2: C;
  3: D;
endcase
```





Shift operators

Logical right shift by 2

 

  - ◆ Fixed size shift operation is cheap in hardware – just wire the circuit appropriately
- ◆ Other types of shifts are similar



Sign extension is useful for converting say, a 32-bit integer into a 64-bit integer


September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-15

Logical right shift by n

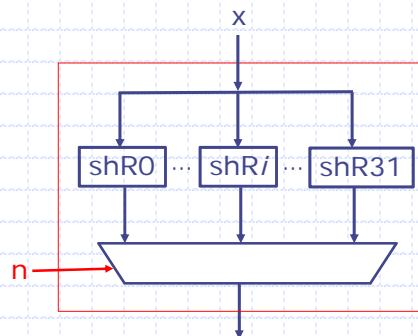- ◆ Suppose we want to build a shifter which shift a value x by n where n is between 0 and 31
- ◆ One way to do this is by connecting 31 different shifters via a mux



September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-16

Logical right shift by n


- ◆ Shift n can be broken down in $\log n$ steps of fixed-length shifts of size 1, 2, 4, ...
 - For example, we can perform Shift 3 ($=2+1$) by doing shifts of size 2 and 1
 - Shift 5 ($=4+1$) by doing shifts of size
 - Shift 21 ($=16+4+1$) by doing shifts of size
- ◆ For a 32-bit number, a 5-bit n can specify all the needed shifts
 - $3_{10} = 00011_2$, $5_{10} = 00101_2$, $21_{10} = 10101_2$
- ◆ The bit encoding of n tells us which shifters are needed; if the value of the i^{th} (least significant) bit is 1 then we need to shift by 2^i bits

September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-17

 Conditional operation: shift versus no-shift



- ◆ We need a mux to select the appropriate wires: if s is one the mux will select the wires on the left otherwise it would select wires on the right

```
(s==0)?{a,b,c,d}:{0,0,a,b};
```


September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-18

Logical right shift ckt

 - ◆ Define $\log n$ shifters of sizes 1, 2, 4, ...
- ◆ Define $\log n$ muxes to perform a particular size shift
- ◆ Shift circuit can be expressed as $\log n$ nested conditional expressions where $s_0, s_1 \dots$ Represent the bits of n



September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-19

Complex Combinational Circuits

September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-20

Multiplication by repeated addition

b Multiplicand 1101 (13)
 a Multiplier * 1011 (11)

		0000	
	x	1101	
m0		1101	
m1	+	1101	
m2	+	0000	
m3	+	1101	
		10001111	(143)

At each step we add either 1101 or 0 to the result depending upon a bit in the multiplier

`mi = (a[i]==0)? 0 : b;`

We also shift the result by one position at every step

However, our addN circuit adds only two numbers at a time!

Multiplication by repeated addition *cont.*

b Multiplicand 1101 (13)
 a Multiplier * 1011 (11)

tp		0000	
m0	+	1101	
tp		01101	
m1	+	1101	
tp			
m2			
tp			
m3			
tp			

At each step we add either 1101 or 0 to the result depending upon a bit in the multiplier

`mi = (a[i]==0)? 0 : b;`

We also shift the result by one position at every step

Multiplication by repeated addition ckt


```

b Multiplicand 1101 (13)
a Multiplier  * 1011 (11)

tp           0000
m0  + 1101
-----
tp           01101
m1  + 1101
-----
tp           100111
m2  + 0000
-----
tp           0100111
m3  + 1101
-----
tp           10001111 (143)

```

$m_i = (a[i]==0)? 0 : b;$

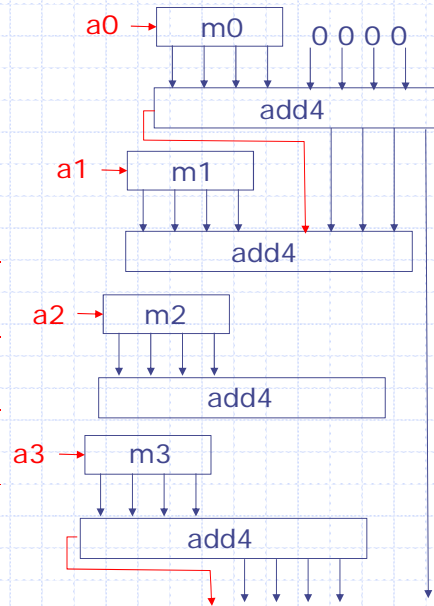

September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-23

Combinational 32-bit multiply

```

function Bit#(64) mul32(Bit#(32) a, Bit#(32) b);
  Bit#(32) tp = 0;
  Bit#(32) prod = 0;
  for(Integer i = 0; i < 32; i = i+1)
  begin
    Bit#(32) m = (a[i]==0)? 0 : b;
    Bit#(33) sum = add32(m, tp, 0);
    prod[i] = sum[0];
    tp = sum[32:1];
  end
  return {tp, prod};
endfunction

```

◆ Long chains of gates

- 32-bit multiply has 32 ripple carry adders in sequence!
- 32-bit ripple carry adder has a 32-long chain of gates
- Total delay ?

September 11, 2017

<http://csg.csail.mit.edu/6.175>

L03-24