

Constructive Computer Architecture





Sequential Circuits:

Circuits with state

Arvind



Computer Science & Artificial Intelligence Lab.
Massachusetts Institute of Technology

Combinational circuits

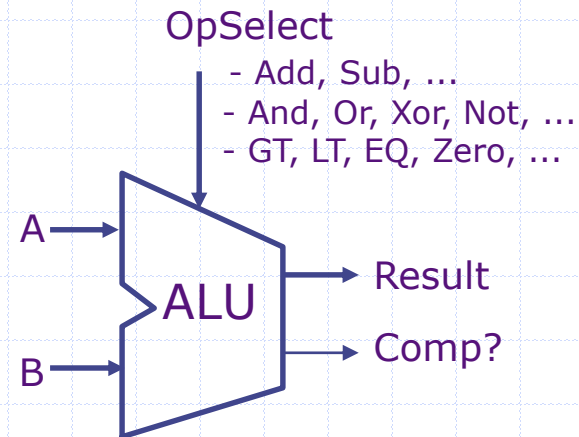   

Such circuits have no cycles (feedback) or state elements

  
Edge-Triggered Flip flop: the basic storage element



Data is sampled at the rising edge of the clock and must be stable at that time

Flip-flops with Write Enables:

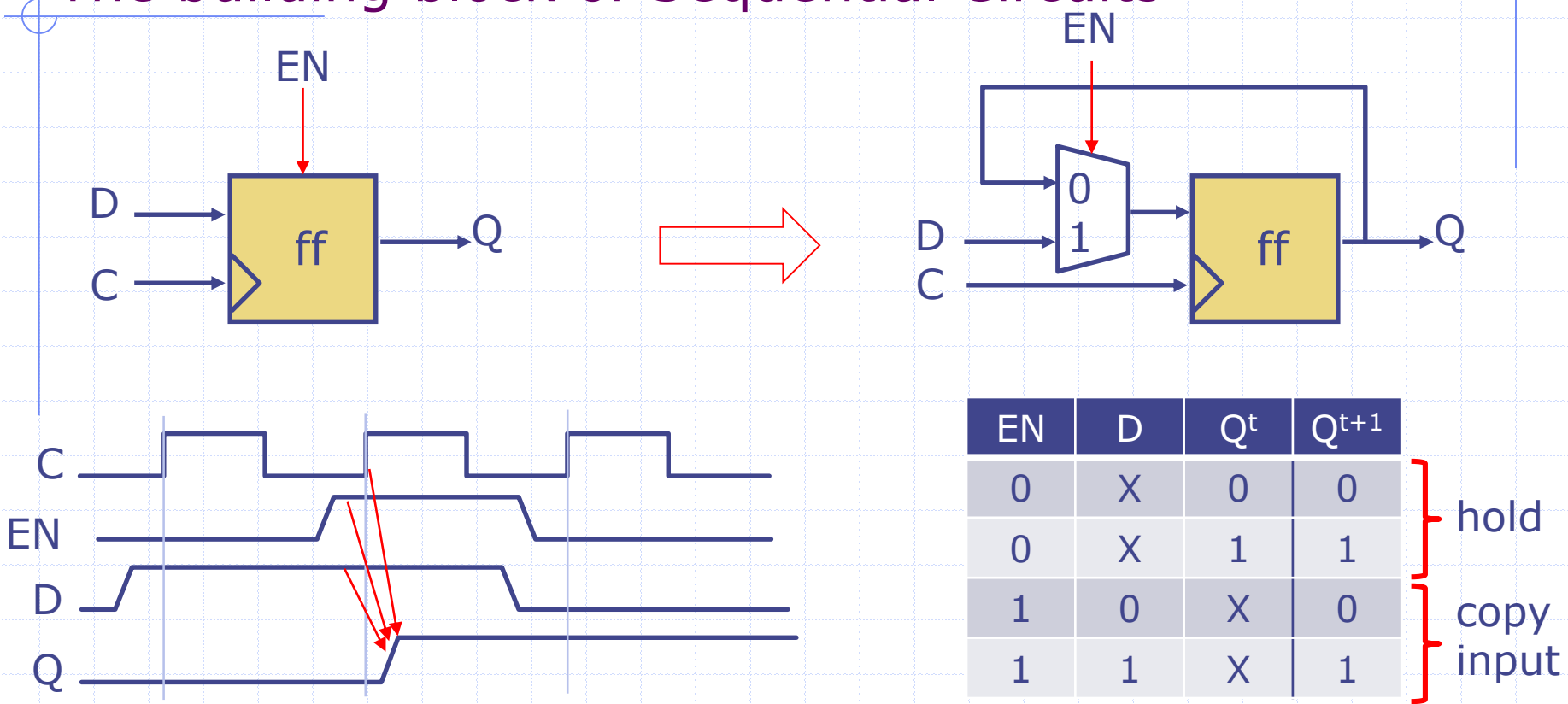
The building block of Sequential Circuits



Data is captured only if EN is on

No need to show clock explicitly

Registers

 


Register: A group of flip-flops with a common clock and enable

Register file: A group of registers with a common clock, input and output port(s)

An example

Modulo-4 counter

Prev State q1q0	NextState	
	inc = 0	inc = 1
00	00	01
01	01	10
10	10	11
11	11	00

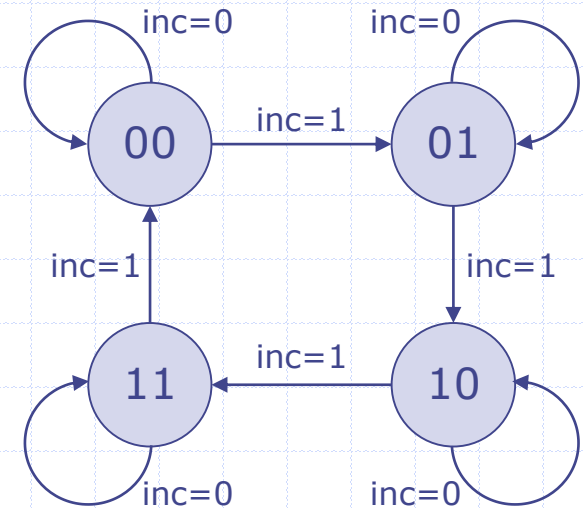


Finite State Machine (FSM) representation

$$\begin{aligned}q_0^{t+1} &= \sim \text{inc} \cdot q_0^t + \text{inc} \cdot \sim q_0^t \\ &= \text{inc} \oplus q_0^t\end{aligned}$$

$$\begin{aligned}q_1^{t+1} &= \sim \text{inc} \cdot q_1^t + \text{inc} \cdot \sim q_1^t \cdot q_0^t + \text{inc} \cdot q_1^t \cdot \sim q_0^t \\ &= (\text{inc} == 1) ? q_0^t \oplus q_1^t : q_1^t\end{aligned}$$


Finite State Machines (FSM) and Sequential Ckts

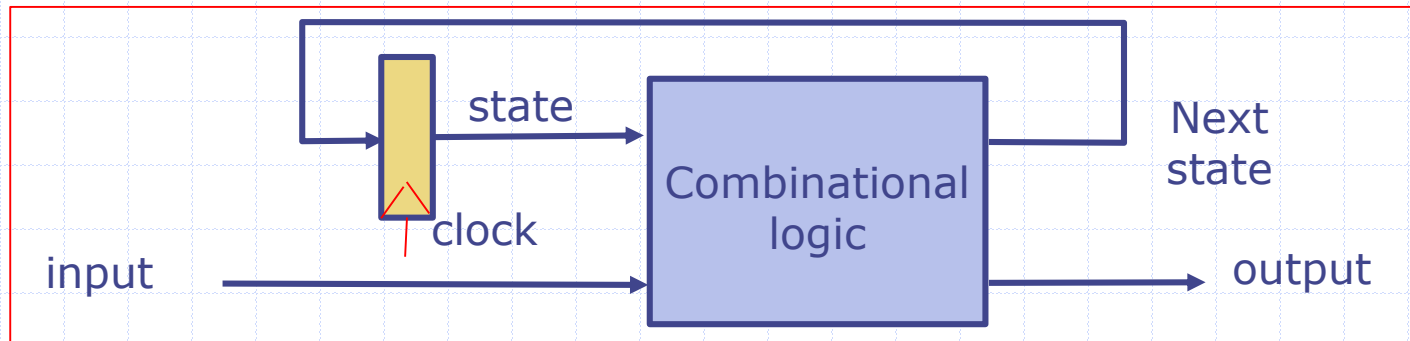- ◆ FSMs are a mathematical object like the Boolean Algebra
 - A computer (in fact any digital hardware) is an FSM
- ◆ Synchronous Sequential Circuits is a method to implement FSMs in hardware



- ◆ Large circuits need to be described as a *collection of cooperating FSMs*
 - State diagrams and next-state tables are not suitable for such descriptions

Modulo-4 counter in BSV

 

```
interface Counter;  
  method Action inc;  
  method Bit#(2) read;  
endinterface
```

```
module moduloCounter(Counter);  
  - Reg#(Bit#(2)) cnt <- mkReg(0);  
  method Action inc;  
    - cnt <={cnt[1]^cnt[0], ~cnt[0]};  
  endmethod  
  method Bit#(2) read;  
    return cnt;  
  endmethod  
endmodule
```

State
specification

Initial value


An action to specify
how the value of the
cnt is to be set

Modules

- ◆ A module in BSV is like a class definition in Java or C++
 - It has internal state
 - The internal state can only be read and manipulated by the (interface) methods
 - An action specifies which state elements are to be modified
 - Actions are atomic -- either all the specified state elements are modified or none of them are modified (no partially modified state is visible)

```
interface Counter;  
    method Action inc;  
    method Bit#(2) read;  
endinterface
```

Inside the Modulo-4 counter

 

```
module moduloCounter(Counter);  
  Reg#(Bit#(2)) cnt <- mkReg(0);  
  method Action inc;  
    cnt <={cnt[1]^cnt[0], ~cnt[0]};  
  endmethod  
  method Bit#(2) read;  
    return cnt;  
  endmethod  
endmodule
```



Examples

A hardware module for computing GCD


Euclid's algorithm for computing the Greatest Common Divisor (GCD):

15	6	
9	6	<i>subtract</i>
3	6	<i>subtract</i>
6	3	<i>swap</i>
3	3	<i>subtract</i>
0	3	<i>subtract</i>

answer

```
gcd (a,b) = if a==0 then b           \\ stop
            else if a>=b then gcd(a-b,b) \\ subtract
            else gcd (b,a)           \\ swap
```

GCD module

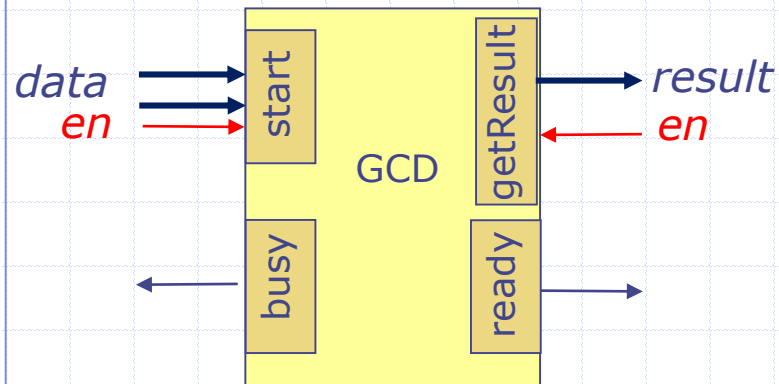

GCD can be started if the module is not *busy*;
Results can be read when *ready*

```
interface GCD;  
  method Action start (Bit#(32) a, Bit#(32) b);  
  method ActionValue#(Bit#(32)) getResult;  
  method Bool busy;  
  method Bool ready;  
endinterface
```

GCD in BSV

```
module mkGCD (GCD);  
Reg#(Bit#(32)) x <- mkReg(0);  
Reg#(Bit#(32)) y <- mkReg(0);  
Reg#(Bool) busy_flag <- mkReg(False);  
rule gcd;  
  if (x >= y) begin x <= x - y; end //subtract  
  else if (x != 0) begin x <= y; y <= x; end //swap  
endrule  
method Action start(Bit#(32) a, Bit#(32) b);  
  x <= a; y <= b; busy_flag <= True;  
endmethod  
method ActionValue#(Bit#(32)) getResult;  
  busy_flag <= False; return y;  
endmethod  
method busy = busy_flag;  
method ready = x==0;  
endmodule
```

Assume b /= 0

start should be called only
if the module is not busy;
getResult should be called
only when ready is true.

Rule

A module may contain rules

parallel
composition
of actions

```
rule gcd;  
  if (x >= y) begin x <= x - y; end //subtract  
  else if (x != 0) begin x <= y; y <= x; end //swap  
endrule
```

- ◆ A rule is a collection of actions, which invoke methods
- ◆ All actions in a rule execute in parallel
- ◆ A rule can execute any time and when it executes all of its actions must execute

atomicity

Parallel Composition of Actions & Double-Writes

```
rule one;  
  y <= 3; x <= 5; x <= 7; endrule
```

Double write

```
rule two;  
  y <= 3; if (b) x <= 7; else x <= 5; endrule
```

No double write

```
rule three;  
  y <= 3; x <= 5; if (b) x <= 7; endrule
```

Possibility of a
double write

- ◆ Parallel composition, and consequently a rule containing it, is illegal if a double-write possibility exists
- ◆ The BSV compiler **rejects** a program if there is a possibility of a double write




Defining FIFOs and it's uses

FIFO Module Interface


```
interface Fifo#(numeric type size, type t);  
  method Bool notFull;  
  method Bool notEmpty;  
  method Action enq(t x);  
  method Action deq;  
  method t first;  
endinterface
```

 - enq should be called only if notFull returns True;
- deq and first should be called only if notEmpty returns True




An Implementation: One-Element FIFO
 
```
module mkFifo (Fifo#(1, t));  
  Reg#(t)    d  <- mkRegU;  
  Reg#(Bool) v  <- mkReg(False);  
  method Bool notFull;  
    return !v;  
  endmethod  
  method Bool notEmpty;  
    return v;  
  endmethod  
  method Action enq(t x);  
    v <= True; d <= x;  
  endmethod  
  method Action deq;  
    v <= False;  
  endmethod  
  method t first;  
    return d;  
  endmethod  
endmodule
```




Streaming a function

 

```
rule stream;  
  if(inQ.notEmpty && outQ.notFull)  
    begin outQ.enq(f(inQ.first)); inQ.deq; end  
endrule
```

Boolean & ("AND") operation

Streaming a module

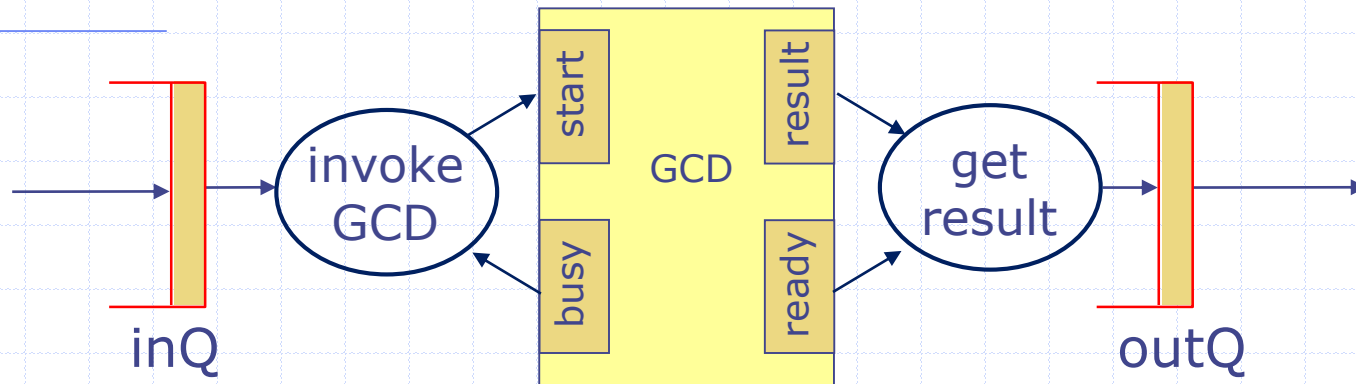


```
rule invokeGCD;
  if(inQ.notEmpty && !gcd.busy)
    begin gcd.start(inQ.first); inQ.deq; end
endrule
```

```
rule getResult;
  if(outQ.notFull && gcd.ready)
    begin x <- gcd.result; outQ.enq(x); end
endrule
```

Action value method

Switch

 red messages go into redQ, green into greenQ




red messages go into redQ, green into greenQ

```
rule switch;  
  if (inQ.first.color == Red) begin  
    redQ.enq(inQ.first.value); inQ.deq;  
  end  
  else begin  
    greenQ.enq(inQ.first.value); inQ.deq;  
  end;  
endrule
```

The code is not correct because it does not include tests for empty inQ or full redQ or full greenQ conditions!

 
Switch with empty/full tests on queues - 1



```
rule switch;  
  if (inQ.first.color == Red) begin  
    redQ.enq(inQ.first.value); inQ.deq;  
  end  
  else begin  
    greenQ.enq(inQ.first.value); inQ.deq;  
  end  
endrule
```

first and deq operations can be performed only if inQ is not empty

 
Switch with empty/full tests on queues -2



```
rule switch;  
  if (inQ.notEmpty)  
    if (inQ.first.color == Red) begin  
      redQ.enq(inQ.first.value); inQ.deq;  
    end  
    else begin  
      greenQ.enq(inQ.first.value); inQ.deq;  
    end  
  endrule
```


When can an enq operation be performed on redQ?

Switch with empty/full tests on queues

 

```
rule switch;  
  if (inQ.notEmpty)  
    if (inQ.first.color == Red) begin1  
      if (redQ.notFull) begin2  
        redQ.enq(inQ.first.value); inQ.deq;  
      end2  
    end1  
  else begin3  
    if (greenQ.notFull) begin4  
      greenQ.enq(inQ.first.value); inQ.deq;  
    end4  
  end3  
endrule
```

A wrong optimization

 

```
rule switch;
```

```
if (inQ.notEmpty)
```

```
if (inQ.first.color == Red) begin1
```

```
if (redQ.notFull) begin2
```

```
redQ.enq(inQ.first.value); inQ.deq;
```

```
end2
```

```
end1
```

```
else begin3
```

```
if (greenQ.notFull) begin4
```

```
greenQ.enq(inQ.first.value); inQ.deq;
```

```
end4
```

```
end3
```

```
inQ.deq;
```

Can we move the deq here?

```
endrule
```

*inQ value
may get lost
if redQ (or
greenQ) is full*

**Atomicity
violation!**

Observations

- ◆ These sample programs are not very complex and yet it would have been tedious to express these programs in a state table or as a circuit directly
- ◆ The meaning of **double-write errors** is not standardized across Verilog tools
- ◆ Interface methods are not available in Verilog/VHDL