

# Bluespec-3: Architecture exploration using static elaboration


Arvind

Computer Science & Artificial Intelligence Lab  
Massachusetts Institute of Technology


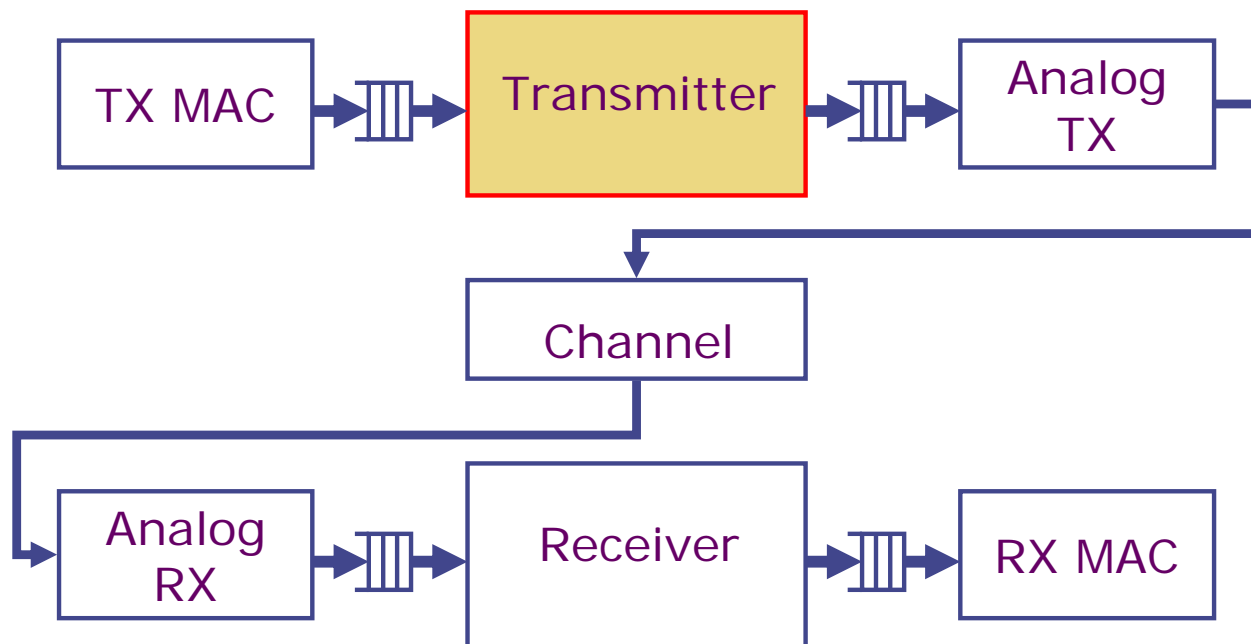
# Design a 802.11a Transmitter

- ◆ 802.11a is an IEEE Standard for wireless communication
- ◆ Frequency of Operation: 5Ghz band
- ◆ Modulation: Orthogonal Frequency Division Multiplexing (OFDM)




# Nomenclature

- ◆ Base data unit of the system: 24 uncoded bits
- ◆ Sample – One complex baseband value
- ◆ Symbol – One OFDM symbol that will be transmitted
  - In time domain: 64 Samples long
  - In frequency domain: 64 Tones (48 data, 4 pilot, 12 unused)
  - Represented in fixed point (16 bit real, 16 bit imag)
- ◆ Frame - A unit of data, corresponds to:
  - 1 Symbol at 6 Mbps (i.e. 1 frame represents one symbol)
  - $\frac{1}{2}$  Symbol at 12 Mbps (i.e. 2 frames represent one symbol)
  - $\frac{1}{4}$  Symbol at 24 Mbps (i.e. 4 frames represent one symbol)
- ◆ Message – A sequence of data Symbols preceded by a header Symbol (SIGNAL)

# Need Fixed Point Arithmetic

- ◆ Floating point is too inefficient to use
- ◆ We need to represent fractional values between -1 and 1 in our system
- ◆ Fixed Point: use a 16 bit integer to represent each value
  - Store the value multiplied by  $2^{15}$  (32,768)
  - Use 2's compliment arithmetic on fixed point values, but watch for overflow
  - MSB indicates sign of number (1 for negative)
- ◆ Examples:
  - 1.0       => 0x8000    (-32768)
  - $1/\sqrt{2}$     => 0x5a82    ( 23170)
  - $-3/\sqrt{10}$  => 0x8692    (-31086)

# Transmitter Overview

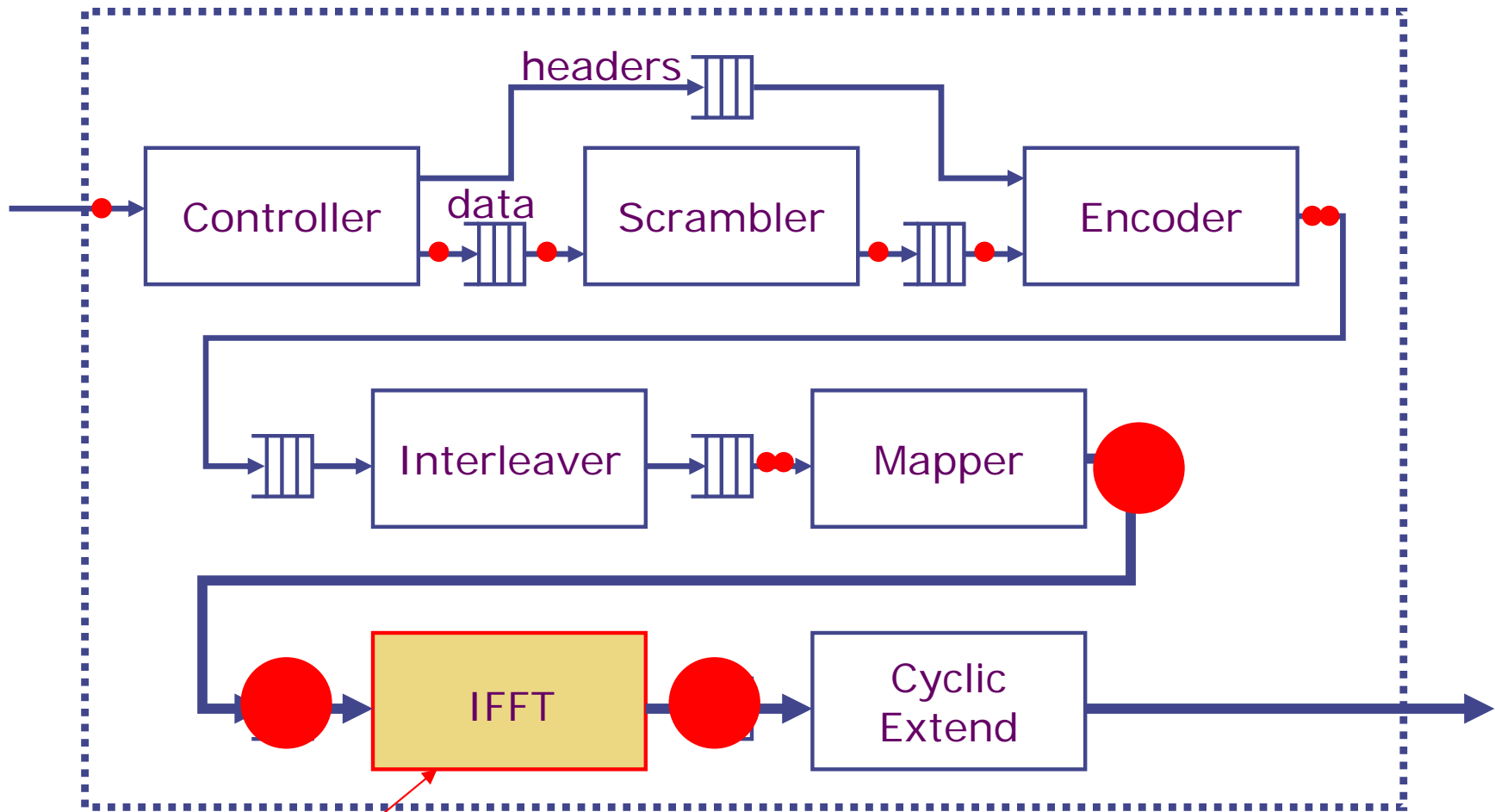

IFFT Transforms 64 (frequency domain) complex numbers into 64 (time domain) complex numbers

 compute intensive


# Mapper

- ◆ Maps incoming data to tones based on rate
- ◆ Outputs 1 OFDM symbol to the IFFT
- ◆ Depending on the rate, 48, 96, or 192 bits of input may be required to fill one symbol.

Input: [rate (2), data (48)]

Output: [data (64 complex numbers)]

# Receiver Overview

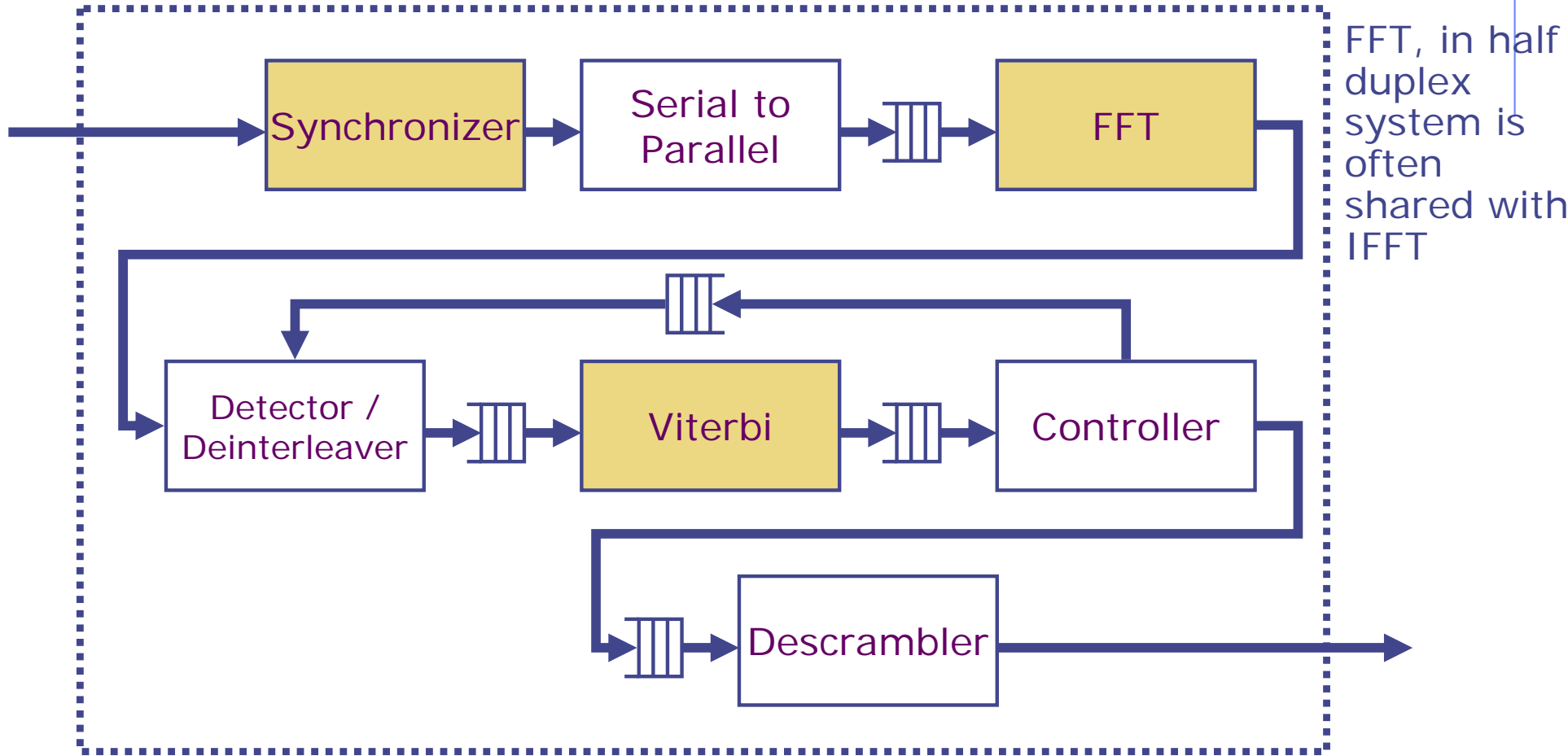

 compute intensive

# Synchronizer

- ◆ Performs two important tasks:
  - Timing estimation and synchronization
    - ◆ Decides when a new message is present
    - ◆ Tells rest of receiver at which sample the incoming symbol starts
  - Frequency offset estimation and correction
    - ◆ Estimates the offset of the transmitter and receiver clocks
    - ◆ Rotates input data to correct for this offset

*Extremely complicated !*



# Viterbi Decoder

- ◆ Uses the Viterbi algorithm to decode convolutionally encoded symbols
- ◆ Requires three 48-bit inputs to perform sufficient traceback
  - Will only output a frame after it receives the two subsequent frames
  - Detector flushes the Viterbi module with zeros after header and end of message


# IFFT Requirements

- ◆ 802.11a needs to process a symbol in 4  $\mu$ sec (250KHz)
  - IFFT must output a symbol every 4  $\mu$ sec
    - ◆ i.e. perform an Inverse FFT of 64 complex numbers
  - Each module before IFFT must process every 4  $\mu$ sec
    - ◆ 1 frame for 6Mbps rate
    - ◆ 2 frames for 12Mbps rate
    - ◆ 4 frames for 24Mbps rate
  - Even in the worst case (24Mbps) the clock frequency can be as low as 1Mhz.

But what about the area & power?

 
# Area-Frequency Tradeoff

We can decrease the area by multiplexing some circuits and running the system at a higher frequency




Reuse


Twice the frequency  
but half the area

 

# Combinational IFFT

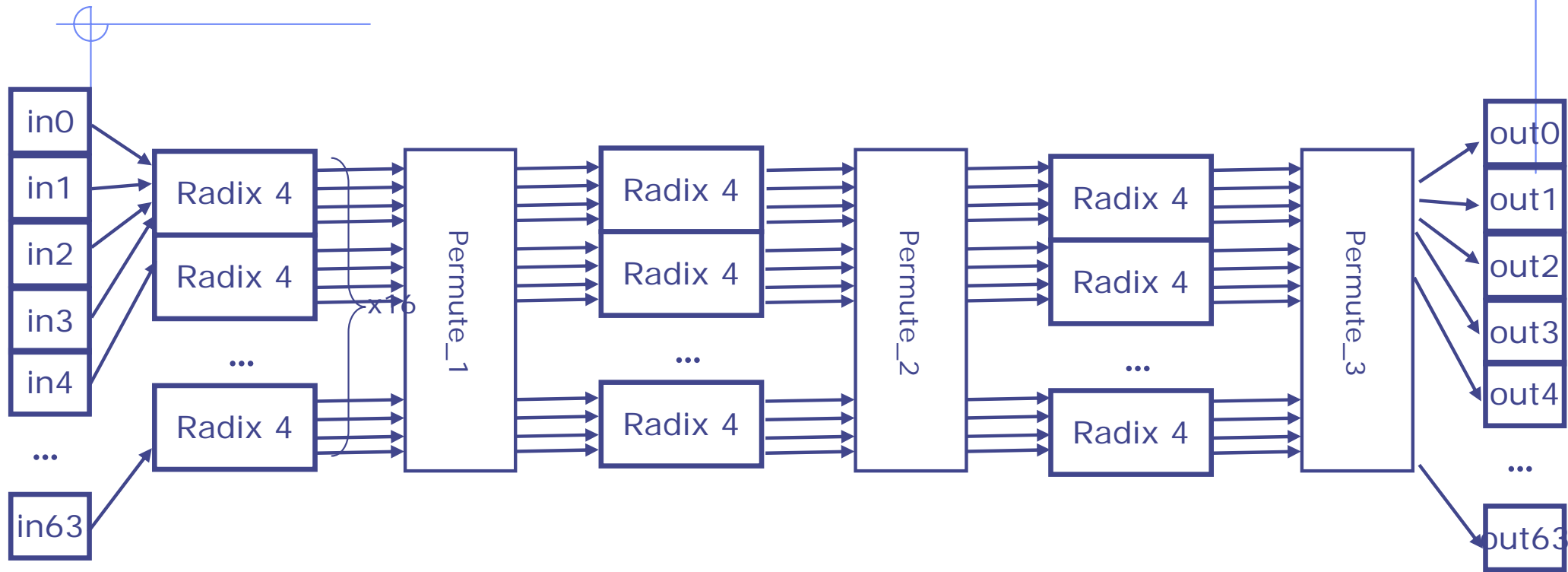

# Radix-4 Node

 

# Bluespec code: Radix-4 Node

```
function Tuple4#(Complex, Complex, Complex, Complex)
    radix4(Tuple4#(Complex, Complex, Complex, Complex) twids,
           Complex k0, Complex k1, Complex k2, Complex k3);

match {.t0, .t1, .t2, .t3} = twids;
Complex m0 = k0 * t0; Complex m1 = k1 * t1;
Complex m2 = k2 * t2; Complex m3 = k3 * t3;

Complex y0 = m0 + m2; Complex y1 = m0 - m2;
Complex y2 = m1 + m3; Complex y3 = m1 - m3;

Complex y3_j = Complex {i: negate(y3.q), q: y3.i};

Complex z0 = y0 + y2; Complex z1 = y1 - y3_j;
Complex z2 = y0 - y2; Complex z3 = y1 - y3_j;

return tuple4(z0, z1, z2, z3);

endfunction
```

# Bluespec code for pure Combinational Circuit


```
function SVector#(64, Complex) ifft (SVector#(64, Complex) in_data);
//Declare vectors
  SVector#(64, Complex) stage12_data = newSVector();
  SVector#(64, Complex) stage12_permuted = newSVector();
  SVector#(64, Complex) stage12_out = newSVector();
  SVector#(64, Complex) stage23_data = newSVector();
  ...
//Radix 4 stage 1 (unpermuted)
  for (Integer i = 0; i < 16; i = i + 1)
  begin
    Integer idx = i * 4;
    let twiddle0 = getTwiddle(0, fromInteger(i));
    match {.y0, .y1, .y2, .y3} = radix4(twiddle0,
                                        in_data[idx], in_data[idx + 1],
                                        in_data[idx + 2], in_data[idx + 3]);
    stage12_data[idx] = y0;    stage12_data[idx + 1] = y1;
    stage12_data[idx + 2] = y2; stage12_data[idx + 3] = y3;
  end
//Stage 1 permutation
  for (Integer i = 0; i < 64; i = i + 1)
    stage12_permuted[i] = stage12_data[permute_1to2[i]];
//Continued on next slide...
```

# Bluespec code for pure Combinational Circuit *continued*

```
// (* continued from previous *)
stage12_out = stage12_permuted; //Later implementations will change this
//Radix 4 stage 2 (unpermuted)
for (Integer i = 0; i < 16; i = i + 1)
begin
  Integer idx = i * 4;
  let twidl = getTwiddle(1, fromInteger(i));
  match {.y0, .y1, .y2, .y3} = radix4(twidl,
                                     stage12_out[idx], stage12_out[idx + 1],
                                     stage12_out[idx + 2], stage12_out[idx + 3]);
  stage23_data[idx] = y0;      stage23_data[idx + 1] = y1;
  stage23_data[idx + 2] = y2; stage23_data[idx + 3] = y3;
end
//Stage 2 permutation
for (Integer i = 0; i < 64; i = i + 1)
  stage23_permuted[i] = stage23_data[permute64_2to3[i]];
...
//Repeat for Stage 3
...
return stage3out_permuted;
endfunction
```



# Pipelined IFFT

 

Put a register to hold 64 complex numbers at the output of each stage.

Even more hardware but clock can go faster – less combinational circuitry between two stages

# Bluespec code for Pipeline Stage

```
module mkIFFT_Pipelined() (I_IFFT);
  //Declare vectors
  SVector#(64, Complex) in_data;
  SVector#(64, Complex) stage12_data = newSVector();
  ...
  //Declare FIFOs
  FIFO#(SVector#(64, Complex)) in_fifo <- mkFIFO();
  //Declare pipeline registers
  Reg#(SVector#(64, Complex)) stage12_reg <- mkReg(newSVector());
  Reg#(SVector#(64, Complex)) stage23_reg <- mkReg(newSVector());
  //Read input
  in_data = in_fifo.first();
  //Radix 4 stage 1 (unpermuted)
  for (Integer i = 0; i < 16; i = i + 1)
  begin
    Integer idx = i * 4;
    let twid0 = getTwiddle(0, fromInteger(i));
    match {.y0, .y1, .y2, .y3} = radix4(twid0,
                                         in_data[idx], in_data[idx + 1],
                                         in_data[idx + 2], in_data[idx + 3]);
  end
  //Continue as before...
```

# Bluespec code for Pipeline Stage

```
...
//Read from pipe register for stage 2
stage12_out = stage12_reg;

//Radix 4 stage 2 (unpermuted)
for (Integer i = 0; i < 16; i = i + 1)
...


//Read from pipe register for stage 3
stage23_out = stage23_reg;

rule writeRegs (True);
    stage12_reg <= stage12_permuted;
    stage23_reg <= stage23_permuted;
    in_fifo.deq(); out_fifo.enq(stage3out_permuted);
endrule

method Action inp (Vector#(64, Complex) data);
    in_fifo.enq(data);
endmethod

...
endmodule
```
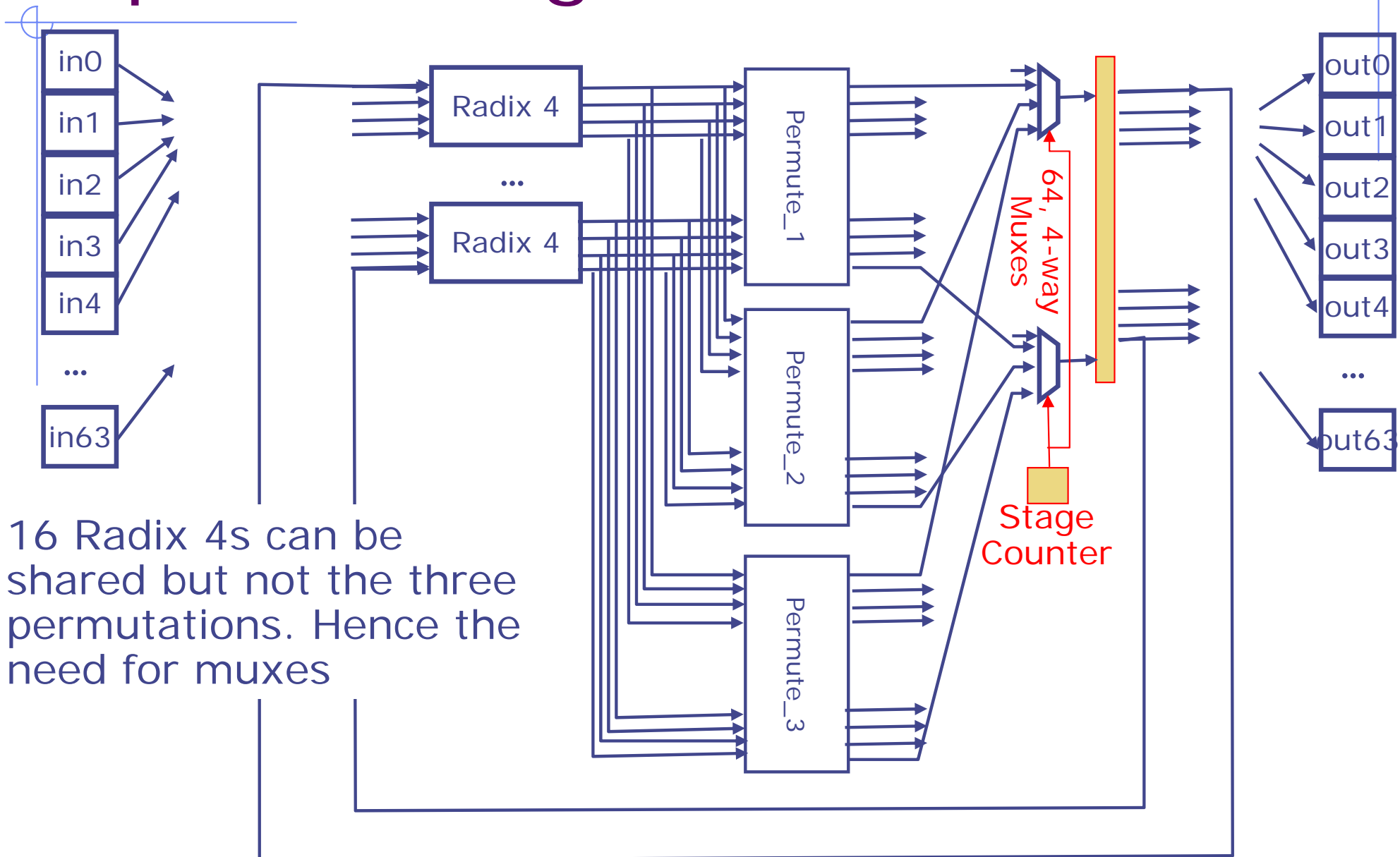
# Circular pipeline: Reusing the Pipeline Stage



16 Radix 4s can be shared but not the three permutations. Hence the need for muxes

# Bluespec Code for Circular Pipeline

```
module mkIFFT_Circular (I_IFFT);
  SVector#(64, Complex) in_data = newSVector();
  SVector#(64, Complex) stage_data = newSVector();
  SVector#(64, Complex) stage_permuted = newSVector();
  //State elements
  Reg#(SVector#(64, Complex)) data_reg <- mkReg(newSVector());
  Reg#(Bit#(2)) stage_counter <- mkReg(0);
  FIFO#(SVector#(64, Complex)) in_fifo <- mkFIFO();
  //Read input
  in_data = data_reg;
  //Perform a single Radix 4 stage (unpermuted)
  for (Integer i = 0; i < 16; i = i + 1)
  begin
    Integer idx = i * 4;
    let twiddle = getTwiddle(stage_counter, fromInteger(i));
    match {.y0, .y1, .y2, .y3} = radix4(twiddle,
                                         in_data[idx], in_data[idx + 1],
                                         in_data[idx + 2], in_data[idx + 3]);
    stage_data[idx] = y0;      stage_data[idx + 1] = y1;
    stage_data[idx + 2] = y2; stage_data[idx + 3] = y3;
  end
  //Continued...
```

# Bluespec Code for Circular Pipeline


```
//Stage permutation
  for (Integer i = 0; i < 64; i = i + 1)
    stage_permuted[i] = case (stage_counter)
      0: return in_wire._read[i];
      1: return stage_data[permute64_1to2[i]];
      2: return stage_data[permute64_2to3[i]];
      3: return stage_data[permute64_3toOut[i]];
    endcase;

  rule writeRegs (True);
    data_reg <= stage_permuted;
    stage_counter <= stage_counter + 1;
  endrule

  method Action inp(SVector#(64, Complex) data) if (stage_counter == 0);
    in_fifo.enq(data);
    stage_counter <= 1;
  endmethod

  ...
endmodule
```

# Just one Radix-4 node!

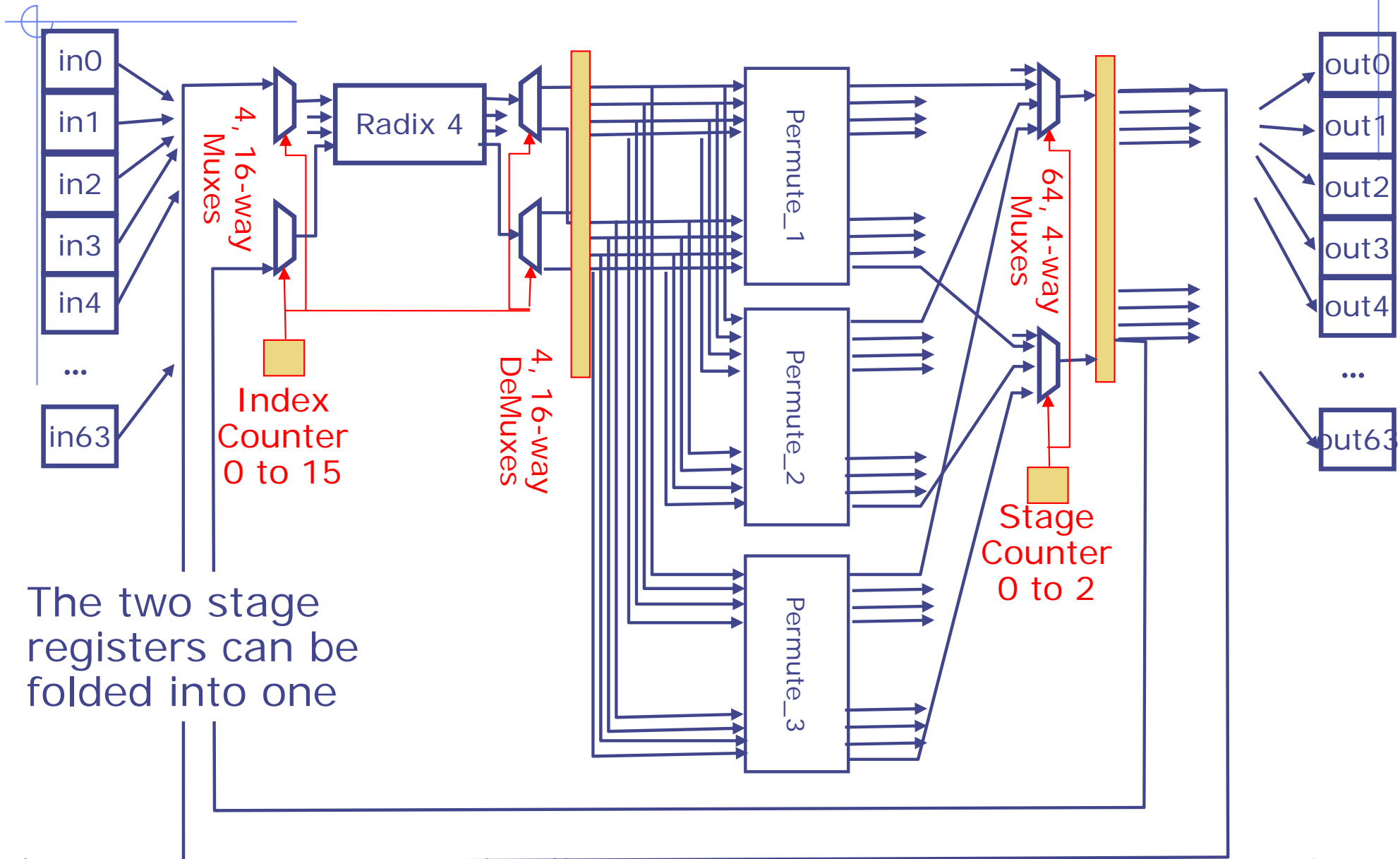

The two stage registers can be folded into one

# Bluespec Code for Extreme Reuse

```
module mkIFFT_SuperCircular (I_IFFT);
  SVector#(64, Complex) new_post_reg = newSVector();
//State
  Reg#(SVector#(64, Complex)) data_reg <- mkReg(newSVector());
  Reg#(SVector#(64, Complex)) post_reg <- mkReg(newSVector());
  Reg#(Bit#(2)) stage_counter <- mkReg(0); //Stage Counter =0 => no value
  Reg#(Bit#(5)) idx_counter <- mkReg(16); //Idx_Counter =16 => permute
  FIFO#(SVector#(64, Complex)) in_fifo <- mkFIFO();

  let twid = getTwiddle(stage_counter, idx_counter);
  match {.y0, .y1, .y2, .y3} =
    radix4(twid, select(in_data, {idx_counter, 2'b00}),
           select(in_data, {idx_counter, 2'b01}),
           select(in_data, {idx_counter, 2'b01}),
           select(in_data, {idx_counter, 2'b10}));
//Permutation takes post_reg's values back to data_reg
  for (Integer i = 0; i < 64; i = i + 1)
    permutedV[i] = case (stage_counter)
      1: return post_reg[permute64_1to2[i]];
      2: return post_reg[permute64_2to3[i]];
      3: return post_reg[permute64_3toOut[i]];
      default: return in_fifo.first()[i];
    endcase;
endmodule
```



# Bluespec Code for Extreme Reuse-2


```
rule doRadix(stage_counter != 0);
  if (idx_counter < 16) //We need to calc new radix values
    begin
      //generates new_post_reg value: post_reg after writing in the
4 new values
      let stage_data0 = post_reg;
      let stage_data1 = update(stage_data, idx, y0);
      let stage_data2 = update(stage_data1,idx + 1, y1);
      let stage_data3 = update(stage_data2,idx + 2, y2);
      new_post_reg     = update(stage_data3,idx + 3, y3);
      post_reg <= new_post_reg;
    end
  else  //(idx_counter == 16) We need to permute
    begin
      data_reg <= premutedV;
    end

  //We always increment counters
  idx_counter <= (idx_counter == 16) ? 0: idx_counter + 1;
  if (idx_counter == 16)
    stage_counter <= stage_counter + 1;
endrule
//Everything else as before...
```

# Synthesis results

- ◆ Did not have time to synthesize these various designs
- ◆ But we have results from a term project from last year
  - Steve Gerding, Elizabeth Basha & Rose Liu

# IFFT Initial Design

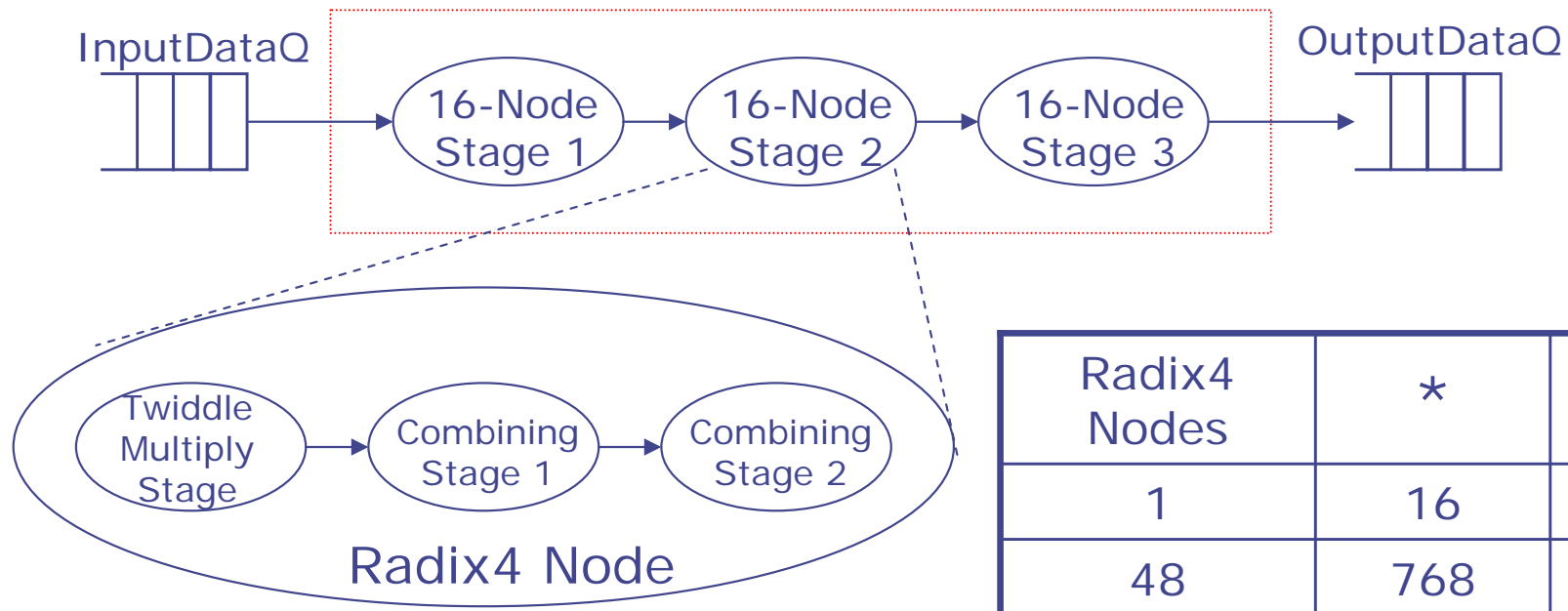


Radix4 Nodes	*	+
1	16	24
48	768	1152

- ◆ Area =  $29.12\mu\text{m}^2$
- ◆ Cycle Time = 63.18ns
- ◆ Throughput = 1 Symbol / 63.18ns

Steve Gerding, Elizabeth Basha & Rose Liu


# IFFT Initial Design

 

- ◆ Area =  $29.12\mu\text{m}^2$
- ◆ Cycle Time = 63.18ns
- ◆ Throughput = 1 Symbol / 63.18ns

Steve Gerding, Elizabeth Basha & Rose Liu


# IFFT Design Exploration 1

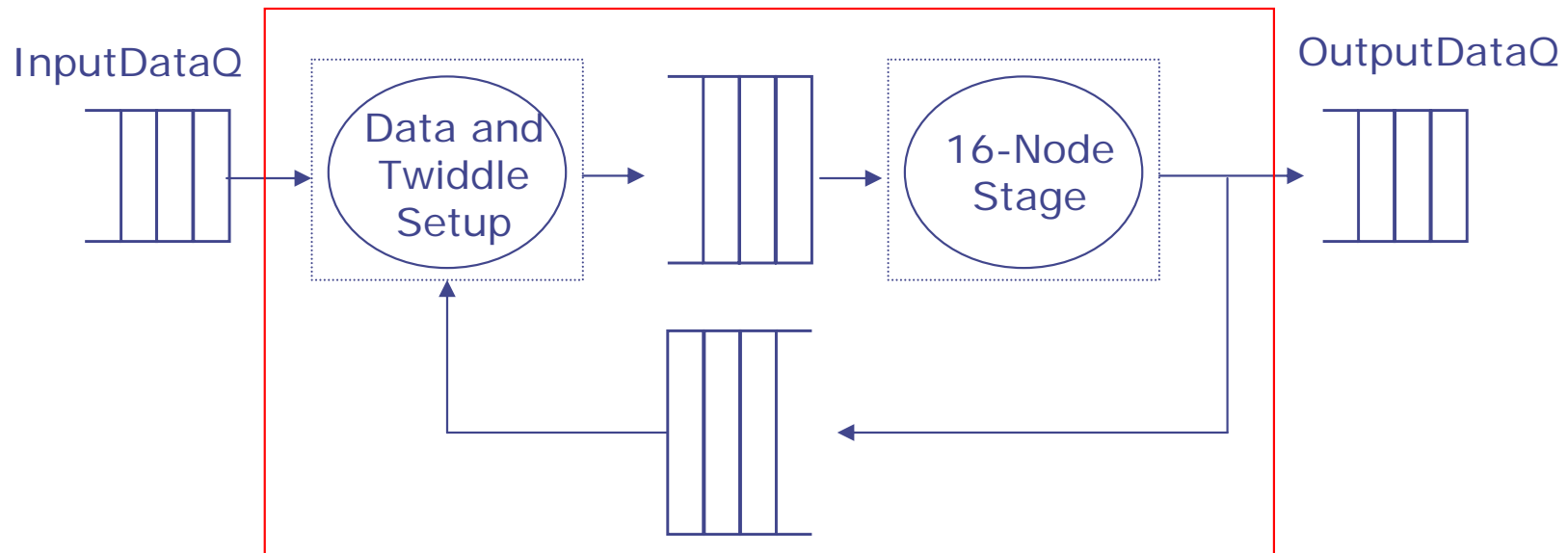

- ◆ Area =  $5.19\mu\text{m}^2$
- ◆ Cycle Time = 30.50ns
- ◆ Throughput = 1 Symbol /  $3 \times 30.50\text{ns}$   
= 1 Symbol / 91.50ns

Steve Gerding, Elizabeth Basha & Rose Liu

# IFFT Design Exploration 2

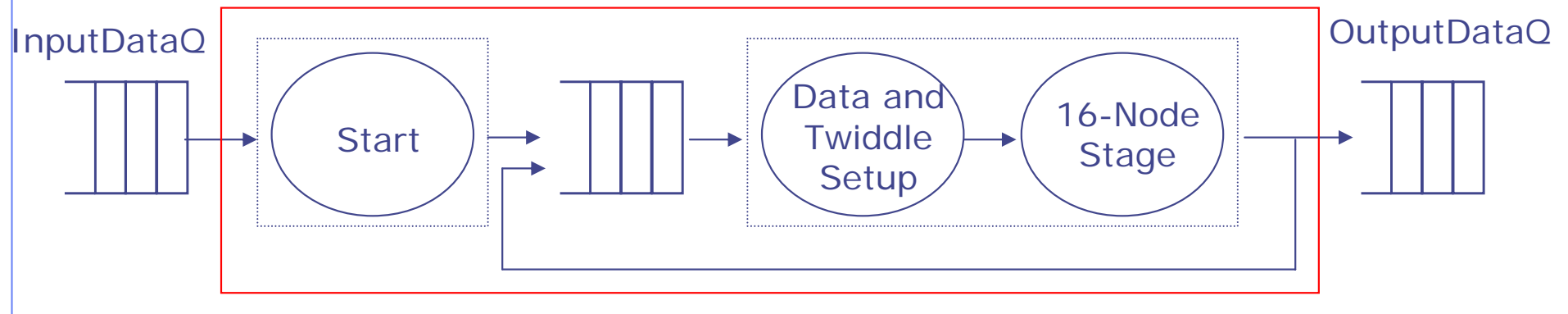

- ◆ Area = 4.57mm<sup>2</sup>
- ◆ Cycle Time = 32.89ns
- ◆ Throughput = 1 symbol / 3x 32.89ns  
= 1 symbol / 98.67ns