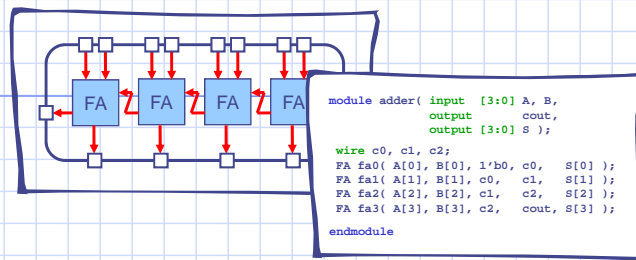


# Verilog 1 - Fundamentals




6.375 Complex Digital Systems

Arvind

February 8, 2007

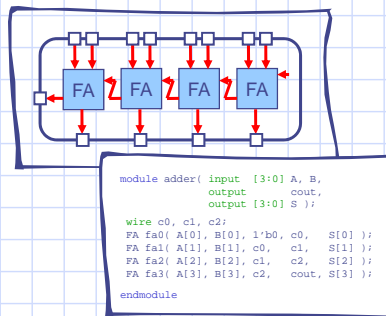
# Verilog Fundamentals

- ◆ History of hardware design languages
- ◆ Data types
- ◆ Structural Verilog
- ◆ Simple behaviors



# Originally designers used breadboards for prototyping


Solderless Breadboard

 

[ranger3011.net/electronics/breadboard.html](http://ranger3011.net/electronics/breadboard.html)

No symbolic execution or testing

Printed circuit board

 


[home.cogeco.ca](http://home.cogeco.ca)

Number of Gates in Design




# HDLs enabled logic level simulation and testing

Gate Level Description

 


Number of Gates in Design

 


HDL = Hardware Description Language

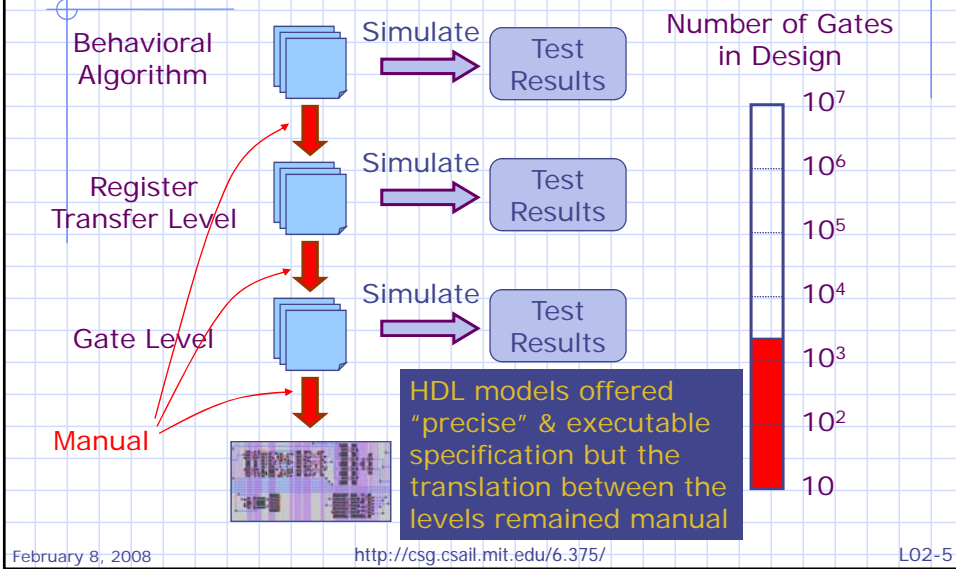
# Designers began to use HDLs for higher level design



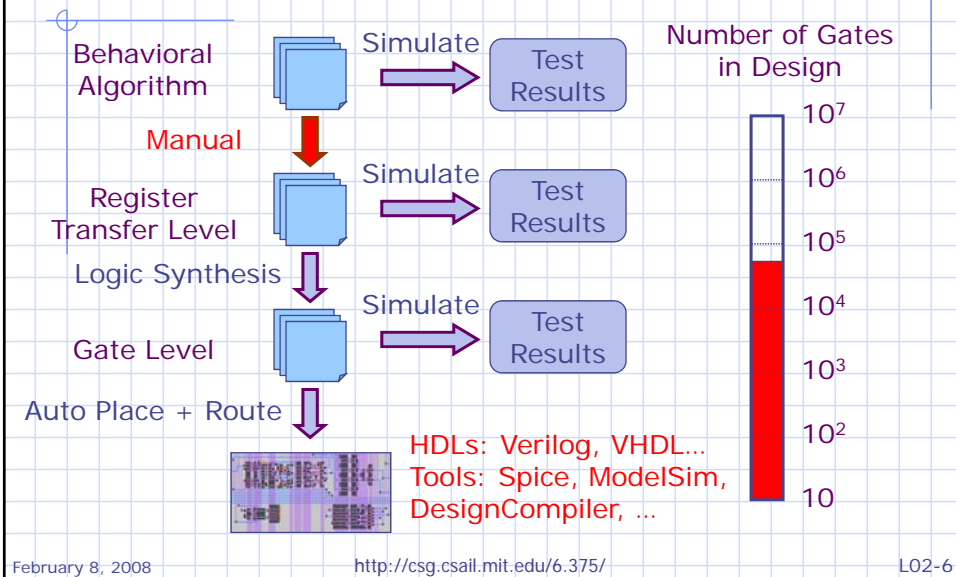
# HDLs led to tools for automatic translation



# Raising the abstraction further ...

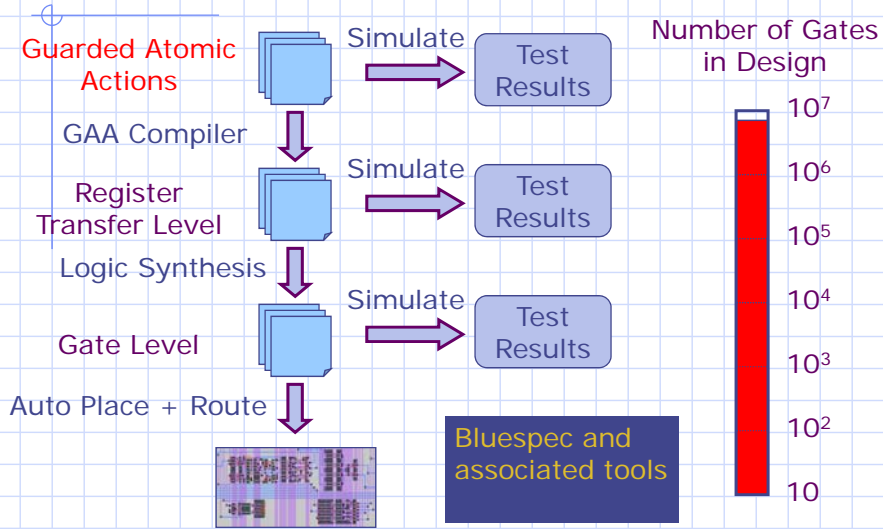

# The current situation

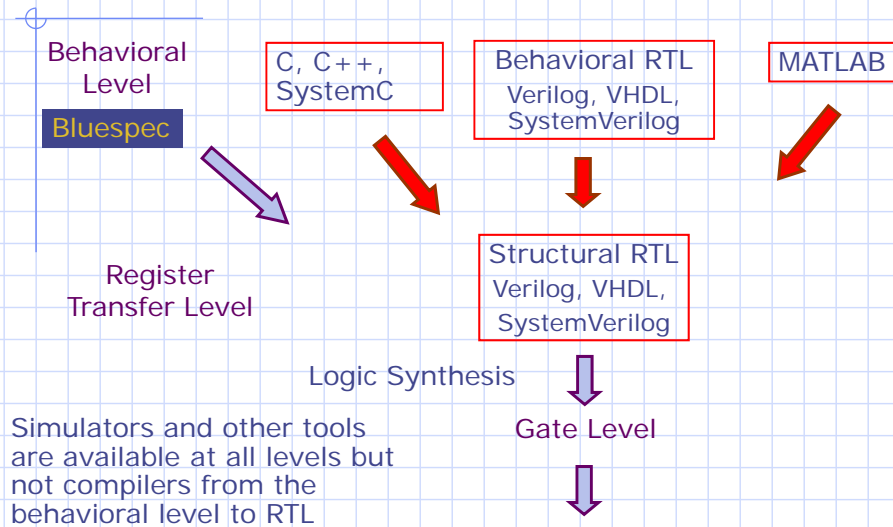


# Common misconceptions

- ◆ Behavioral Languages = C
- ◆ RTL languages are necessarily lower-level than behavioral languages
  - Yes- in the sense that C or SystemC is farther away from hardware
  - No- in the sense that HDLs can incorporate the most advanced language ideas.

Bluespec is a modern high-level language and at the same time can describe hardware to the same level of precision as RTL
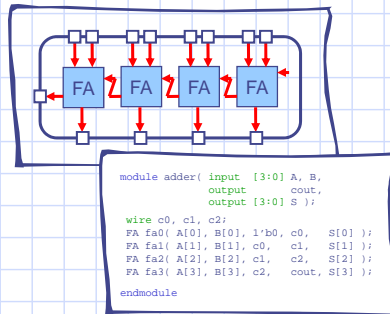
# Verilog Fundamentals

- ◆ History of hardware design languages
- ◆ Data types
- ◆ Structural Verilog
- ◆ Simple behaviors



# Bit-vector is the only data type in Verilog

A bit can take on one of four values



Value	Meaning
0	Logic zero
1	Logic one
X	Unknown logic value
Z	High impedance, floating

An X bit might be a 0, 1, Z, or in transition. We can set bits to be X in situations where we don't care what the value is. This can help catch bugs and improve synthesis quality.
  
# "wire" is used to denote a hardware net


```
wire [15:0] instruction;  
wire [15:0] memory_req;  
wire [ 7:0] small_net;
```

Absolutely no type safety when connecting nets!



# Bit literals

4'b10\_11

 


We'll learn how to actually assign literals to nets a little later


- ◆ Binary literals
  - 8'b0000\_0000
  - 8'b0xx0\_1xx1
- ◆ Hexadecimal literals
  - 32'h0a34\_def1
  - 16'haxxx
- ◆ Decimal literals
  - 32'd42
 
# Verilog Fundamentals

- ◆ History of hardware design languages
- ◆ Data types
- ◆ Structural Verilog
- ◆ Simple behaviors


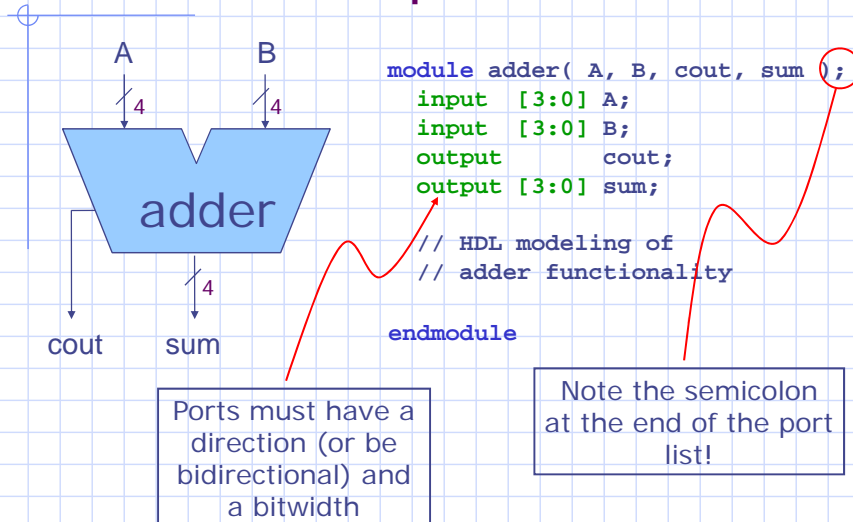
# A Verilog module has a name and a port list




February 8, 2008

<http://csg.csail.mit.edu/6.375/>

L02-15

# Alternate syntax

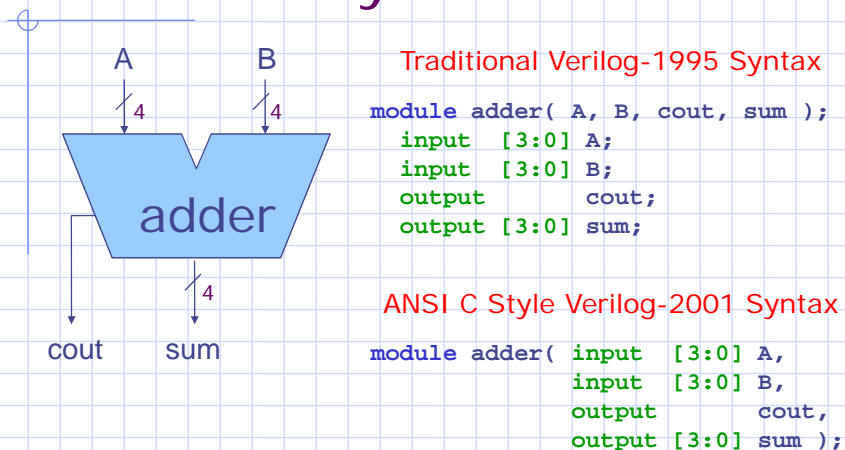


February 8, 2008

<http://csg.csail.mit.edu/6.375/>

L02-16



# A module can instantiate other modules

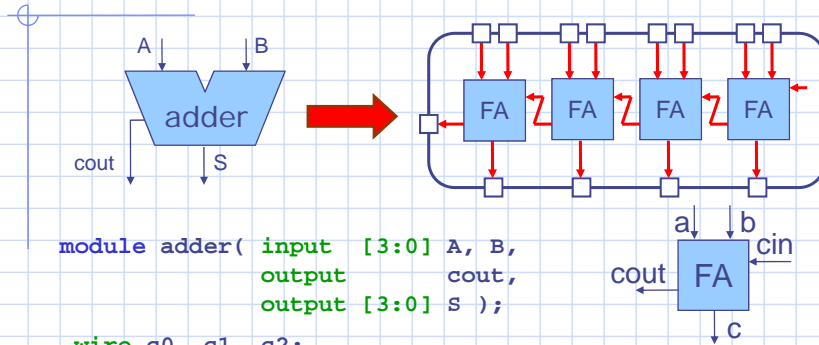

```

module adder( input  [3:0] A, B,
              output   cout,
              output  [3:0] S );

  wire c0, c1, c2;
  FA fa0( ... );
  FA fa1( ... );
  FA fa2( ... );
  FA fa3( ... );

endmodule


```

```

module FA( input  a, b, cin
          output cout, sum );
  // HDL modeling of 1 bit
  // full adder functionality
endmodule

```

# Connecting modules

 

```

module adder( input  [3:0] A, B,
              output   cout,
              output  [3:0] S );

  wire c0, c1, c2;
  FA fa0( A[0], B[0], c0, S[0] );
  FA fa1( A[1], B[1], c0, S[1] );
  FA fa2( A[2], B[2], c1, S[2] );
  FA fa3( A[3], B[3], c2, S[3] );

endmodule

```

Carry Chain

# Alternative syntax

## Connecting ports by ordered list

```
FA fa0( A[0], B[0], 1'b0, c0, S[0] );
```

## Connecting ports by name (compact)

```
FA fa0( .a(A[0]), .b(B[0]),  
        .cin(1'b0), .cout(c0), .sum(S[0]) );
```


## Connecting ports by name

```
FA fa0  
( .a    (A[0]),  
  .b    (B[0]),  
  .cin  (1'b0),  
  .cout (c0),  
  .sum  (S[0])  
);
```

For all but the smallest modules, connecting ports by name yields clearer and less buggy code.
 
# Verilog Fundamentals

- ◆ History of hardware design languages
- ◆ Data types
- ◆ Structural Verilog
- ◆ Simple behaviors




A module's behavior can be described in many different ways but it should not matter from outside

Example: mux4
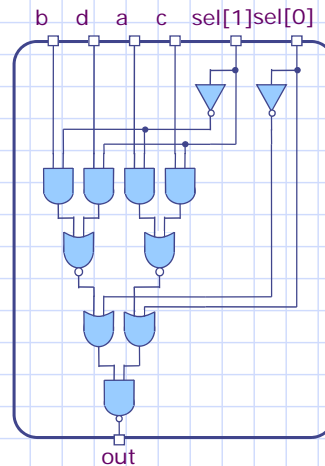
## mux4: Gate-level structural Verilog

```
module mux4( input a, b, c, d, input [1:0] sel, output out );  
    wire [1:0] sel_b;  
    not not0( sel_b[0], sel[0] );  
    not not1( sel_b[1], sel[1] );  
  
    wire n0, n1, n2, n3;  
    and and0( n0, c, sel[1] );  
    and and1( n1, a, sel_b[1] );  
    and and2( n2, d, sel[1] );  
    and and3( n3, b, sel_b[1] );  
  
    wire x0, x1;  
    nor nor0( x0, n0, n1 );  
    nor nor1( x1, n2, n3 );  
  
    wire y0, y1;  
    or or0( y0, x0, sel[0] );  
    or or1( y1, x1, sel_b[0] );  
    nand nand0( out, y0, y1 );  
  
endmodule
```



## mux4: Using continuous assignments

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

  wire out, t0, t1;
  assign t0 = ~( (sel[1] & c) | (~sel[1] & a) );
  assign t1 = ~( (sel[1] & d) | (~sel[1] & b) );
  assign out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );

endmodule
```

Language defined operators

The order of these continuous assignment statements does not matter.  
They essentially happen in parallel!

## mux4: Behavioral style

```
// Four input multiplexer
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

  assign out = ( sel == 0 ) ? a :
               ( sel == 1 ) ? b :
               ( sel == 2 ) ? c :
               ( sel == 3 ) ? d : 1'bx;

endmodule
```

If input is undefined we want to propagate that information.

## mux4: Using “always block”

```
module mux4( input a, b, c, d
             input [1:0] sel,
             output out );

    reg out, t0, t1;

    always @( a or b or c or d or sel )
    begin
        t0 = ~( (sel[1] & c) | (~sel[1] & a) );
        t1 = ~( (sel[1] & d) | (~sel[1] & b) );
        out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    end

endmodule
```

Motivated by simulation

The order of these procedural assignment statements does matter. They essentially happen sequentially!

## “Always blocks” permit more advanced sequential idioms

```
module mux4( input a, b, c, d
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        if ( sel == 2'd0 )
            out = a;
        else if ( sel == 2'd1 )
            out = b;
        else if ( sel == 2'd2 )
            out = c;
        else if ( sel == 2'd3 )
            out = d;
        else
            out = 1'bx;
    end

endmodule
```

```
module mux4( input a, b, c, d
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
            2'd3 : out = d;
            default : out = 1'bx;
        endcase
    end

endmodule
```

Typically we will use always blocks only to describe sequential circuits

## What happens if the case statement is not complete?

```
module mux3( input a, b, c
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
        endcase
    end
endmodule
```

If sel = 3, mux will output  
the previous value.  
What have we created?

## What happens if the case statement is not complete?

```
module mux3( input a, b, c
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
            default : out = 1'bx;
        endcase
    end
endmodule
```

We can prevent creating  
state with a default  
statement

## Parameterized mux4

```
module mux4 #( parameter WIDTH = 1 )
    ( input[WIDTH-1:0] a, b, c, d
      input [1:0] sel,
      output[WIDTH-1:0] out );

    wire [WIDTH-1:0] out, t0, t1;

    assign t0 = (sel[1]? c : a);
    assign t1 = (sel[1]? d : b);
    assign out = (sel[0]? t0 : t1);
endmodule
```

default value

Parameterization is a good practice for reusable modules

### Instantiation Syntax


```
mux4#(32) alu_mux
(
    .a (op1),
    .b (op2),
    .c (op3),
    .d (op4),
    .sel (alu_mux_sel),
    .out (alu_mux_out)
);
```

## Verilog Registers "reg"


- ◆ Wires are line names – they do not represent storage and can be assigned only once
- ◆ Regs are imperative variables (as in C):
  - "nonblocking" assignment  $r \leq v$
  - can be assigned multiple times and holds values between assignments
 
# flip-flops

```
module FF0 (input clk, input d,
            output reg q);
always @(posedge clk)
begin
    q <= d;
end
endmodule
```



 
```
module FF (input clk, input d,
            input en, output reg q);
always @(posedge clk)
begin
    if (en)
        q <= d;
end
endmodule
```



# flip-flops with reset

```
always @(posedge clk)
begin
    if (~resetN)
        Q <= 0;
    else if (enable)
        Q <= D;
end
```

synchronous reset

 

```
always @(posedge clk or
         negedge resetN)
begin
    if (~resetN)
        Q <= 0;
    else if (enable)
        Q <= D;
end
```

asynchronous reset

What is the difference?



## Latches versus flip-flops

```
module latch
(
  input  clk,
  input  d,
  output reg q
);

always @( clk or d )
begin
  if ( clk )
    q <= d;
end
endmodule

module flipflop
(
  input  clk,
  input  d,
  output reg q
);

always @( posedge clk )
begin
  q <= d;
end
endmodule
```

Edge-triggered  
always block

## Register

```
module register#(parameter WIDTH = 1)
(
  input  clk,
  input  [WIDTH-1:0] d,
  input  en,
  output [WIDTH-1:0] q
);

always @( posedge clk )
begin
  if (en)
    q <= d;
end
endmodule
```

# Register in terms of Flipflops

```
module register2
(
  input  clk,
  input  [1:0] d,
  input  en,
  output [1:0] q
);

always @( posedge clk )
begin
  if (en)
    q <= d;
end
endmodule
```

```
module register2
(
  input  clk,
  input  [1:0] d,
  input  en,
  output [1:0] q
);

FF ff0 (.clk(clk), .d(d[0]), .en(en),
        .q(q[0]));

FF ff1 (.clk(clk), .d(d[1]), .en(en),
        .q(q[1]));

endmodule
```

Do they behave the same?

yes

# Static Elaboration: Generate

```
module register#(parameter WIDTH = 1)
(
  input  clk,
  input  [WIDTH-1:0] d,
  input  en,
  output [WIDTH-1:0] q
);

  genvar i;
  generate
  for (i = 0; i < WIDTH; i = i + 1)
  begin: regE
    FF ff(.clk(clk), .d(d[i]), .en(en), .q(q[i]));
  end
  endgenerate
endmodule
```

genvars disappear after static elaboration

Generated names will have regE[i]. prefix

# Three abstraction levels for functional descriptions

