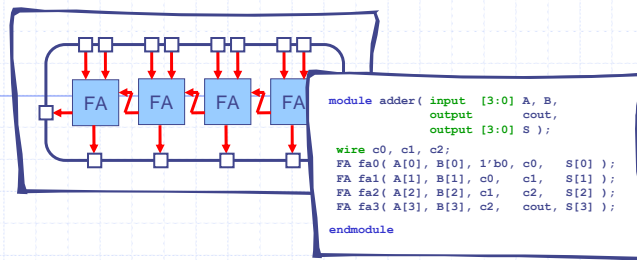


Verilog 1 - Fundamentals



6.375 Complex Digital Systems

Arvind

February 6, 2009


February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-1

Verilog Fundamentals

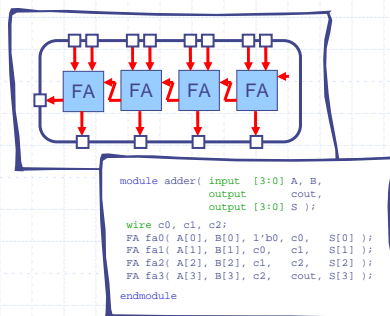- ◆ History of hardware design languages
- ◆ Data types
- ◆ Structural Verilog
- ◆ Simple behaviors




February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-2

Originally designers used breadboards for prototyping


Solderless Breadboard

 

langentsoft.net/elec/breadboard.html

No symbolic execution or testing

Printed circuit board

 

home.cogeco.ca

Number of Gates in Design




February 6, 2009

<http://csg.csail.mit.edu/6.375/>


L02-3

HDLs enabled logic level simulation and testing

Gate Level Description

 

Number of Gates in Design

 


HDL = Hardware Description Language

February 6, 2009


<http://csg.csail.mit.edu/6.375/>

L02-4

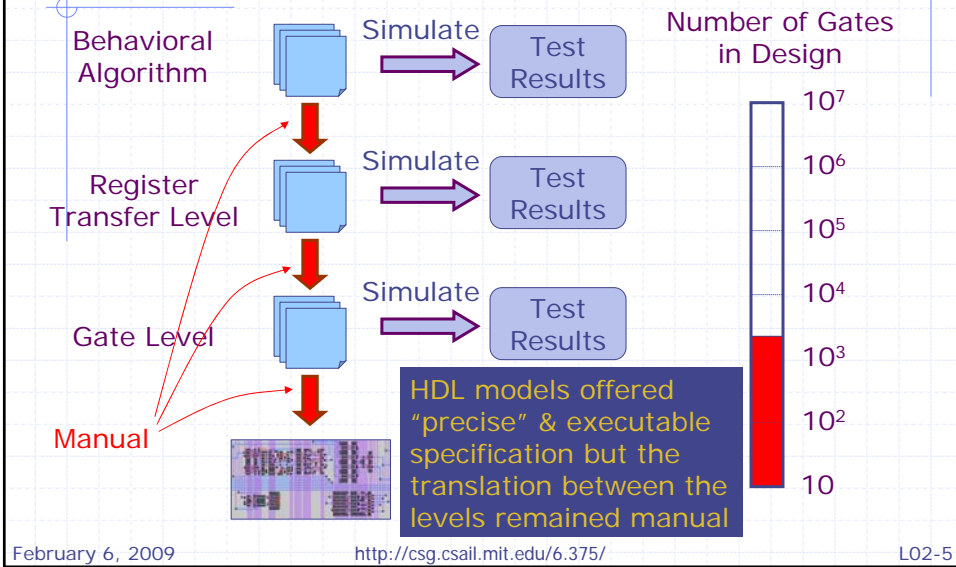
Designers began to use HDLs for higher level design



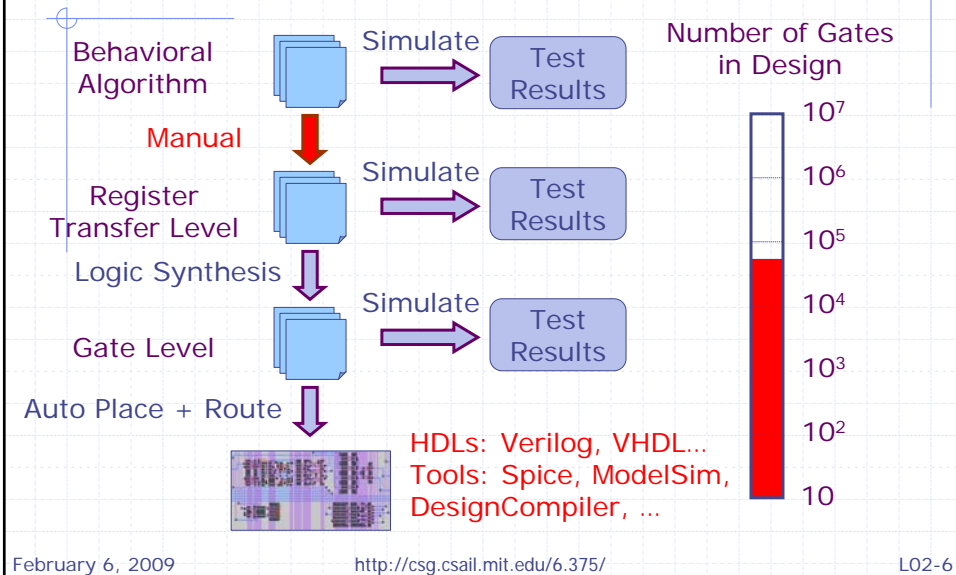HDLs led to tools for automatic translation



Raising the abstraction further ...

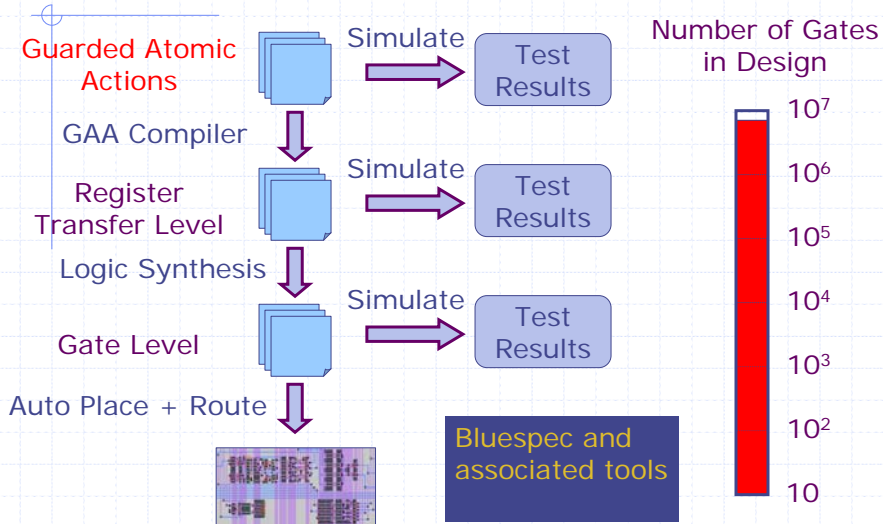


February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-7

The current situation

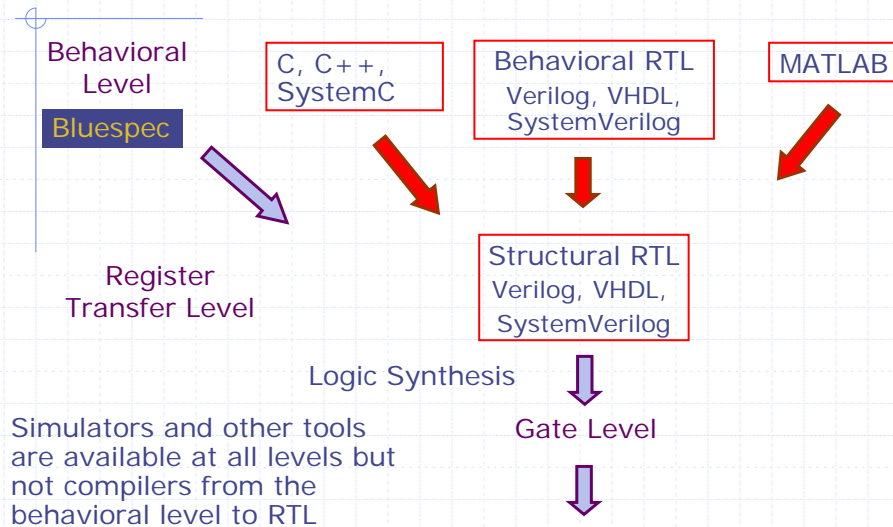

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-8


Common misconceptions

- ◆ The only behavioural languages are C, C++
- ◆ RTL languages are necessarily lower-level than behavioral languages
 - Yes- in the sense that C or SystemC is farther away from hardware
 - No- in the sense that HDLs can incorporate the most advanced language ideas.

Bluespec is a modern high-level language and at the same time can describe hardware to the same level of precision as RTL

Verilog Fundamentals

 - ◆ History of hardware design languages
- ◆ Data types
- ◆ Structural Verilog
- ◆ Simple behaviors



Bit-vector is the only data type in Verilog

A bit can take on one of four values

Value	Meaning
0	Logic zero
1	Logic one
X	Unknown logic value
Z	High impedance, floating

An X bit might be a 0, 1, Z, or in transition. We can set bits to be X in situations where we don't care what the value is. This can help catch bugs and improve synthesis quality.

February 6, 2009



<http://csg.csail.mit.edu/6.375/>

L02-11

"wire" is used to denote a hardware net

```
wire [15:0] instruction;  
wire [15:0] memory_req;  
wire [ 7:0] small_net;
```

  Absolutely no type safety when connecting nets!




February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-12

Bit literals

4'b10_11

 


We'll learn how to actually assign literals to nets a little later


- ◆ Binary literals
 - 8'b0000_0000
 - 8'b0xx0_1xx1
- ◆ Hexadecimal literals
 - 32'h0a34_def1
 - 16'haxxx
- ◆ Decimal literals
 - 32'd42

Verilog Fundamentals

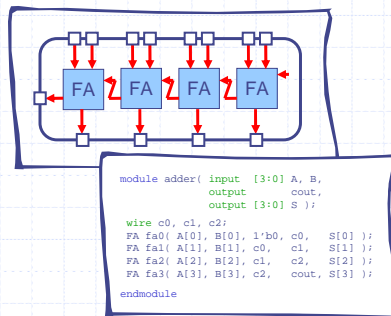- ◆ History of hardware design languages
- ◆ Data types
- ◆ Structural Verilog
- ◆ Simple behaviors



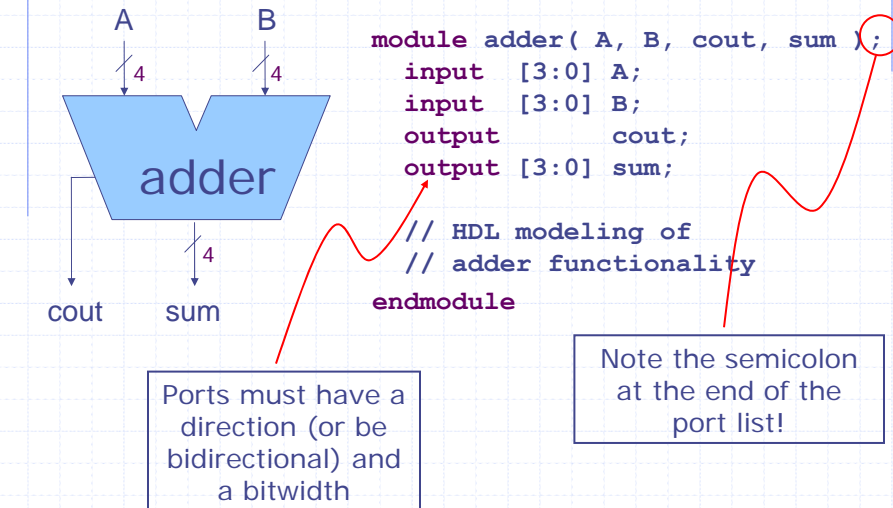A Verilog module has a name and a port list




February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-15

Alternate syntax

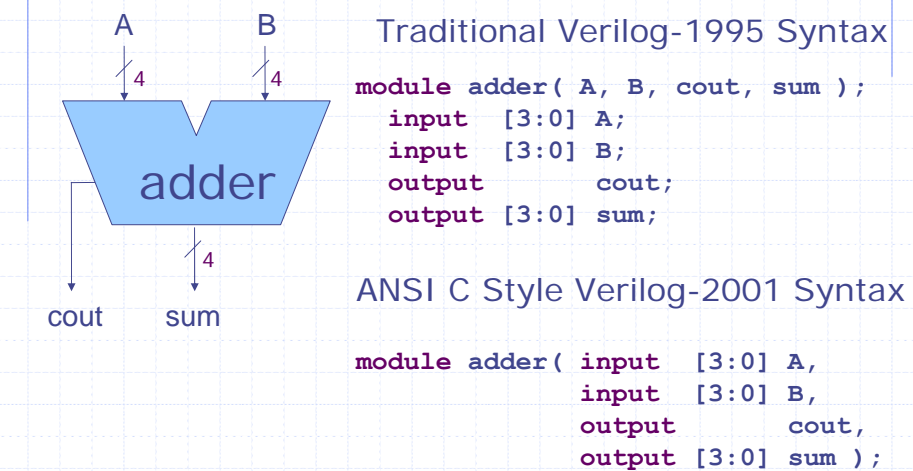


February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-16

A module can instantiate other modules

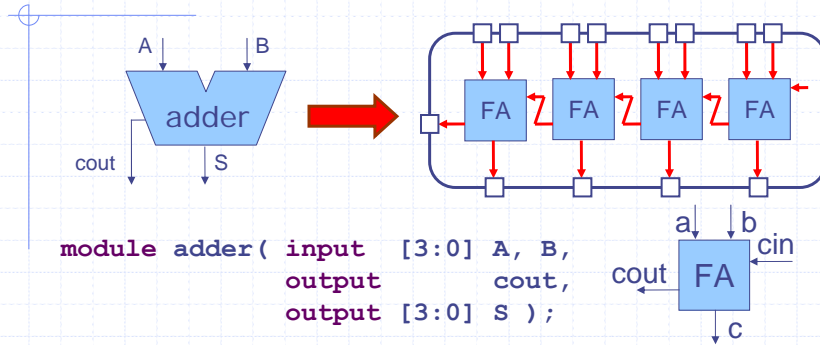

```

module adder( input  [3:0] A, B,
              output   cout,
              output  [3:0] S );

  wire c0, c1, c2;
  FA fa0( ... );
  FA fa1( ... );
  FA fa2( ... );
  FA fa3( ... );

endmodule

module FA( input  a, b, cin
          output cout, sum );
  // HDL modeling of 1 bit
  // full adder functionality
endmodule


```

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-17

Connecting modules

 

```

module adder( input  [3:0] A, B,
              output   cout,
              output  [3:0] S );

  wire c0, c1, c2;
  FA fa0( A[0], B[0], 1'b0, c0, S[0] );
  FA fa1( A[1], B[1], c0, c1, S[1] );
  FA fa2( A[2], B[2], c1, c2, S[2] );
  FA fa3( A[3], B[3], c2, cout, S[3] );

endmodule

```

Carry Chain

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-18

Alternative syntax

Connecting ports by ordered list

```
FA fa0( A[0], B[0], 1'b0, c0, S[0] );
```

Connecting ports by name (compact)

```
FA fa0( .a(A[0]), .b(B[0]),  
        .cin(1'b0), .cout(c0), .sum(S[0]) );
```

Argument order does not matter when ports are connected by name

```
FA fa0  
( .a    (A[0]),  
  .cin  (1'b0),  
  .b    (B[0]),  
  .cout (c0),  
  .sum  (S[0]) );
```

Connecting ports by name
yields clearer and less
buggy code.


February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-19

Verilog Fundamentals

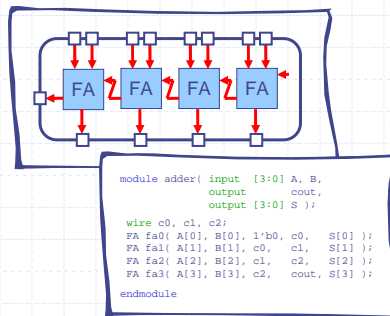- ◆ History of hardware design languages
- ◆ Data types
- ◆ Structural Verilog
- ◆ Simple behaviors



February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-20

A module's behavior can be described in many different ways but it should not matter from outside

Example: mux4


February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-21

mux4: Gate-level structural Verilog

```
module mux4(input a,b,c,d, input [1:0] sel, output out);  
  wire [1:0] sel_b;  
  not not0( sel_b[0], sel[0] );  
  not not1( sel_b[1], sel[1] );  
  
  wire n0, n1, n2, n3;  
  and and0( n0, c, sel[1] );  
  and and1( n1, a, sel_b[1] );  
  and and2( n2, d, sel[1] );  
  and and3( n3, b, sel_b[1] );  
  
  wire x0, x1;  
  nor nor0( x0, n0, n1 );  
  nor nor1( x1, n2, n3 );  
  
  wire y0, y1;  
  or or0( y0, x0, sel[0] );  
  or or1( y1, x1, sel_b[0] );  
  nand nand0( out, y0, y1 );  
endmodule
```

 

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-22

mux4: Using continuous assignments

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    wire out, t0, t1;
    assign out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    assign t1 = ~( (sel[1] & d) | (~sel[1] & b) );
    assign t0 = ~( (sel[1] & c) | (~sel[1] & a) );

endmodule
```

Language defined operators

The order of these continuous assignment statements does not matter.
They essentially happen in parallel!

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-23

mux4: Behavioral style

```
// Four input multiplexer
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    assign out = ( sel == 0 ) ? a :
                 ( sel == 1 ) ? b :
                 ( sel == 2 ) ? c :
                 ( sel == 3 ) ? d : 1'bx;

endmodule
```

If input is undefined we want to propagate that information.

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-24

mux4: Using "always block"

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    reg out, t0, t1;

    always @( a or b or c or d or sel )`
begin
    t0 = ~( (sel[1] & c) | (~sel[1] & a) );
    t1 = ~( (sel[1] & d) | (~sel[1] & b) );
    out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
end

endmodule
```

Motivated by simulation

The order of these procedural assignment statements DOES matter. They essentially happen sequentially!

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-25

"Always blocks" permit more advanced sequential idioms

```
module mux4( input  a,b,c,d
             input [1:0] sel,
             output out );

    reg out;
    always @( * )
begin
    if ( sel == 2'd0 )
        out = a;
    else if ( sel == 2'd1 )
        out = b;
    else if ( sel == 2'd2 )
        out = c;
    else if ( sel == 2'd3 )
        out = d;
    else
        out = 1'bx;
end
endmodule
```

```
module mux4( input  a,b,c,d
             input [1:0] sel,
             output out );

    reg out;
    always @( * )
begin
    case ( sel )
        2'd0 : out = a;
        2'd1 : out = b;
        2'd2 : out = c;
        2'd3 : out = d;
        default : out = 1'bx;
    endcase
end
endmodule
```

Typically we will use always blocks only to describe sequential circuits

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-26

What happens if the case statement is not complete?

```
module mux3( input  a, b, c
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
        endcase
    end

endmodule
```

If sel = 3, mux will output
the previous value!

What have we created?

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-27

What happens if the case statement is not complete?

```
module mux3( input  a, b, c
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
            default : out = 1'bx;
        endcase
    end

endmodule
```

We CAN prevent creating
state with a default
statement

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-28

Parameterized mux4

```
module mux4 #( parameter WIDTH = 1 ) default value
  ( input[WIDTH-1:0] a, b, c, d
    input [1:0] sel,
    output[WIDTH-1:0] out );
```

```
  wire [WIDTH-1:0] out, t0, t1;
```

```
  assign t0 = (sel[1]? c : a);
```

```
  assign t1 = (sel[1]? d : b);
```

```
  assign out = (sel[0]? t0 : t1);
```

```
endmodule
```

Parameterization is a good
practice for reusable modules

Writing a mux n is challenging

Instantiation Syntax

```
mux4#(32) alu_mux
  ( .a (op1),
    .b (op2),
    .c (op3),
    .d (op4),
    .sel (alu_mux_sel),
    .out (alu_mux_out) );
```

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-29

Verilog Registers "reg"

- ◆ Wires are line names – they do not represent storage and can be assigned only once
- ◆ Regs are imperative variables (as in C):
 - "nonblocking" assignment $r <= v$
 - can be assigned multiple times and holds values between assignments


February 6, 2009

<http://csg.csail.mit.edu/6.375/>


L02-30

flip-flops
 
```
module FF0 (input clk, input d,
            output reg q);
always @( posedge clk )
begin
    q <= d;
end
endmodule
```



 
```
module FF (input clk, input d,
            input en, output reg q);
always @( posedge clk )
begin
    if ( en )
        q <= d;
end
endmodule
```



flip-flops with reset

```
always @( posedge clk)
begin
    if (~resetN)
        Q <= 0;
    else if ( enable )
        Q <= D;
end
```

synchronous reset

 

```
always @( posedge clk or
           negedge resetN)
begin
    if (~resetN)
        Q <= 0;
    else if ( enable )
        Q <= D;
end
```

asynchronous reset

What is the difference?

Latches versus flip-flops

```
module latch
(
  input  clk,
  input  d,
  output reg q
);

always @( clk or d )
begin
  if ( clk )
    q <= d;
end
endmodule

module flipflop
(
  input  clk,
  input  d,
  output reg q
);

always @( posedge clk )
begin
  q <= d;
end
endmodule
```

Edge-triggered
always block

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-33

Register

```
module register#(parameter WIDTH = 1)
(
  input  clk,
  input  [WIDTH-1:0] d,
  input  en,
  output [WIDTH-1:0] q
);

always @( posedge clk )
begin
  if (en)
    q <= d;
end
endmodule
```

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-34

Register in terms of Flipflops

```
module register2
  ( input  clk,
    input  [1:0] d,
    input  en,
    output [1:0] q );

  always @(posedge clk)
  begin
    if (en)
      q <= d;
  end

endmodule
```

```
module register2
  ( input  clk,
    input  [1:0] d,
    input  en,
    output [1:0] q
  );
  FF ff0 (.clk(clk), .d(d[0]),
          .en(en), .q(q[0]));

  FF ff1 (.clk(clk), .d(d[1]),
          .en(en), .q(q[1]));

endmodule
```

Do they behave the same?

yes

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-35

Static Elaboration: Generate

```
module register#(parameter WIDTH = 1)
  ( input  clk,
    input  [WIDTH-1:0] d,
    input  en,
    output [WIDTH-1:0] q
  );

  genvar i;
  generate
  for (i = 0; i < WIDTH; i = i + 1)
    begin: regE
      FF ff(.clk(clk), .d(d[i]), .en(en), .q(q[i]));
    end
  endgenerate
endmodule
```

genvars disappear after static elaboration


Generated names will have regE[i]. prefix

February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-36

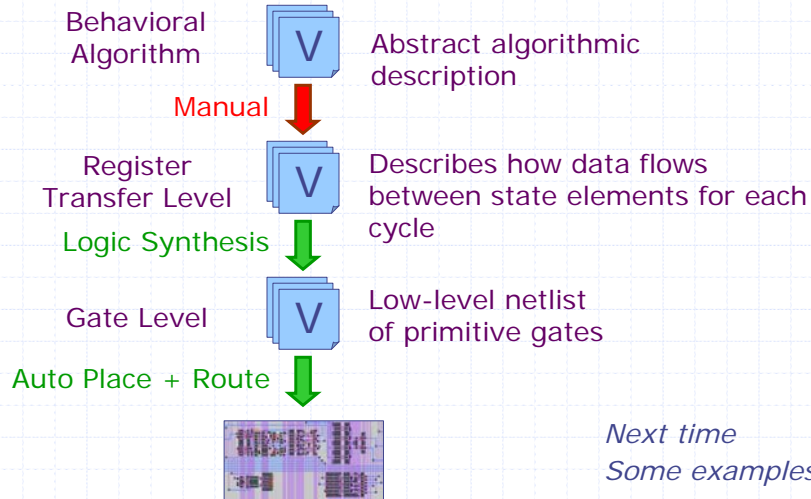Three abstraction levels for functional descriptions



February 6, 2009

<http://csg.csail.mit.edu/6.375/>

L02-37