

Folded Combinational Circuits as an example of Sequential Circuits

Arvind
Computer Science & Artificial Intelligence Lab
Massachusetts Institute of Technology

February 19, 2013


<http://csg.csail.mit.edu/6.375>

L04-1

Multiplication by repeated addition

b	Multiplicand	1101	(13)
a	Multiplier	* 1011	(11)
		1101	
		+ 1101	
		+ 0000	
		+ 1101	
		10001111	(143)

$$m_i = (a[i]==0)? 0 : b;$$

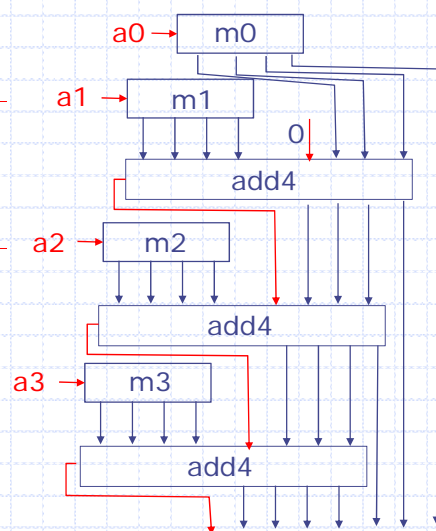

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-2

Combinational 32-bit multiply

```
function Bit#(64) mul32(Bit#(32) a, Bit#(32) b);
    Bit#(32) prod = 0;
    Bit#(32) tp = 0;
    for(Integer i = 0; i < 32; i = i+1)
    begin
        let m = (a[i]==0)? 0 : b;
        let sum = add32(m,tp,0);
        prod[i] = sum[0];
        tp = truncateLSB(sum);
    end
    return {tp,prod};
endfunction
```

Combinational circuit uses 31 add32 circuits

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-3

Design issues with combinational multiply

- ◆ Lot of hardware
 - 32-bit multiply uses 31 add32 circuits
- ◆ Long chains of gates
 - 32-bit ripple carry adder has a 31-long chain of gates
 - 32-bit multiply has 31 ripple carry adders in sequence!

The speed of a combinational circuit is determined by its longest input-to-output path

Can we do better?





February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-4

We can reuse the same add32 circuit if we can store the partial results in some storage device, e.g., *register*



Combinational circuits

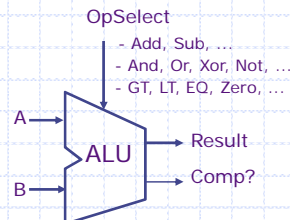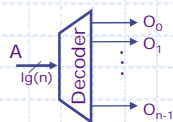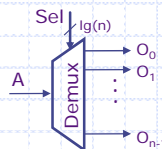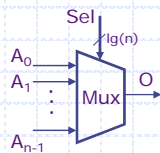

Such circuits have no cycles (feedback) or state elements

A simple synchronous state element

Edge-Triggered Flip-flop

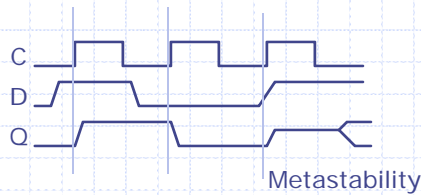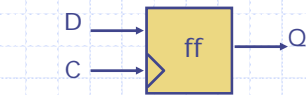





Data is sampled at the rising edge of the clock

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-7

Flip-flops with Write Enables

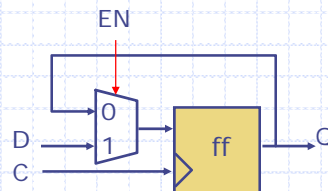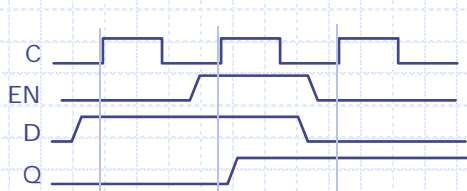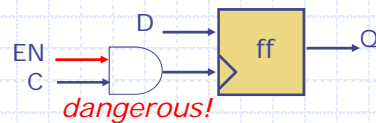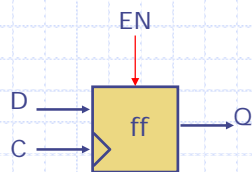


Data is captured only if EN is on

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-8

Registers

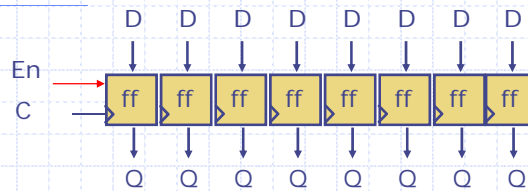

Register: A group of flip-flops with a common clock and enable

Register file: A group of registers with a common clock, input and output port(s)

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-9

We can build useful and compact circuits using registers

Circuits containing state elements are called *sequential circuits*

February 19, 2013

<http://csg.csail.mit.edu/6.375>


L04-10

Expressing a loop using registers

```
int s = s0;
for (int i = 0; i < 32; i = i+1) {
  s = f(s);
}
return s;
C-code
```

We need two registers to hold s and i values from one iteration to the next.

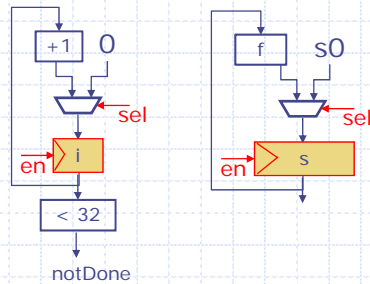These registers are initialized when the computation starts and updated every cycle until the computation terminates



sel = start
en = start | notDone

Expressing sequential circuits in BSV

◆ Sequential circuits, unlike combinational circuits, are not expressed structurally (as wiring diagrams) in BSV

◆ For sequential circuits a designer defines:

- State elements by instantiating modules

```
Reg#(Bit#(32)) s <- mkRegU();
Reg#(Bit#(6)) i <- mkReg(32);
```

make a 32-bit register which is uninitialized

- Rules which define how state is to be transformed atomically

```
rule step if (i < 32);
  s <= f(s);
  i <= i+1;
endrule
```

make a 6-bit register with initial value 32

actions to be performed when the rule executes

the rule can execute only when its guard is true

Rule Execution

◆ When a rule executes:


- all the registers are read at the beginning of a clock cycle
- the guard and computations to evaluate the next value of the registers are performed
- at the end of the clock cycle registers are updated iff the guard is true

```

Reg#(Bit#(32)) s <- mkRegU();
Reg#(Bit#(6)) i <- mkReg(32);

rule step if (i < 32);
  s <= f(s);
  i <= i+1;
endrule
    
```

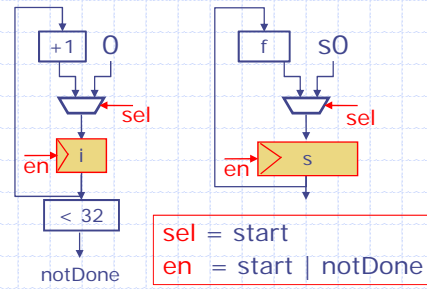◆ Muxes are need to initialize the registers



Multiply using registers

```

function Bit#(64) mul32(Bit#(32) a, Bit#(32) b);
  Bit#(32) prod = 0;
  Bit#(32) tp = 0;
  for(Integer i = 0; i < 32; i = i+1)
  begin
    let m = (a[i]==0)? 0 : b;
    let sum = add32(m,tp,0);
    prod[i] = sum[0];
    tp = truncateLSB(sum);
  end
  return {tp,prod};
endfunction
    
```

Combinational version

Need registers to hold a, b, tp, prod and i

Update the registers every cycle until we are done

Sequential multiply

```
Reg#(Bit#(32)) a <- mkRegU();
Reg#(Bit#(32)) b <- mkRegU();
Reg#(Bit#(32)) prod <-mkRegU();
Reg#(Bit#(32)) tp <- mkRegU();
Reg#(Bit#(6)) i <- mkReg(32);

rule mulStep if (i < 32);
  let m = (a[i]==0)? 0 : b;
  let sum = add32(m,tp,0);
  prod[i] <= sum[0];
  tp <= sum[32:1];
  i <= i+1;
endrule
```


state elements

a rule to describe the dynamic behavior


similar to the loop body in the combinational version

So that the rule won't fire until i is set to some other value

Dynamic selection requires a mux

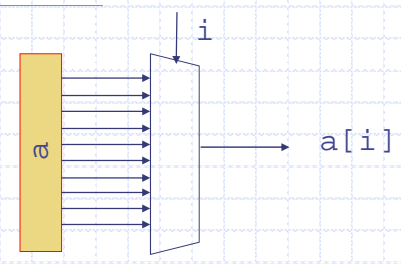

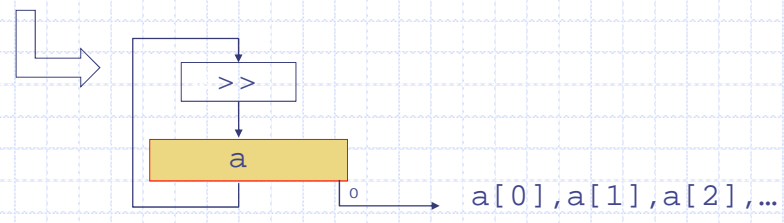when the selection indices are regular then it is better to use a shift operator (no gates!)



Replacing repeated selections by shifts

```

Reg#(Bit#(32)) a <- mkRegU();
Reg#(Bit#(32)) b <- mkRegU();
Reg#(Bit#(32)) prod <-mkRegU();
Reg#(Bit#(32)) tp <- mkRegU();
Reg#(Bit#(6)) i <- mkReg(32);


```

```

rule mulStep if (i < 32);
let m = (a[0]==0)? 0 : b;
a <= a >> 1;
let sum = add32(m,tp,0);
prod <= {sum[0], (prod >> 1)[30:0]};
tp <= sum[32:1];
i <= i+1;
endrule

```

Circuit for Sequential Multiply

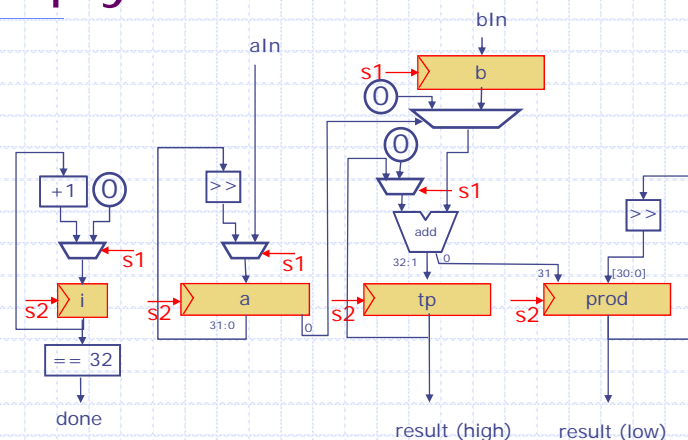

s1 = start_en
s2 = start_en | !done

Circuit analysis


- ◆ Number of add32 circuits has been reduced from 31 to one, though some registers and muxes have been added
- ◆ The longest combinational path has been reduced from 31 serial add32's to one add32 plus a few muxes
- ◆ The sequential circuit will take 31 clock cycles to compute an answer

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-19

Combinational IFFT

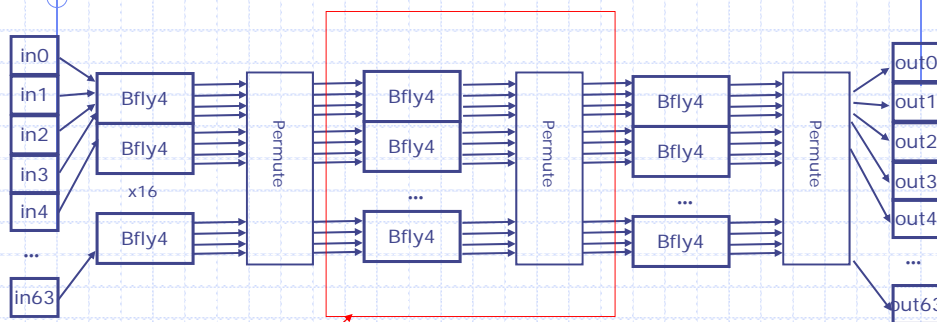

Reuse the same circuit three times
to reduce area

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-20

BSV Code for stage_f

```
function Vector#(64, Complex#(n)) stage_f
  (Bit#(2) stage, Vector#(64, Complex#(n)) stage_in);
Vector#(64, Complex#(n)) stage_temp, stage_out;
  for (Integer i = 0; i < 16; i = i + 1)
    begin
      Integer idx = i * 4;
      Vector#(4, Complex#(n)) x;
      x[0] = stage_in[idx];  x[1] = stage_in[idx+1];
      x[2] = stage_in[idx+2]; x[3] = stage_in[idx+3];
      let twid = getTwiddle(stage, fromInteger(i));
      let y = bfly4(twid, x);
      stage_temp[idx] = y[0]; stage_temp[idx+1] = y[1];
      stage_temp[idx+2] = y[2]; stage_temp[idx+3] = y[3];
    end
  //Permutation
  for (Integer i = 0; i < 64; i = i + 1)
    stage_out[i] = stage_temp[permute[i]];
  return(stage_out);
endfunction
```

twid's are
mathematically
derivable
constants

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-21

Higher-order functions: Stage functions f1, f2 and f3

```
function f0(x)= stage_f(0,x);
function f1(x)= stage_f(1,x);
function f2(x)= stage_f(2,x);
```

What is the type of f0(x) ?


```
function Vector#(64, Complex) f0
  (Vector#(64, Complex) x);
```

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-22

Folded Combinational Ckts

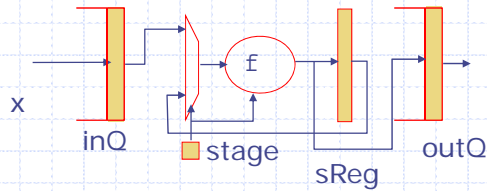


```

rule folded-pipeline (True);
let sxIn = ?;
if (stage==0)
begin sxIn= inQ.first(); inQ.deq(); end
else sxIn= sReg;
let sxOut = f(stage sxIn);
if (stage==n-1) outQ.enq(sxOut);
else sReg <= sxOut;
stage <= (stage==n-1)? 0 : stage+1;
endrule
    
```

no for-loop

Shared Circuit

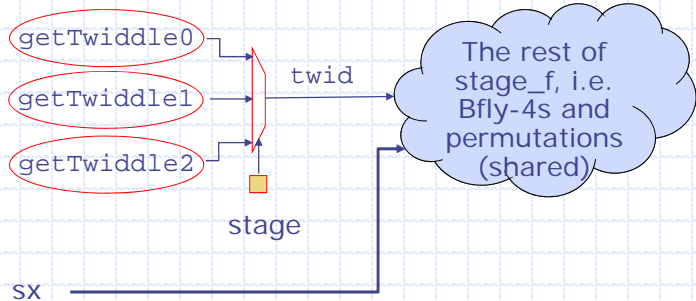

◆ The Twiddle constants can be expressed in a table or in a case or nested case expression

Superfolded pipeline

One Bfly-4 case

- ◆ `f` will be invoked for 48 dynamic values of stage
 - each invocation will modify 4 numbers in `sReg`
 - after 16 invocations a permutation would be done on the whole `sReg`

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-25

Superfolded IFFT: stage function `f`

```
function Vector#(64, Complex) stage_f  
    (Bit#(2) stage, Vector#(64, Complex) stage_in);  
    Vector#(64, Complex#(n)) stage_temp, stage_out;  
for (Integer i = 0; i < 16; i = i + 1)  
    begin Bit#(2) stage  
        Integer idx = i * 4;  
        let twid = getTwiddle(stage, fromInteger(i));  
        let y = bfly4(twid, stage_in[idx:idx+3]);  
        stage_temp[idx] = y[0]; stage_temp[idx+1] = y[1];  
        stage_temp[idx+2] = y[2]; stage_temp[idx+3] = y[3];  
    end  
    //Permutation  
    for (Integer i = 0; i < 64; i = i + 1)  
        stage_out[i] = stage_temp[permute[i]];  
    return(stage_out);  
endfunction
```

should be done only when `i=15`

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-26

Code for the Superfolded stage function

```
Function Vector#(64, Complex) f
    (Bit#(6) stagei, Vector#(64, Complex) stage_in);
let i = stagei `mod` 16;
let twiddle = getTwiddle(stagei `div` 16, i);
let y = bfly4(twiddle, stage_in[i:i+3]);

let stage_temp = stage_in;
stage_temp[i] = y[0];
stage_temp[i+1] = y[1];
stage_temp[i+2] = y[2];
stage_temp[i+3] = y[3];

let stage_out = stage_temp;
if (i == 15)
    for (Integer i = 0; i < 64; i = i + 1)
        stage_out[i] = stage_temp[permute[i]];
return(stage_out);
endfunction
```

One Bfly-4 case

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-27

802.11a Transmitter

[MEMOCODE 2006] Dave, Gerding, Pellauer, Arvind

Design Block	Lines of Code (BSV)	Relative Area
Controller	49	0%
Scrambler	40	0%
Conv. Encoder	113	0%
Interleaver	76	1%
Mapper	112	11%
IFFT	95	85%
Cyc. Extender	23	3%

Complex arithmetic libraries constitute another 200 lines of code

February 19, 2013

<http://csg.csail.mit.edu/6.375>

L04-28

802.11a Transmitter Synthesis results (Only the IFFT block is changing)

IFFT Design	Area (mm ²)	Throughput Latency (CLKs/sym)	Min. Freq Required
Pipelined	5.25	04	1.0 MHz
Combinational	4.91	04	1.0 MHz
Folded (16 Bfly-4s)	3.97	04	1.0 MHz
Super-Folded (8 Bfly-4s)	3.69	06	1.5 MHz
SF(4 Bfly-4s)	2.45	12	3.0 MHz
SF(2 Bfly-4s)	1.84	24	6.0 MHz
SF (1 Bfly4)	1.52	48	12 MHz

The same source code

All these designs were done in less than 24 hours!

TSMC .18 micron; numbers reported are before place and route.

February 19, 2013 <http://csg.csail.mit.edu/6.375> L04-29

Why are the areas so similar

- ◆ Folding should have given a 3x improvement in IFFT area
- ◆ BUT a constant twiddle allows low-level optimization on a Bfly-4 block
 - a 2.5x area reduction!