

# Sequential Circuits: Modules with Guarded Interfaces

Arvind

Computer Science & Artificial Intelligence Lab  
Massachusetts Institute of Technology

# What is needed to make hardware design easier


---

- Extreme IP reuse **“Intellectual Property”**
  - Multiple instantiations of a block for different performance and application requirements
  - Packaging of IP so that the blocks can be assembled easily to build a large system (black box model)
- Ability to do modular refinement
- Whole system simulation to enable concurrent hardware-software development

# IP Reuse sounds wonderful until you try it ...

---

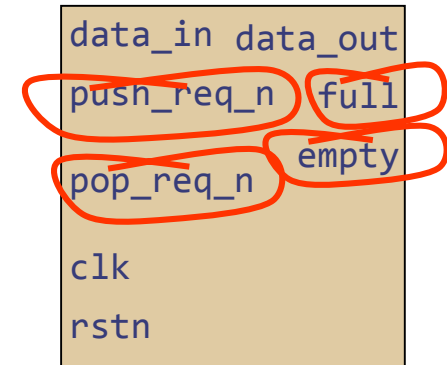Example: Commercially available FIFO IP block



An error occurs if a push is attempted while the FIFO is full.

Thus, there is no conflict in a simultaneous push and pop when the FIFO is full. A simultaneous push and pop cannot occur when the FIFO is empty, since there is no pop data to prefetch. However, push data is captured in the FIFO.


A pop operation occurs when pop\_req\_n is asserted (LOW), as long as the FIFO is not empty. Asserting pop\_req\_n causes the internal read pointer to be incremented on the next rising edge of clk. Thus, the RAM read data must be captured on the clk following the assertion of pop\_req\_n.

These constraints are spread over many pages of the documentation...

# IP Reuse sounds wonderful until you try it ...

---

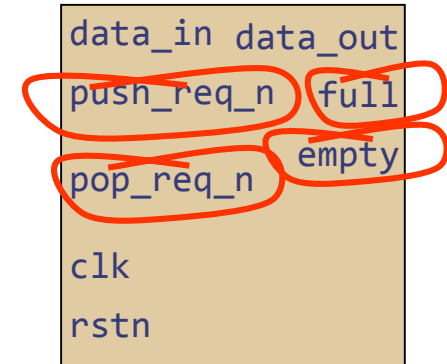Example: Commercially available FIFO IP block



An error occurs if a push is attempted while the FIFO is full.

Thus, there is no conflict in a simultaneous push and pop when the FIFO is full. A simultaneous push and pop is not possible when the FIFO is empty, since there is no pop data to prefetch. However, a pop is possible when data is present in the FIFO.

A pop is possible when pop\_req\_n is asserted (LOW), as long as the FIFO is not empty. pop\_req\_n causes the internal read pointer to be incremented on the next clock edge. Thus, the RAM read data must be captured on the clk following the assertion of pop\_req\_n.

*No machine verification of such informal constraints is feasible*

These constraints are spread over many pages of the documentation...

# A different view of Digital Hardware


---

- Complex Digital Systems are a collection of cooperating sequential machines, which all operate concurrently
- A sequential machine is like an object in an Object-Oriented language like C++ or Java
- A sequential machine can be manipulated only via its interface methods

...but first the basics

# Finite State Machines (FSMs)





---

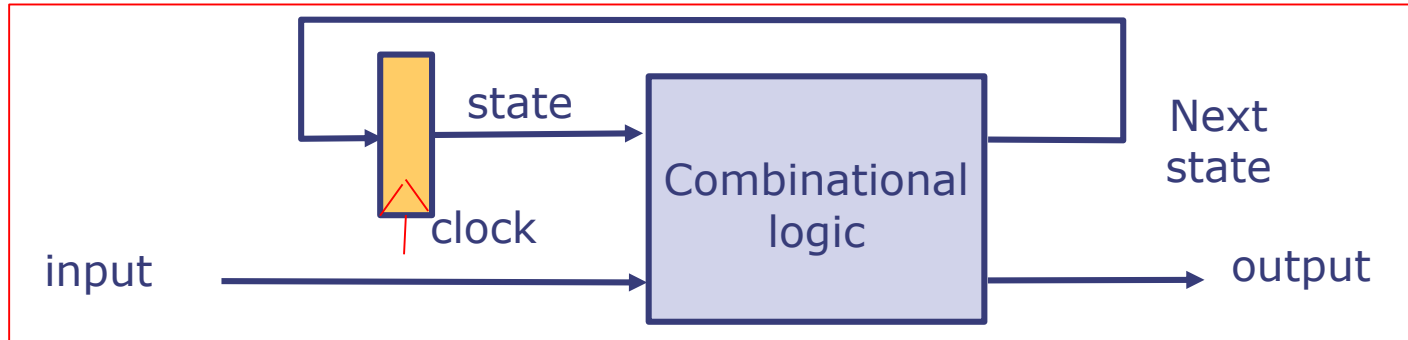

- FSMs are a much studied mathematical object like the Boolean Algebra
  - FSMs are used extensively in software as well
  - A computer (in fact any digital hardware) is an FSM, though we don't think of it as such!
- Synchronous Sequential Circuits are a method to implement FSMs in hardware
   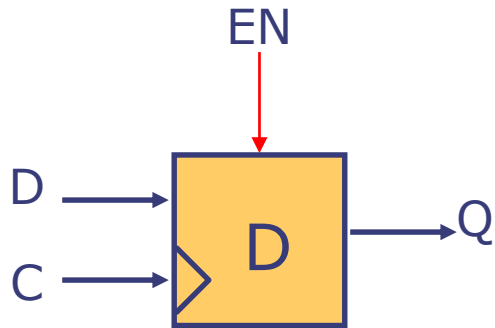
# D Flip-flop with Write Enable

The building block of Sequential Circuits



EN	D	$Q^t$	$Q^{t+1}$
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1


} hold  
} copy input

Data is captured only if EN is on

No need to show the clock explicitly

# Registers

---

 

*Register:* A group of flip-flops with a common clock and enable

*Register file:* A group of registers with a common clock, a shared set of input and output ports




# Clocked Sequential Circuits

---

- In this class we will deal with only clocked sequential circuits
- We will also assume that all flip-flops are connected to the same clock
- To avoid clutter, the clock input will be implicit and not shown in diagrams
- Clock inputs are not needed in BSV descriptions unless we design multi-clock circuits

# An example Modulo-4 counter

Prev State q1q0	NextState	
	inc = 0	inc = 1
00	00	01
01	01	10
10	10	11
11	11	00

 

Finite State  
Machine (FSM)  
representation


$$\begin{aligned}q_0^{t+1} &= \sim inc \cdot q_0^t + inc \cdot \sim q_0^t \\ &= inc \oplus q_0^t\end{aligned}$$

$$\begin{aligned}q_1^{t+1} &= \sim inc \cdot q_1^t + inc \cdot \sim q_1^t \cdot q_0^t + inc \cdot q_1^t \cdot \sim q_0^t \\ &= \sim inc \cdot q_1^t + inc \cdot (q_1^t \oplus q_0^t)\end{aligned}$$
 
# Circuit for the modulo counter using D flip-flops with enables


- Use two D flip-flops, q0 and q1, to store the counter value
- Notice, the state of flip-flop changes only when inc is true

$$\{q1^{t+1}, q0^{t+1}\} = \{(q1^t \oplus q0^t), q0^t\} \quad (\text{assume inc is True})$$



# Sequential Circuit as a module with Interface

---

 


```
interface Counter;  
    method Action inc;  
    method Bit#(2) read;  
endinterface
```

- A module has internal state and an interface
- The internal state can be read and manipulated only by its interface methods
- An *action* method specifies which state elements are to be modified; it has an *enable* wire which must be true to execute the action
- Actions are *atomic* -- either all the specified state elements are modified or none of them are modified (no partially modified state is visible)
- Informally we refer to the *interface* of a module as its type

A module in Bluespec is like a class definition in Java or C++
 
# Modulo-4 counter: An implementation in Bluespec



```
interface Counter;
  method Action inc;
  method Bit#(2) read;
endinterface
```

```
module mkCounter(Counter);
  Reg#(Bit#(2)) cnt <- mkReg(0);
  method Action inc;
  cnt <= {cnt[1]^cnt[0], ~cnt[0]};
endmethod
method Bit#(2) read;
  return cnt;
endmethod
endmodule
```

type  
instantiate

State specification

Initial value

Register assignment

Action to specify how the value of the cnt is to be set


$$q_0^{t+1} = \sim q_0^t$$

$$q_1^{t+1} = q_1^t \oplus q_0^t$$

## Modulo-4 counter

# The generated circuit

---

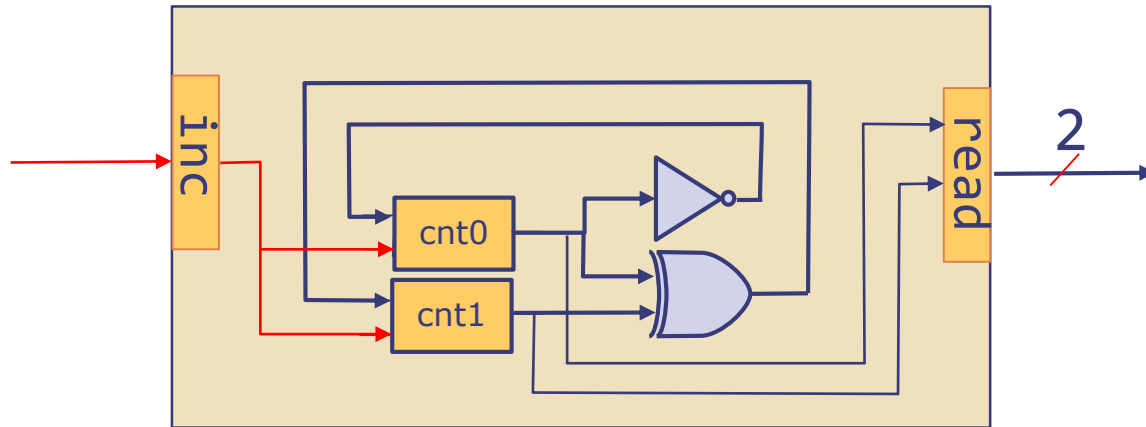

1

```
module mkCounter(Counter);  
  Reg#(Bit#(2)) cnt <- mkReg(0);  
  method Action inc;  
    cnt <={cnt[1]^cnt[0],~cnt[0]};  
  endmethod  
  method Bit#(2) read;  
    return cnt;  
  endmethod  
endmodule
```

# GCD: Euclid's Algorithm

---


Euclid's algorithm for computing the Greatest Common Divisor (GCD):

a: 15	b: 6	
9	6	<i>subtract</i>
3	6	<i>subtract</i>
6	3	<i>swap</i>
3	3	<i>subtract</i>
0	3	<i>subtract</i>

*answer*

# GCD module

---

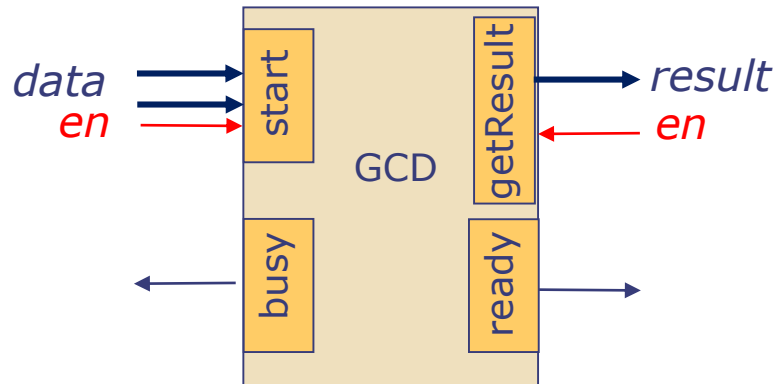


GCD can be started if the module is not *busy*;  
Results can be read when *ready*

```
interface GCD;  
    method Action start (Bit#(32) a, Bit#(32) b);  
    method ActionValue#(Bit#(32)) getResult;  
    method Bool busy;  
    method Bool ready;  
endinterface
```



# GCD implementation

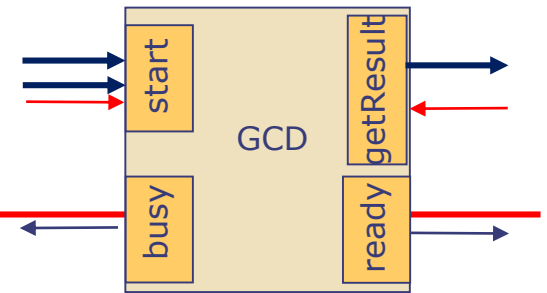

Instantiate state

```
module mkGCD (GCD); Type
```

```
  Reg#(Bit#(32)) x <- mkReg(0); Reg#(Bit#(32)) y <- mkReg(0);
  Reg#(Bool) busy_flag <- mkReg(False);
```

```
  rule gcd; Rule gcd will execute repeatedly until x becomes 0
```

```
    if (x >= y) begin x <= x - y; end //subtract
    else if (x != 0) begin x <= y; y <= x; end //swap
```

```
endrule
```

```
method Action start(Bit#(32) a, Bit#(32) b) ;
```

Assume b != 0

```
  x <= a; y <= b; busy_flag <= True;
```

```
endmethod
```

```
method ActionValue#(Bit#(32)) getResult ;
```

```
  busy_flag <= False; return y;
```

start should be called only if the busy is false; getResult should be called only when ready is true.

```
endmethod
```

```
method Bool busy
  = busy_flag;
```

```
method Bool ready
  = (x==0);
```

```
endmodule
```

```
interface GCD;
  method Action start(Bit#(32) a, Bit#(32) b);
  method ActionValue#(Bit#(32)) getResult;
  method Bool busy;
  method Bool ready;
```

```
endinterface
```

# Method calls

---

- Value method: Only observe the internal state
  - `let counterValue = mod4counter.read;`
  - `Bool isGcdBusy = gcd.busy;`
- Action method: Updates the state of the module
  - `mod4counter.inc;`
  - `gcd.start(13,27);`
- `ActionValue#(t)`: Updates the state and returns a value
  - `let resultGcd <- gcd.getResult;`

Notice the use of '`<-`' instead of '`=`'

- Suppose we wrote
  - `let badResultGCD = gcd.getResult;`
  - then the type of `badResultGCD` would be `ActionValue#(t)` instead of `t`.
  - '`=`' just names the value on the right hand side while '`<-`' indicates a side effect in addition to a return value

# Rule

A module may contain rules

```
rule gcd;  
  if (x >= y) begin x <= x - y; end //subtract  
  else if (x != 0) begin  $x^{t+1} <= y^t$ ;  $y^{t+1} <= x^t$ ; end //swap  
endrule
```

What is meaning of this?

Swap!

- A rule has a name (e.g., gcd)
- A rule is a collection of actions, which invoke methods
- All actions in a rule execute in parallel
- A rule can execute any time and when it executes all of its actions must execute

atomicity

# Parallel Composition of Actions & Double-Writes

---

```
rule one;
```

```
  y <= 3; x <= 5; x <= 7; endrule
```

Double write

```
rule two;
```

```
  y <= 3; if (b) x <= 7; else x <= 5; endrule
```

No double write

```
rule three;
```


```
  y <= 3; x <= 5; if (b) x <= 7; endrule
```

Possibility of a  
double write

- Parallel composition, and consequently a rule containing it, is illegal if a double-write possibility exists
- The Bluespec compiler **rejects** a program if there is any possibility of a double write in a rule or method
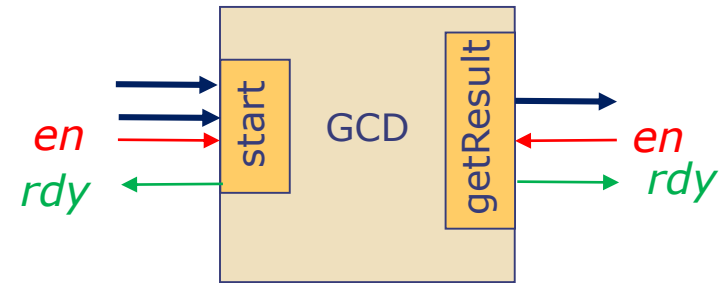
# Guarded interfaces

- Make the life of the programmers easier: Include some checks (not busy, ready, ...) in the method definition itself, so that the user does not have to test the applicability of the method explicitly from outside
- Guarded Interface:
  - Every method has a *guard* (*rdy* wire)
  - The value returned by a method is meaningful only if its guard is true
  - Every action method has an *enable signal* (*en* wire) and it can be invoked (en can be set to true) only if its guard is true



```
interface GCD;  
  method Action start (Bit#(32) a, Bit#(32) b);  
  method ActionValue#(Bit#(32)) getResult;  
method Bool busy;  
method Bool ready;  
endinterface
```

*en* and *rdy* wires  
are implicit;  
derived by the  
type of the method

# GCD with Guards

---

```
module mkGCD (GCD);
  Reg#(Bit#(32)) x <- mkReg(0); Reg#(Bit#(32)) y <- mkReg(0);
  Reg#(Bool) busy_flag <- mkReg(False);

  rule gcd;
    if (x >= y) begin x <= x - y; end //subtract
    else if (x != 0) begin x <= y; y <= x; end //swap
  endrule

  method Action start(Bit#(32) a, Bit#(32) b) ✗ if (!busy_flag);
    x <= a; y <= b; busy_flag <= True;
  endmethod

  method ActionValue#(Bit#(32)) getResult ✗ if (busy_flag&&(x==0));
    busy_flag <= False; return y;
  endmethod
endmodule
```

Assume b != 0

Guard?

```
interface GCD;
  method Action start (Bit#(32) a, Bit#(32) b);
  method ActionValue#(Bit#(32)) getResult;
endinterface
```

# Rules with guards

- Like a method, a rule can also have a guard

```
rule foo if (p);          guard
  begin x1 <= e1; x2 <= e2; end
endrule
```



*Syntax: In rules, "if" is optional before the guard!*

- A rule can execute only if it's guard is true, i.e., if the guard is false the rule has no effect
- True guards can be omitted. Equivalently, the absence of a guard means the guard is always true
- For example we can attach a guard to gcd to prevent its unnecessary execution:

```
rule gcd if (busy_flag);
  if (x >= y) begin x <= x - y; end //subtract
  else if (x != 0) begin x <= y; y <= x; end //swap
endrule
```
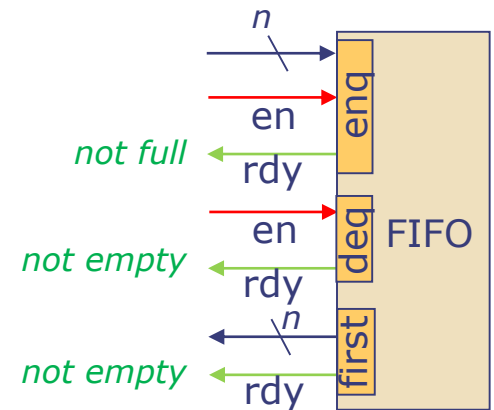 
# First-In-First-Out queue (FIFO)

- FIFO data structure is used extensively both in hardware and software to connect *things*
- In hardware, fifo have fixed size which is often as small as 1, and therefore the producer blocks when enqueueing into a full fifo and the consumer blocks when dequeueing from an empty fifo





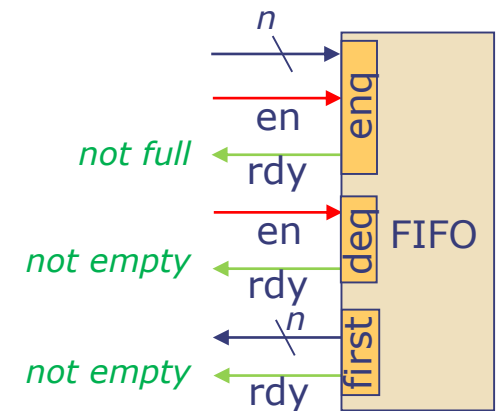
# One-Element FIFO Implementation with guards

```
module mkFifo (Fifo#(1, Bit#(n)));
  Reg#(Bit#(n))    d  <- mkRegU;
  Reg#(Bool) v    <- mkReg(False);
  method Action enq(Bit#(n) x) if (!v);
    v <= True; d <= x;
  endmethod
  method Action deq if (v);
    v <= False;
  endmethod
  method Bit#(n) first if (v);
    return d;
  endmethod
endmodule
```


Syntax: lack of semicolon turns the if into a guard



Guard expression is what is connected to the rdy wire of a method

# Streaming a function using a FIFO with guarded interfaces

---

 


```
if(inQ.notEmpty && outQ.notFull)
```

```
rule stream;  
  outQ.enq(f(inQ.first));  
  inQ.deq;  
endrule
```

implicit guard

The implicit guards of the method calls are sufficient because a rule can execute only if the guards of all of its method calls are true

# Streaming a module

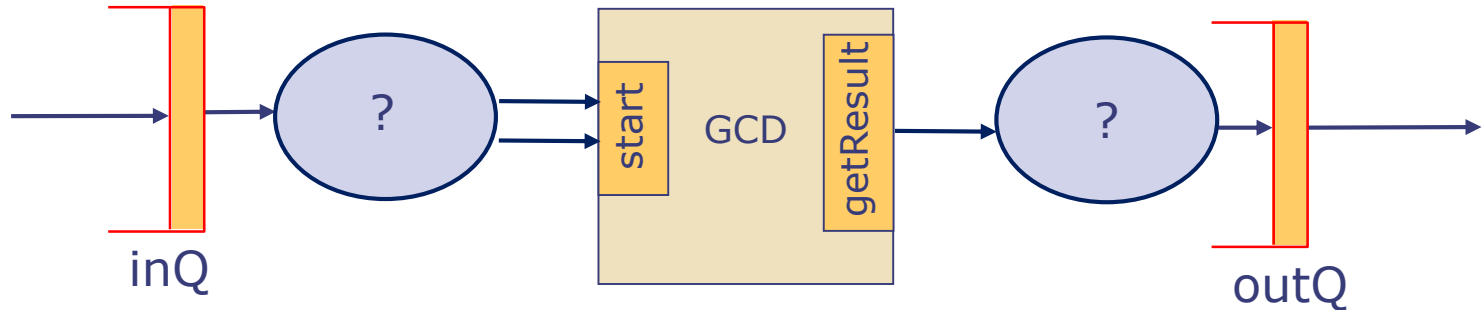


- Suppose we have a queue of pairs of numbers and we want to compute their GCDs and put the results in an output queue
- We can build such a system by creating the following modules

```
Fifo#(1,Vector#(2,t)) inQ <- mkFifo;  
Fifo#(1,t) outQ <- mkFifo;  
GCD gcd <- mkGCD;
```

- To glue these modules together we define two rules:
  - `invokeGCD` to push data from `inQ` into `gcd`
  - `getResult` to fetch result from `gcd` and put it into `outQ`

# Streaming a module: code

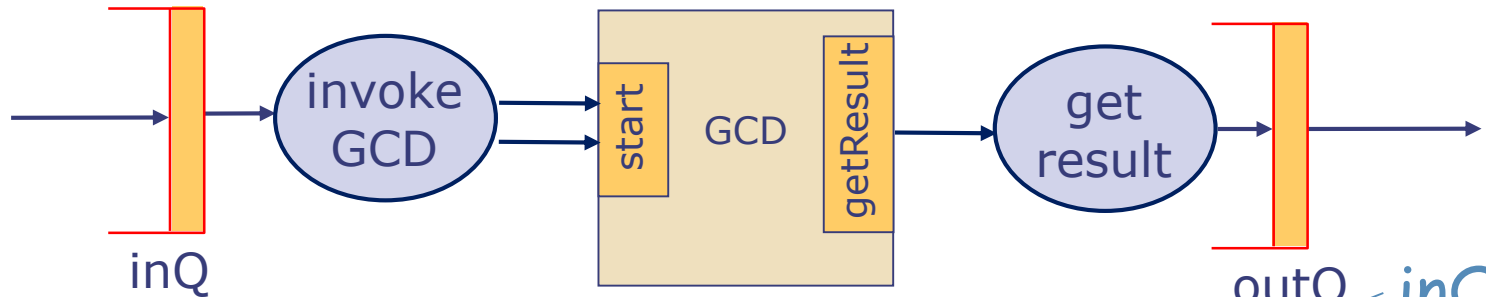

```
rule invokeGCD X if(inQ.first.rdy && inQ.deq.rdy  
  let x = inQ.first[0];  
  let y = inQ.first[1];  
  gcd.start(x,y);  
  inQ.deq;  
endrule
```

inQ is not empty

gcd is not busy


```
rule getResult X if(gcd.getResult.rdy  
  let x <- gcd.getResult;  
  outQ.enq(x);  
endrule
```

Action value method

Implicit guards?

# Power of Abstraction:

## Another GCD implementation

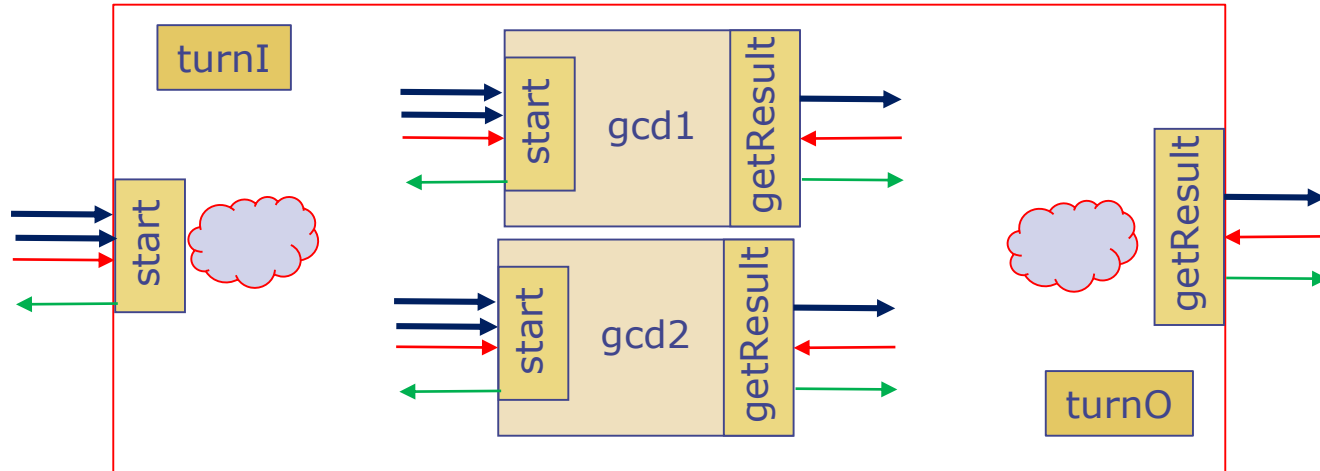


- A GCD module with the same interface but with twice the throughput; uses two gcd modules in parallel
- turnI is used by the start method to direct the input to the gcd whose turn it is and then turnI is flipped
- Similarly, turnO is used by getResult to get the output from the appropriate gcd, and then turnO is flipped

```
interface GCD;  
    method Action start (Bit#(32) a, Bit#(32) b);  
    method ActionValue#(Bit#(32)) getResult;  
endinterface
```
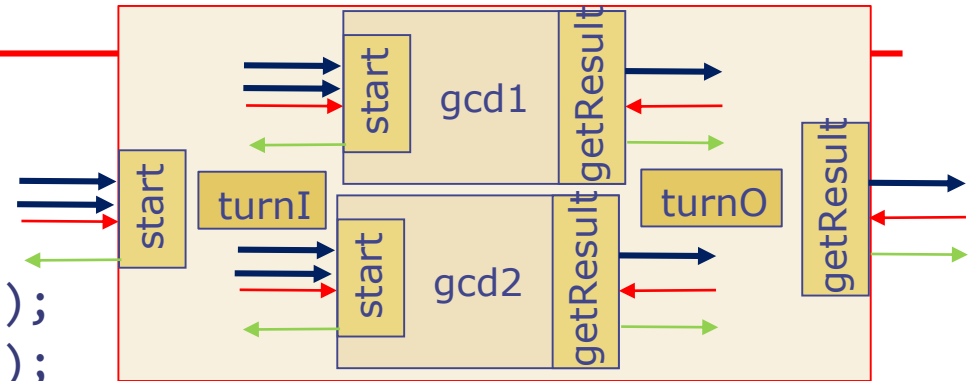
# High-throughput GCD code

```
module mkMultiGCD (GCD);
  GCD gcd1 <- mkGCD();
  GCD gcd2 <- mkGCD();
  Reg#(Bool) turnI <- mkReg(False);
  Reg#(Bool) turnO <- mkReg(False);
  method Action start(Bit#(32) a, Bit#(32) b);
    if (turnI) gcd1.start(a,b); else gcd2.start(a,b);
    turnI <= !turnI;
  endmethod
  method ActionValue (Bit#(32)) getResult;
    Bit#(32) y;
    if (turnO) y <- gcd1.getResult
    else y <- gcd2.getResult;
    turnO <= !turnO
    return y;
  endmethod
endmodule
```



```
interface GCD;
  method Action start (Bit#(32) a, Bit#(32) b);
  method ActionValue#(Bit#(32)) getResult;
endinterface
```