 


# Instruction Set Architecture & Hardwired, Non-pipelined ISA Implementation

*Joel Emer*

Computer Science & Artificial Intelligence Lab  
M.I.T.

# The IBM 650 (1953-4)



# Programmer's view of a machine: IBM 650

---

A drum machine with 44 instructions

Instruction:      60 1234 1009

- “Load the contents of location 1234 into the *distribution*; put it also into the *upper accumulator*; set *lower accumulator* to zero; and then go to location 1009 for the next instruction.”

- Programmer's view of the machine was inseparable from the actual hardware implementation
- Good programmers optimized the placement of instructions on the drum to reduce latency!

# Compatibility Problem at IBM

---

By early 60's, *IBM had 4 incompatible lines of computers!*

|      |   |      |
|------|---|------|
| 701  | → | 7094 |
| 650  | → | 7074 |
| 702  | → | 7080 |
| 1401 | → | 7010 |

Each system had its own

- Instruction set
- I/O system and Secondary Storage:  
magnetic tapes, drums and disks
- assemblers, compilers, libraries,...
- market niche  
business, scientific, real time, ...

⇒ **IBM 360**

# IBM 360: Design Premises

*Amdahl, Blaauw and Brooks, 1964*

---

The design must lend itself to *growth and successor machines*

- General method for connecting I/O devices
- Total performance - answers per month rather than bits per microsecond  $\Rightarrow$  *programming aids*
- Machine must be capable of *supervising itself* without manual intervention
- Built-in *hardware fault checking* and locating aids to reduce down time
- Simple to assemble systems with redundant I/O devices, memories etc. for *fault tolerance*
- Some problems required floating point words larger than 36 bits

# Processor State and Data Types

---

*The information held in the processor at the end of an instruction to provide the processing context for the next instruction.*

Program Counter, Accumulator, . . .

- The information held in the processor will be interpreted as having data types manipulated by the instructions.
- If the processing of an instruction can be interrupted then the *hardware* must save and restore the state in a transparent manner

*Programmer's machine model* is a **contract** between the hardware and software

# Instruction set

---

*The control for changing the information held in the processor are specified by the instructions available in the instruction set architecture or ISA.*

Some things an ISA must specify:

- *A way to reference registers and memory*
- *The computational operations available*
- *How to control the sequence of instructions*
- *A binary representation for all of the above*

*ISA must satisfy the needs of the software:  
- assembler, compiler, OS, VM*

# IBM 360: *A General-Purpose Register (GPR) Machine*

---

- Processor State
  - 16 General-Purpose 32-bit Registers
  - 4 Floating Point 64-bit Registers
  - A Program Status Word (PSW)
    - *PC, Condition codes, Control flags*
- Data Formats
  - 8-bit bytes, 16-bit half-words, 32-bit words, 64-bit double-words
  - 24-bit addresses
- A 32-bit machine with 24-bit addresses
  - *No instruction contains a 24-bit address!*
- Precise interrupts



# IBM 360: Initial Implementations (1964)


|                        | <i>Model 30</i>       | <i>. . .</i> | <i>Model 70</i>    |
|------------------------|-----------------------|--------------|--------------------|
| <i>Memory Capacity</i> | 8K - 64 KB            |              | 256K - 512 KB      |
| <i>Memory Cycle</i>    | 2.0 $\mu$ s           | <i>...</i>   | 1.0 $\mu$ s        |
| <i>Datapath</i>        | 8-bit                 |              | 64-bit             |
| <i>Circuit Delay</i>   | 30 nsec/level         |              | 5 nsec/level       |
| <i>Registers</i>       | in Main Store         |              | in Transistor      |
| <i>Control Store</i>   | Read only 1 $\mu$ sec |              | Dedicated circuits |

- Six implementations (Models, 30, 40, 50, 60, 62, 70)
- 50x performance difference across models
- *ISA completely hid the underlying technological differences between various models*

With minor modifications, IBM 360 ISA is still in use

# IBM 360: Forty-Six years later... zEnterprise196 Microprocessor

- 1.4 billion transistors, Quad core design
- Up to 96 cores (80 visible to OS) in one multichip module
- 5.2 GHz, IBM 45nm SOI CMOS technology
- 64-bit virtual addressing
  - original 360 was 24-bit; 370 was a 31-bit extension
- Superscalar, out-of-order
  - Up to 72 instructions in flight
- Variable length instruction pipeline: 15-17 stages
- Each core has 2 integer units, 2 load-store units and 2 floating point units
- 8K-entry Branch Target Buffer
  - Very large buffer to support commercial workloads
- Four Levels of caches:
  - 64KB L1 I-cache, 128KB L1 D-cache
  - 1.5MB L2 cache per core
  - 24MB shared on-chip L3 cache
  - 192MB shared off-chip L4 cache

 

*[ September 2010 ]*

# Instruction Set Architecture (ISA) versus Implementation

---

- ISA is the hardware/software interface
  - Defines set of programmer visible state
  - Defines data types
  - Defines instruction semantics (operations, sequencing)
  - Defines instruction format (bit encoding)
  - Examples: *MIPS, Alpha, x86, IBM 360, VAX, ARM, JVM*
- Many possible implementations of one ISA
  - 360 implementations: *model 30 (c. 1964), zEnterprise196 (c. 2010)*
  - x86 implementations: *8086 (c. 1978), 80186, 286, 386, 486, Pentium, Pentium Pro, Pentium-4, Core i7, AMD Athlon, AMD Opteron, Transmeta Crusoe, SoftPC*
  - MIPS implementations: *R2000, R4000, R10000, ...*
  - JVM: *HotSpot, PicoJava, ARM Jazelle, ...*

# Processor Performance

$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} * \frac{\text{Cycles}}{\text{Instruction}} * \frac{\text{Time}}{\text{Cycle}}$$

- Instructions per program depends on source code, compiler technology and ISA
- Cycles per instructions (CPI) depends upon the ISA and the microarchitecture
- Time per cycle depends upon the microarchitecture and the base technology


rest of  
this lecture  
→

| Microarchitecture        | CPI | cycle time |
|--------------------------|-----|------------|
| Microcoded               | >1  | short      |
| Single-cycle unpipelined | 1   | long       |
| Pipelined                | 1   | short      |

# Hardware Elements


- Combinational circuits

- Mux, Demux, Decoder, ALU, ...

 



- Synchronous state elements

 - Flipflop, Register, Register file, SRAM, DRAM




*Edge-triggered: Data is sampled at the rising edge*

# Register Files

  

No timing issues in reading a selected register


# Register File Implementation

 

- Register files with a large number of ports are difficult to design
  - Area scales with ports<sup>2</sup>
  - Almost all Alpha instructions have exactly 2 register source operands
  - *Intel's Itanium GPR File has 128 registers with 8 read ports and 4 write ports!!!*

# A Simple Memory Model

---

 

- Reads and writes are always completed in one cycle
  - A Read can be done any time (i.e., combinational)
  - If enabled, a Write is performed at the rising clock edge (*the write address and data must be stable at the clock edge*)

*Later in the course we will present a more realistic model of memory*



# Implementing MIPS:

## Single-cycle per instruction datapath & control logic

# The MIPS ISA

---

## Processor State

- 32 32-bit GPRs, R0 always contains a 0
- 32 single precision FPRs, may also be viewed as
  - 16 double precision FPRs
- FP status register, used for FP compares & exceptions
- PC, the program counter
- Some other special registers

## Data types

- 8-bit byte, 16-bit half word
- 32-bit word for integers
- 32-bit word for single precision floating point
- 64-bit word for double precision floating point

## Load/Store style instruction set

- Data addressing modes: immediate & indexed
- Branch addressing modes: PC relative & register indirect
- Byte-addressable memory, big-endian mode

All instructions are 32 bits

# Instruction Execution



---

Execution of an instruction involves

1. Instruction fetch
2. Decode
3. Register fetch
4. ALU operation
5. Memory operation (optional)
6. Write back

And computing the address of the  
*next instruction (next PC)*



# Datapath: Reg-Reg ALU Instructions

 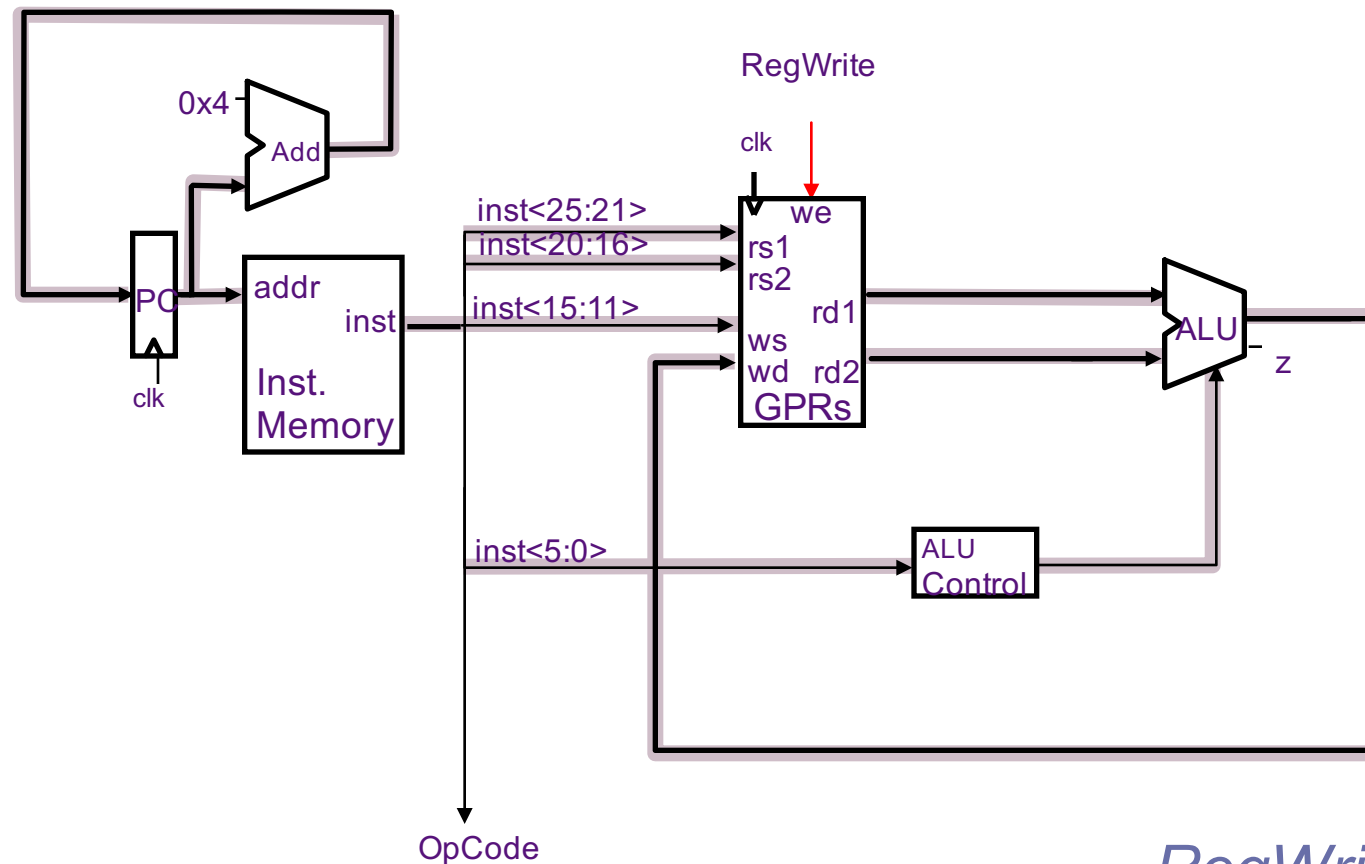

*RegWrite Timing?*



$$rd \leftarrow (rs) \text{ func } (rt)$$

# Datapath: Reg-Imm ALU Instructions

 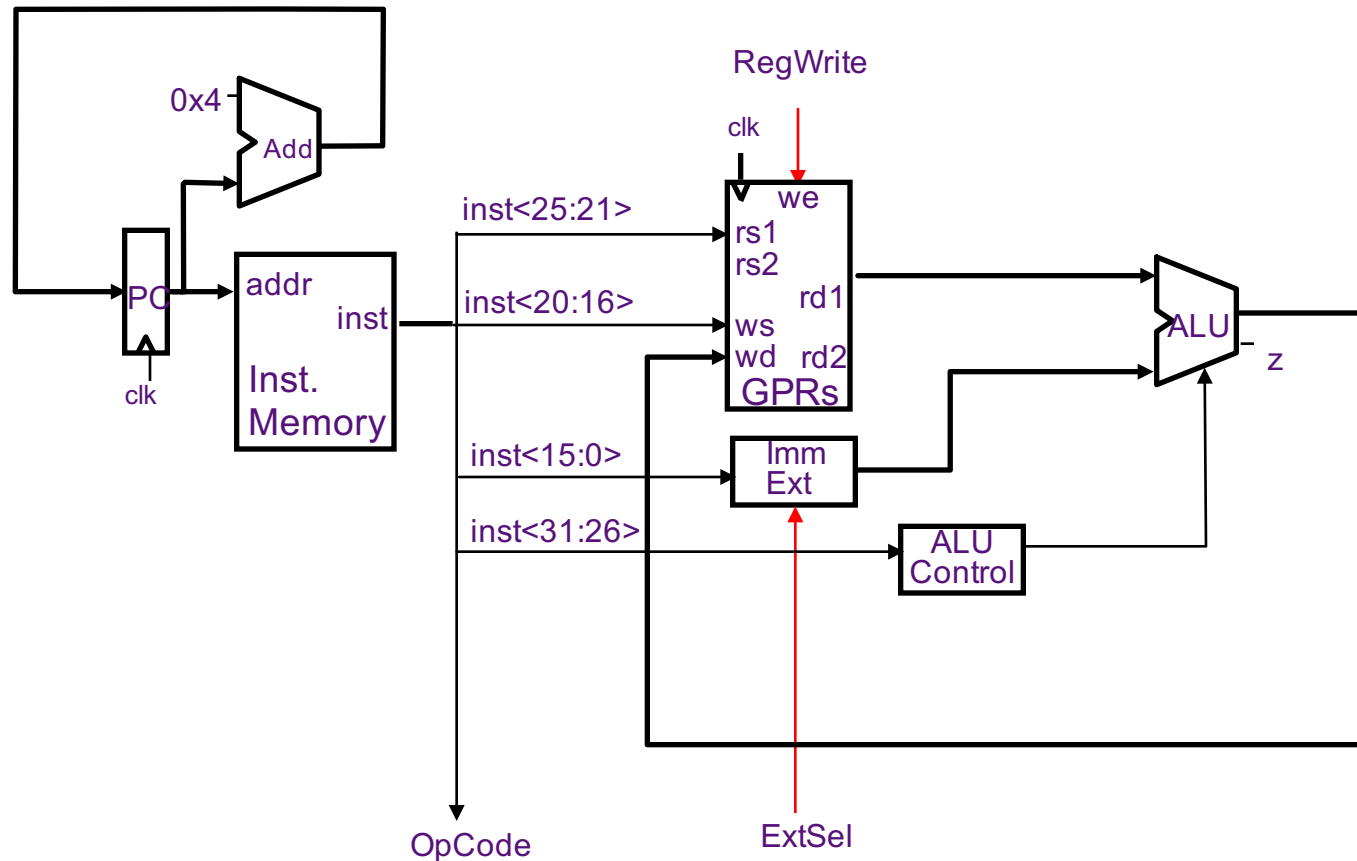

$rt \leftarrow (rs) \text{ op immediate}$


# Conflicts in Merging Datapath

 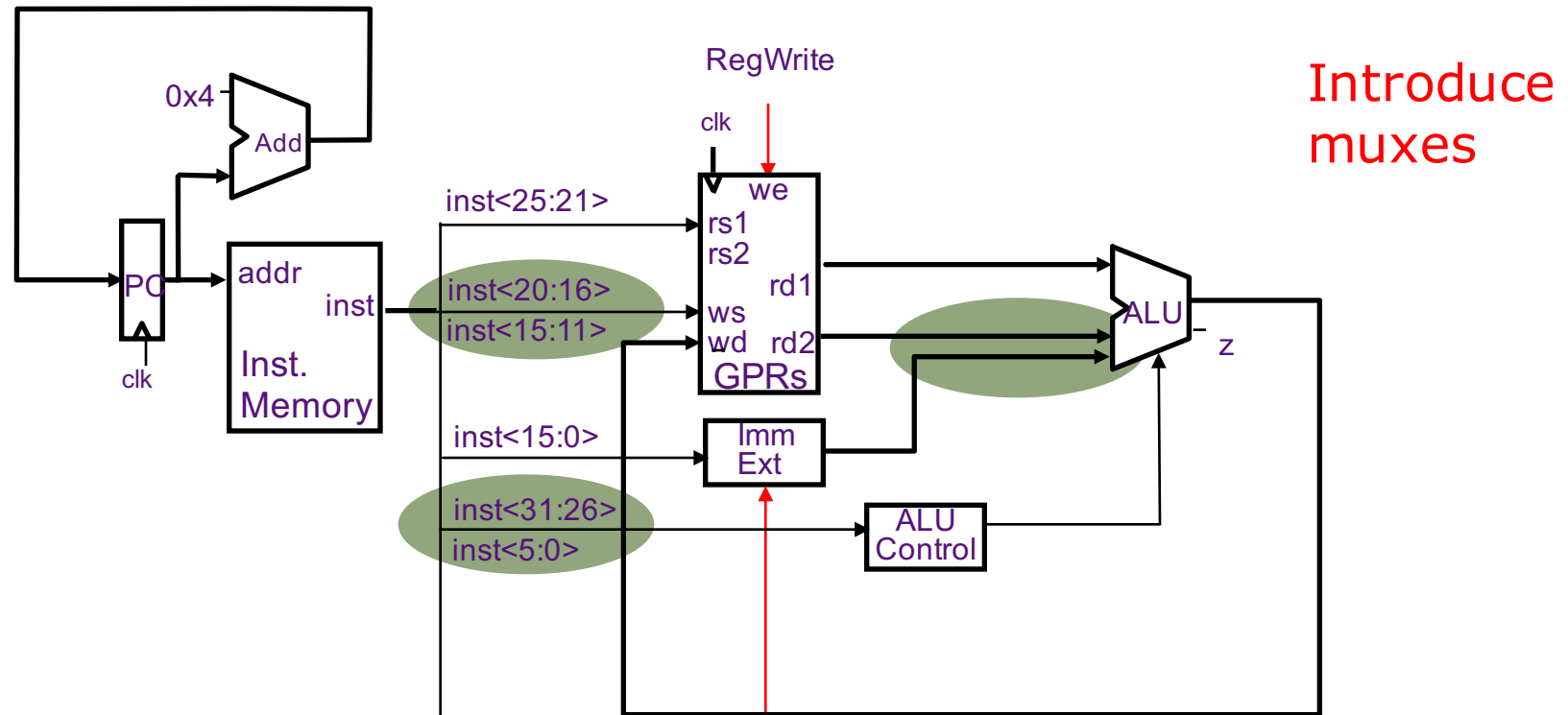

$$rd \leftarrow (rs) \text{ func } (rt)$$

$$rt \leftarrow (rs) \text{ op } \text{immediate}$$

# Datapath for ALU Instructions

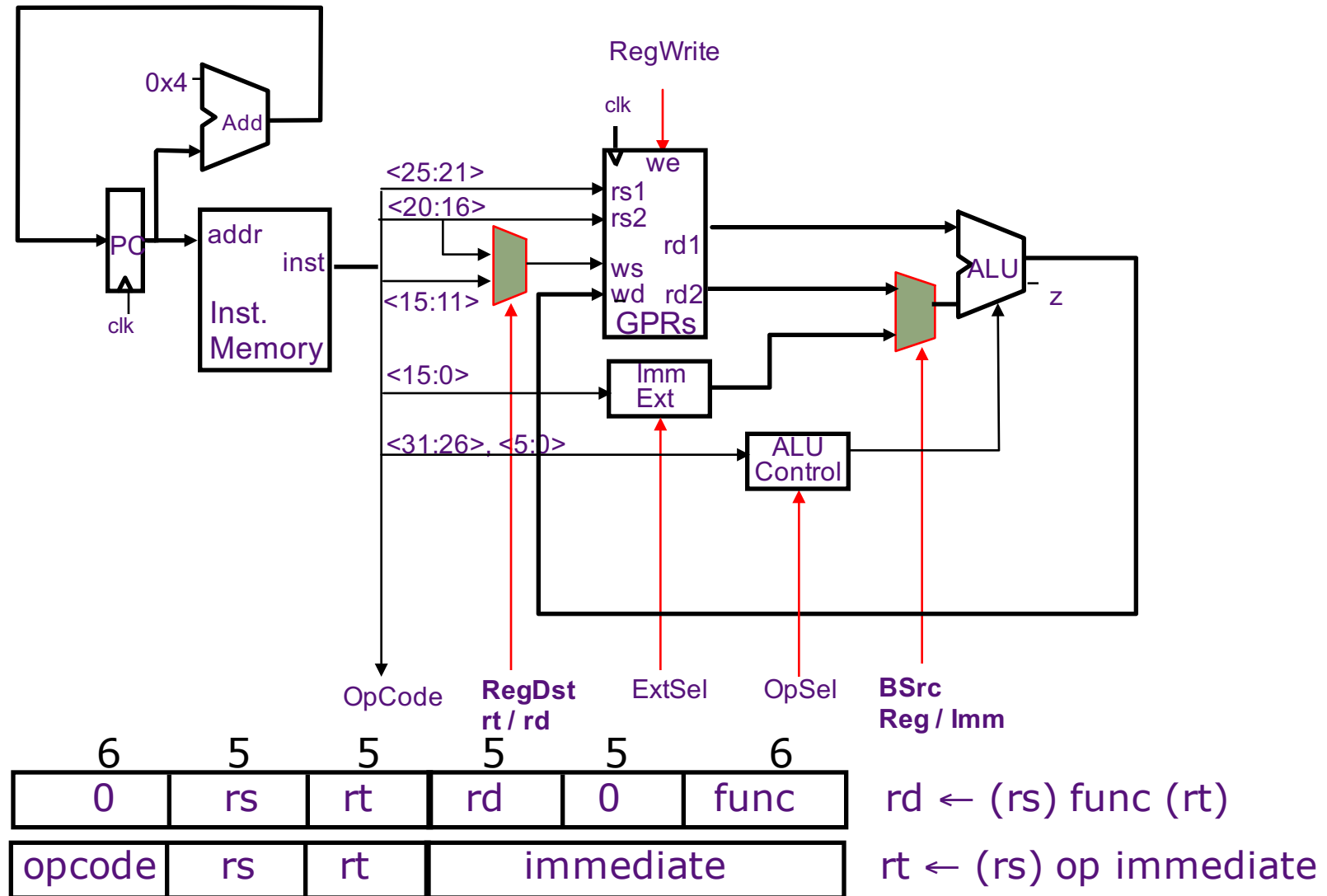

# Datapath for Memory Instructions

---

Should program and data memory be separate?

*Harvard style: separate* (Aiken and Mark 1 influence)

- read-only program memory
- read/write data memory

- Note:

There must be a way to load the program memory

*Princeton style: the same* (von Neumann's influence)

- single read/write memory for program and data



- Note:

Executing a Load or Store instruction requires accessing the memory more than once



# Load/Store Instructions

## Harvard Datapath

 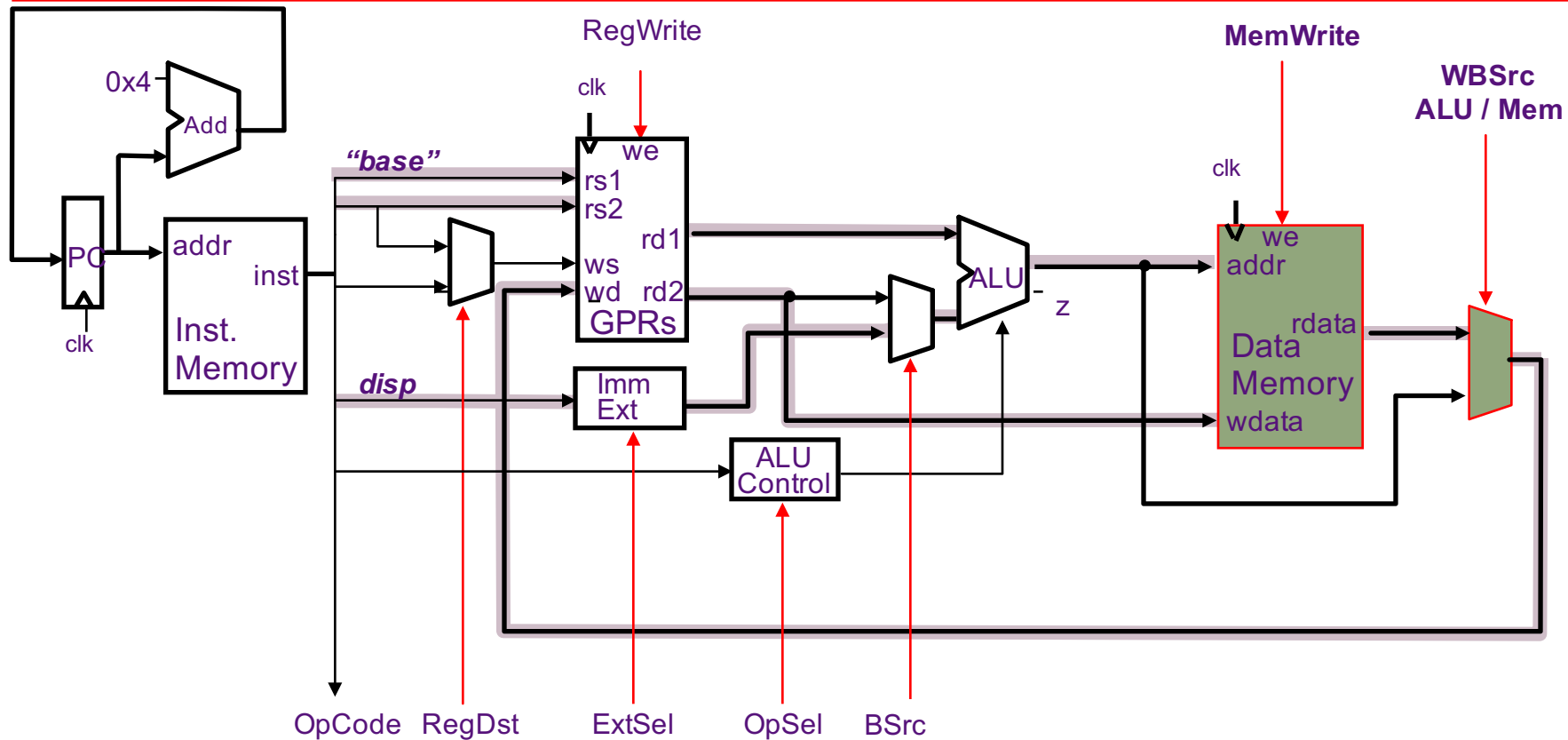

addressing mode  
(rs) + displacement


rs is the base register

rt is the destination of a Load or the source for a Store


# MIPS Control Instructions

---

Conditional (on GPR) PC-relative branch

 

Unconditional register-indirect jumps

 


Unconditional absolute jumps




- PC-relative branches add  $\text{offset} \times 4$  to  $\text{PC} + 4$  to calculate the target address (offset is in words):  $\pm 128$  KB range
- Absolute jumps append  $\text{target} \times 4$  to  $\text{PC} \langle 31:28 \rangle$  to calculate the target address: 256 MB range
- Jump-&-link stores  $\text{PC} + 4$  into the link register (R31)
- Control transfers are not delayed  
*we will worry about the branch delay slot later*


# Conditional Branches (BEQZ, BNEZ)

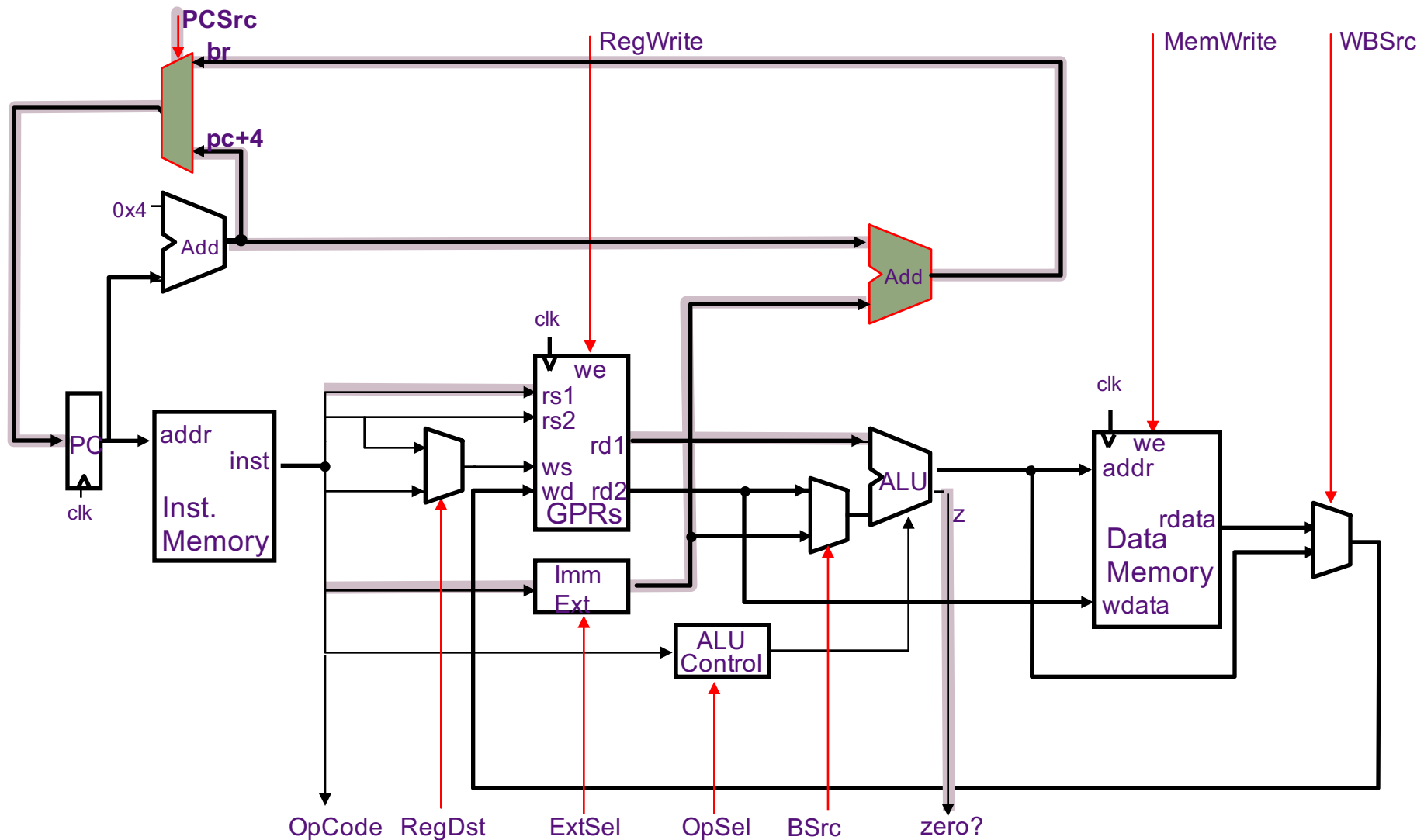


# Register-Indirect Jumps (JR)

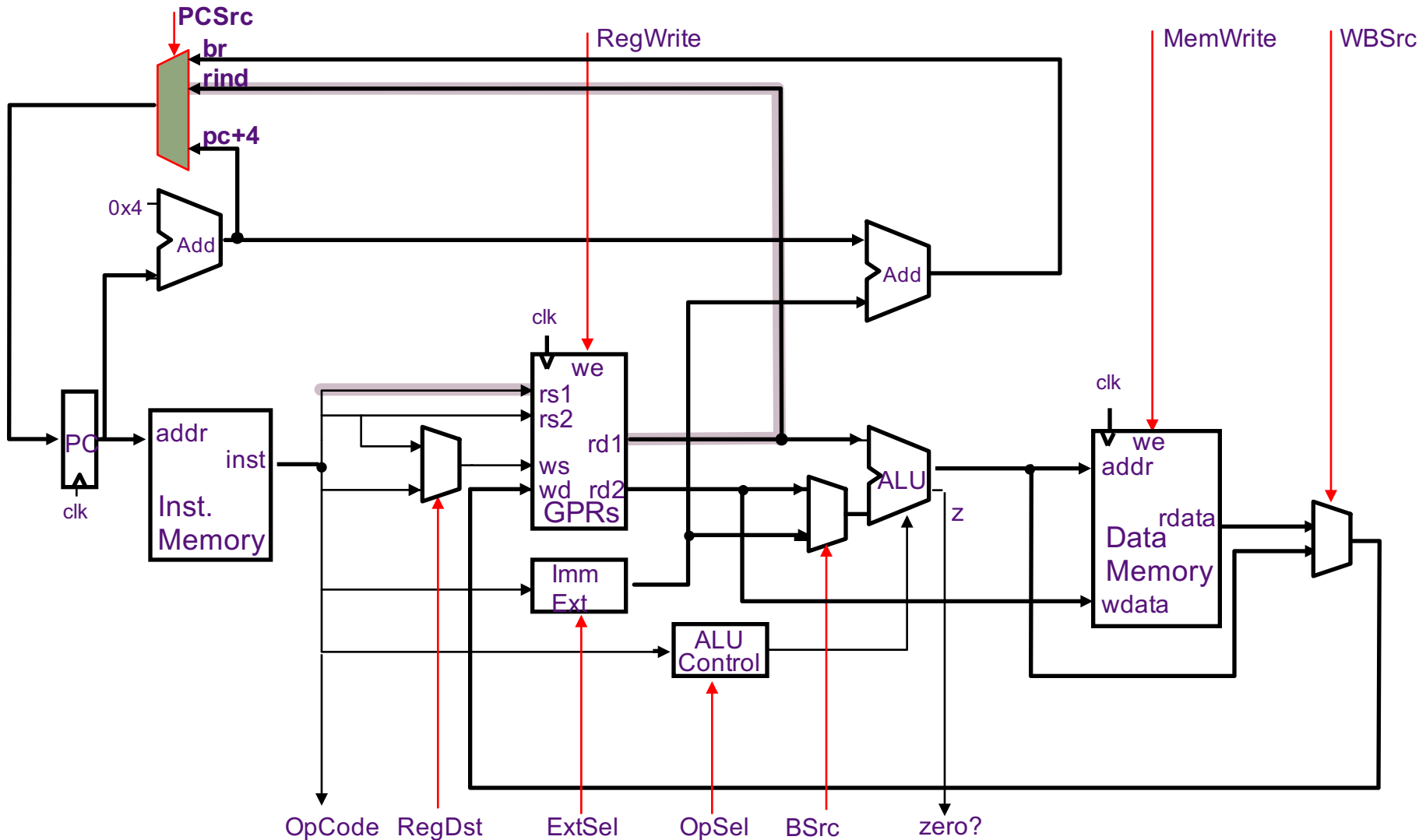


# Register-Indirect Jump-&-Link (JALR)

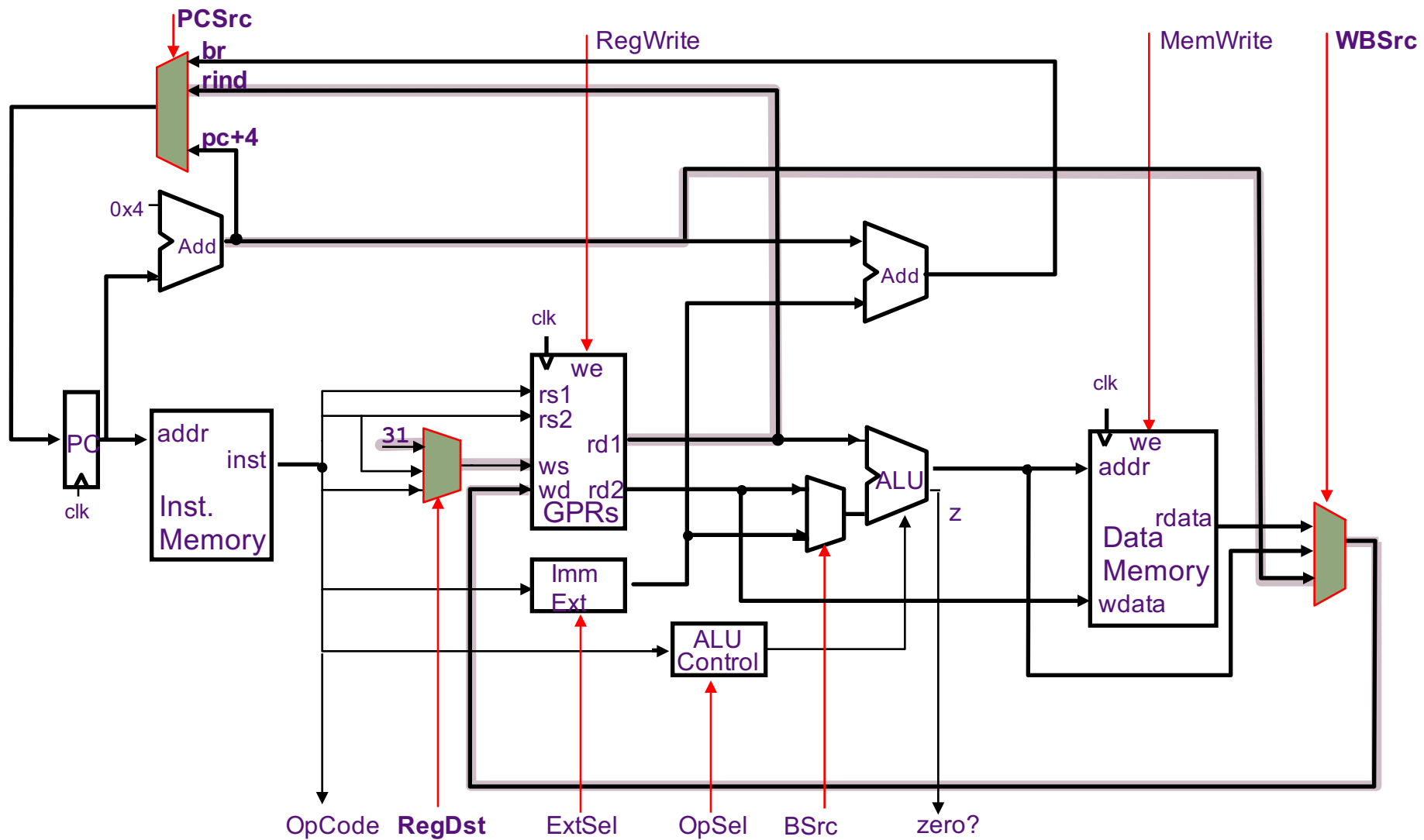

# Absolute Jumps (J, JAL)

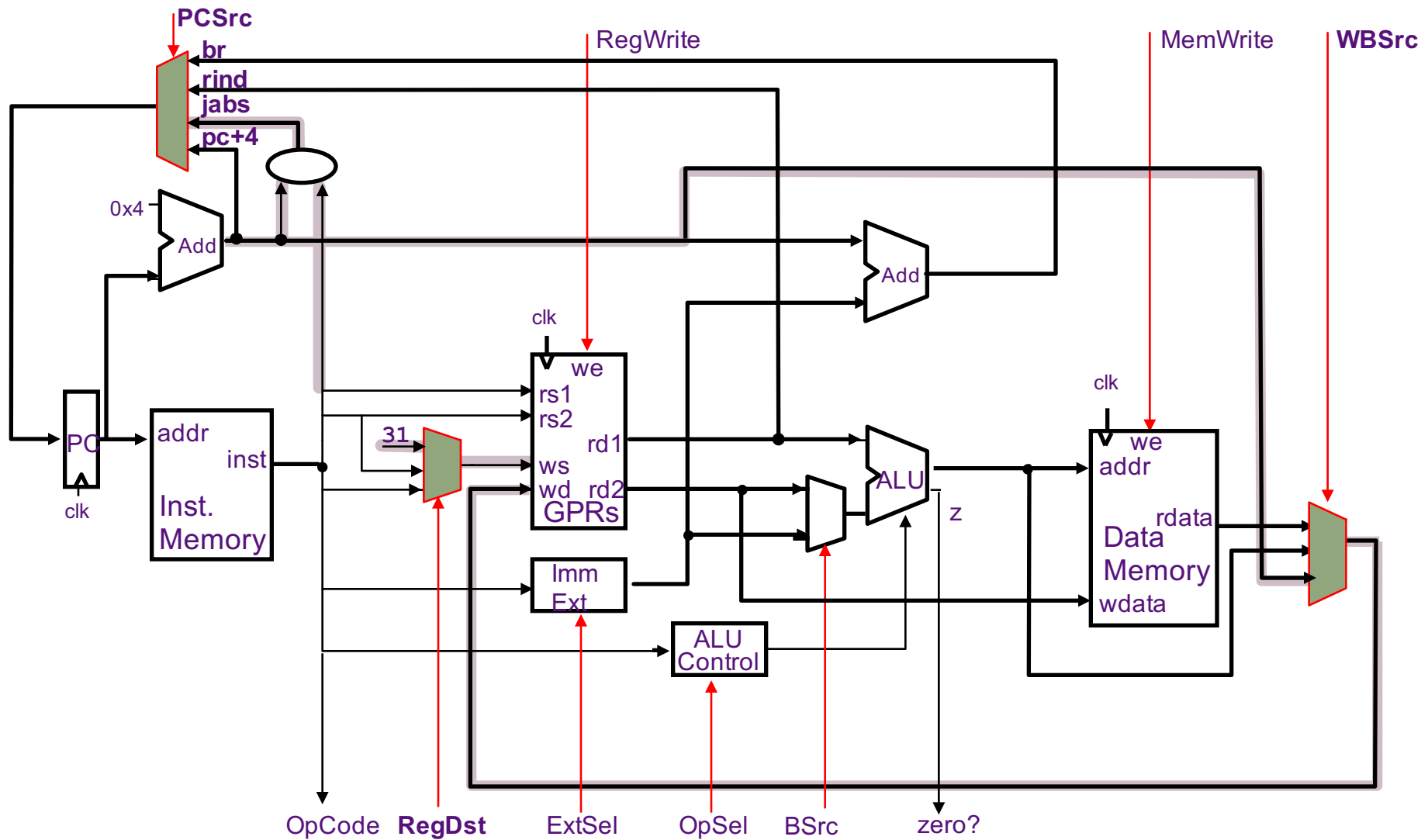


# Harvard-Style Datapath for MIPS

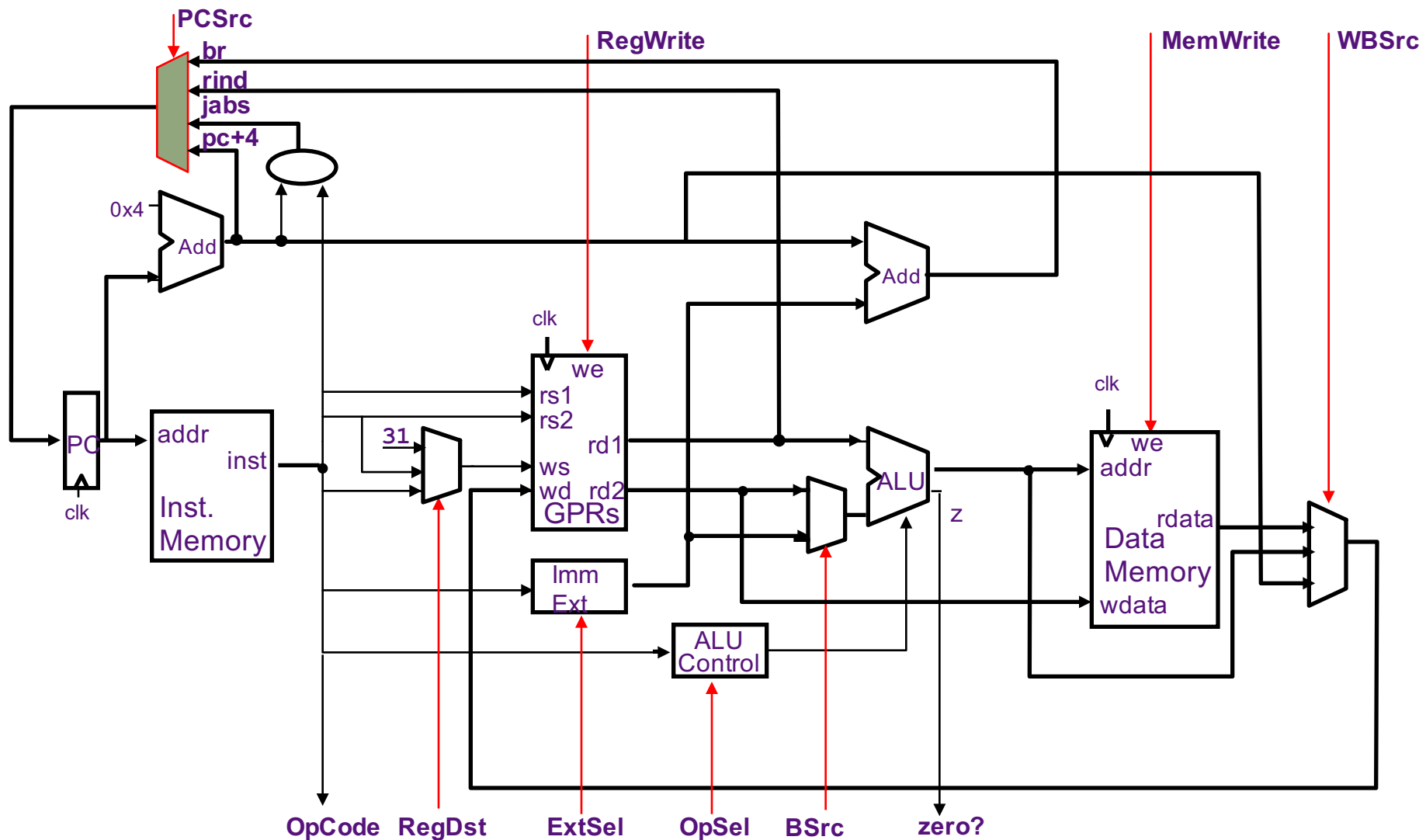


# Hardwired Control is pure Combinational Logic

---

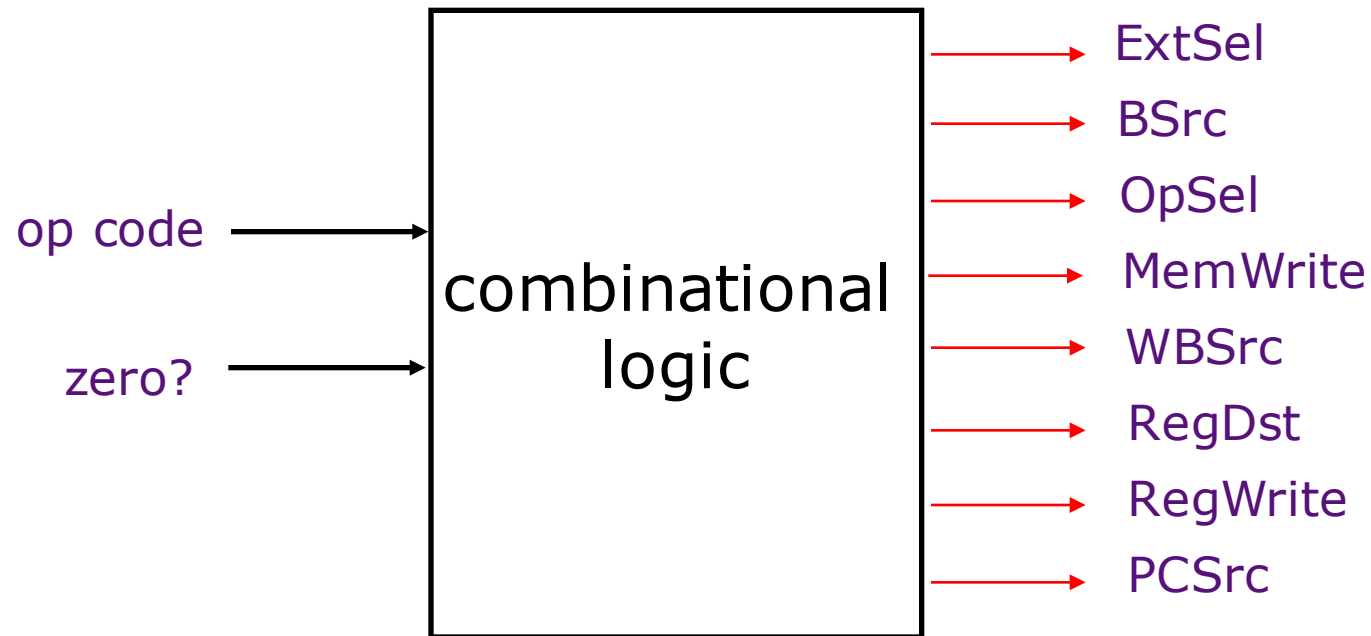



# ALU Control & Immediate Extension

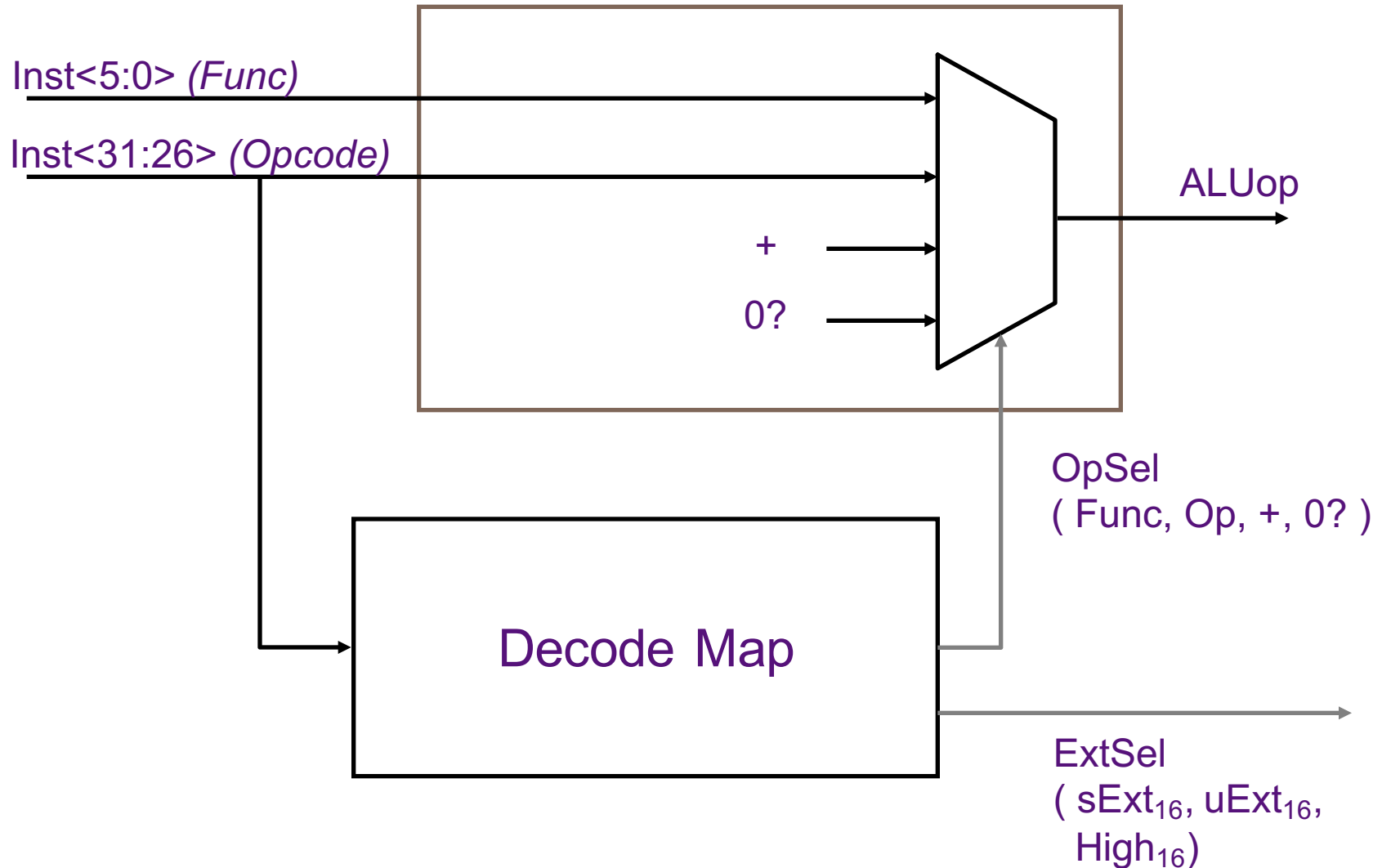

# Hardwired Control Table

| Opcode              | ExtSel             | BSrc | OpSel | MemW | RegW | WBSrc | RegDst | PCSrc |
|---------------------|--------------------|------|-------|------|------|-------|--------|-------|
| ALU                 | *                  | Reg  | Func  | no   | yes  | ALU   | rd     | pc+4  |
| ALUi                | sExt <sub>16</sub> | Imm  | Op    | no   | yes  | ALU   | rt     | pc+4  |
| ALUiu               | uExt <sub>16</sub> | Imm  | Op    | no   | yes  | ALU   | rt     | pc+4  |
| LW                  | sExt <sub>16</sub> | Imm  | +     | no   | yes  | Mem   | rt     | pc+4  |
| SW                  | sExt <sub>16</sub> | Imm  | +     | yes  | no   | *     | *      | pc+4  |
| BEQZ <sub>Z=0</sub> | sExt <sub>16</sub> | *    | 0?    | no   | no   | *     | *      | br    |
| BEQZ <sub>Z=1</sub> | sExt <sub>16</sub> | *    | 0?    | no   | no   | *     | *      | pc+4  |
| J                   | *                  | *    | *     | no   | no   | *     | *      | jabs  |
| JAL                 | *                  | *    | *     | no   | yes  | PC    | R31    | jabs  |
| JR                  | *                  | *    | *     | no   | no   | *     | *      | rind  |
| JALR                | *                  | *    | *     | no   | yes  | PC    | R31    | rind  |

BSrc = Reg / Imm

RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC

PCSrc = pc+4 / br / rind / jabs

# Single-Cycle Hardwired Control:

## *Harvard architecture*

---

We will assume

- clock period is sufficiently long for all of the following steps to be “completed”:

1. instruction fetch
2. decode and register fetch
3. ALU operation
4. data fetch if required
5. register write-back setup time

$$\Rightarrow t_C > t_{IFetch} + t_{RFetch} + t_{ALU} + t_{DMem} + t_{RWB}$$

- At the rising edge of the following clock, the PC, the register file and the memory are updated

# Princeton challenge

---


- What problem arises if instructions and data reside in the same memory?

At least the instruction fetch and a Load (or Store) cannot be executed in the same cycle

Structural hazard

# Princeton Microarchitecture


## Datapath & Control

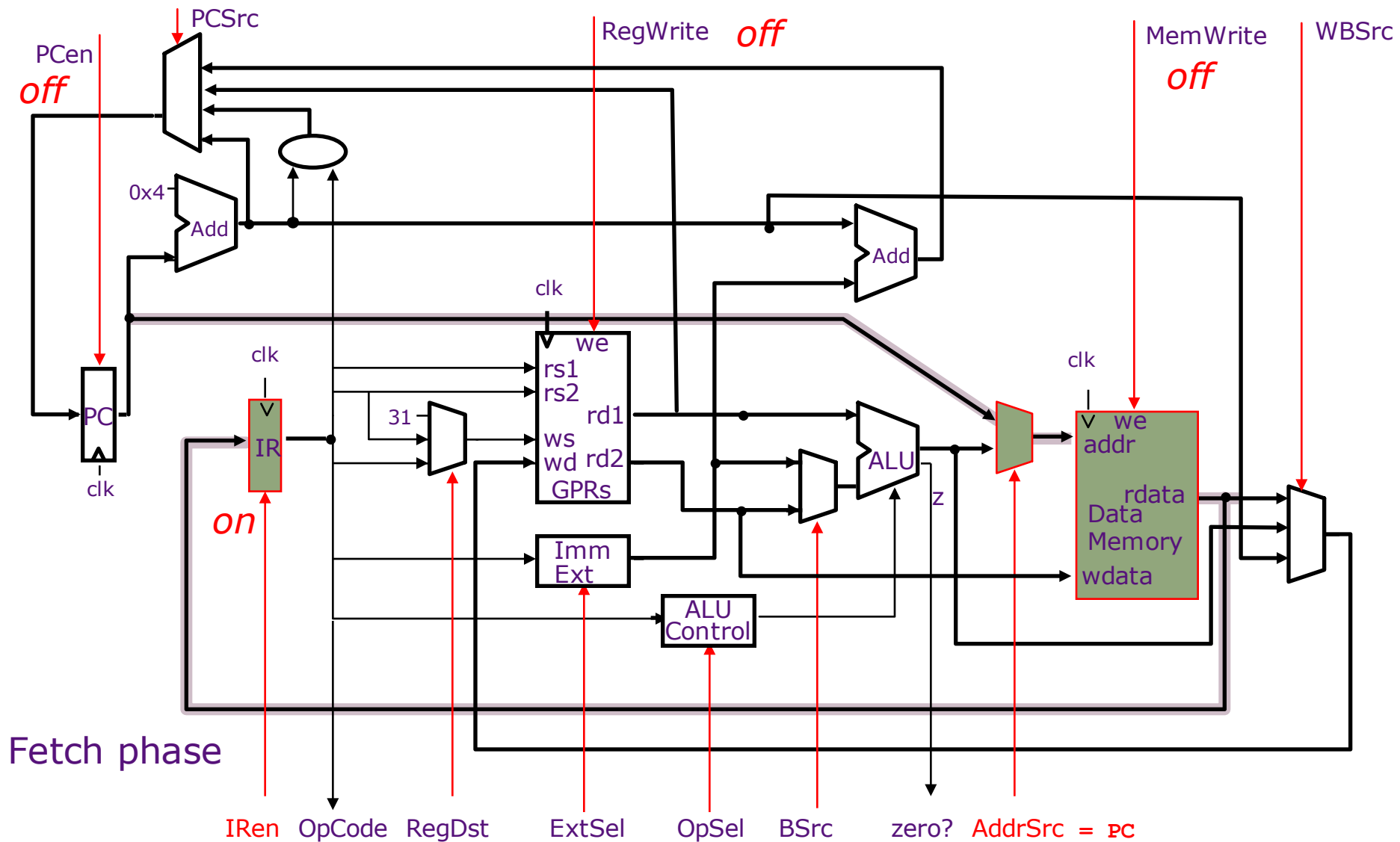

# Two-State Controller:

## *Princeton Architecture*


---

 

A flipflop can be used to remember the phase

# Hardwired Controller:

## *Princeton Architecture*

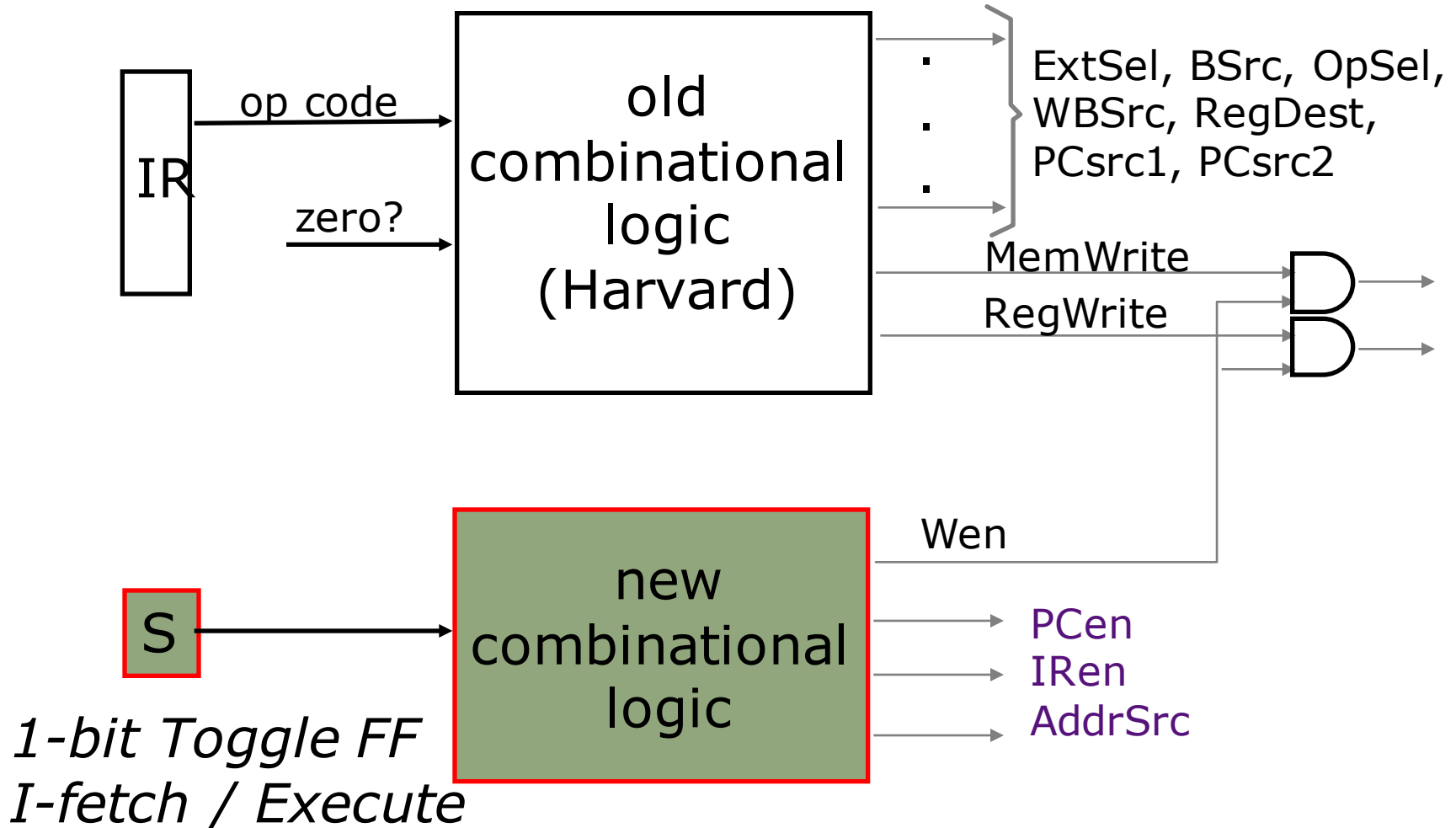

# Clock Rate vs CPI

$$t_{C\text{-Princeton}} > \max \{t_M, t_{RF} + t_{ALU} + t_M + t_{WB}\}$$

$$t_{C\text{-Princeton}} > t_{RF} + t_{ALU} + t_M + t_{WB}$$

$$t_{C\text{-Harvard}} > t_M + t_{RF} + t_{ALU} + t_M + t_{WB}$$

Suppose  $t_M \gg t_{RF} + t_{ALU} + t_{WB}$

$$t_{C\text{-Princeton}} = 0.5 * t_{C\text{-Harvard}}$$

$$CPI_{\text{Princeton}} = 2$$

$$CPI_{\text{Harvard}} = 1$$

*No difference in performance!*

Is it possible to design a controller for the Princeton architecture with  $CPI < 2$  ?

*CPI = Clock cycles Per Instruction*

*Stay tuned!*