 


Instruction Set Architecture & Hardwired, Non-pipelined ISA Implementation

Daniel Sanchez

Computer Science & Artificial Intelligence Lab
M.I.T.

The IBM 650 (1953-4)



[From 650 Manual, © IBM]

Programmer's view of a machine: IBM 650

A drum machine with 44 instructions

Instruction: 60 1234 1009

- “Load the contents of location 1234 into the *distribution*; put it also into the *upper accumulator*; set *lower accumulator* to zero; and then go to location 1009 for the next instruction.”

Programmer's view of a machine: IBM 650

A drum machine with 44 instructions

Instruction: 60 1234 1009

- “Load the contents of location 1234 into the *distribution*; put it also into the *upper accumulator*; set *lower accumulator* to zero; and then go to location 1009 for the next instruction.”

- Programmer's view of the machine was inseparable from the actual hardware implementation

Programmer's view of a machine: IBM 650

A drum machine with 44 instructions

Instruction: 60 1234 1009

- “Load the contents of location 1234 into the *distribution*; put it also into the *upper accumulator*; set *lower accumulator* to zero; and then go to location 1009 for the next instruction.”

- Programmer's view of the machine was inseparable from the actual hardware implementation
- Good programmers optimized the placement of instructions on the drum to reduce latency!

Compatibility Problem at IBM

Compatibility Problem at IBM

By early 60's, *IBM had 4 incompatible lines of computers!*

701	→	7094
650	→	7074
702	→	7080
1401	→	7010

Compatibility Problem at IBM

By early 60's, *IBM had 4 incompatible lines of computers!*

701	→	7094
650	→	7074
702	→	7080
1401	→	7010

Each system had its own

- Instruction set
- I/O system and Secondary Storage:
magnetic tapes, drums and disks
- Assemblers, compilers, libraries,...
- Market niche
business, scientific, real time, ...

Compatibility Problem at IBM

By early 60's, *IBM had 4 incompatible lines of computers!*

701	→	7094
650	→	7074
702	→	7080
1401	→	7010

Each system had its own

- Instruction set
- I/O system and Secondary Storage:
magnetic tapes, drums and disks
- Assemblers, compilers, libraries,...
- Market niche
business, scientific, real time, ...

⇒ *IBM 360*

IBM 360: Design Premises

Amdahl, Blaauw, and Brooks, 1964

The design must lend itself to *growth and successor machines*

- General method for connecting I/O devices
- Total performance - answers per month rather than bits per microsecond \Rightarrow *programming aids*
- Machine must be capable of *supervising itself* without manual intervention
- Built-in *hardware fault checking* and locating aids to reduce down time
- Simple to assemble systems with redundant I/O devices, memories, etc. for *fault tolerance*
- Some problems required floating point words larger than 36 bits

Processor State and Data Types

The information held in the processor at the end of an instruction to provide the processing context for the next instruction.

Processor State and Data Types

The information held in the processor at the end of an instruction to provide the processing context for the next instruction.

Program Counter, Accumulator, ...

Processor State and Data Types

The information held in the processor at the end of an instruction to provide the processing context for the next instruction.

Program Counter, Accumulator, ...

- The information held in the processor will be interpreted as having data types manipulated by the instructions.

Processor State and Data Types

The information held in the processor at the end of an instruction to provide the processing context for the next instruction.

Program Counter, Accumulator, ...

- The information held in the processor will be interpreted as having data types manipulated by the instructions.
- If the processing of an instruction can be interrupted then the *hardware* must save and restore the state in a transparent manner

Processor State and Data Types

The information held in the processor at the end of an instruction to provide the processing context for the next instruction.

Program Counter, Accumulator, ...

- The information held in the processor will be interpreted as having data types manipulated by the instructions.
- If the processing of an instruction can be interrupted then the *hardware* must save and restore the state in a transparent manner

Programmer's machine model is a **contract** between the hardware and software

Instruction Set

The control for changing the information held in the processor are specified by the instructions available in the instruction set architecture or ISA.

Instruction Set

The control for changing the information held in the processor are specified by the instructions available in the instruction set architecture or ISA.

Some things an ISA must specify:

Instruction Set

The control for changing the information held in the processor are specified by the instructions available in the instruction set architecture or ISA.

Some things an ISA must specify:

- *A way to reference registers and memory*

Instruction Set

The control for changing the information held in the processor are specified by the instructions available in the instruction set architecture or ISA.

Some things an ISA must specify:

- *A way to reference registers and memory*
- *The computational operations available*

Instruction Set

The control for changing the information held in the processor are specified by the instructions available in the instruction set architecture or ISA.

Some things an ISA must specify:

- *A way to reference registers and memory*
- *The computational operations available*
- *How to control the sequence of instructions*

Instruction Set

The control for changing the information held in the processor are specified by the instructions available in the instruction set architecture or ISA.

Some things an ISA must specify:

- *A way to reference registers and memory*
- *The computational operations available*
- *How to control the sequence of instructions*
- *A binary representation for all of the above*

Instruction Set

The control for changing the information held in the processor are specified by the instructions available in the instruction set architecture or ISA.

Some things an ISA must specify:

- *A way to reference registers and memory*
- *The computational operations available*
- *How to control the sequence of instructions*
- *A binary representation for all of the above*

*ISA must satisfy the needs of the software:
- assembler, compiler, OS, VM*

IBM 360: *A General-Purpose Register (GPR) Machine*

- Processor State
 - 16 General-Purpose 32-bit Registers
 - 4 Floating Point 64-bit Registers
 - A Program Status Word (PSW)
 - *PC, Condition codes, Control flags*

IBM 360: *A General-Purpose Register (GPR) Machine*

- Processor State
 - 16 General-Purpose 32-bit Registers
 - 4 Floating Point 64-bit Registers
 - A Program Status Word (PSW)
 - *PC, Condition codes, Control flags*
- Data Formats
 - 8-bit bytes, 16-bit half-words, 32-bit words, 64-bit double-words
 - 24-bit addresses

IBM 360: *A General-Purpose Register (GPR) Machine*

- Processor State
 - 16 General-Purpose 32-bit Registers
 - 4 Floating Point 64-bit Registers
 - A Program Status Word (PSW)
 - *PC, Condition codes, Control flags*
- Data Formats
 - 8-bit bytes, 16-bit half-words, 32-bit words, 64-bit double-words
 - 24-bit addresses
- A 32-bit machine with 24-bit addresses

IBM 360: *A General-Purpose Register (GPR) Machine*

- Processor State
 - 16 General-Purpose 32-bit Registers
 - 4 Floating Point 64-bit Registers
 - A Program Status Word (PSW)
 - *PC, Condition codes, Control flags*
- Data Formats
 - 8-bit bytes, 16-bit half-words, 32-bit words, 64-bit double-words
 - 24-bit addresses
- A 32-bit machine with 24-bit addresses
 - *No instruction contains a 24-bit address!*

IBM 360: *A General-Purpose Register (GPR) Machine*

- Processor State
 - 16 General-Purpose 32-bit Registers
 - 4 Floating Point 64-bit Registers
 - A Program Status Word (PSW)
 - *PC, Condition codes, Control flags*
- Data Formats
 - 8-bit bytes, 16-bit half-words, 32-bit words, 64-bit double-words
 - 24-bit addresses
- A 32-bit machine with 24-bit addresses
 - *No instruction contains a 24-bit address!*
- Precise interrupts

IBM 360: Initial Implementations (1964)


	<i>Model 30</i>	<i>. . .</i>	<i>Model 70</i>
<i>Memory Capacity</i>	8K - 64 KB		256K - 512 KB
<i>Memory Cycle</i>	2.0 μ s	<i>...</i>	1.0 μ s
<i>Datapath</i>	8-bit		64-bit
<i>Circuit Delay</i>	30 nsec/level		5 nsec/level
<i>Registers</i>	in Main Store		in Transistor
<i>Control Store</i>	Read only 1 μ sec		Dedicated circuits

- Six implementations (Models, 30, 40, 50, 60, 62, 70)
- 50x performance difference across models
- *ISA completely hid the underlying technological differences between various models*

With minor modifications, IBM 360 ISA is still in use

IBM 360: Fifty-five years later... z15 Microprocessor

- 9.2 billion transistors, 12-core design
- Up to 190 cores (2 spare) per system
- 5.2 GHz, 14nm CMOS technology
- 64-bit virtual addressing
 - Original 360 was 24-bit; 370 was a 31-bit extension
- Superscalar, out-of-order
 - 12-wide issue
 - Up to 180 instructions in flight
- 16K-entry Branch Target Buffer
 - Very large buffer to support commercial workloads
- Four Levels of caches
 - 128KB L1 I-cache, 128KB L1 D-cache
 - 4MB L2 cache per core
 - 256MB shared on-chip L3 cache
 - 960MB shared off-chip L4 cache
- Up to 40TB of main memory per system

 

September 2019
Image credit: IBM

Instruction Set Architecture (ISA) versus Implementation

- ISA is the hardware/software interface
 - Defines set of programmer visible state
 - Defines data types
 - Defines instruction semantics (operations, sequencing)
 - Defines instruction format (bit encoding)
 - Examples: *MIPS, RISC-V, Alpha, x86, IBM 360, VAX, ARM, JVM*

Instruction Set Architecture (ISA) versus Implementation

- ISA is the hardware/software interface
 - Defines set of programmer visible state
 - Defines data types
 - Defines instruction semantics (operations, sequencing)
 - Defines instruction format (bit encoding)
 - Examples: *MIPS, RISC-V, Alpha, x86, IBM 360, VAX, ARM, JVM*
- Many possible implementations of one ISA
 - 360 implementations: model 30 (c. 1964), z15 (c. 2019)
 - x86 implementations: *8086 (c. 1978), 80186, 286, 386, 486, Pentium, Pentium Pro, Pentium-4, Core i7, AMD Athlon, AMD Opteron, Transmeta Crusoe, SoftPC*
 - MIPS implementations: *R2000, R4000, R10000, ...*
 - JVM: *HotSpot, PicoJava, ARM Jazelle, ...*

Processor Performance

$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} * \frac{\text{Cycles}}{\text{Instruction}} * \frac{\text{Time}}{\text{Cycle}}$$

- Instructions per program depends on source code, compiler technology and ISA
- Cycles per instructions (CPI) depends upon the ISA and the microarchitecture
- Time per cycle depends upon the microarchitecture and the base technology

Processor Performance

$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} * \frac{\text{Cycles}}{\text{Instruction}} * \frac{\text{Time}}{\text{Cycle}}$$

- Instructions per program depends on source code, compiler technology and ISA
- Cycles per instructions (CPI) depends upon the ISA and the microarchitecture
- Time per cycle depends upon the microarchitecture and the base technology

Microarchitecture	CPI	cycle time
Microcoded	> 1	short
Single-cycle unpipelined	1	long
Pipelined	1	short

Processor Performance

$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} * \frac{\text{Cycles}}{\text{Instruction}} * \frac{\text{Time}}{\text{Cycle}}$$

- Instructions per program depends on source code, compiler technology and ISA
- Cycles per instructions (CPI) depends upon the ISA and the microarchitecture
- Time per cycle depends upon the microarchitecture and the base technology

Microarchitecture	CPI	cycle time
Microcoded	> 1	short
Single-cycle unpipelined	1	long
Pipelined	1	short


rest of
this lecture
→

Hardware Elements

- Combinational circuits
 - Mux, Demux, Decoder, ALU, ...


Hardware Elements

 - Combinational circuits
 - Mux, Demux, Decoder, ALU, ...




Hardware Elements

 - Combinational circuits
 - Mux, Demux, Decoder, ALU, ...



Hardware Elements




 
- Combinational circuits
 - Mux, Demux, Decoder, ALU, ...



Hardware Elements

- Combinational circuits


- Mux, Demux, Decoder, ALU, ...

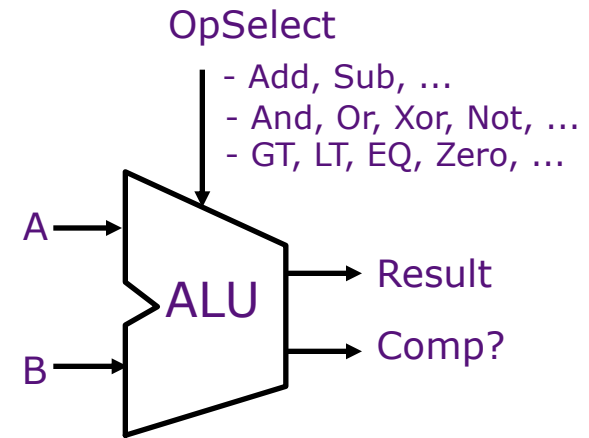   

Hardware Elements

- Combinational circuits

- Mux, Demux, Decoder, ALU, ...

 


- Synchronous state elements

- Flipflop, Register, Register file, SRAM, DRAM

Hardware Elements


- Combinational circuits

- Mux, Demux, Decoder, ALU, ...

 

- Synchronous state elements

 
- Flipflop, Register, Register file, SRAM, DRAM





Edge-triggered: Data is sampled at the rising edge

Register Files



Register Files

 

Register Files

  


Register Files

  


No timing issues when reading and writing the same register
(writes happen at the end of the cycle)

Register File Implementation

 


- Register files with a large number of ports are difficult to design
 - Area scales with ports²
 - Almost all Alpha instructions have exactly 2 register source operands
 - *Intel's Itanium GPR File has 128 registers with 8 read ports and 4 write ports!!*

A Simple Memory Model

 

- Reads and writes are always completed in one cycle
 - A Read can be done any time (i.e., combinational)
 - If enabled, a Write is performed at the rising clock edge
(the write address and data must be stable at the clock edge)

A Simple Memory Model

 

- Reads and writes are always completed in one cycle
 - A Read can be done any time (i.e., combinational)
 - If enabled, a Write is performed at the rising clock edge
(*the write address and data must be stable at the clock edge*)

Later in the course we will present a more realistic model of memory

Implementing MIPS: Single-cycle per instruction datapath & control logic

The MIPS ISA

Processor State

- 32 32-bit GPRs, R0 always contains a 0
- 32 single precision FPRs, may also be viewed as
 - 16 double precision FPRs
- FP status register, used for FP compares & exceptions
- PC, the program counter
- Some other special registers

Data types

- 8-bit byte, 16-bit half word
- 32-bit word for integers
- 32-bit word for single precision floating point
- 64-bit word for double precision floating point

Load/Store style instruction set

- Data addressing modes: immediate & indexed
- Branch addressing modes: PC relative & register indirect
- Byte-addressable memory, big-endian mode

All instructions are 32 bits

Instruction Execution

Execution of an instruction involves

Instruction Execution

Execution of an instruction involves

1. Instruction fetch

Instruction Execution

Execution of an instruction involves

1. Instruction fetch
2. Decode

Instruction Execution

Execution of an instruction involves

1. Instruction fetch
2. Decode
3. Register fetch

Instruction Execution

Execution of an instruction involves

1. Instruction fetch
2. Decode
3. Register fetch
4. ALU operation

Instruction Execution

Execution of an instruction involves

1. Instruction fetch
2. Decode
3. Register fetch
4. ALU operation
5. Memory operation (optional)

Instruction Execution

Execution of an instruction involves

1. Instruction fetch
2. Decode
3. Register fetch
4. ALU operation
5. Memory operation (optional)
6. Write back


Instruction Execution

Execution of an instruction involves

1. Instruction fetch
2. Decode
3. Register fetch
4. ALU operation
5. Memory operation (optional)
6. Write back



And computing the address of the
next instruction (next PC)

Datapath: Reg-Reg ALU Instructions

 



$rd \leftarrow (rs) \text{ func } (rt)$

Datapath: Reg-Reg ALU Instructions

  



$rd \leftarrow (rs) \text{ func } (rt)$

Datapath: Reg-Reg ALU Instructions

  


$rd \leftarrow (rs) \text{ func } (rt)$

Datapath: Reg-Reg ALU Instructions

 
 


$rd \leftarrow (rs) \text{ func } (rt)$

Datapath: Reg-Reg ALU Instructions


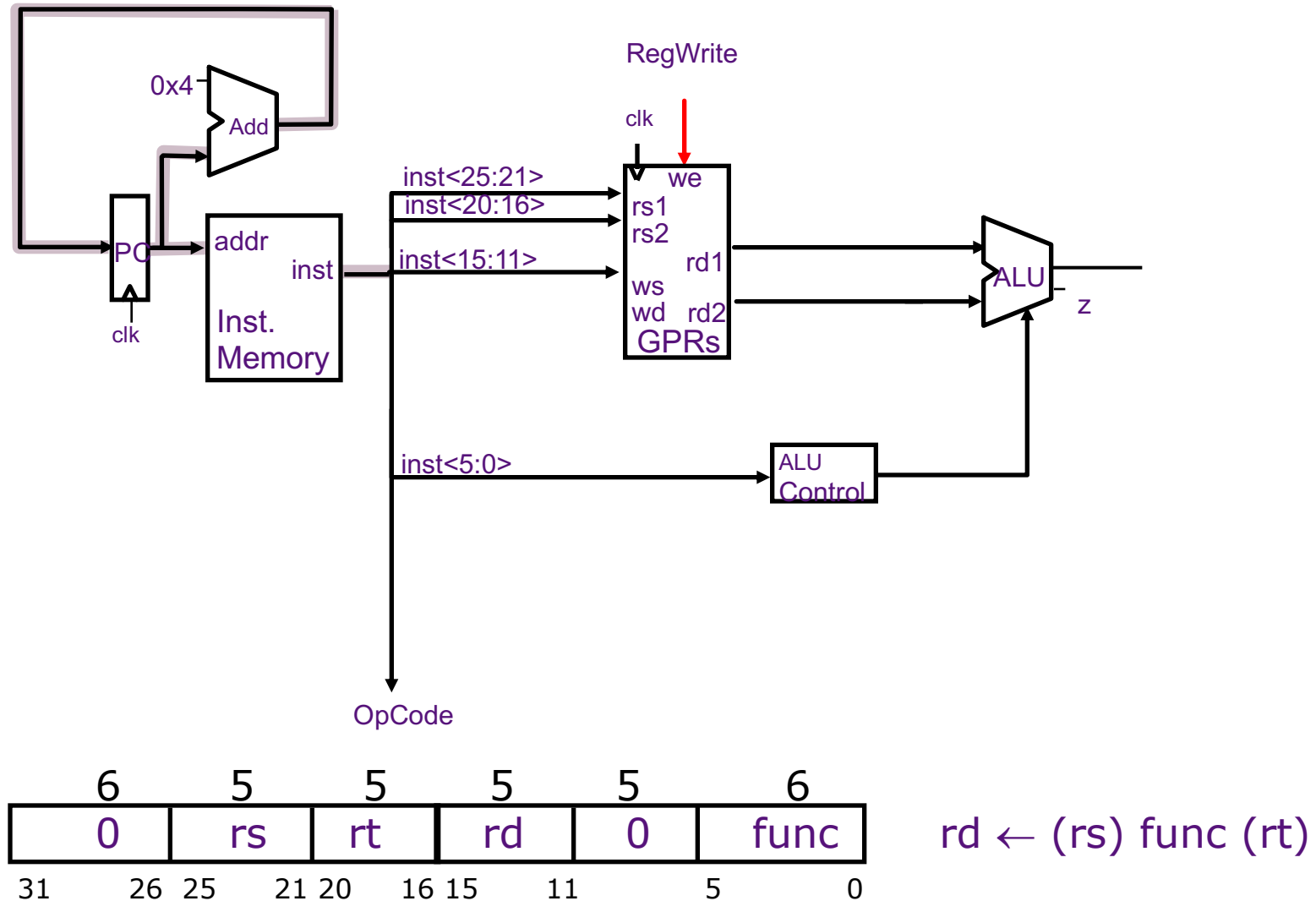


Datapath: Reg-Reg ALU Instructions

 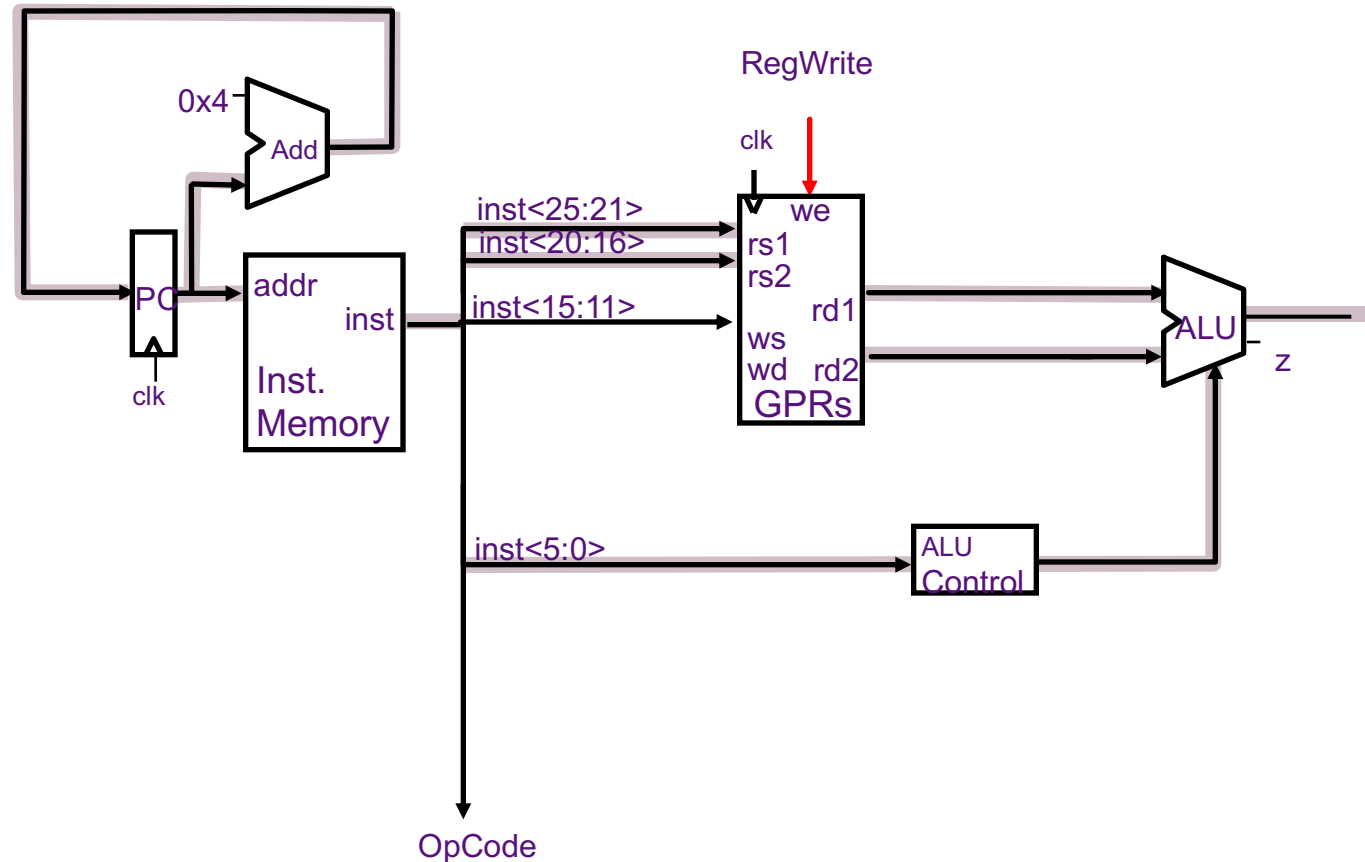

$$rd \leftarrow (rs) \text{ func } (rt)$$



Datapath: Reg-Reg ALU Instructions

  

RegWrite Timing?



$$rd \leftarrow (rs) \text{ func } (rt)$$

Datapath: Reg-Imm ALU Instructions

 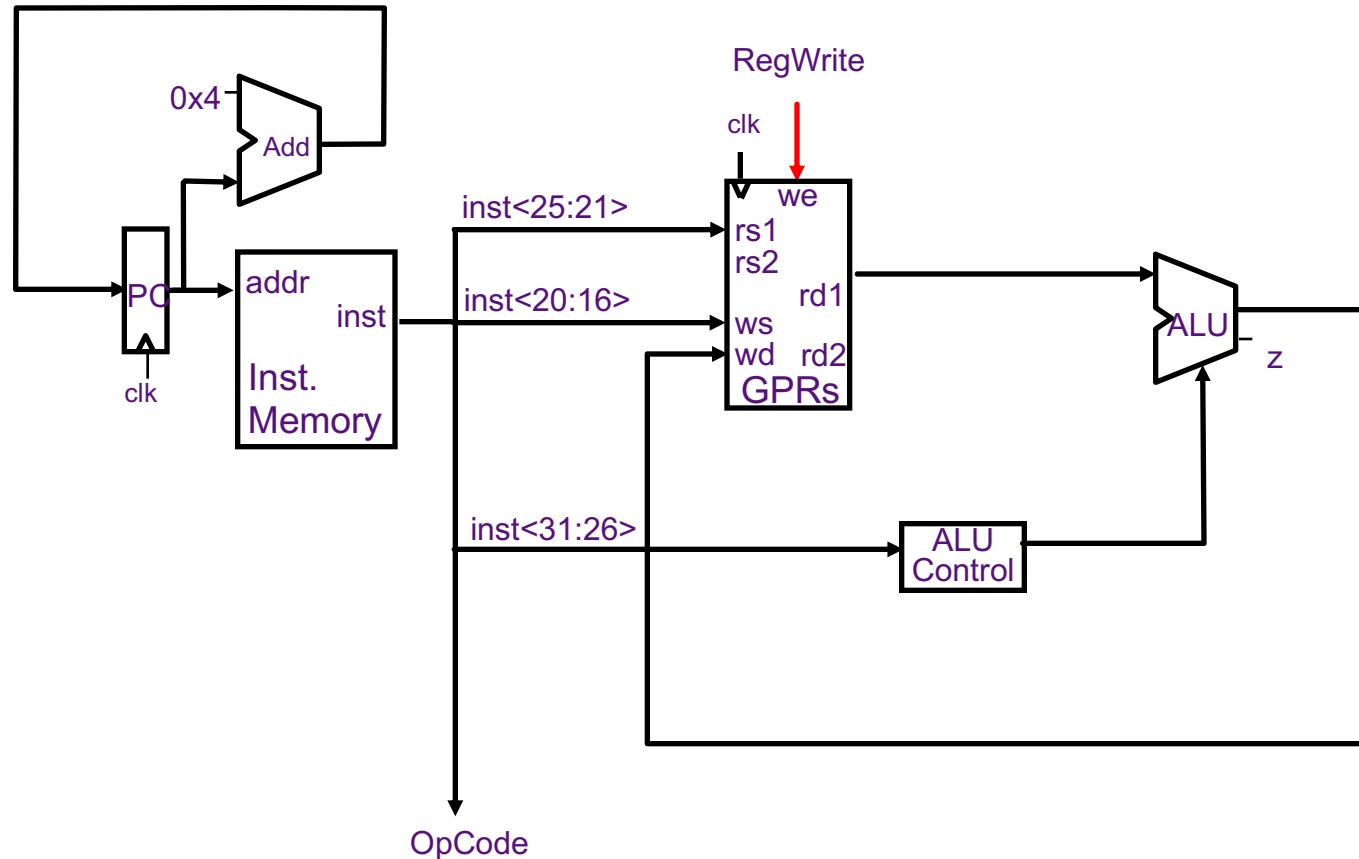



$rt \leftarrow (rs) \text{ op } \text{immediate}$

Datapath: Reg-Imm ALU Instructions

  

$rt \leftarrow (rs) \text{ op } \text{immediate}$



Conflicts in Merging Datapath

 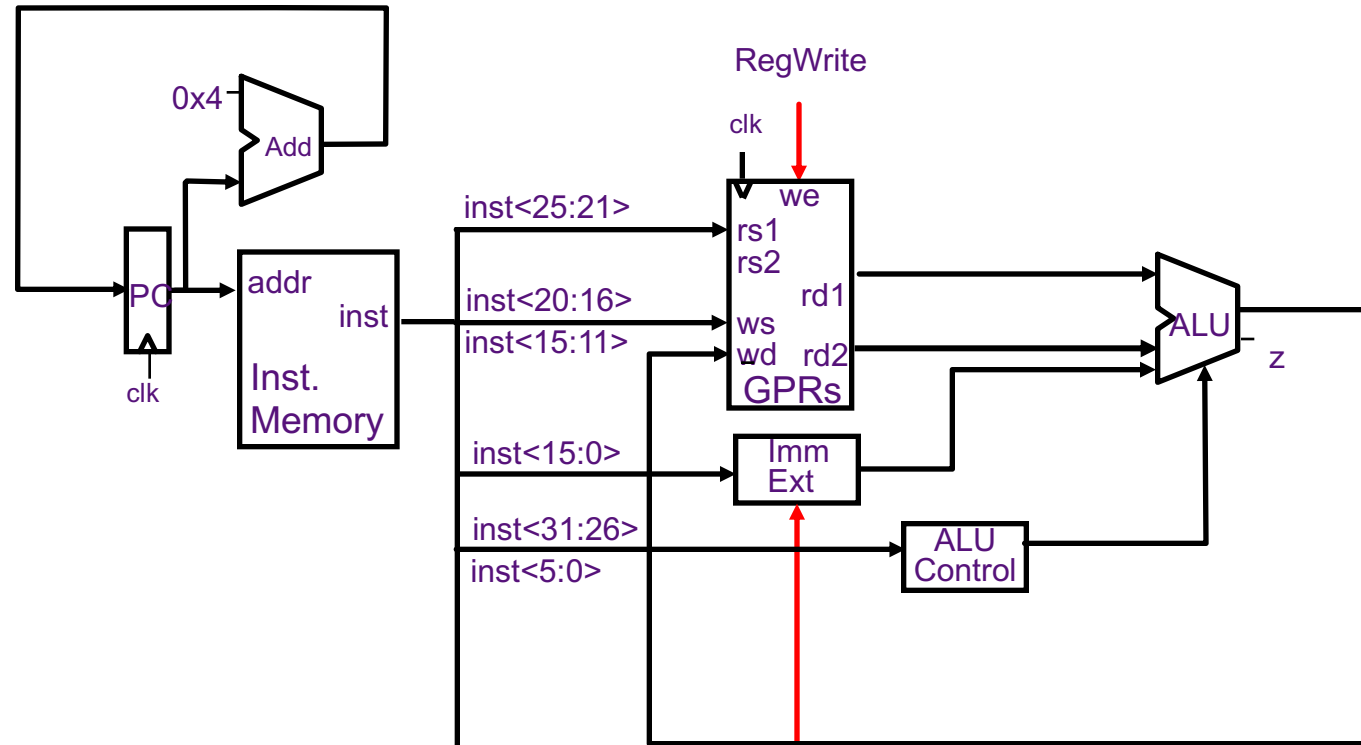

$rd \leftarrow (rs) \text{ func } (rt)$

$rt \leftarrow (rs) \text{ op } \text{immediate}$



Conflicts in Merging Datapath

 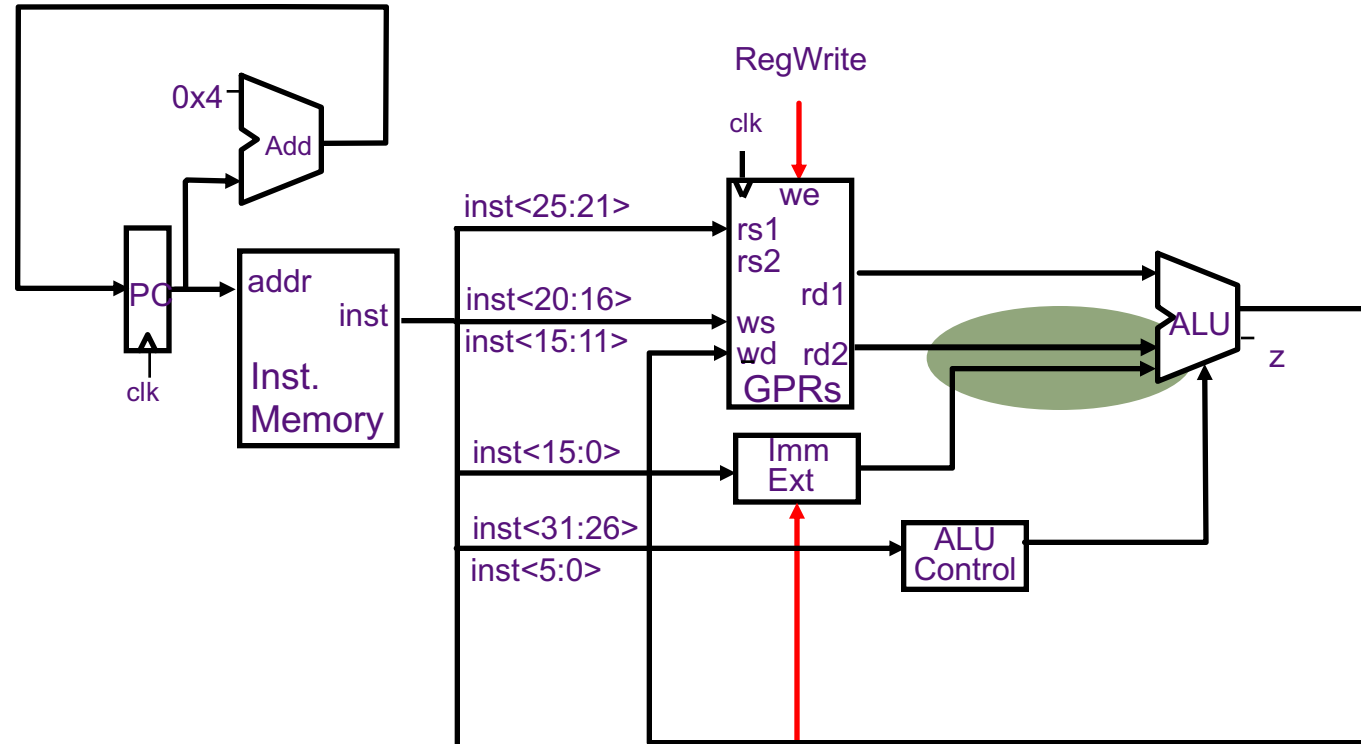

$rd \leftarrow (rs) \text{ func } (rt)$

$rt \leftarrow (rs) \text{ op } \text{immediate}$



Conflicts in Merging Datapath

 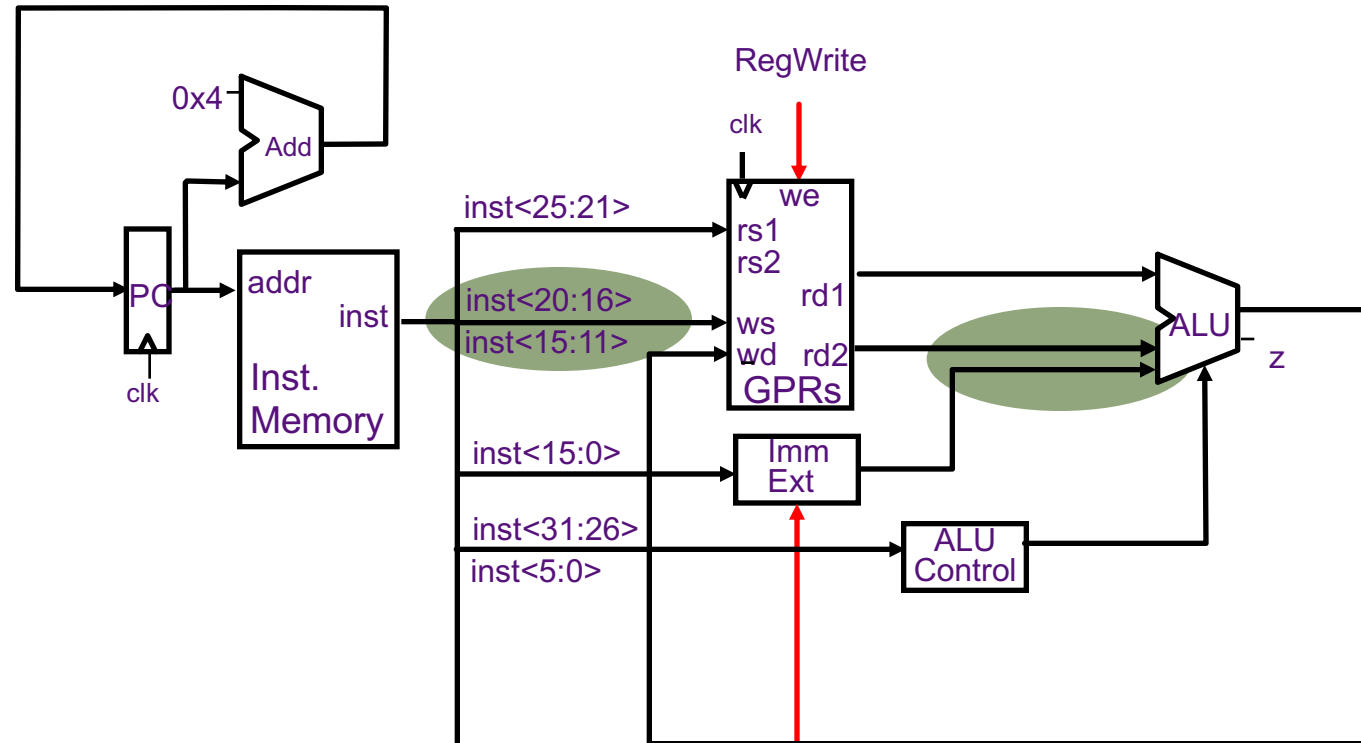

$rd \leftarrow (rs) \text{ func } (rt)$

$rt \leftarrow (rs) \text{ op } \text{immediate}$



Conflicts in Merging Datapath

 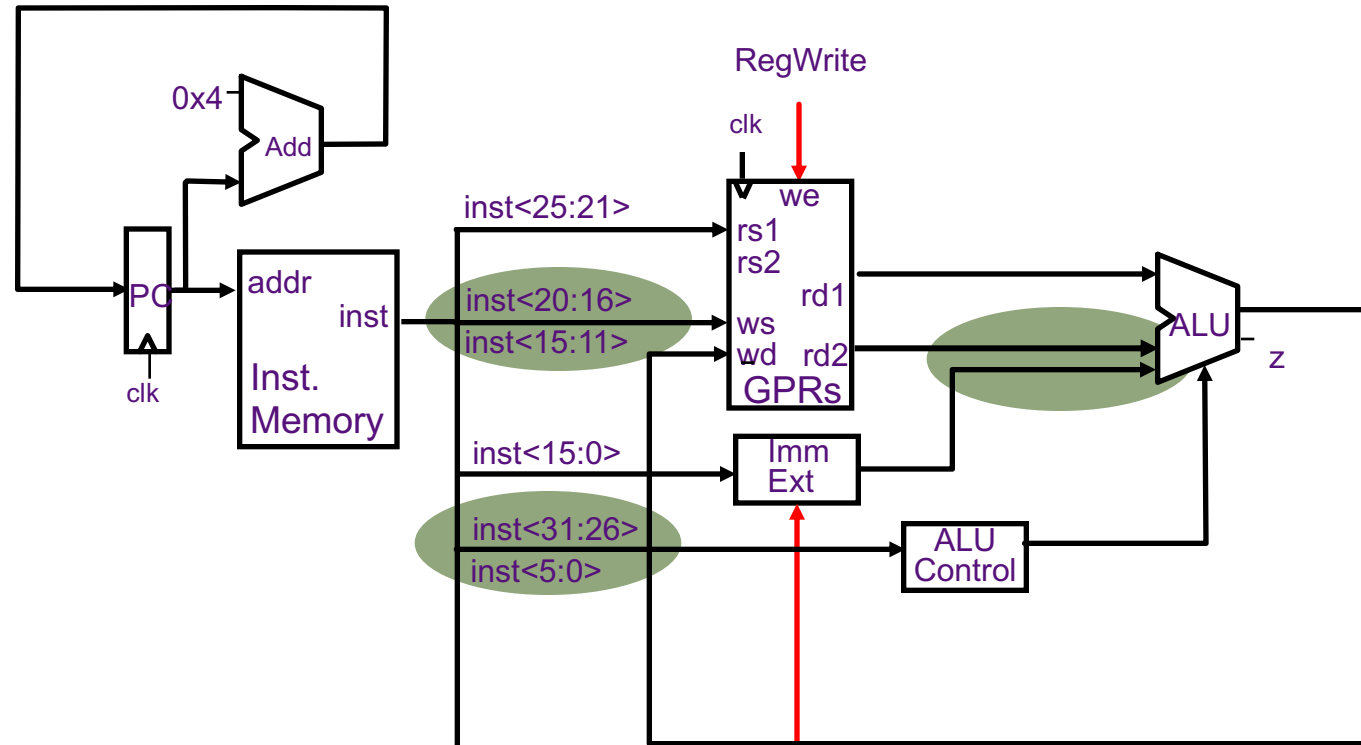

$rd \leftarrow (rs) \text{ func } (rt)$

$rt \leftarrow (rs) \text{ op } \text{immediate}$



Conflicts in Merging Datapath

  

$rd \leftarrow (rs) \text{ func } (rt)$

$rt \leftarrow (rs) \text{ op } \text{immediate}$



Datapath for ALU Instructions

 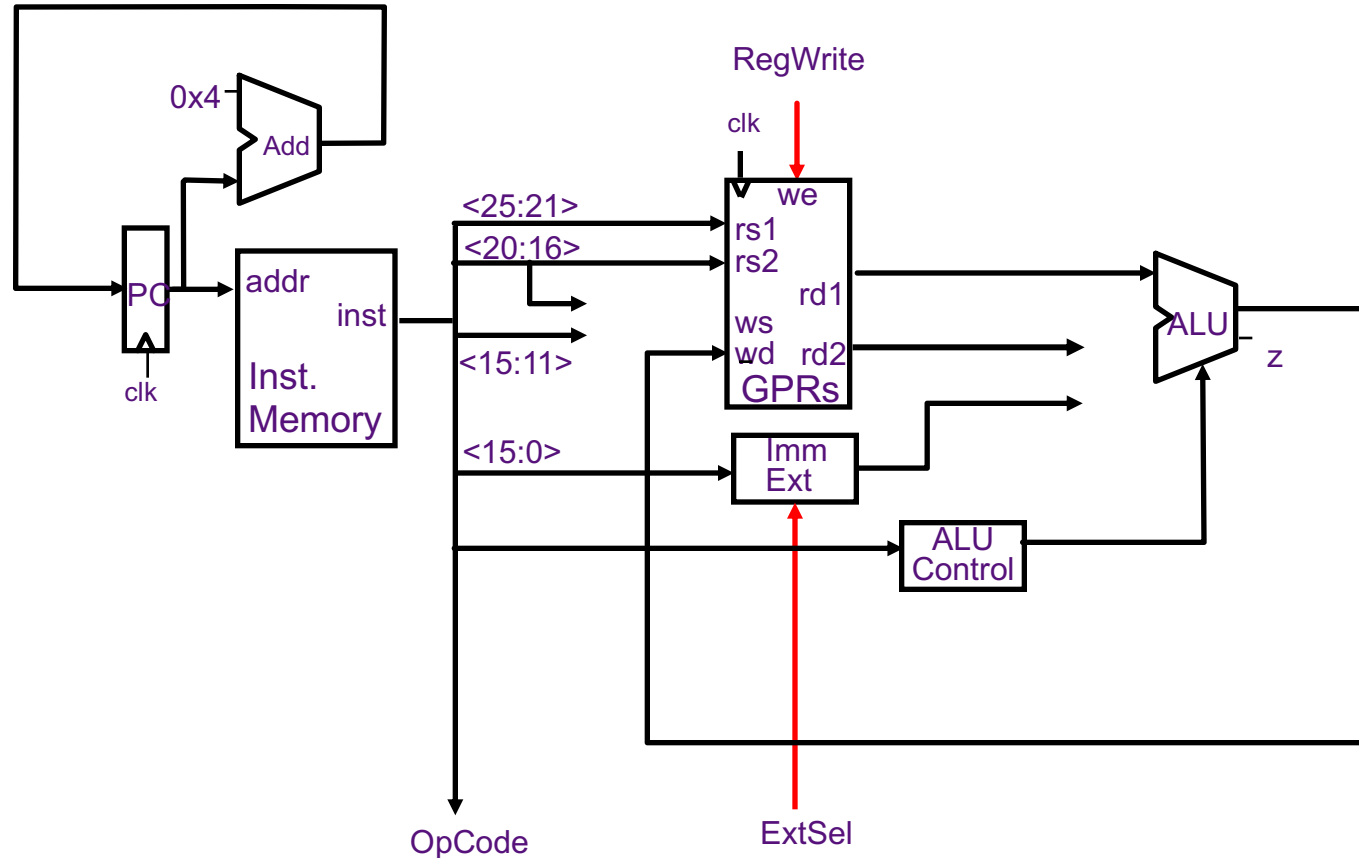

$rd \leftarrow (rs) \text{ func } (rt)$

$rt \leftarrow (rs) \text{ op } \text{immediate}$



Datapath for ALU Instructions

 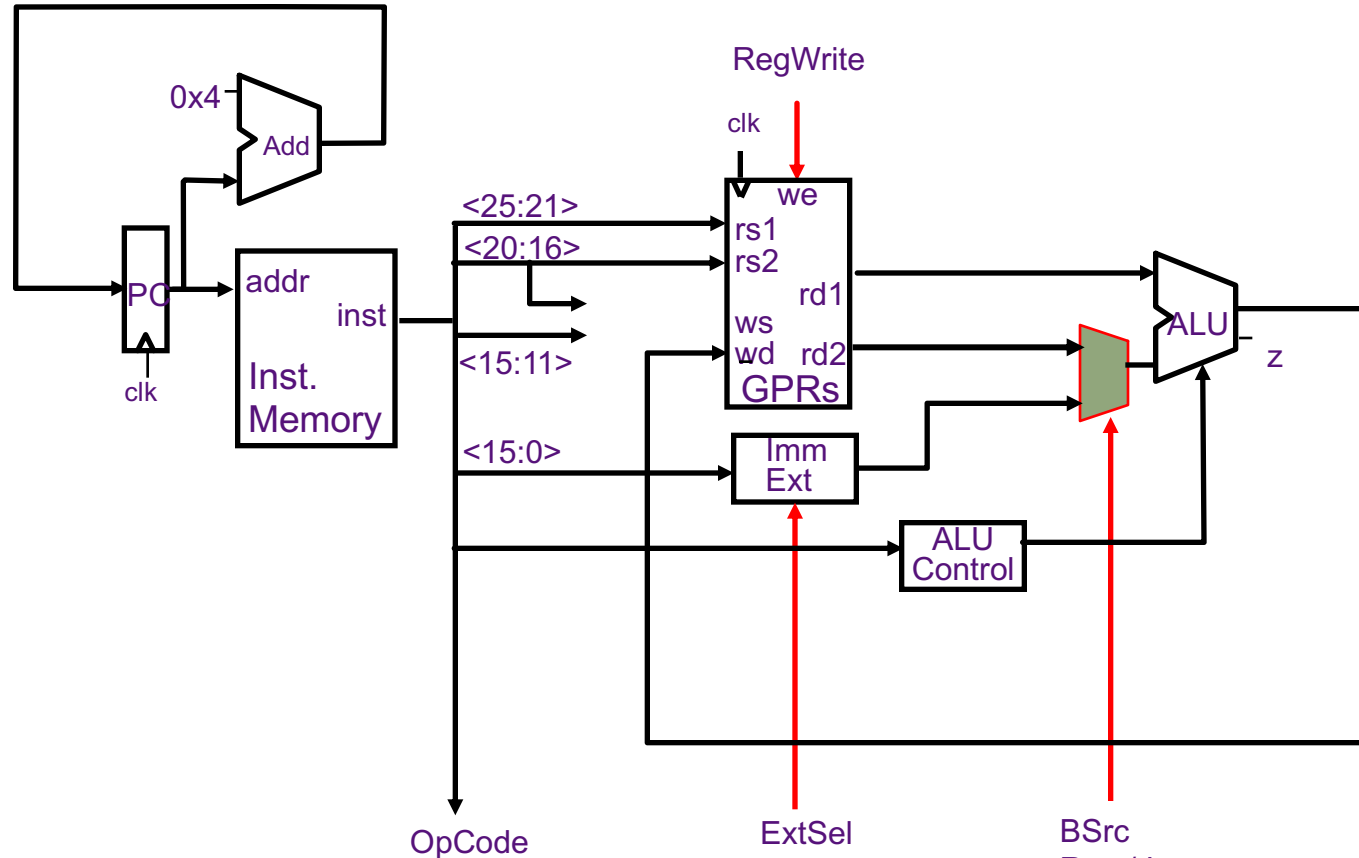

$rd \leftarrow (rs) \text{ func } (rt)$

$rt \leftarrow (rs) \text{ op } \text{immediate}$



Datapath for ALU Instructions

 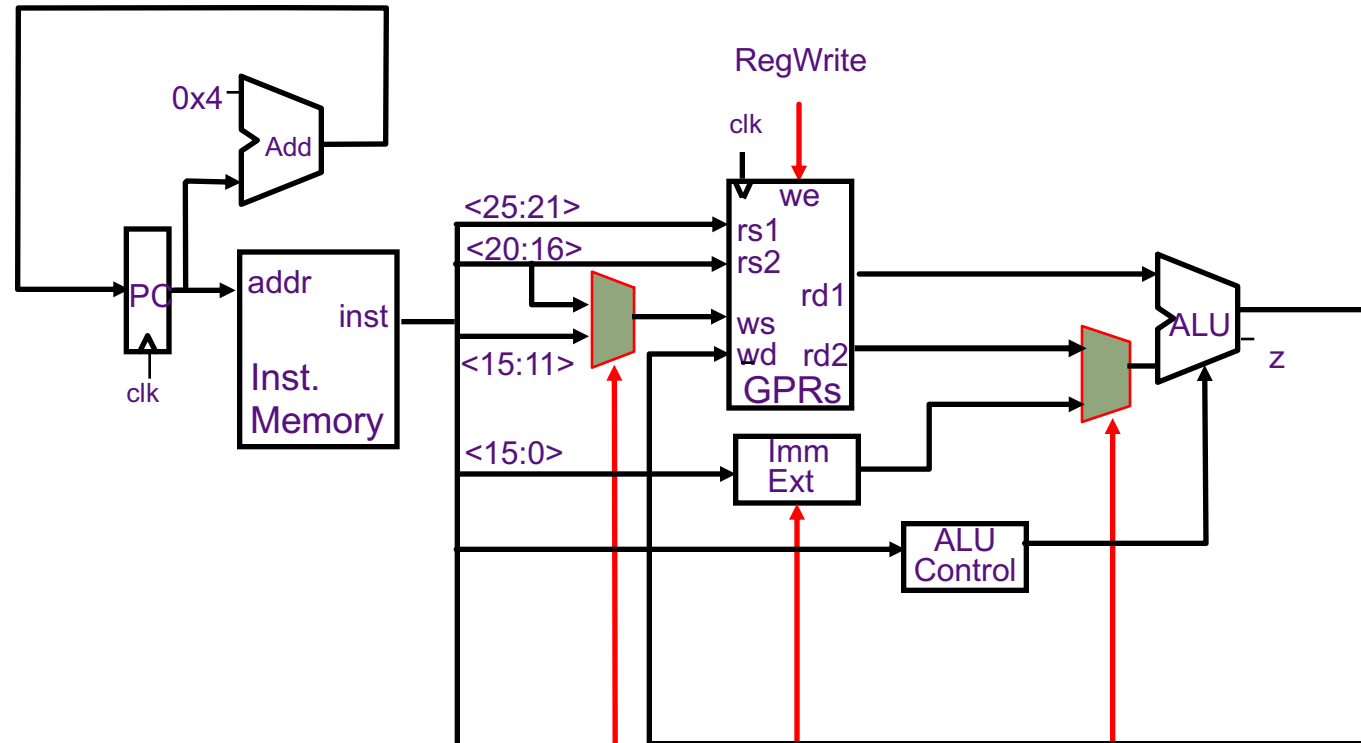

$rd \leftarrow (rs) \text{ func } (rt)$

$rt \leftarrow (rs) \text{ op } \text{immediate}$

Datapath for ALU Instructions

  

$rd \leftarrow (rs) \text{ func } (rt)$

$rt \leftarrow (rs) \text{ op } \text{immediate}$

Datapath for Memory Instructions

Should program and data memory be separate?

Harvard style: separate (Aiken and Mark 1 influence)

- read-only program memory
- read/write data memory

Princeton style: the same (von Neumann's influence)

- single read/write memory for program and data

Datapath for Memory Instructions

Should program and data memory be separate?

Harvard style: separate (Aiken and Mark 1 influence)

- read-only program memory
- read/write data memory

- Note:

There must be a way to load the program memory

Princeton style: the same (von Neumann's influence)

- single read/write memory for program and data

Datapath for Memory Instructions

Should program and data memory be separate?

Harvard style: separate (Aiken and Mark 1 influence)

- read-only program memory
- read/write data memory

- Note:

There must be a way to load the program memory

Princeton style: the same (von Neumann's influence)


- single read/write memory for program and data

- Note:

Executing a Load or Store instruction requires accessing the memory more than once

Load/Store Instructions

Harvard Datapath

 



addressing mode
(rs) + displacement

rs is the base register

rt is the destination of a Load or the source for a Store

Load/Store Instructions

Harvard Datapath

 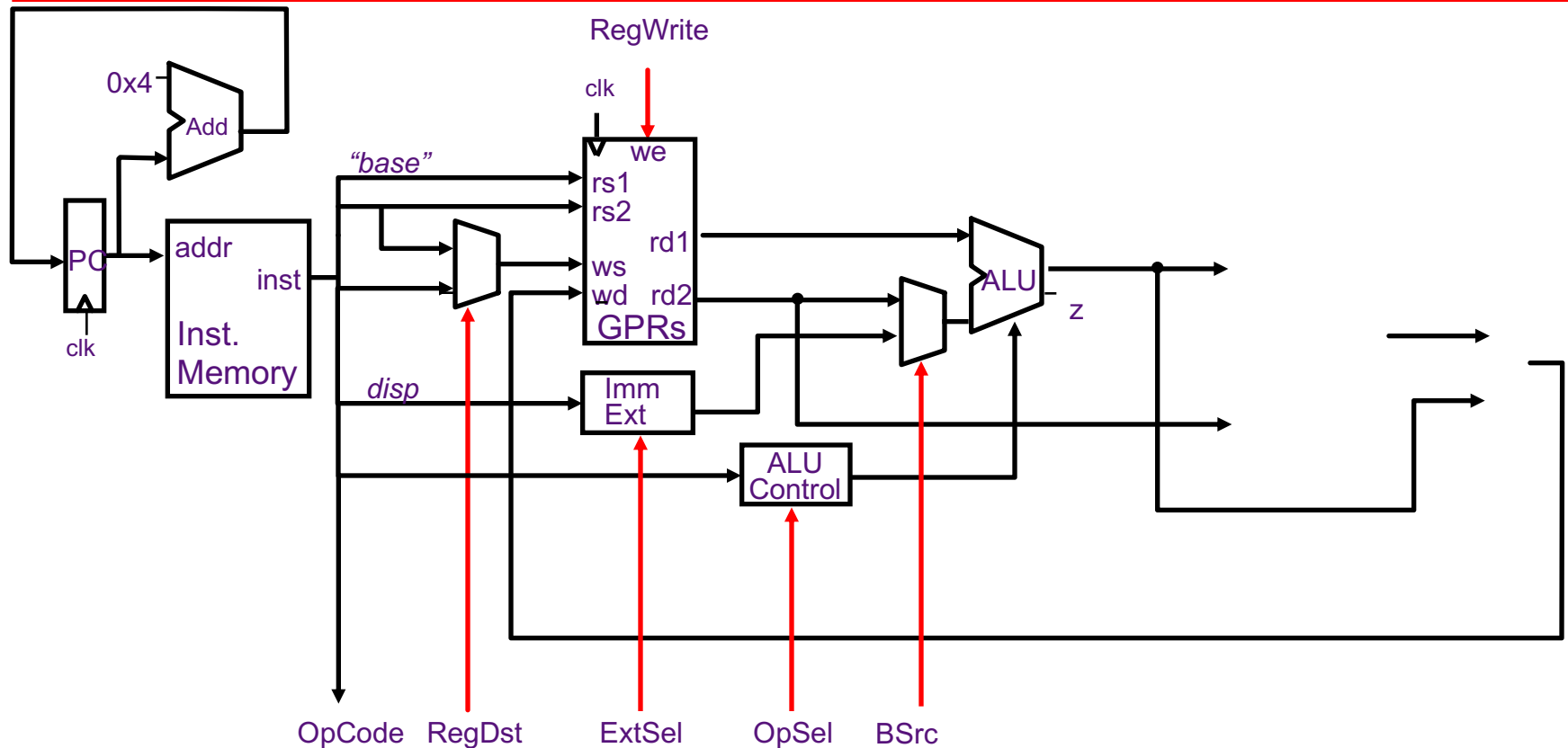



addressing mode
(rs) + displacement

rs is the base register

rt is the destination of a Load or the source for a Store

Load/Store Instructions

Harvard Datapath

 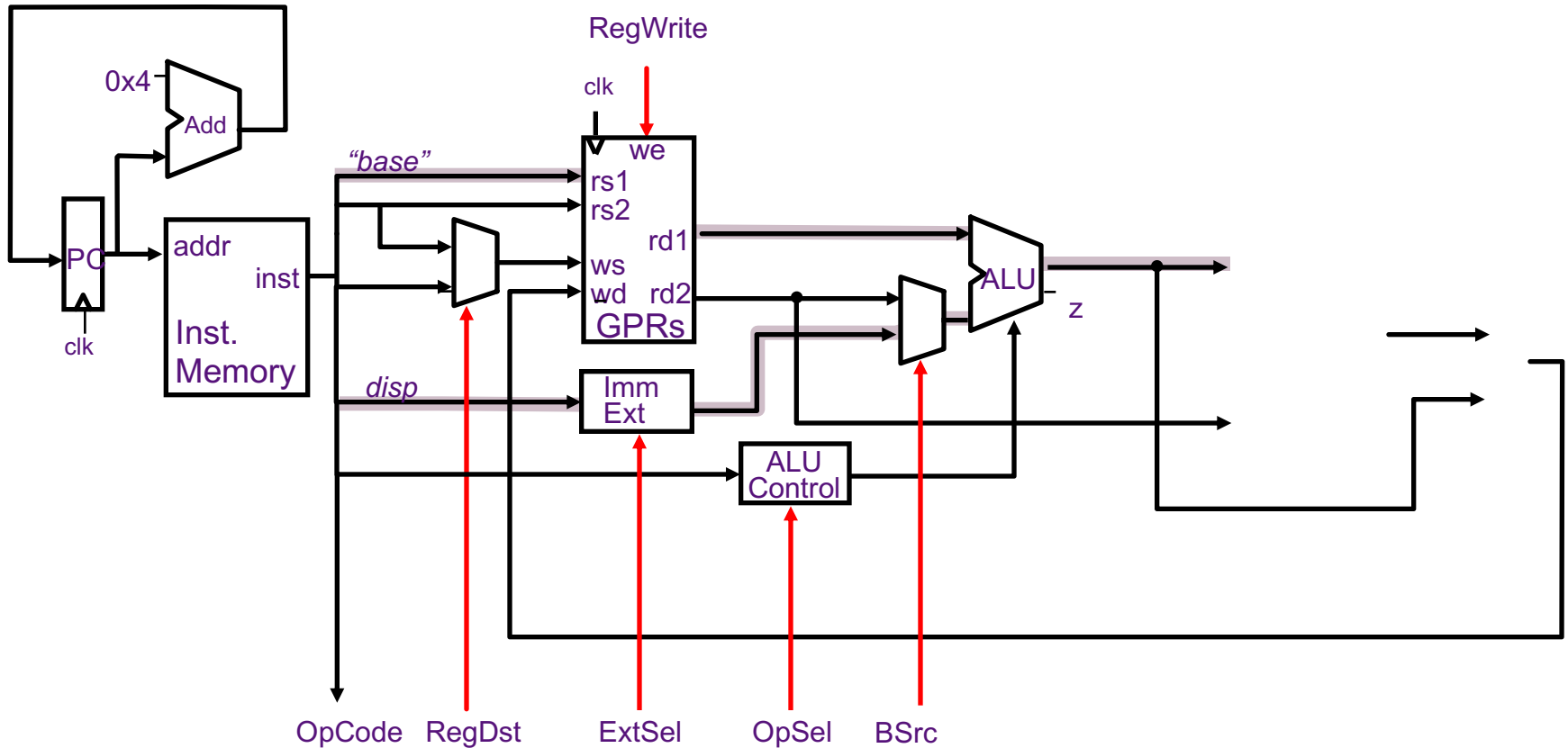



addressing mode
(rs) + displacement

rs is the base register

rt is the destination of a Load or the source for a Store

Load/Store Instructions

Harvard Datapath

 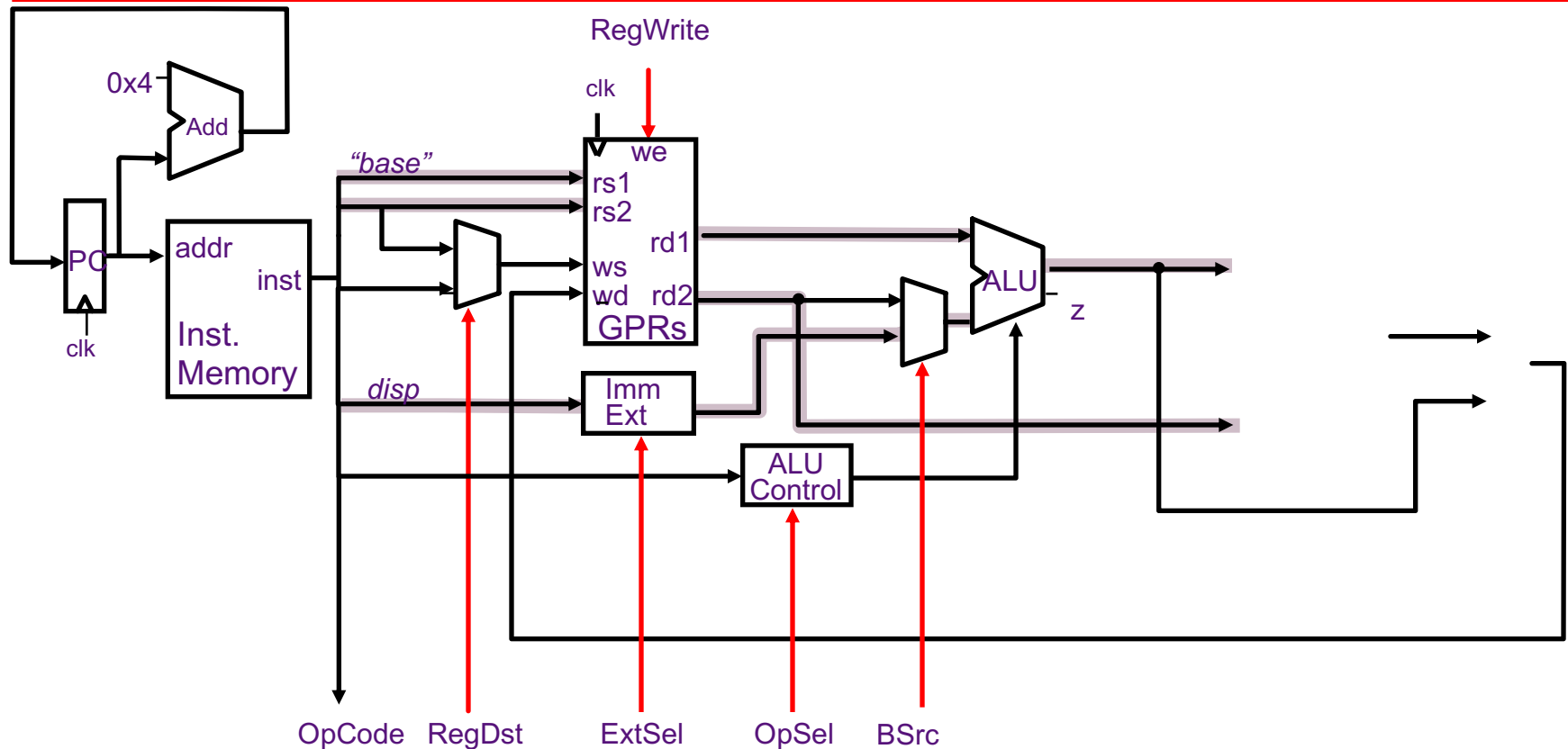



addressing mode
(rs) + displacement

rs is the base register

rt is the destination of a Load or the source for a Store

Load/Store Instructions

Harvard Datapath

 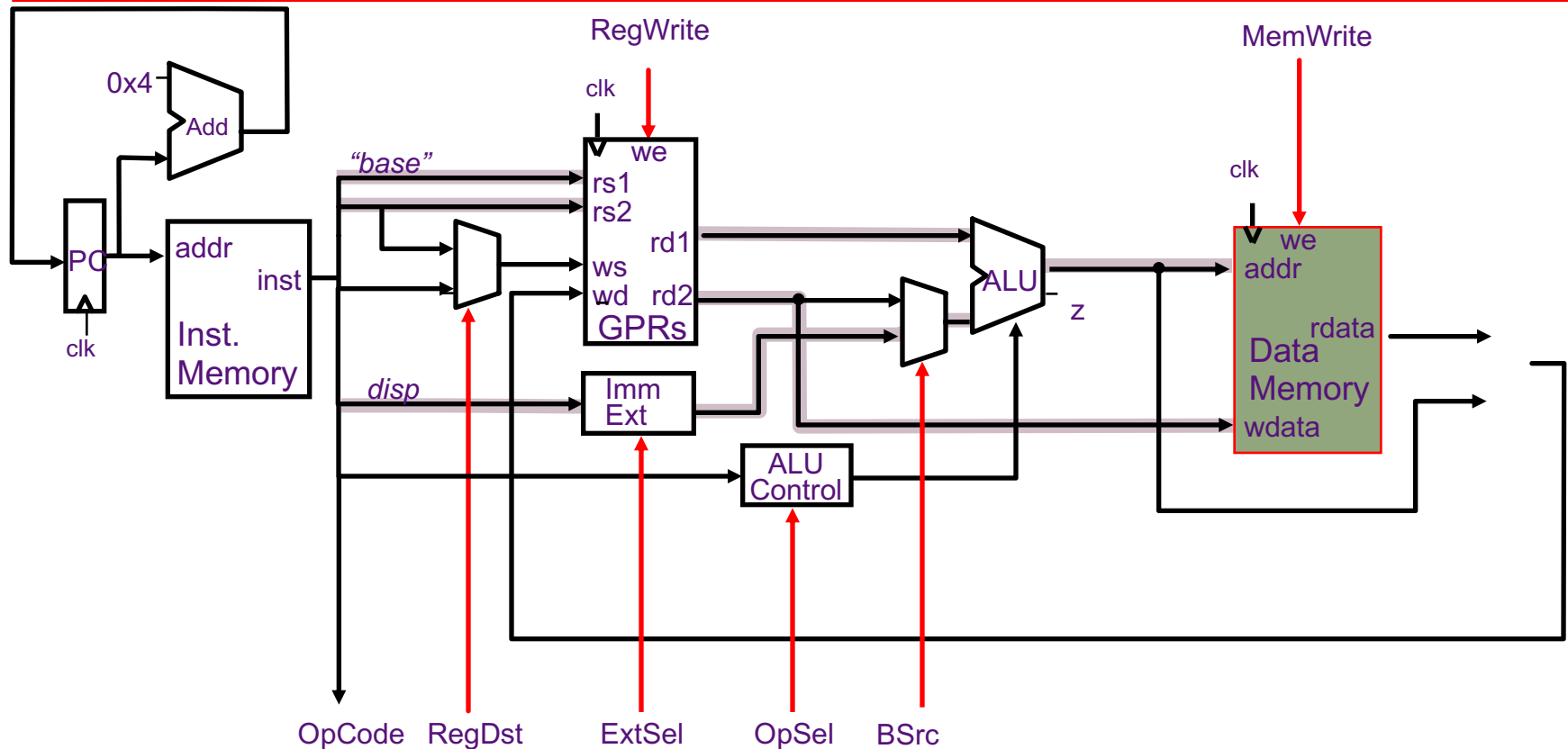



addressing mode
(rs) + displacement

rs is the base register

rt is the destination of a Load or the source for a Store

Load/Store Instructions

Harvard Datapath

 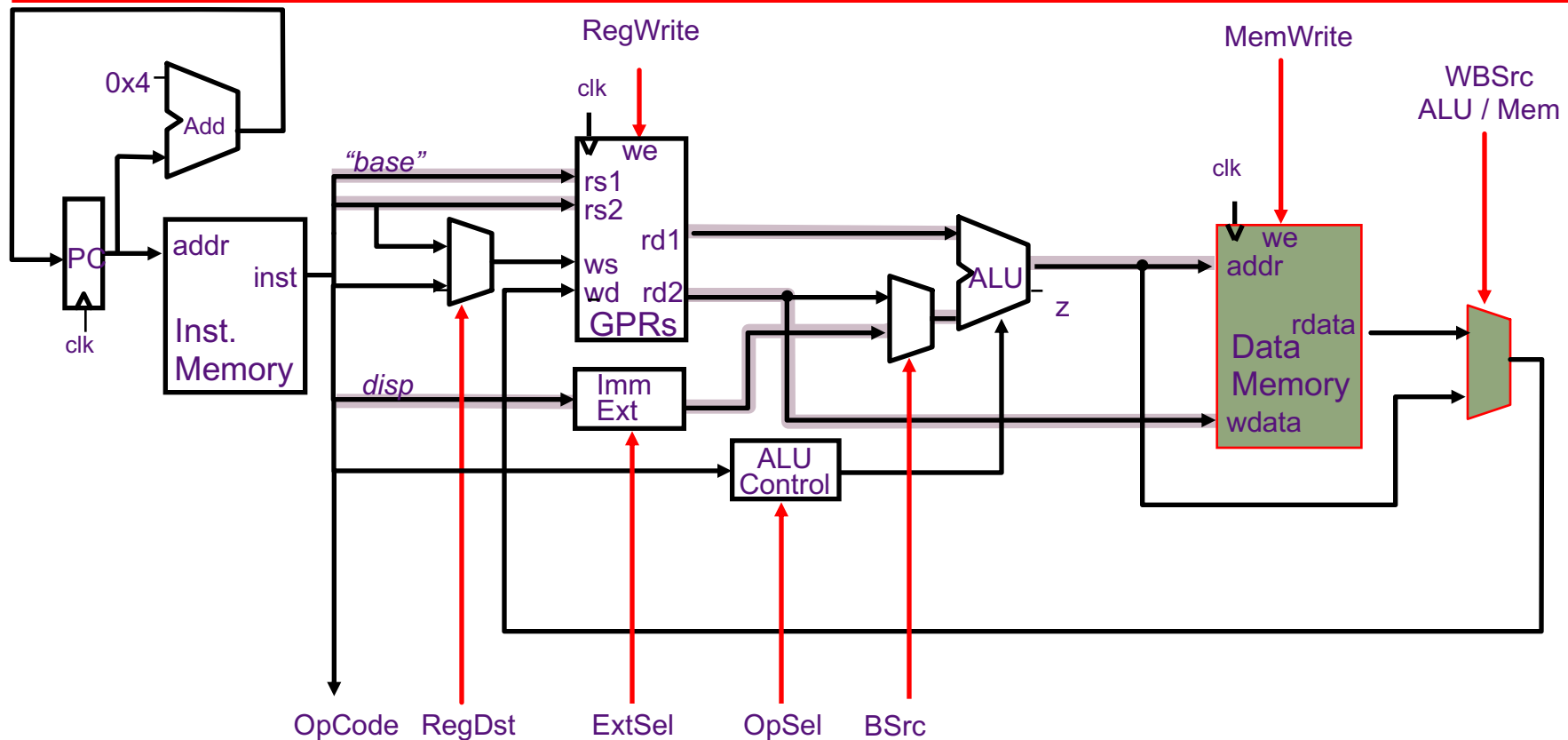



addressing mode
(rs) + displacement

rs is the base register

rt is the destination of a Load or the source for a Store

Load/Store Instructions

Harvard Datapath

  

addressing mode
(rs) + displacement

rs is the base register

rt is the destination of a Load or the source for a Store

MIPS Control Instructions

Conditional (on GPR) PC-relative branch




BEQZ, BNEZ

Unconditional register-indirect jumps



JR, JALR


Unconditional absolute jumps

 

J, JAL

MIPS Control Instructions

Conditional (on GPR) PC-relative branch

 


BEQZ, BNEZ

Unconditional register-indirect jumps



JR, JALR

Unconditional absolute jumps

 


J, JAL

	Target PC	Condition
BEQZ	PC+4+offset*4	(rs)==0
BNEZ		(rs)!=0
JR, JALR	(rs)	Always taken
J, JAL	PC[31:28] target*4	Always taken

- Jump-&-link stores PC+4 into the link register (R31)

MIPS Control Instructions

Conditional (on GPR) PC-relative branch

 


BEQZ, BNEZ

Unconditional register-indirect jumps



JR, JALR

Unconditional absolute jumps

 


J, JAL


	Target PC	Condition
BEQZ	PC+4+offset*4	(rs)==0
BNEZ		(rs)!=0
JR, JALR	(rs)	Always taken
J, JAL	PC[31:28] target*4	Always taken

- Jump-&-link stores PC+4 into the link register (R31)
- Control transfers are not delayed
we will worry about the branch delay slot later


Conditional Branches (BEQZ, BNEZ)

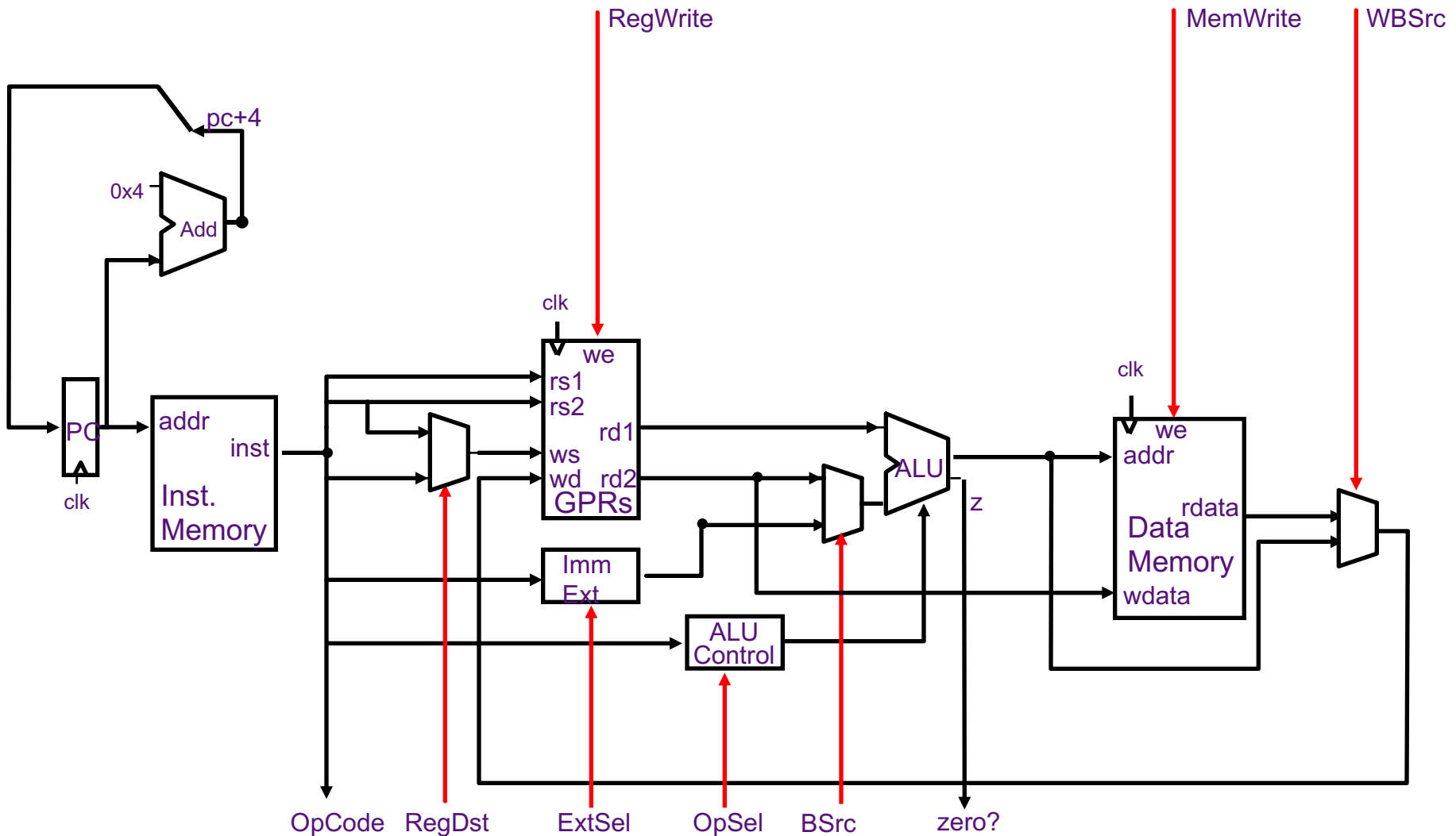


Conditional Branches (BEQZ, BNEZ)

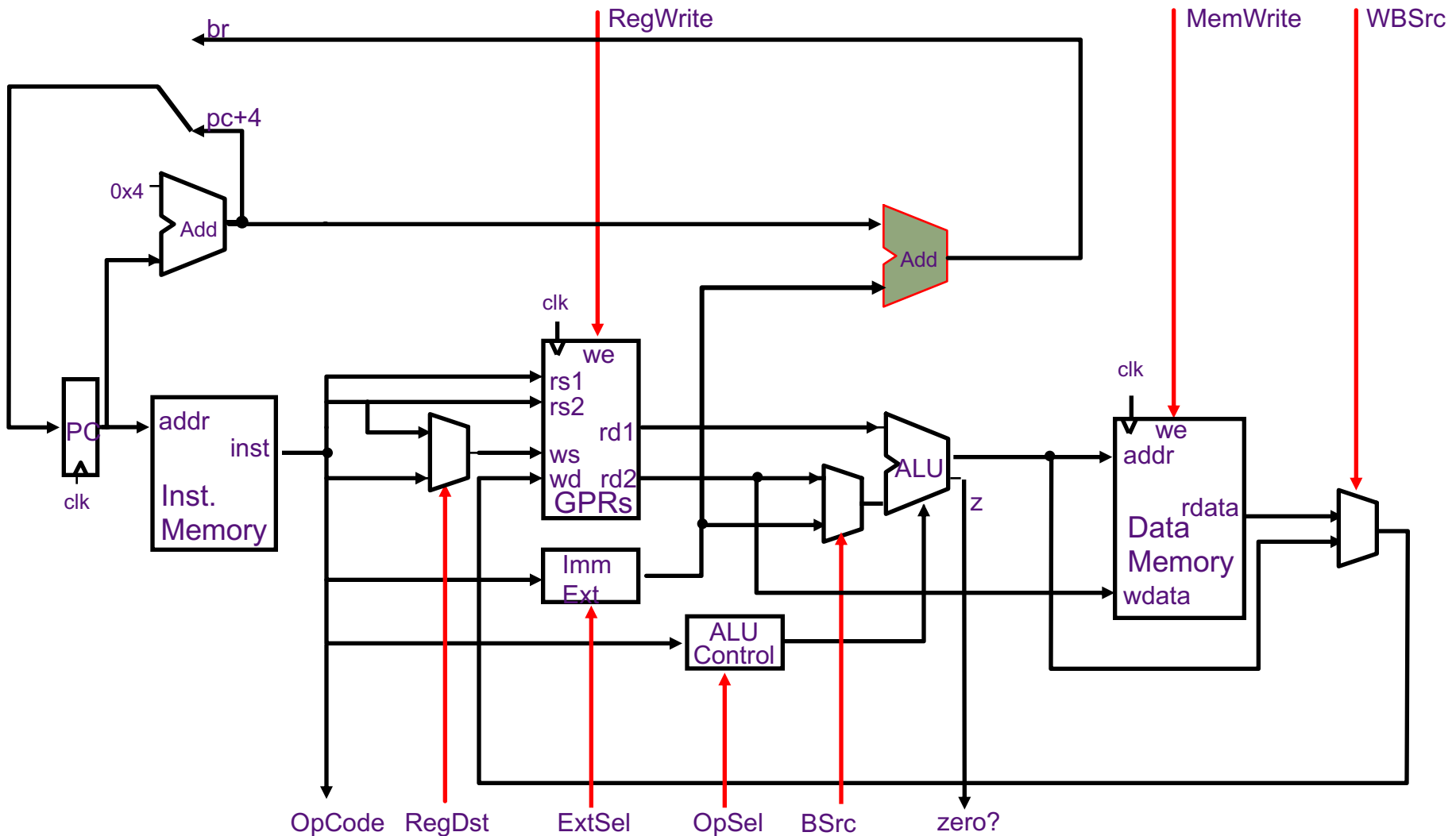


Conditional Branches (BEQZ, BNEZ)

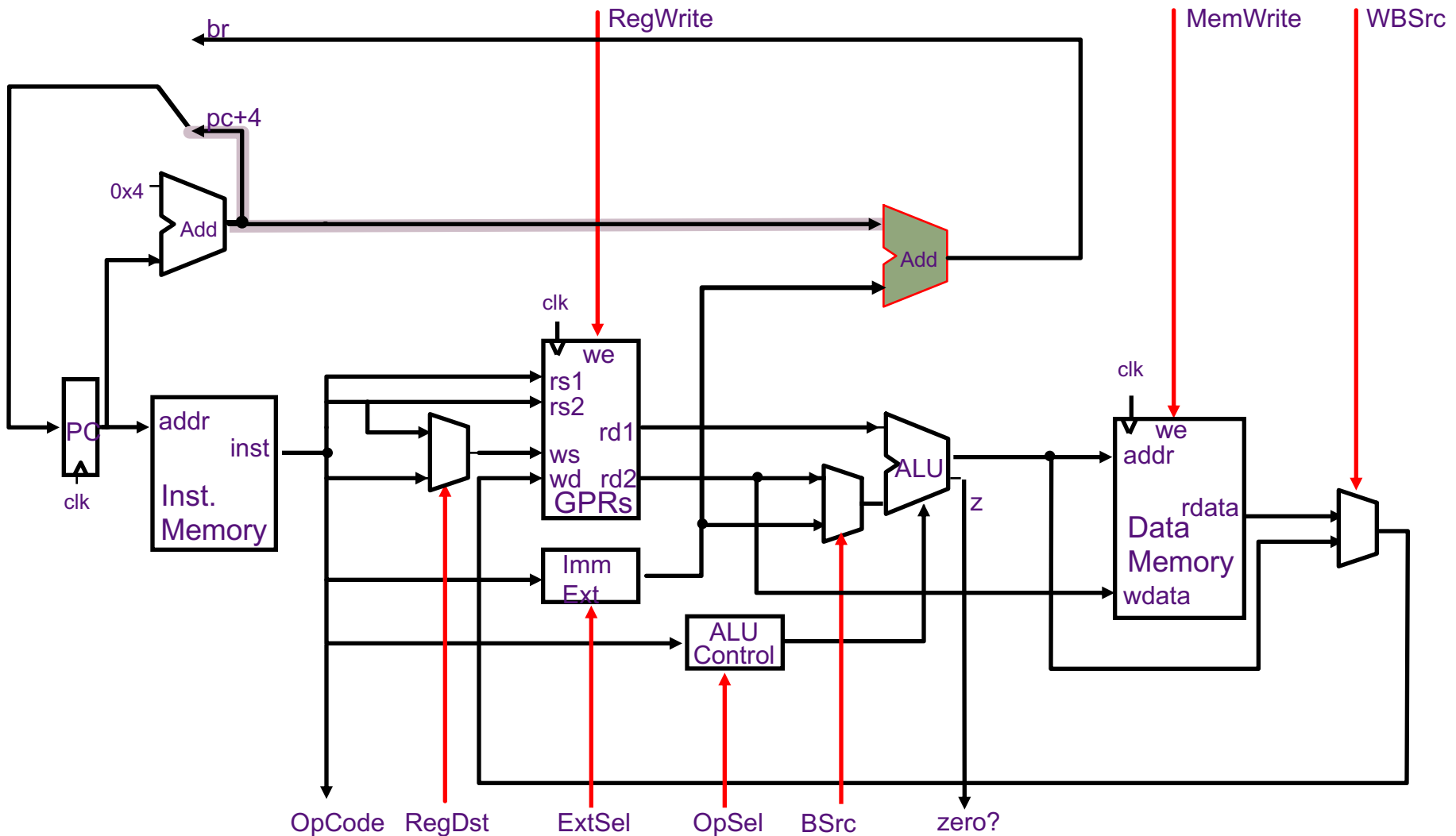


Conditional Branches (BEQZ, BNEZ)

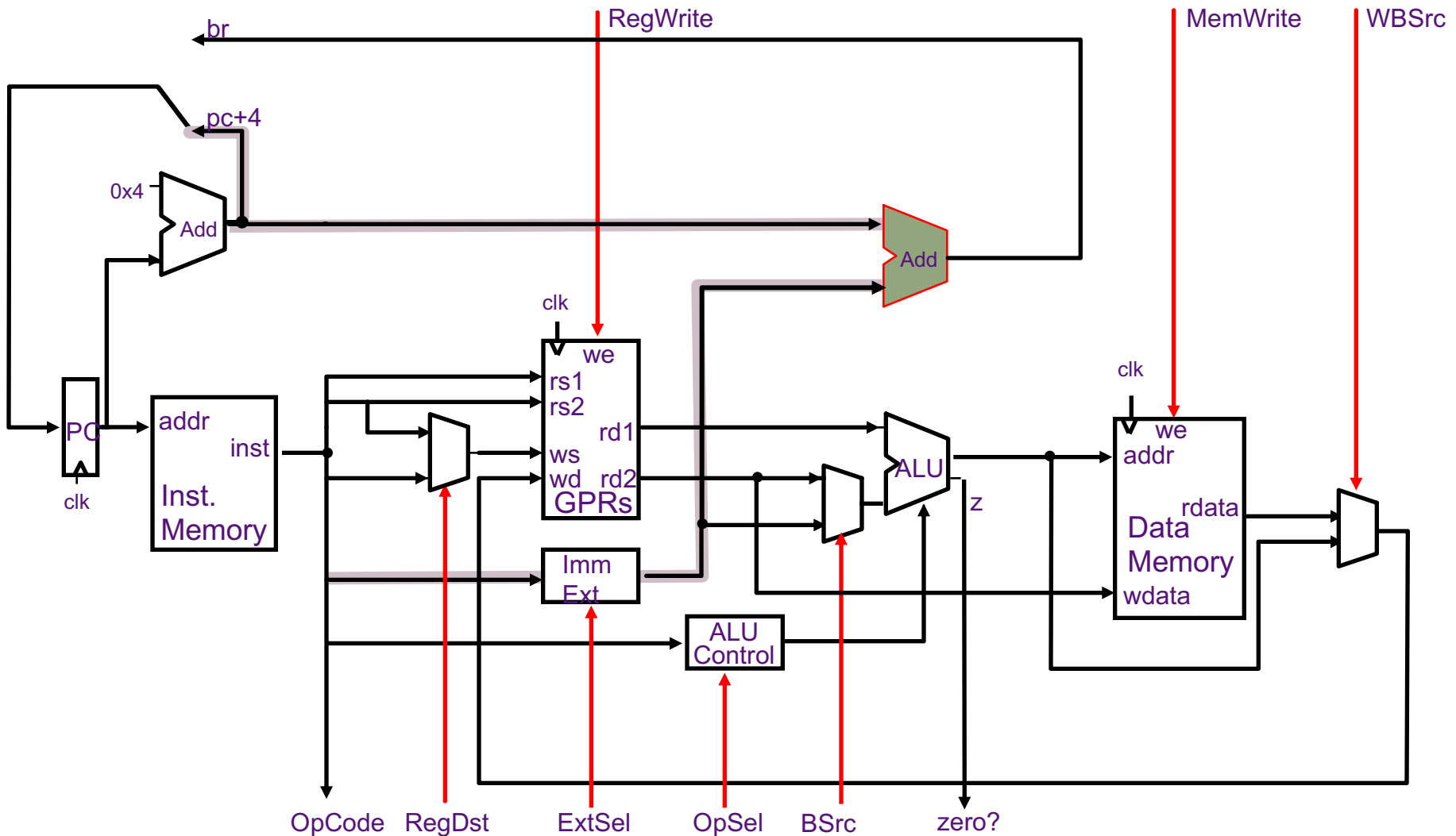


Conditional Branches (BEQZ, BNEZ)

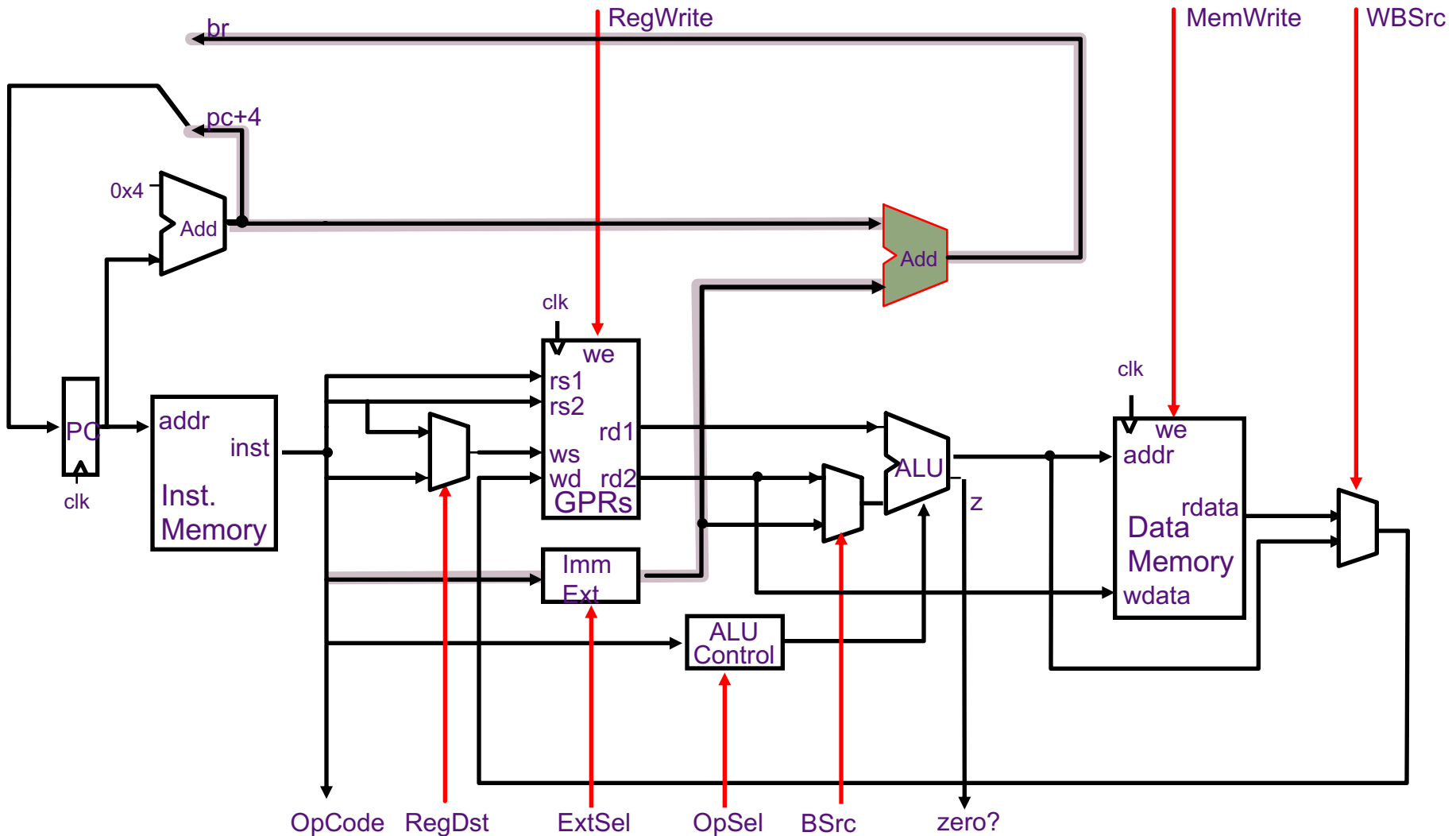


Conditional Branches (BEQZ, BNEZ)

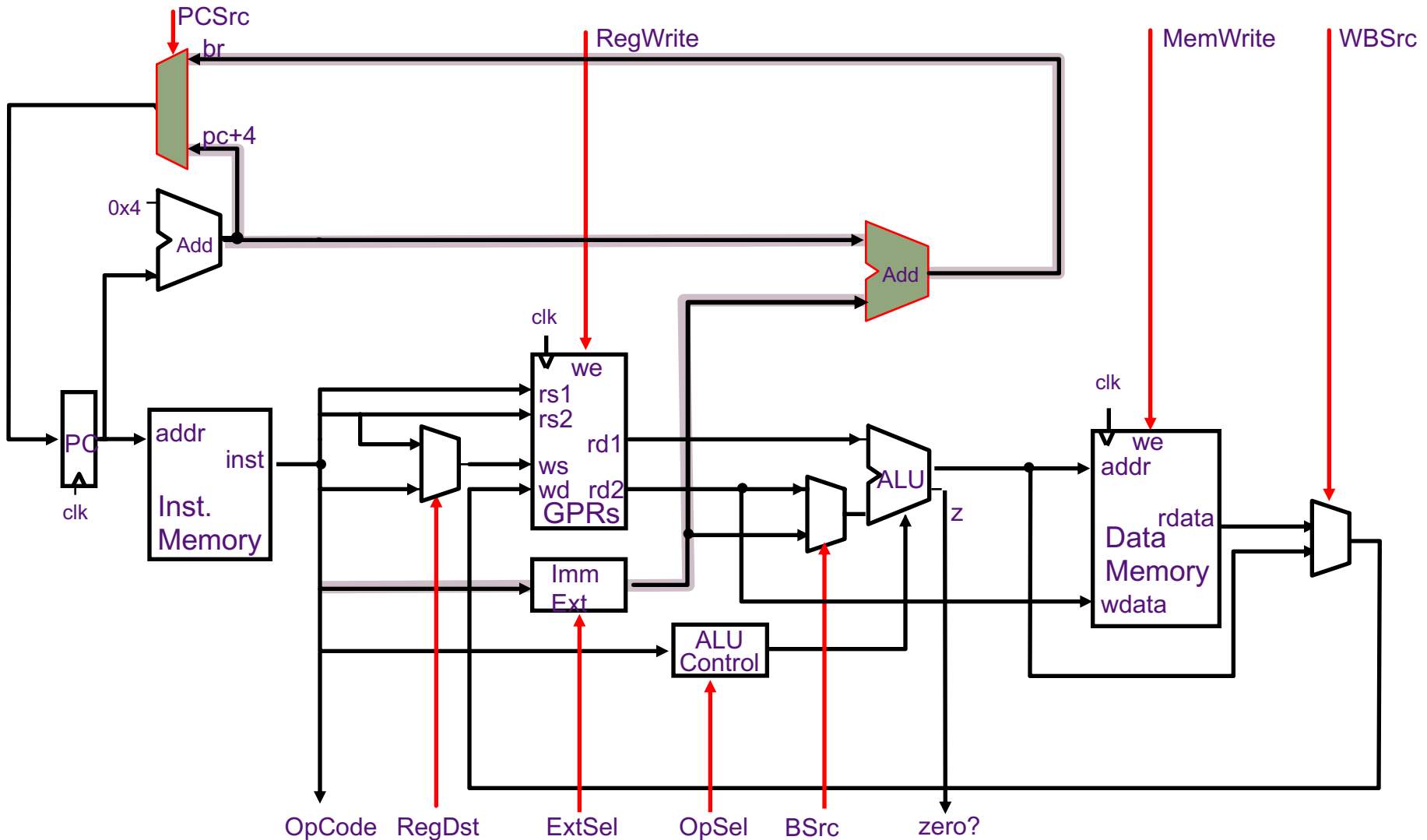


Conditional Branches (BEQZ, BNEZ)

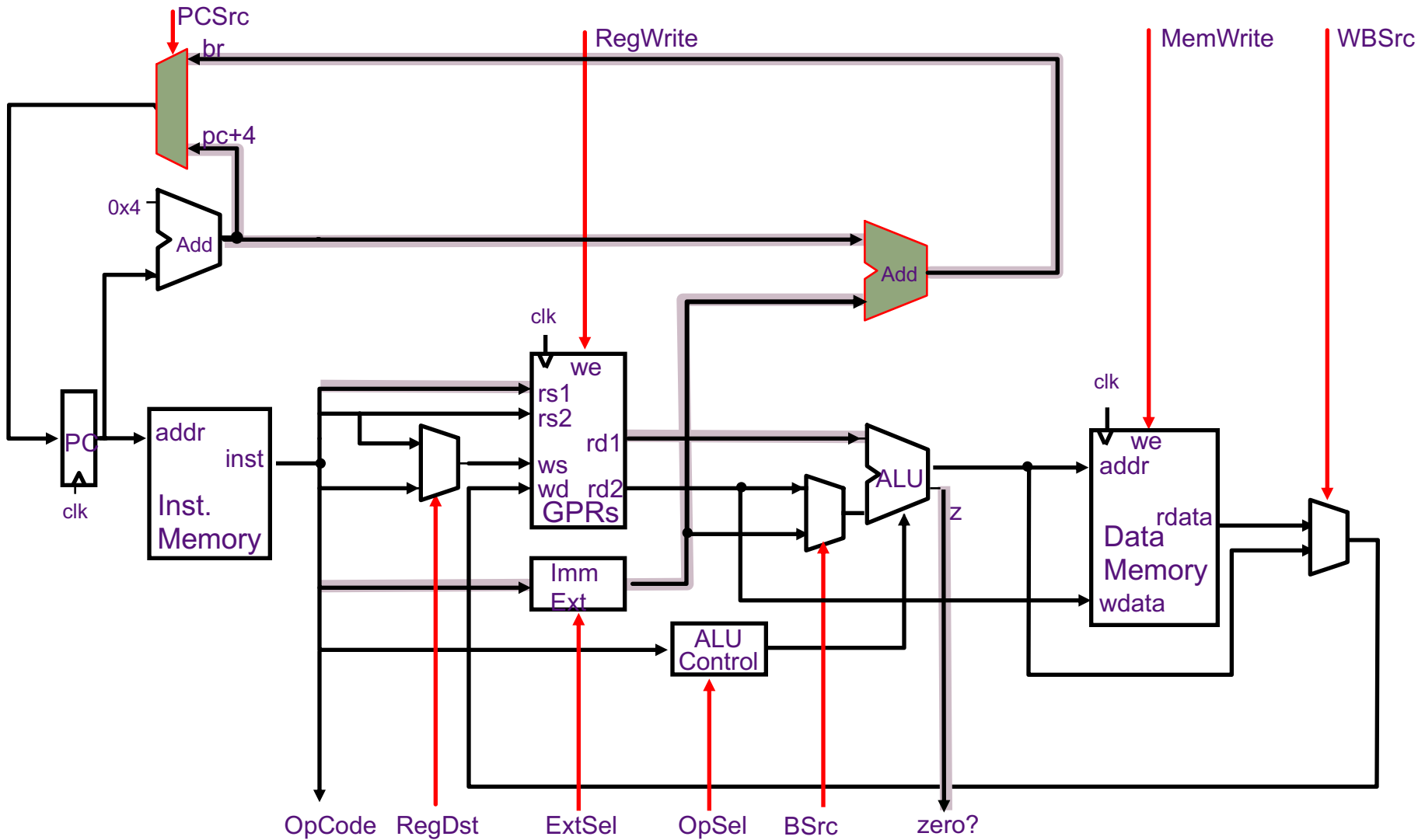


Conditional Branches (BEQZ, BNEZ)

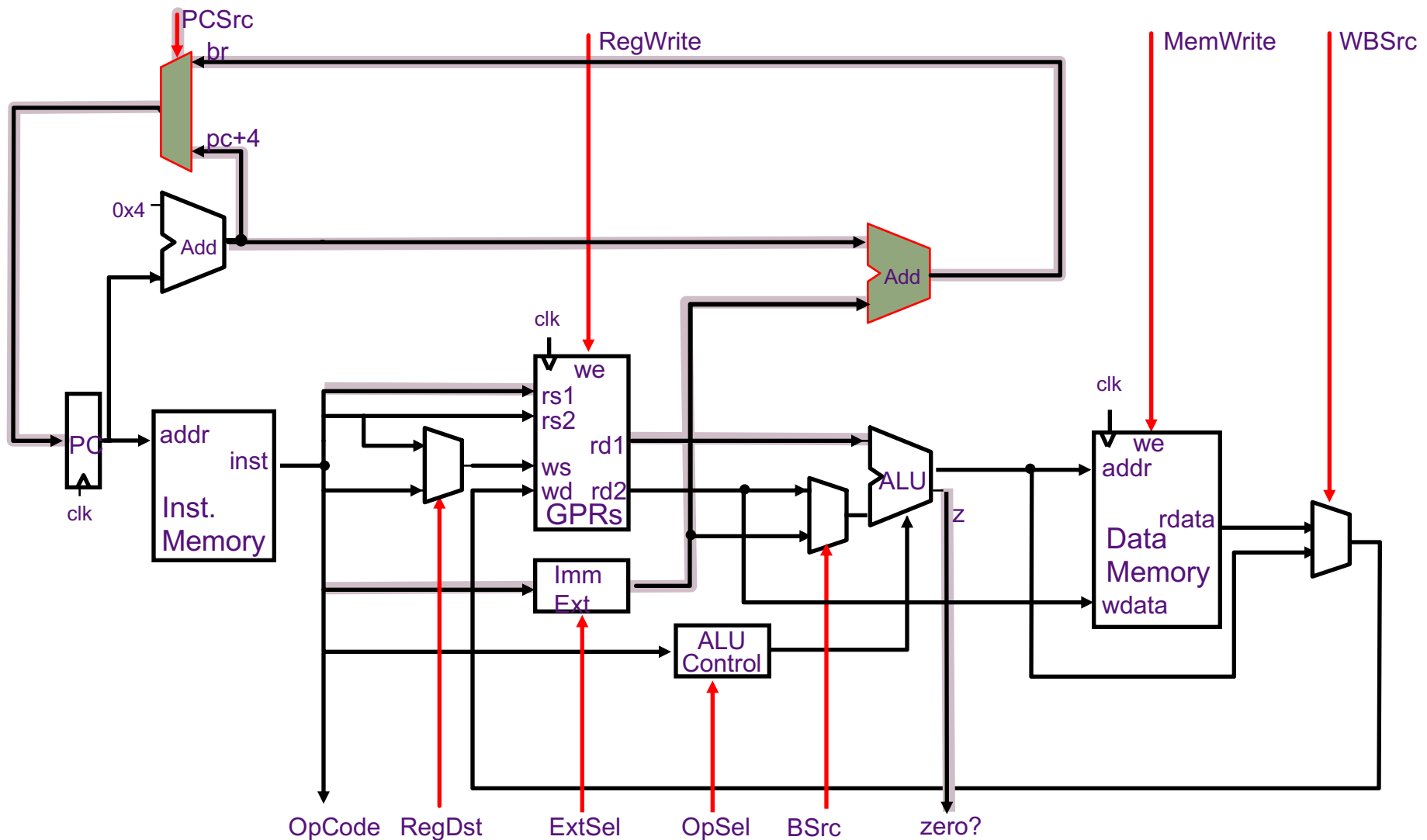


Register-Indirect Jumps (JR)

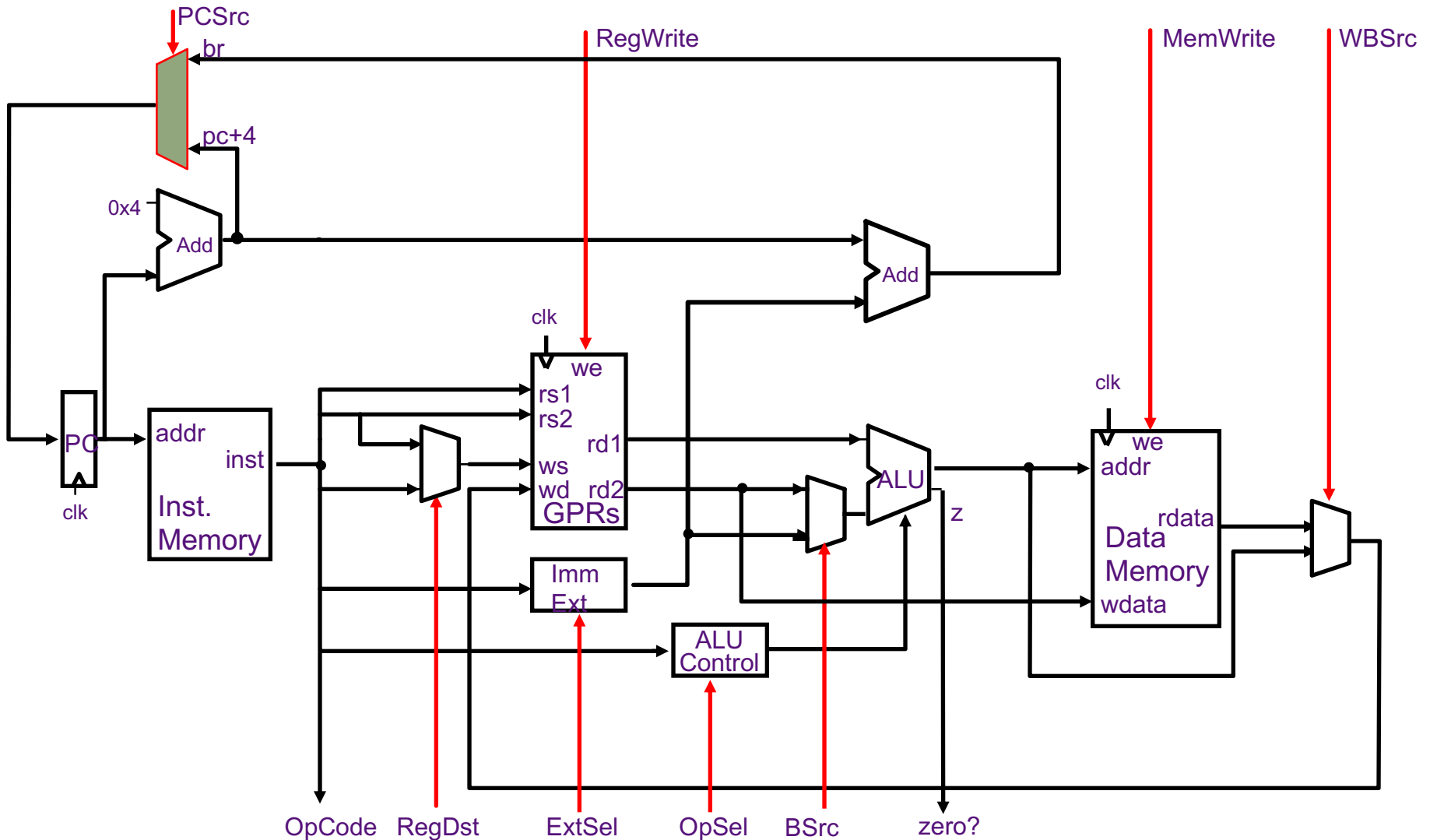


Register-Indirect Jumps (JR)

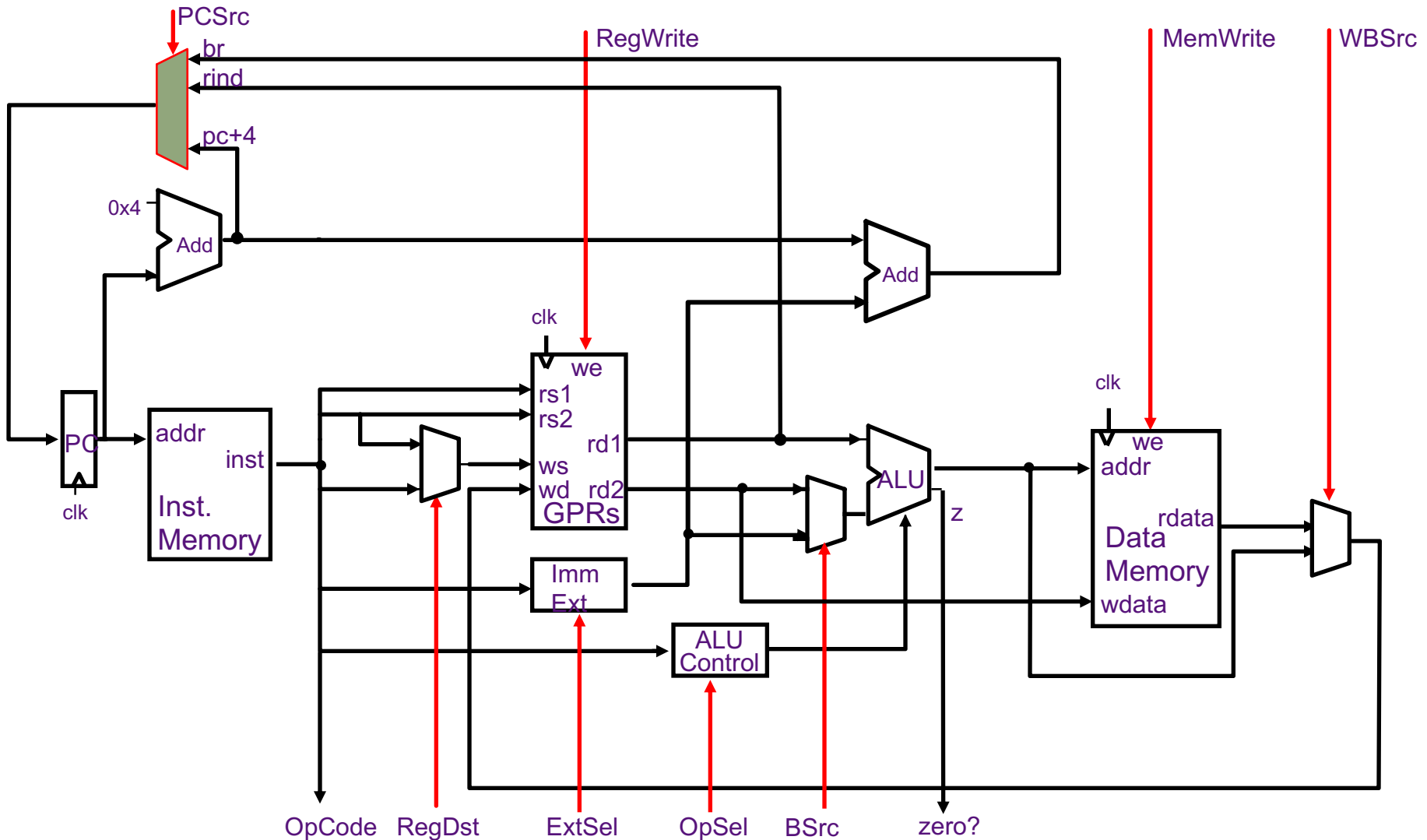


Register-Indirect Jumps (JR)

 


Register-Indirect Jump-&-Link (JALR)

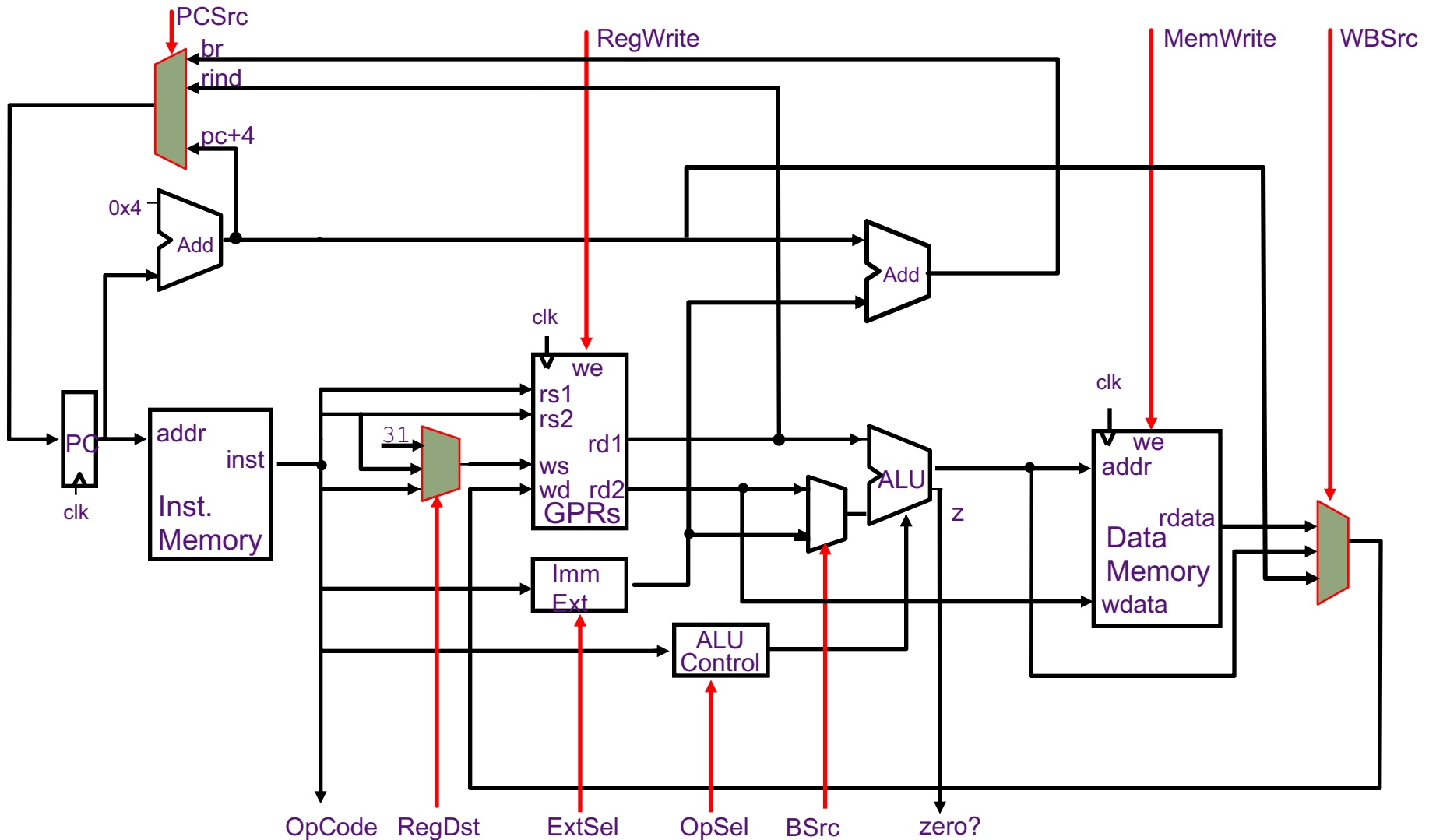


Register-Indirect Jump-&-Link (JALR)

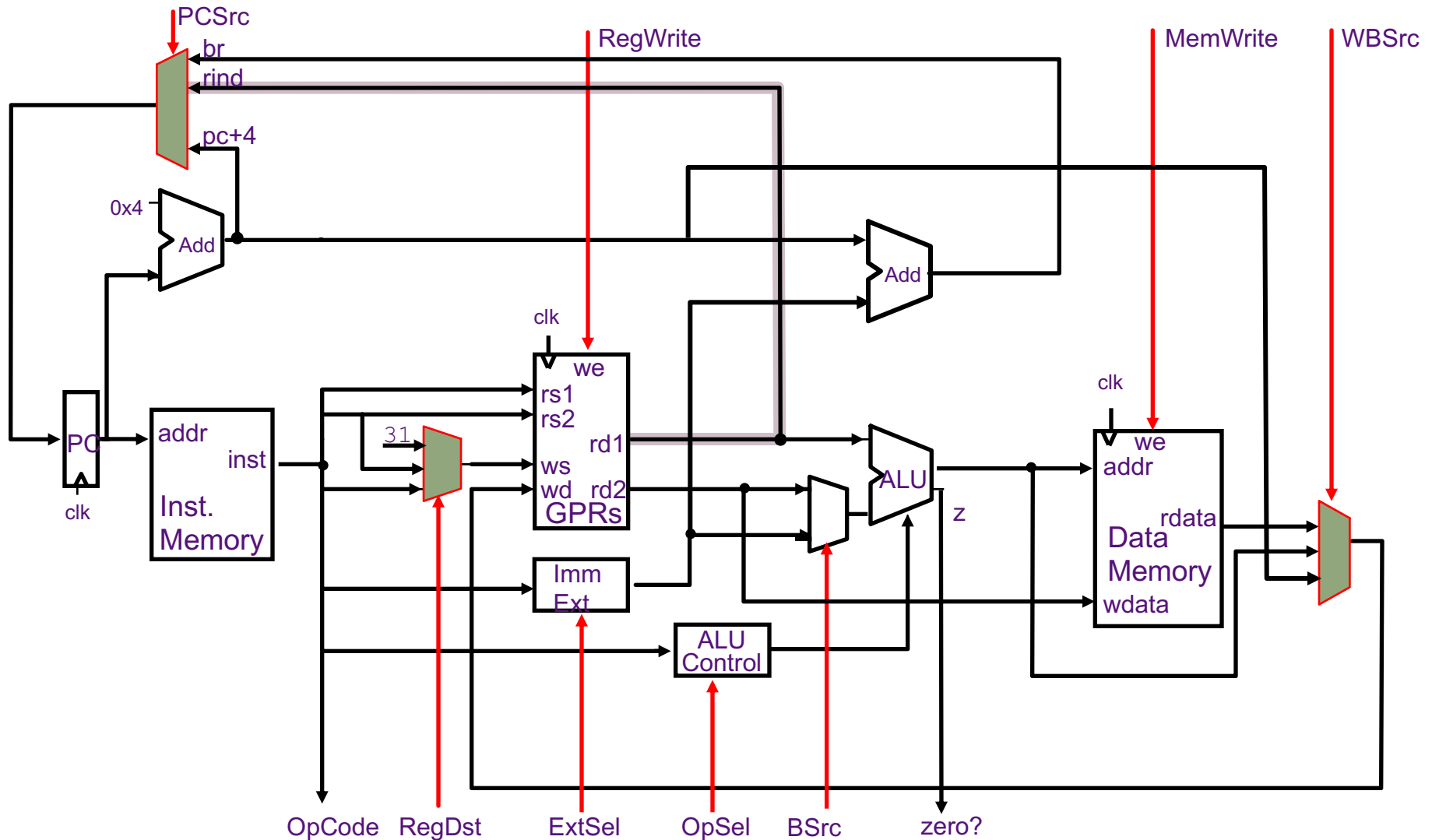


Register-Indirect Jump-&-Link (JALR)

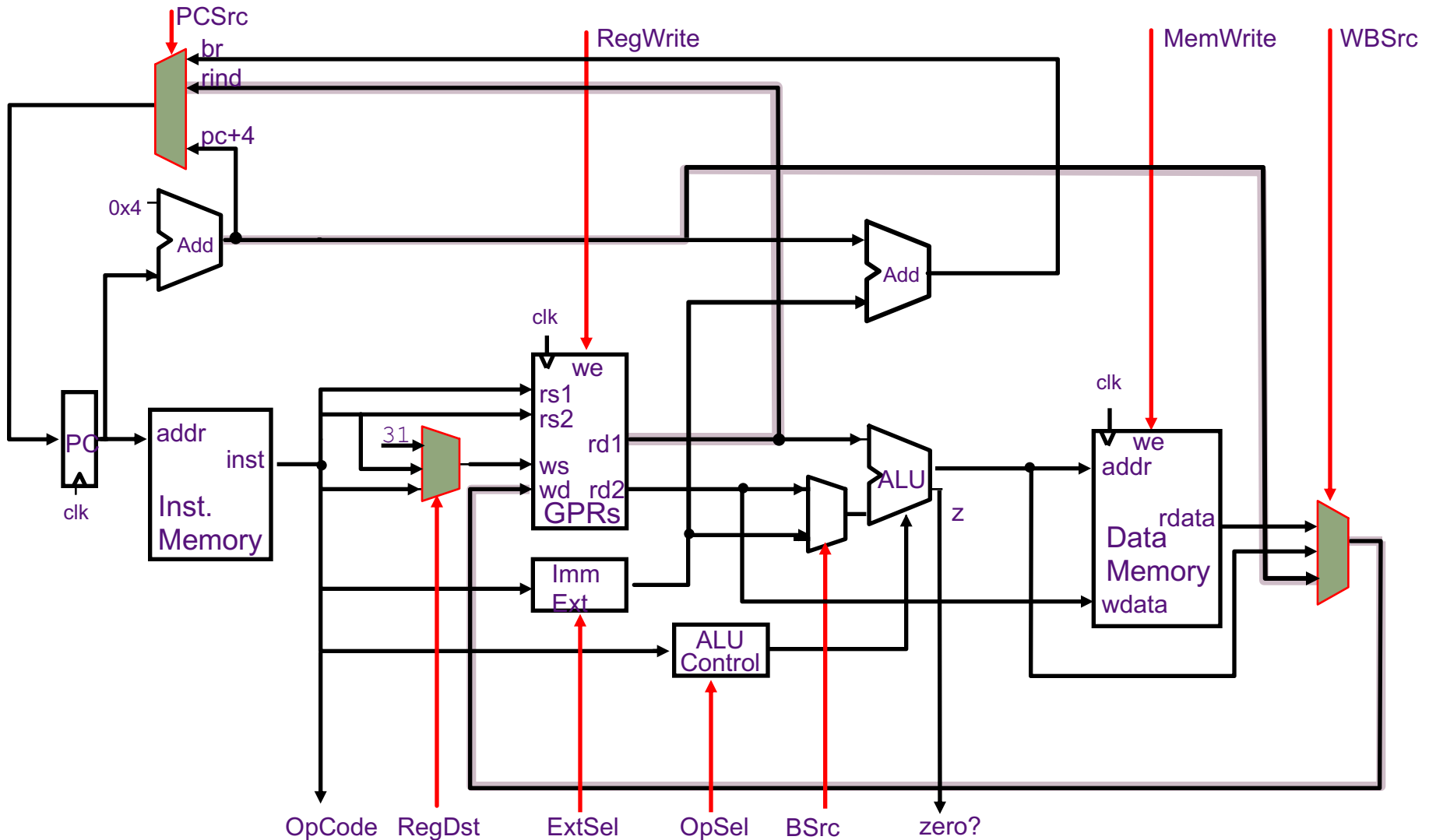


Register-Indirect Jump-&-Link (JALR)

 


Absolute Jumps (J, JAL)

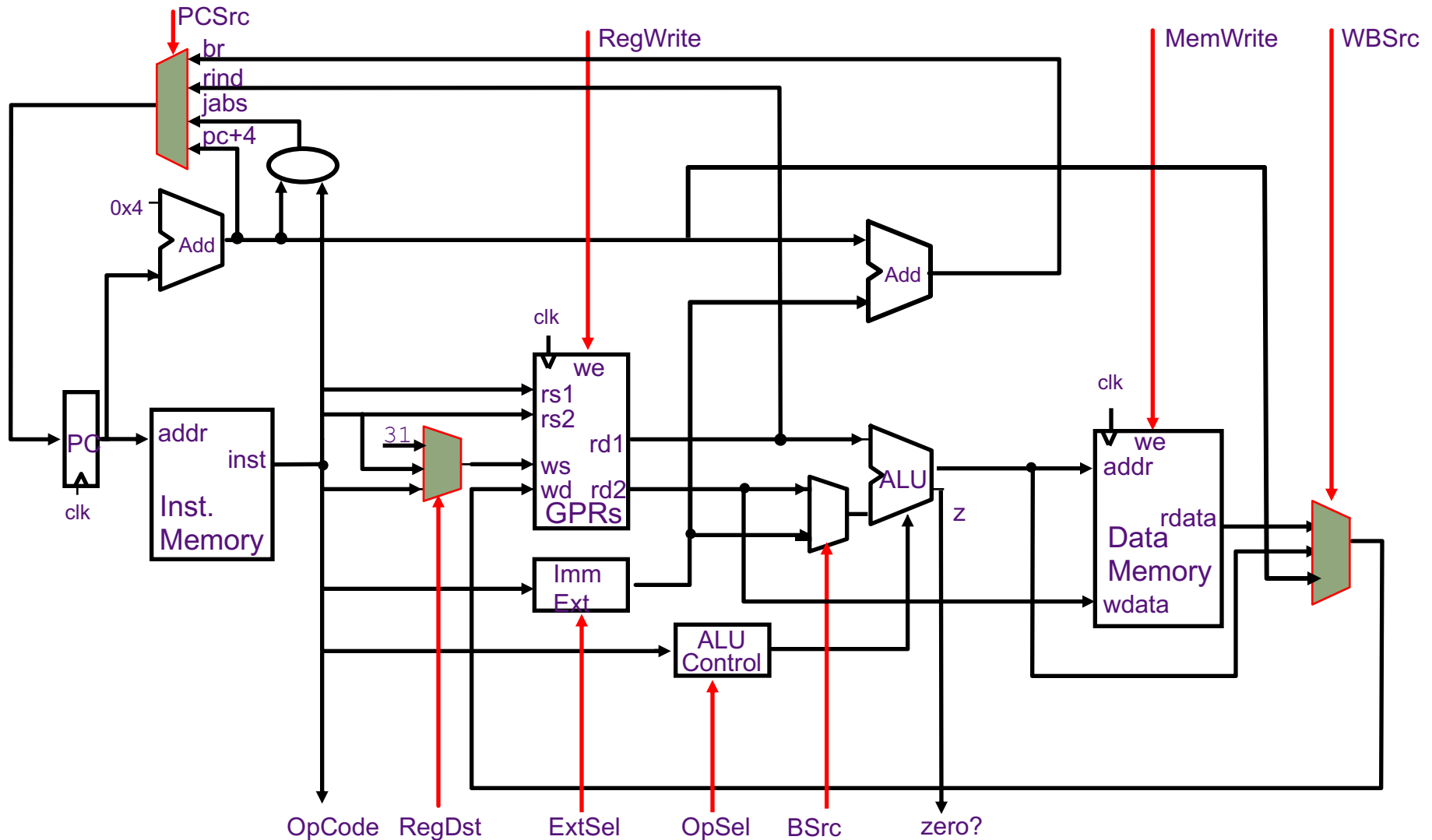


Absolute Jumps (J, JAL)

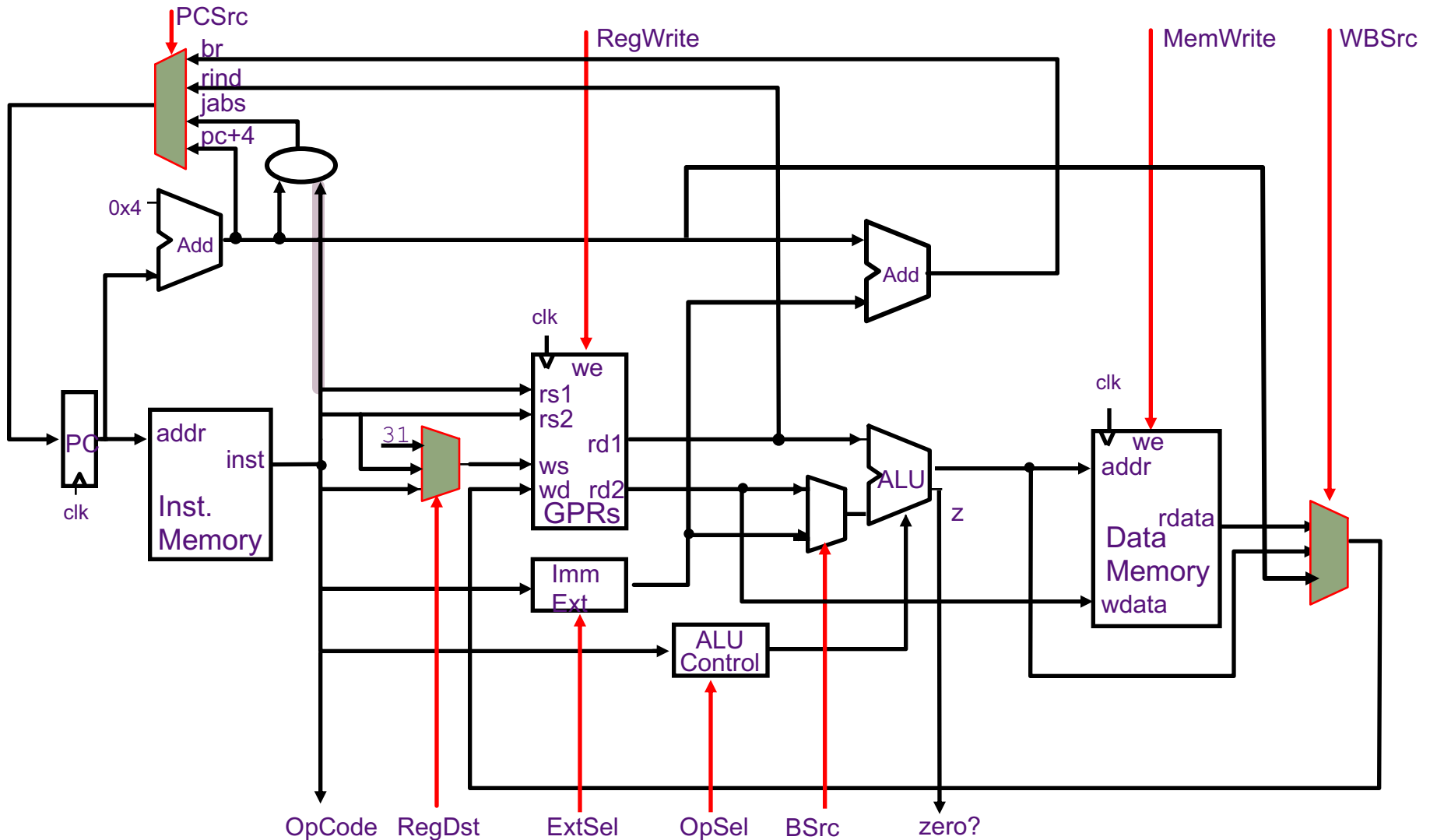


Absolute Jumps (J, JAL)

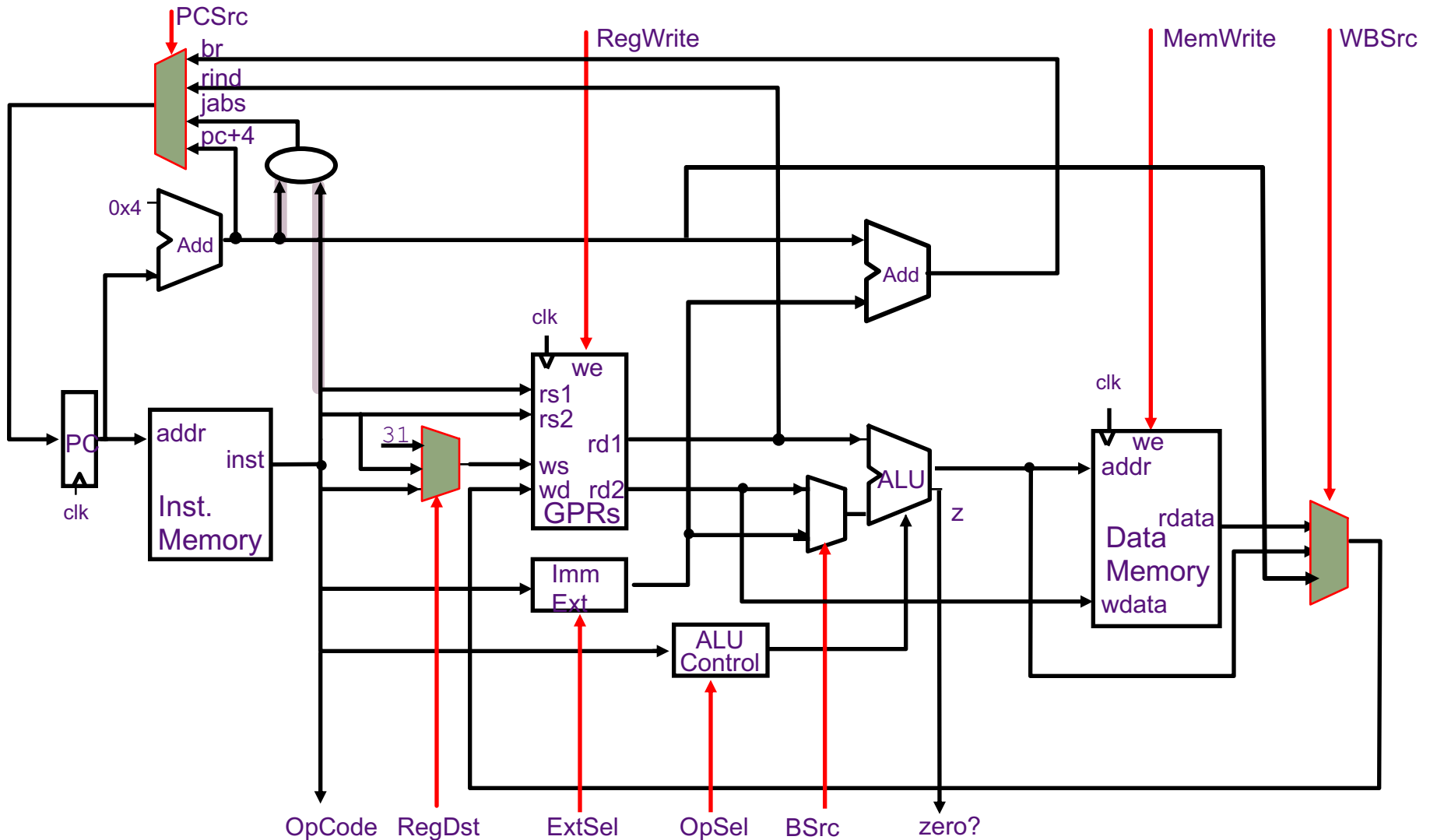


Absolute Jumps (J, JAL)

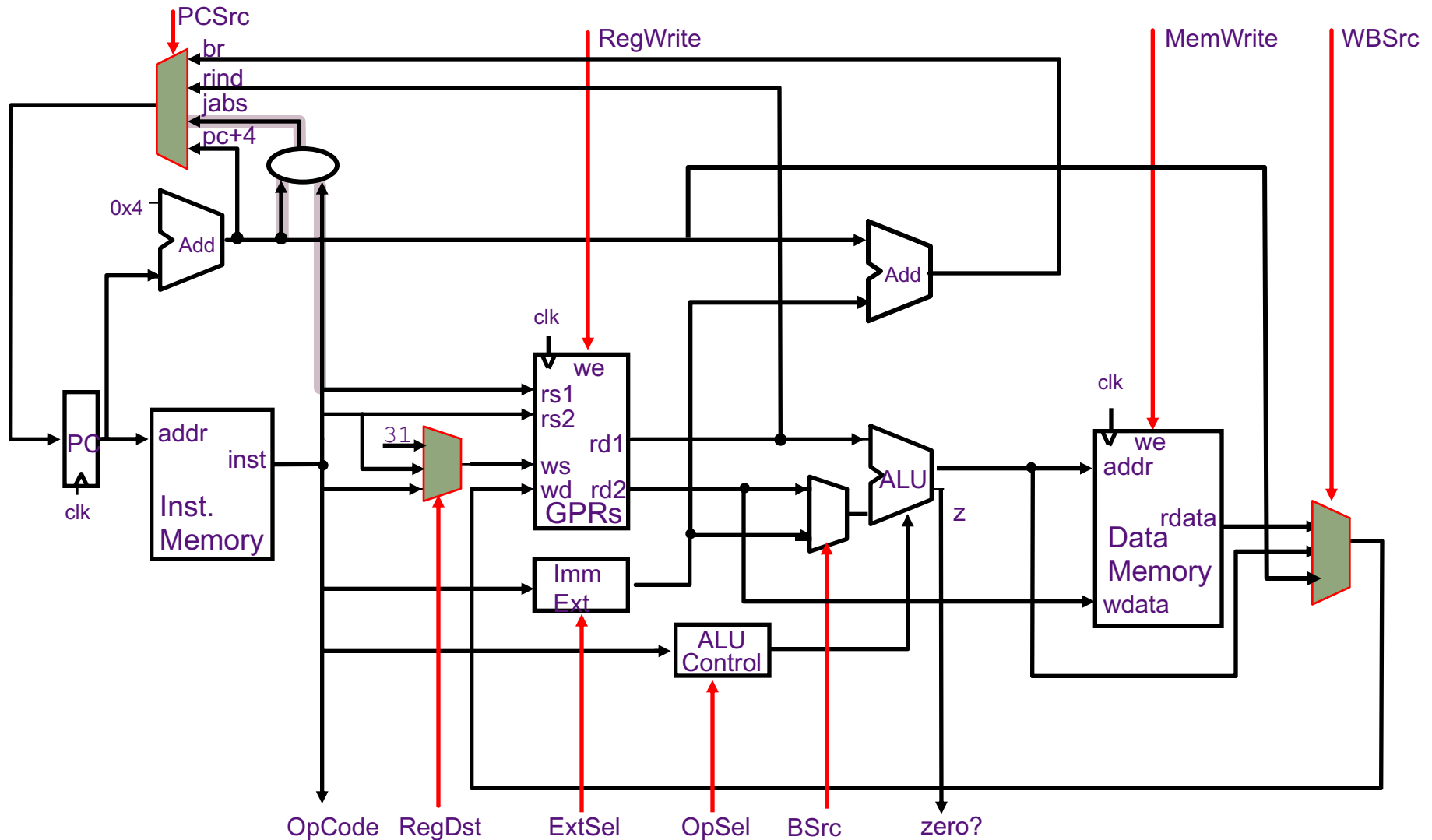


Absolute Jumps (J, JAL)

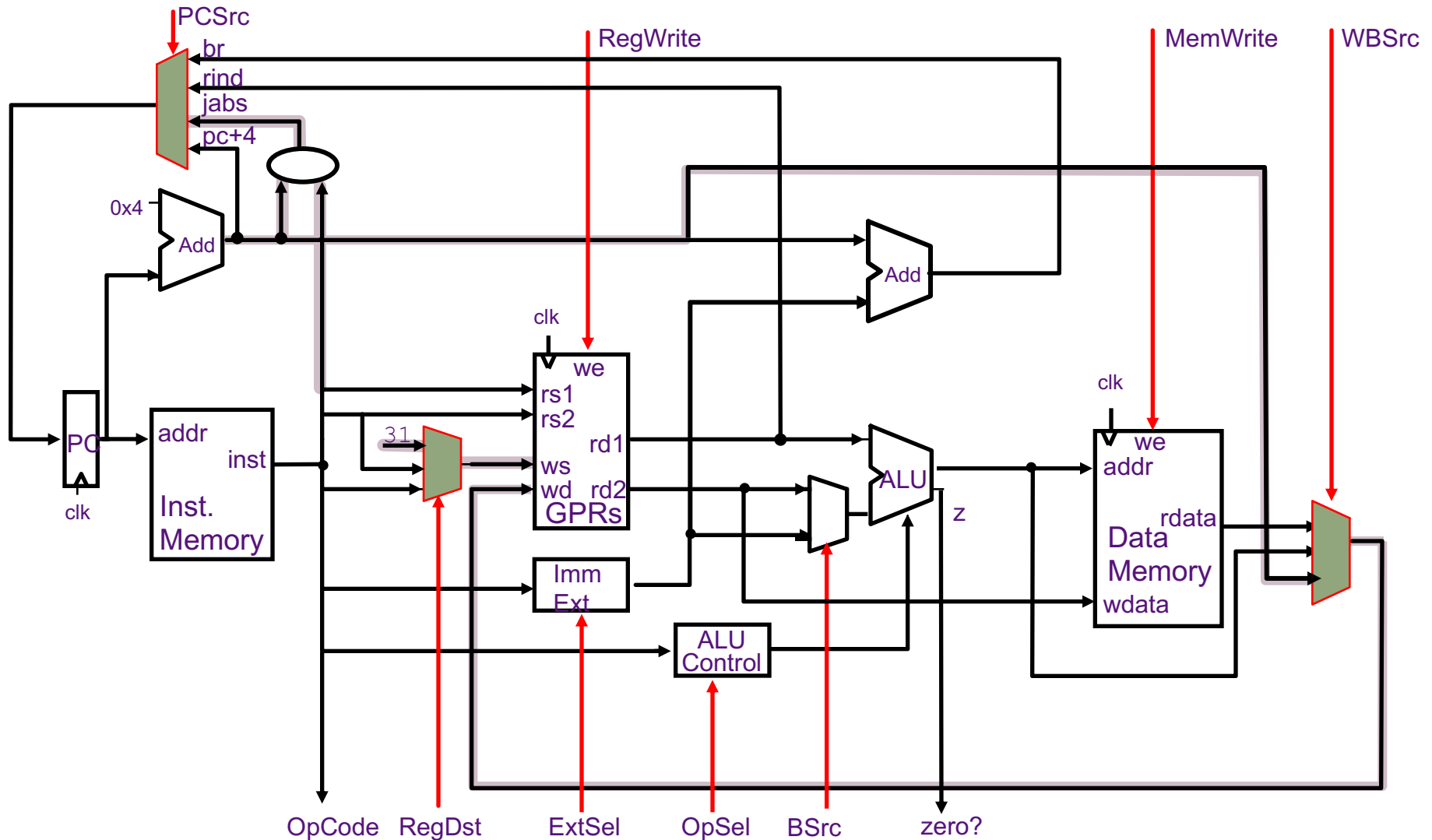


Harvard-Style Datapath for MIPS

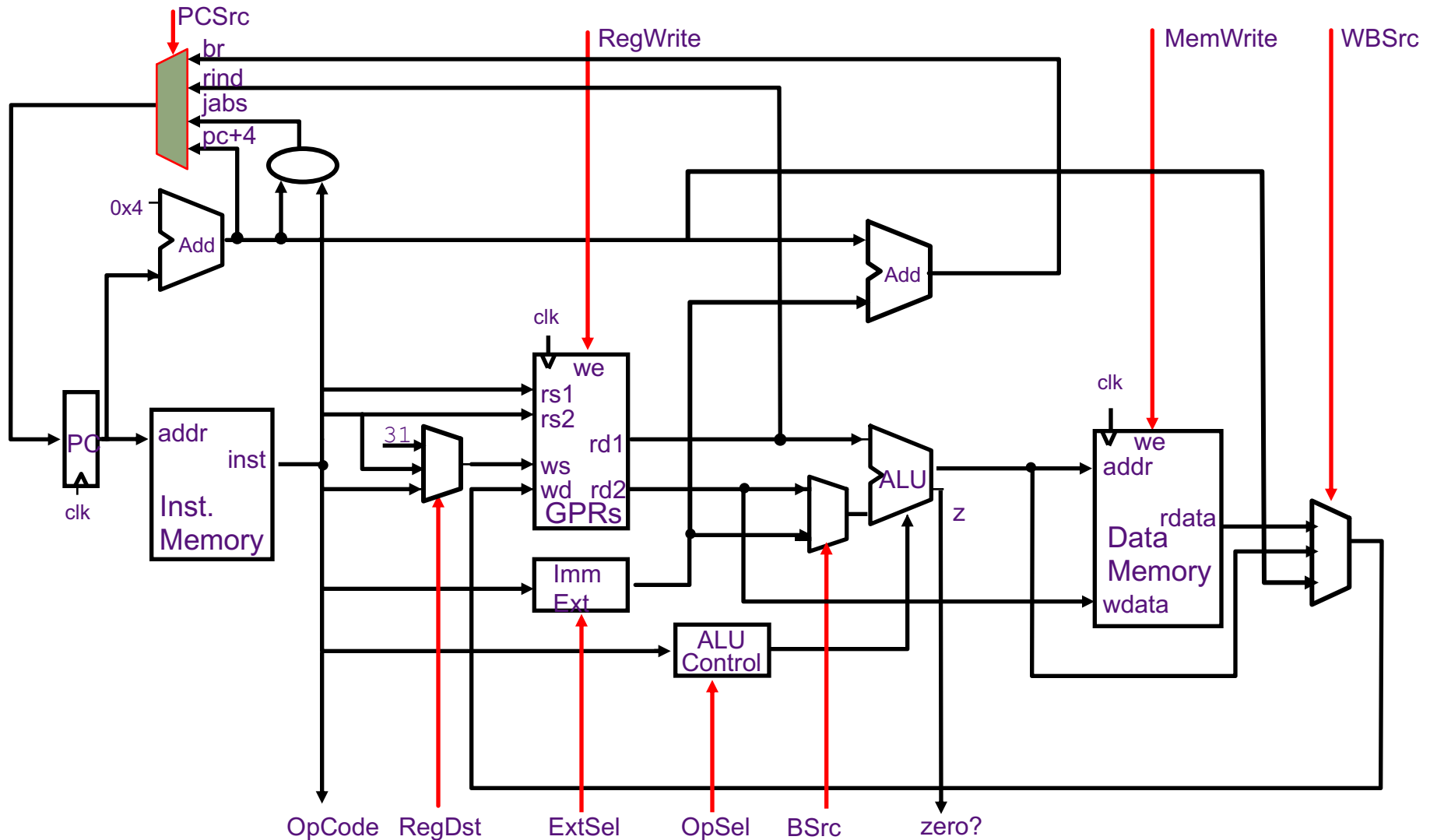

 Hardwired Control is pure Combinational Logic



ALU Control & Immediate Extension

 

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU								
ALUi								
ALUiu								
LW								
SW								
BEQ _{Z=0}								
BEQ _{Z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*							
ALUi								
ALUiu								
LW								
SW								
BEQ _{Z=0}								
BEQ _{Z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg						
ALUi								
ALUiu								
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func					
ALUi								
ALUiu								
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no				
ALUi								
ALUiu								
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes			
ALUi								
ALUiu								
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU		
ALUi								
ALUiu								
LW								
SW								
BEQ _{Z=0}								
BEQ _{Z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	
ALUi								
ALUiu								
LW								
SW								
BEQ _{Z=0}								
BEQ _{Z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi								
ALUiu								
LW								
SW								
BEQ _{Z=0}								
BEQ _{Z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆							
ALUiu								
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm						
ALUiu								
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op					
ALUiu								
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU		pc+4
ALUiu								
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu								
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆							
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW								
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆							
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm						
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+					
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no				
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes			
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem		
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW								
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}								
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆							
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*						
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?					
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}								
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J								
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*					
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL								
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL	*	*	*	no				
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL	*	*	*	no	yes			
JR								
JALR								

BSrc = Reg / Imm
 RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
 PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL	*	*	*	no	yes	PC		
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL	*	*	*	no	yes	PC	R31	
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL	*	*	*	no	yes	PC	R31	jabs
JR								
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL	*	*	*	no	yes	PC	R31	jabs
JR	*	*	*					
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL	*	*	*	no	yes	PC	R31	jabs
JR	*	*	*	no	no	*	*	
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL	*	*	*	no	yes	PC	R31	jabs
JR	*	*	*	no	no	*	*	rind
JALR								

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL	*	*	*	no	yes	PC	R31	jabs
JR	*	*	*	no	no	*	*	rind
JALR	*	*	*	no	yes	PC	R31	rind

BSrc = Reg / Imm
RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC
PCSrc = pc+4 / br / rind / jabs

Single-Cycle Hardwired Control:

Harvard architecture

We will assume

- Clock period is sufficiently long for all of the following steps to be “completed”:

1. instruction fetch
2. decode and register fetch
3. ALU operation
4. data fetch if required
5. register write-back setup time

$$\Rightarrow t_C > t_{IFetch} + t_{RFetch} + t_{ALU} + t_{DMem} + t_{RWB}$$

- At the rising edge of the following clock, the PC, the register file and the memory are updated

Princeton challenge

- What problem arises if instructions and data reside in the same memory?

Princeton challenge

- What problem arises if instructions and data reside in the same memory?

At least the instruction fetch and a Load (or Store) cannot be executed in the same cycle

Princeton challenge


- What problem arises if instructions and data reside in the same memory?

At least the instruction fetch and a Load (or Store) cannot be executed in the same cycle

Structural hazard


Princeton Microarchitecture

Datapath & Control

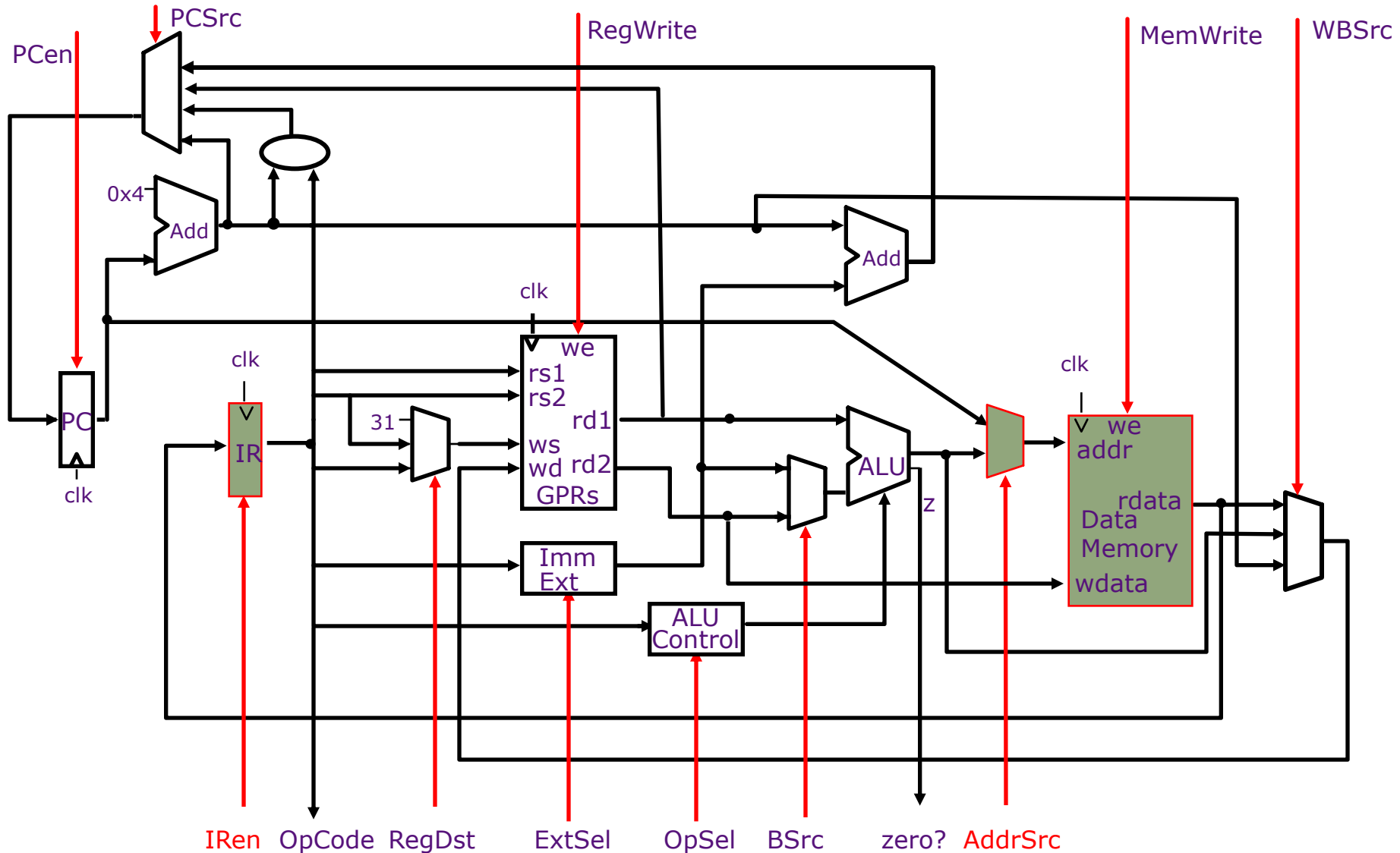


Princeton Microarchitecture

Datapath & Control

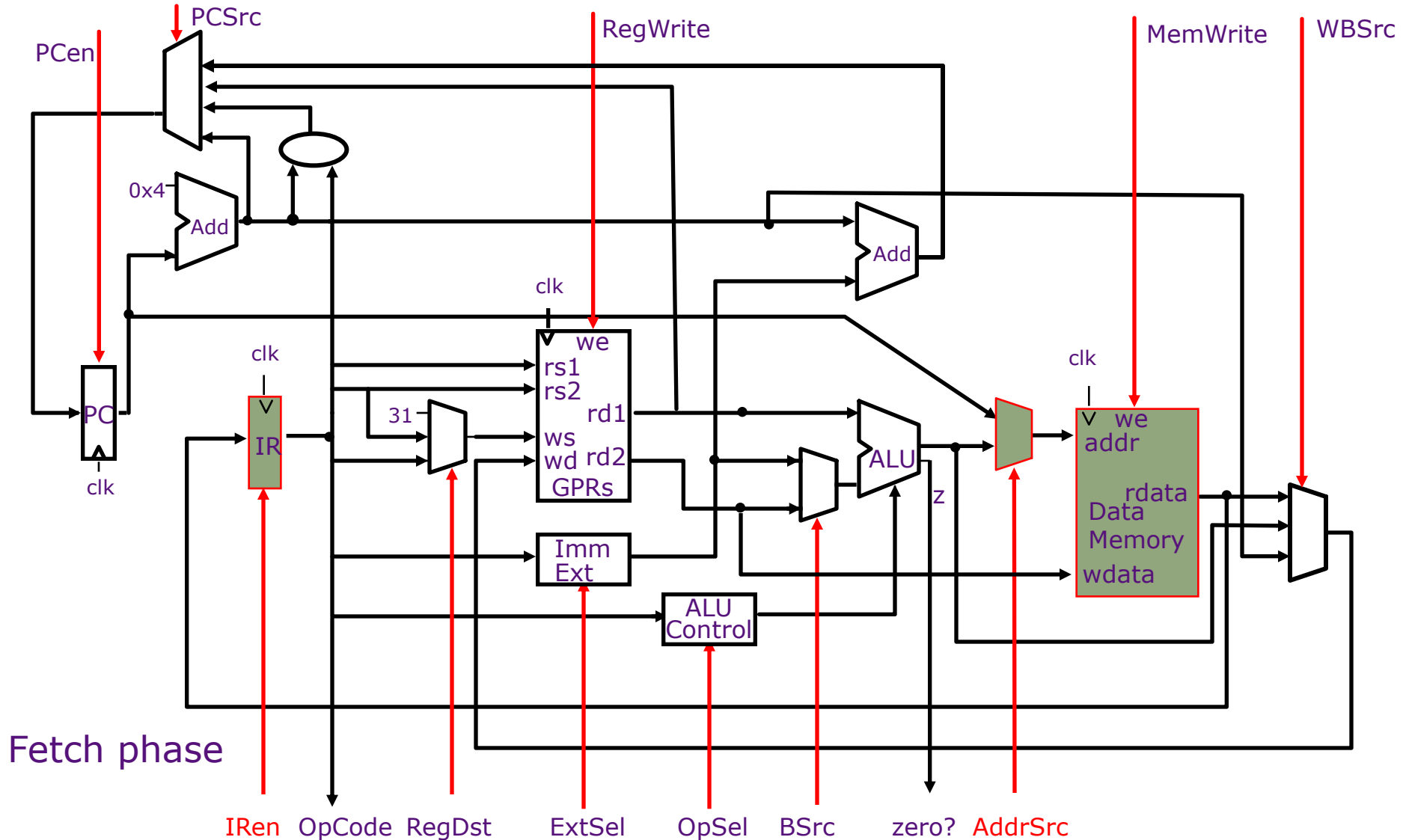


Princeton Microarchitecture

Datapath & Control

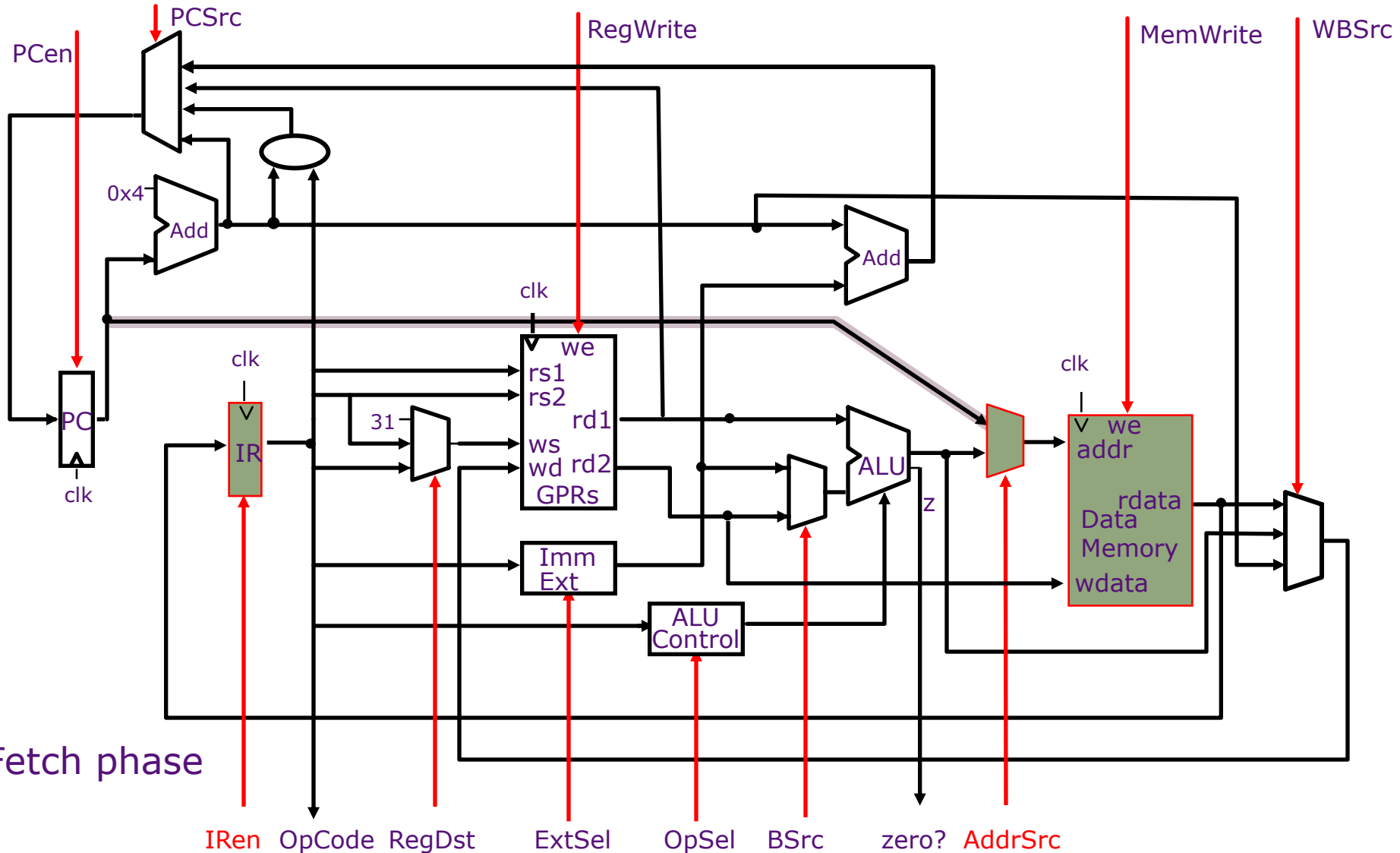


Princeton Microarchitecture

Datapath & Control

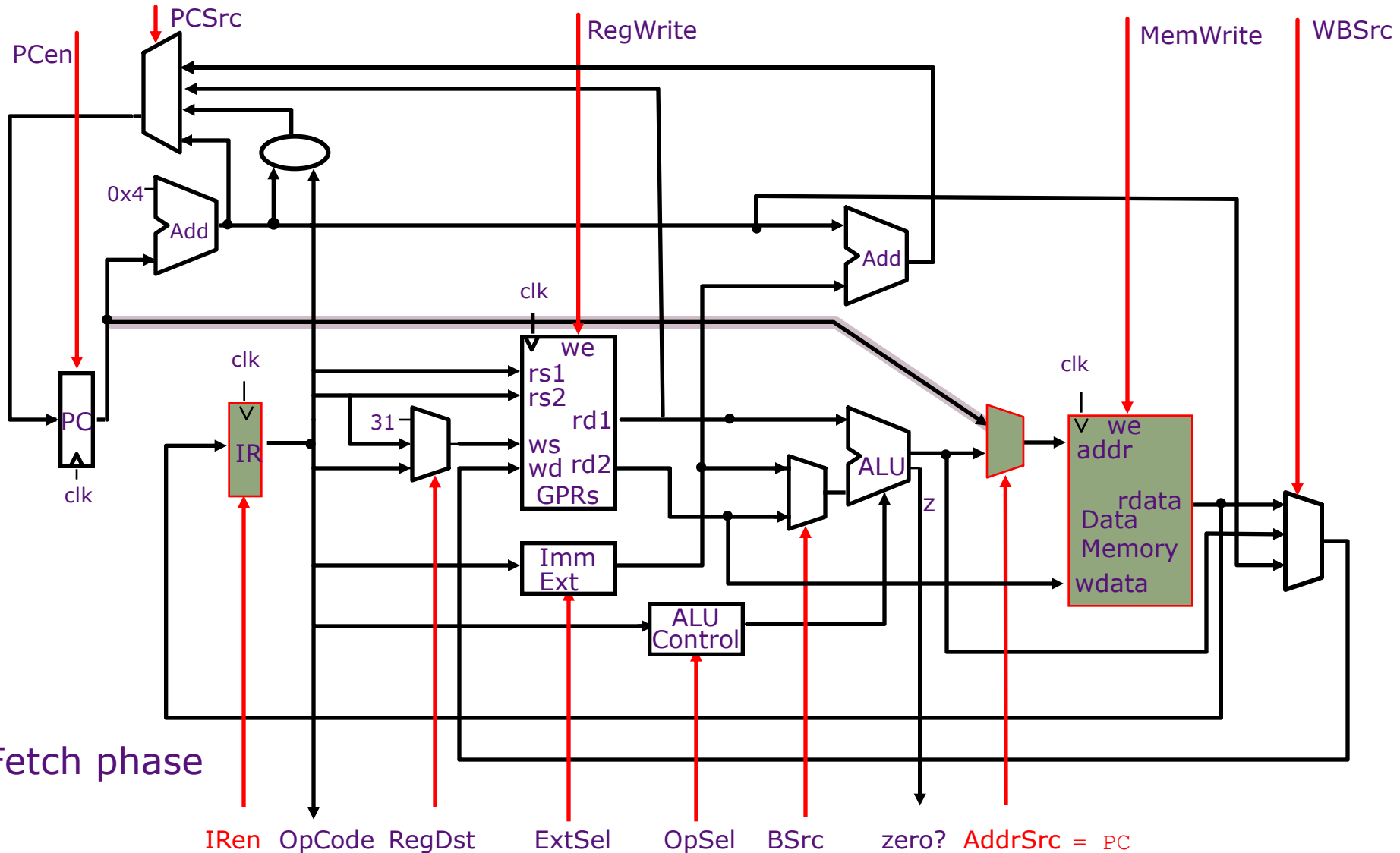


Princeton Microarchitecture

Datapath & Control

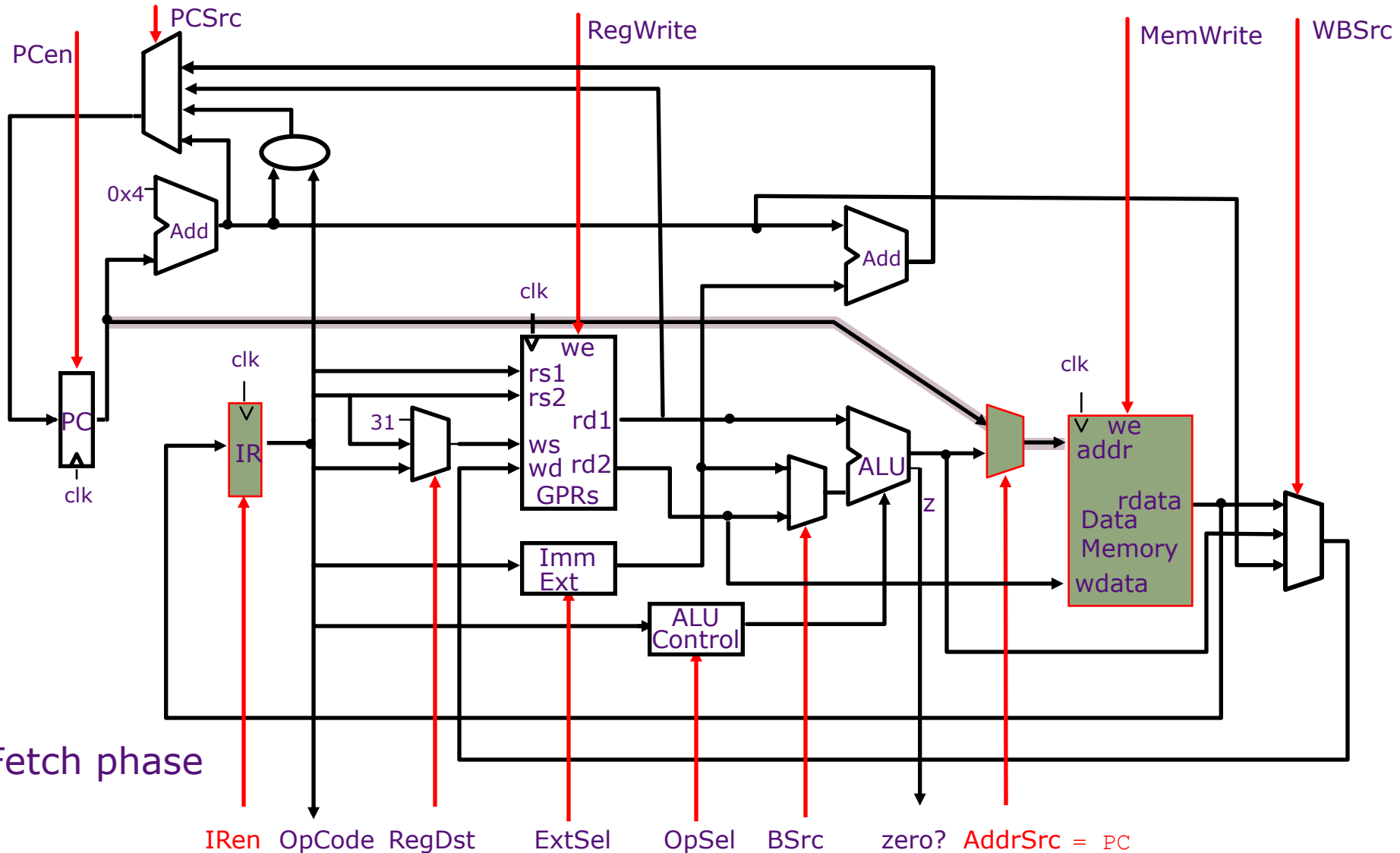


Princeton Microarchitecture

Datapath & Control

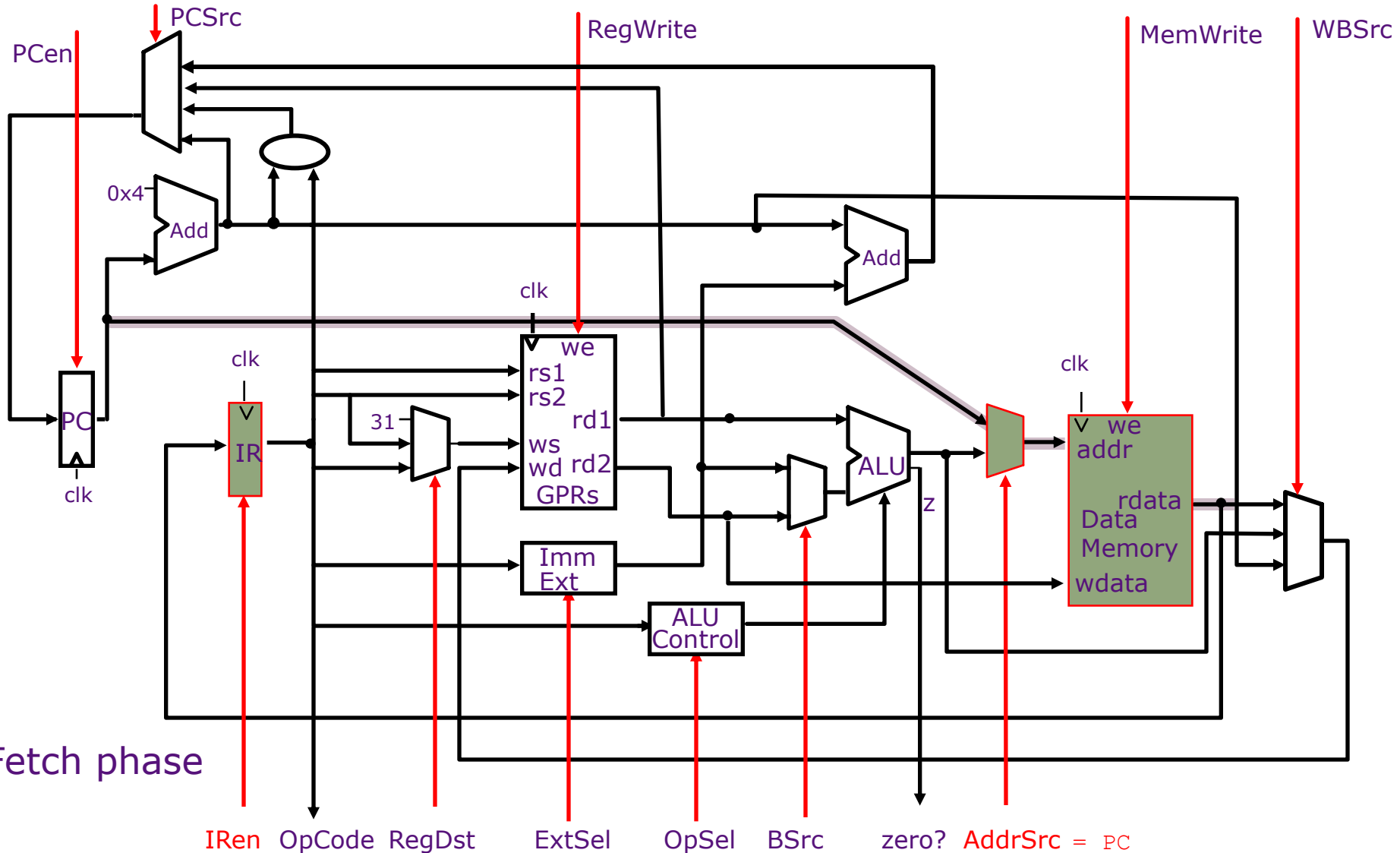


Princeton Microarchitecture

Datapath & Control

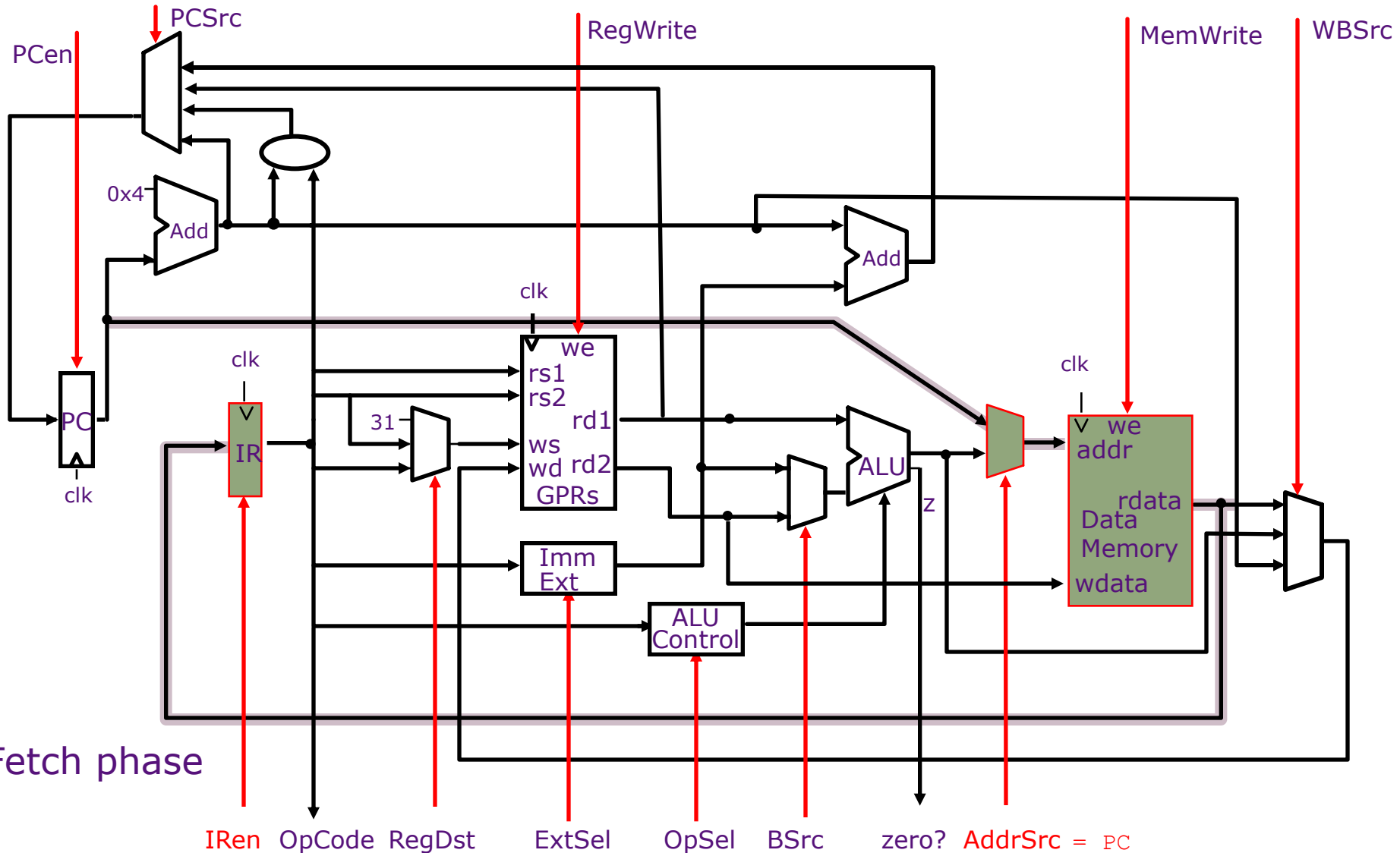


Princeton Microarchitecture

Datapath & Control

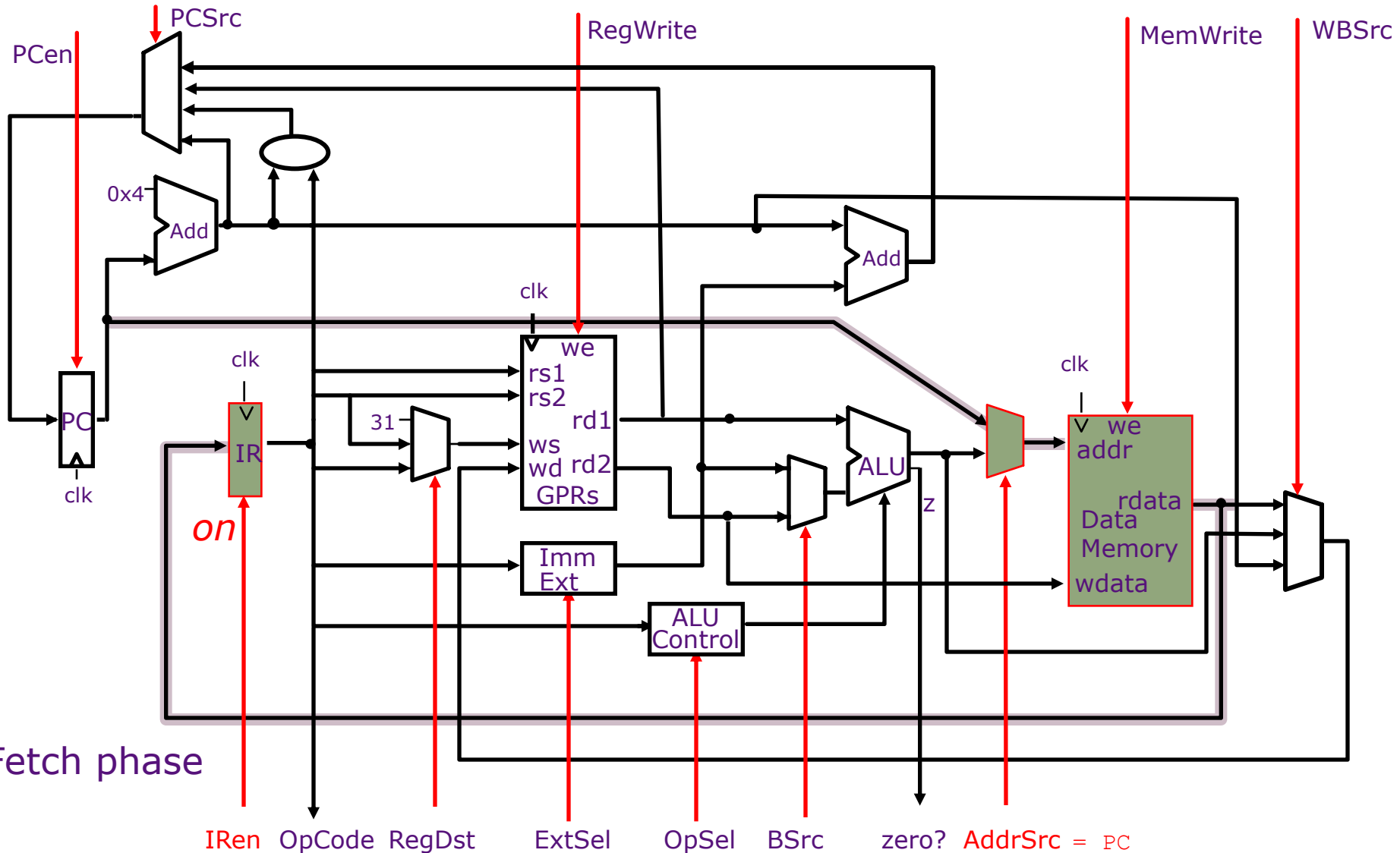


Princeton Microarchitecture

Datapath & Control

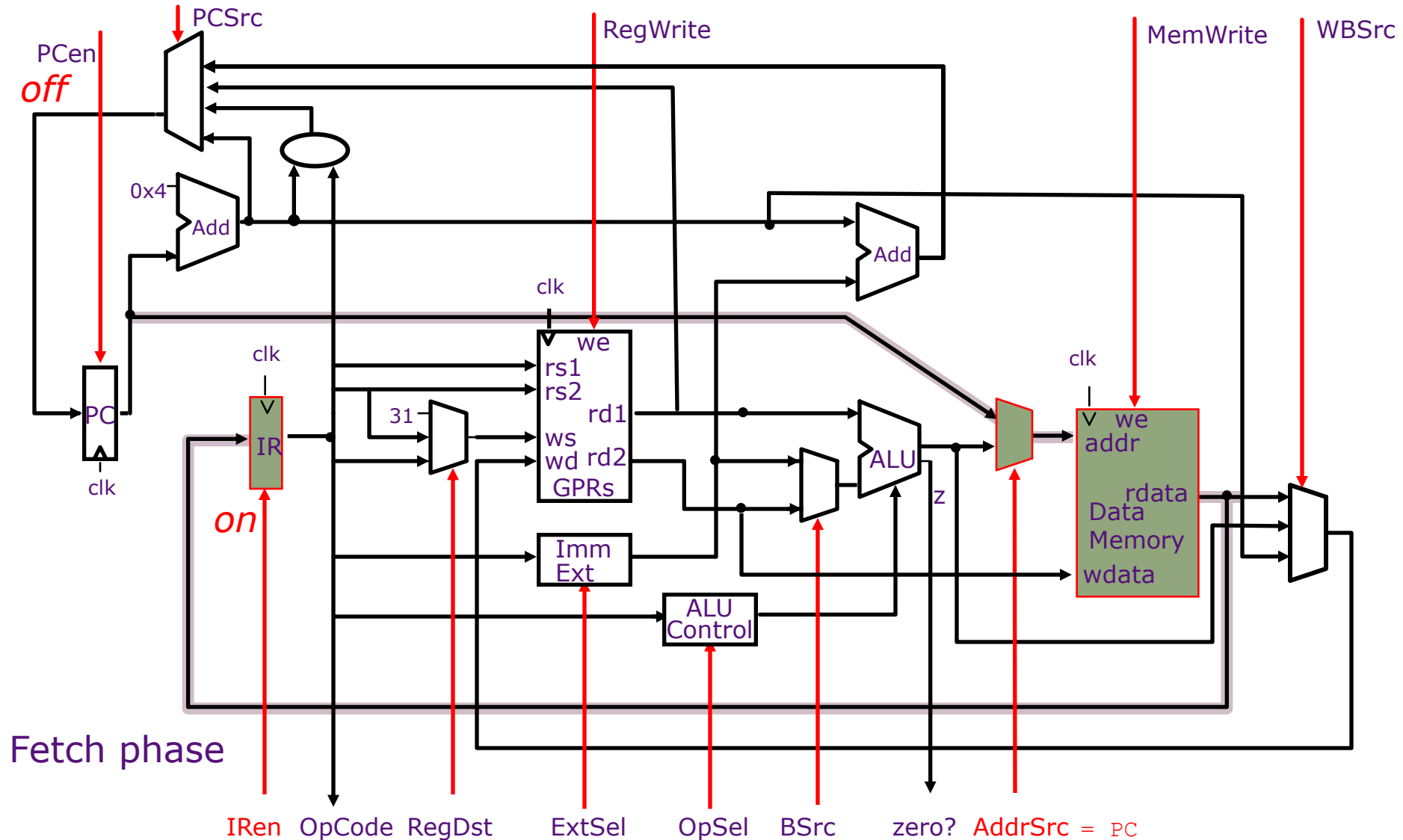

Princeton Microarchitecture


Datapath & Control

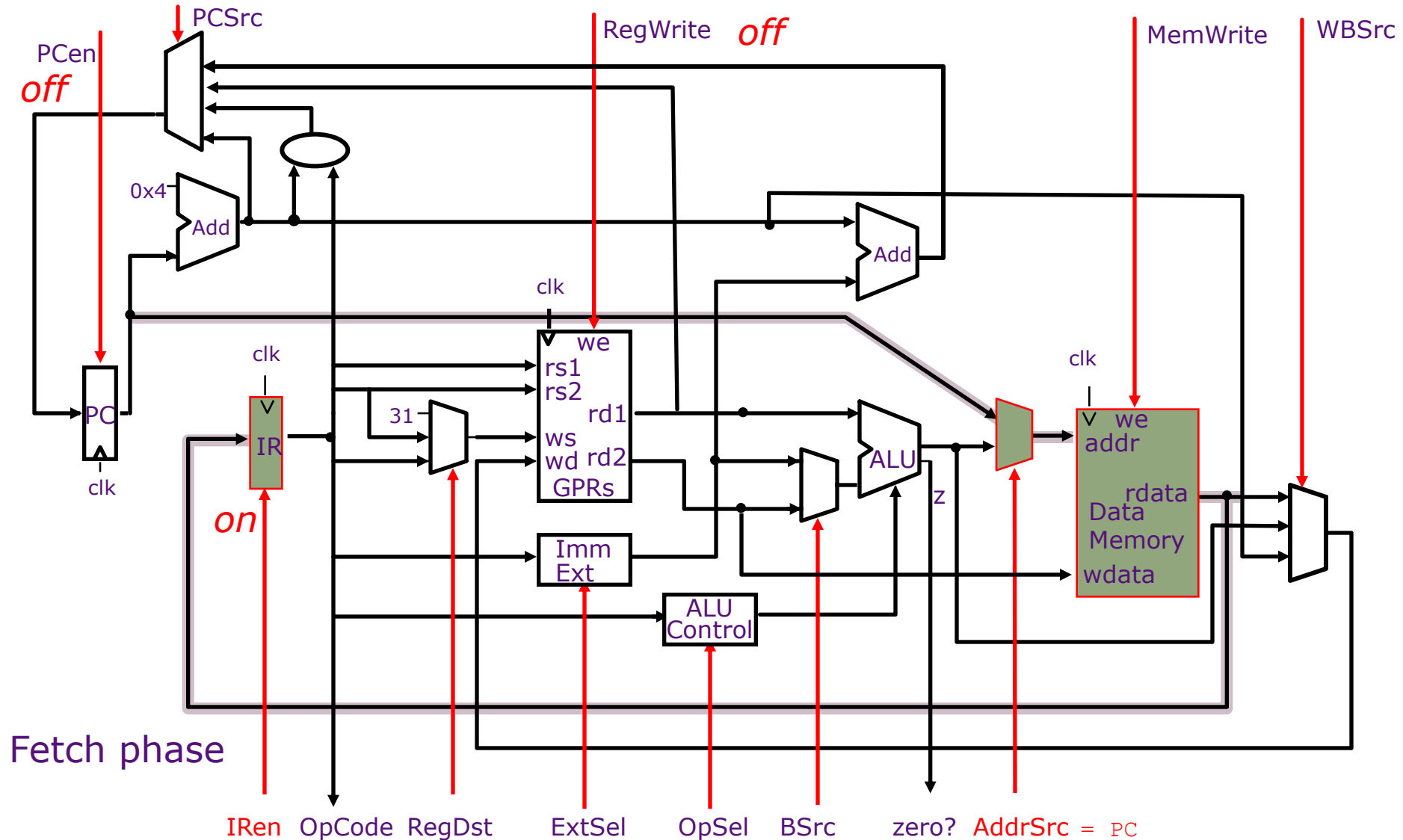

Fetch phase

Princeton Microarchitecture


Datapath & Control

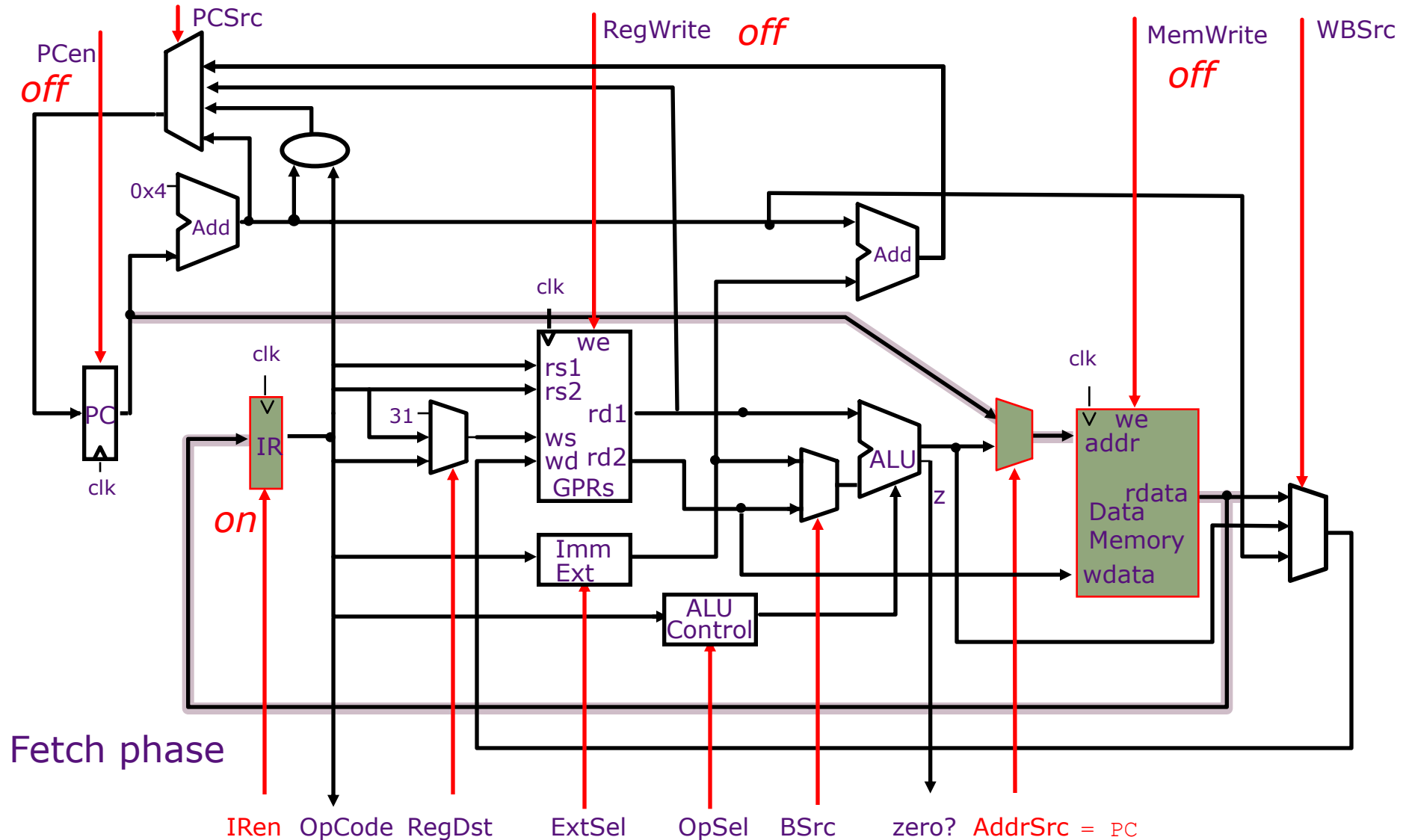



Two-State Controller:

Princeton Architecture

fetch phase

 


execute phase

  

A flipflop can be used to remember the phase

Hardwired Controller:

Princeton Architecture

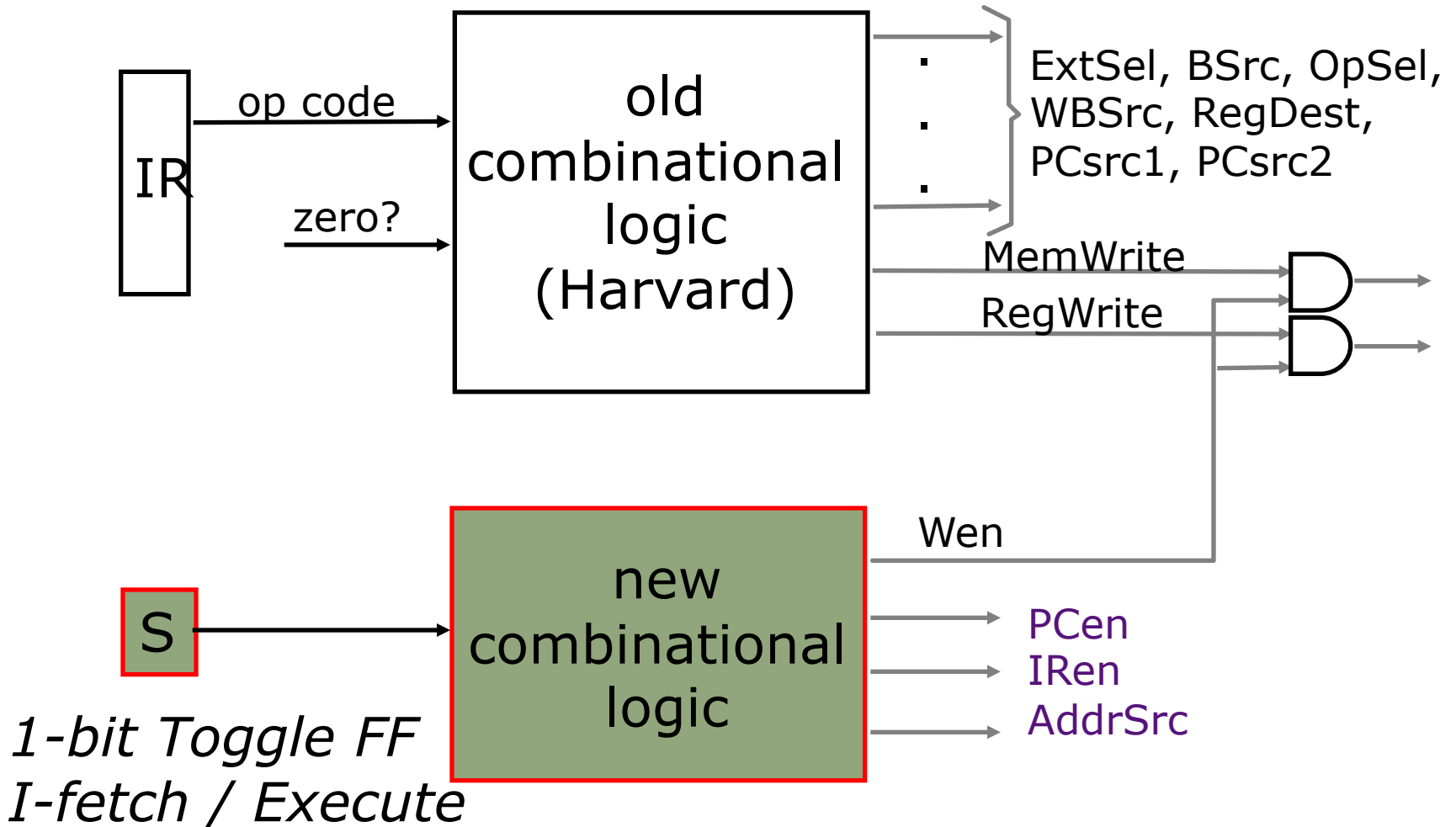

Clock Rate vs CPI

$$t_{\text{C-Princeton}} > \max \{t_M, t_{\text{RF}} + t_{\text{ALU}} + t_M + t_{\text{WB}}\}$$

$$t_{\text{C-Princeton}} > t_{\text{RF}} + t_{\text{ALU}} + t_M + t_{\text{WB}}$$

$$t_{\text{C-Harvard}} > t_M + t_{\text{RF}} + t_{\text{ALU}} + t_M + t_{\text{WB}}$$

Suppose $t_M \gg t_{\text{RF}} + t_{\text{ALU}} + t_{\text{WB}}$

$$t_{\text{C-Princeton}} = 0.5 * t_{\text{C-Harvard}}$$

$$\text{CPI}_{\text{Princeton}} = 2$$

$$\text{CPI}_{\text{Harvard}} = 1$$

No difference in performance!

Is it possible to design a controller for the Princeton architecture with $\text{CPI} < 2$?

CPI = Clock cycles Per Instruction

Stay tuned!