
 


Wires

 

Wires are an Old Problem

Cray-1, 1976



Cray-1 Wiring

Cray-3, 1993




Cray-3 wiring


Interconnect Problems

- A lot of circuit designers are very worried about what's happening with wires in CMOS technology
- Device technology has been scaling well, with gate performance increasing linearly with decreasing feature size
- Wires scale differently, and long wires have been getting relatively slower over time
- Wire delay is a function of wire resistance and capacitance

Modern Interconnect Stack

 

© IBM Tungsten local interconnect

 


© IBM

IBM CMOS7 process

6 layers of copper wiring

1 layer of tungsten local interconnect

Wire Resistance

 


$$\text{resistance} = \frac{(\text{length} \times \text{resistivity})}{(\text{height} \times \text{width})}$$

- bulk aluminum $2.8 \times 10^{-8} \Omega\text{-m}$
- bulk copper $1.7 \times 10^{-8} \Omega\text{-m}$
- bulk silver $1.6 \times 10^{-8} \Omega\text{-m}$


- Height (Thickness) fixed in given manufacturing process
- Resistances quoted as Ω/square
- TSMC 0.18 μm 6 Aluminum metal layers
 - M1-5 0.08 Ω/square (0.5 μm \times 1mm wire = 160 Ω)
 - M6 0.03 Ω/square (0.5 μm \times 1mm wire = 60 Ω)

Local Interconnect

 - Use contact material (tungsten) to provide extra layer of connectivity below metal 1
- Can also play same trick with silicided poly to connect gates to diffusion directly in RAMs
- Typically used to shrink memory cells or standard cells
- Contacts directly to poly gate or diffusion



Via Resistance

 


Vias made from Tungsten in Aluminum processes.
Vias are Copper in Copper processes

- Via resistance significant
- TSMC 0.18 μm 6-Al

Diff-M1	11.0 Ω
Poly-M1	10.4 Ω
M2-M1	4.5 Ω
M3-M1	9.5 Ω
M4-M1	15.0 Ω
M5-M1	19.6 Ω
M6-M1	21.8 Ω


- Resistance of two via stacks at each end of M1 wire equivalent to about 0.1 mm wire ($\sim 20 \Omega$)
- Resistance of two via stacks at each end of M6 wire about the same as 1 mm narrow M6 wire ($\sim 60 \Omega$)!!!
- Use multiple vias in parallel to reduce effective contact resistance
- Copper processes have lower via resistance

Wire Capacitance

 

- Capacitance depends on geometry of surrounding wires and relative permittivity, ϵ_r , of insulating dielectric
 - silicon dioxide, SiO_2 $\epsilon_r = 3.9$
 - silicon flouride, SiOF $\epsilon_r = 3.1$
 - SiLKTM polymer, $\epsilon_r = 2.6$
- Can have different materials between wires and between layers, and also different materials on higher layers


IBM Experimental 130nm Process

 

 E. Barth, IBM Microelectronics


Capacitance Scaling

parallel plate capacitance $\propto \frac{\text{width}}{\text{spacing}} \times \text{length}$



- Capacitance/unit length ~constant with feature size scaling (width and spacing scale together)
 - Isolated wire sees approx. 100 fF/mm
 - With close neighbors about 160 fF/mm
- Need to use capacitance extractor to get accurate values


RC Delay Estimates

 


Penfield-Rubenstein model estimates:

$$\text{Delay} = \sum_i \left(\sum_{j=1}^{j=i} R_j \right) C_i$$

Wire Delay Models

 

 - Wire has distributed R and C per unit length
 - wire delay increases quadratically with length
 - edge rate also degrades quadratically with length
- Simple lumped Π model gives reasonable approximation
 - R_w is lumped resistance of wire
 - C_w is lumped capacitance (put half at each end)




$$\text{Delay} = R_{\text{driver}} \times \frac{C_w}{2} + (R_{\text{driver}} + R_w) \times \left(\frac{C_w}{2} + C_{\text{load}} \right)$$

Wire Delay Example

- In 0.18 μ m TSMC, 5x minimum inverter with effective resistance of 3 k Ω , driving FO4 load (25fF)
- Delay = Rdriver x Cload = 75 ps
- Now add 1mm M1 wire, 0.25 μ m wide
 - R_w = 320 Ω wire + 22 Ω vias = 344 Ω
 - C_w = 160fF

$$\begin{aligned} \text{Delay} &= R_{\text{driver}} \times \frac{C_w}{2} + (R_{\text{driver}} + R_w) \times \left(\frac{C_w}{2} + C_{\text{load}} \right) \\ &= 3\text{k}\Omega \times 80\text{fF} + (3\text{k}\Omega + 344\Omega) \times (80\text{fF} + 25\text{fF}) \\ &= 591\text{ps} \end{aligned}$$


Wire Delay Scaling, Local Wires

 

- For wire crossing same amount of circuitry
 - Resistance stays roughly constant
 - length decreases by same amount as width, height stays large and/or change material to copper
 - Capacitance decreases by scaling factor
 - cap/unit length constant, length decreases
- Wire delay tracks improvement in gate delay

[From Mark Horowitz, DAC 2000]

Wire Delay Scaling, Global Wires

 

- For wire crossing whole chip
 - Resistance grows linearly
 - Capacitance stays fixed
- Wire delay increases relative to gate delay

[From Mark Horowitz, DAC 2000]

Fewer Gates per Clock Cycle

- Processors in Intel 386 generation, around 50 FO4 gate delays per clock cycle
- Pentium-4 around 16 FO4 in normal clock, around 8 FO4 delays in fast ALU section
- Fastest 64-bit adder around 7 FO4 delays
- As measured in distance per clock cycle, wires are getting much slower


Process Technology Fixes

- **Reduce R**
 - use copper instead of aluminum, 40% reduction
 - provide upper layers with thicker metal for long range wires
 - provide more layers to improve density, makes wires shorter
- **Reduce C**
 - use low-k dielectric, >2x reduction possible
 - increase inter-layer spacing (limited effect, problems with via formation)
 - provide more layers to improve density, makes wires shorter

Layout Fixes


- **Reduce R**
 - make wires wider, increase in C is less than increase in R because of fringing fields
 - use parallel vias at contacts
 - floorplanning to keep wires short
 - careful routing to avoid unnecessary layer changes (vias)
- **Reduce C**
 - space wires further apart than minimum
 - avoid parallel wiring

Circuit Fixes - Repeaters

 


- **Use repeaters**
- **Converts quadratic dependence into linear dependence on length (but watch the constants)**
- **Can determine optimal repeater sizing for minimum delay**

Repeater Issues

 

- **Repeater must connect to transistor layers**
- **Blocks other routes with vias that connect down**
- **Requires space on active layers for buffer transistors and power connections**
- **Repeaters often grouped in preallocated repeater boxes spread around chip**
 - repeater location might not give ideal spacing

Repeater Staging In and Out

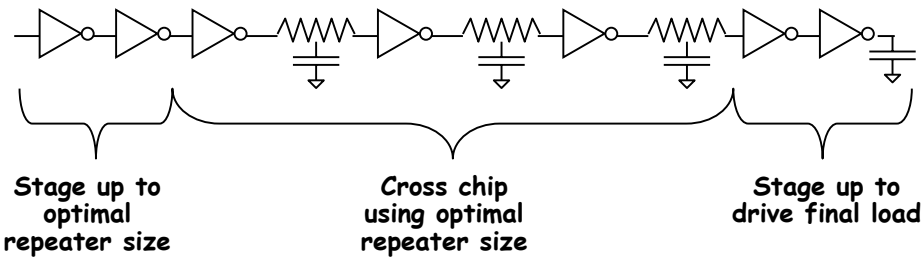


- For minimum delay, must stage up to repeater size at start of wire, and stage up to load at end of wire


Architectural Fixes: Pentium-4

1	TC Next IP
2	
3	TC Fetch
4	
5	Drive
6	Alloc
7	Rename
8	
9	Queue
10	Schedule 1
11	Schedule 2
12	Schedule 3
13	Dispatch 1
14	Dispatch 2
15	Register File 1
16	Register File 2
17	Execute
18	Flags
19	Branch Check
20	Drive

 Pipeline stages dedicated to driving signals across chip




Scalable Layout

 


- Design such that critical paths are gate dominated not interconnect dominated on first target process
- This helps ensure feature size shrinks give frequency improvements
- If critical path contains too much interconnect RC, then shrink won't see much frequency gain

Coupling Capacitances

 


- Most capacitance is to neighboring wires
- If A switches, injects voltage noise on B
 - magnitude depends on capacitive divider formed: $C_{AB}/(C_{AB}+C_B)$
- If A switches in opposite direction while B switches, coupling capacitance effectively doubles - Miller effect
- If A switches in same direction while B switches, coupling capacitance disappears
- These effects can lead to large variance in possible delay of B driver, possibly factor of 5 or 6 between best and worst case

Fixing Coupling Problems

 

- Avoid placing simultaneously switching signals next to each other for long parallel runs
- Reroute signals which will be quiet during switching inbetween simultaneous switching signals
- Route signals close to power rails to provide capacitance ballast
- Tough problem to solve - moving one wire can introduce new problems
 - "timing closure" causes many real-world schedule slips

Electromigration

 

- The electrons from a DC current flow will tend to push metal atoms out of place (AC current flow OK)
- Main problem is power lines, but some signal lines have unidirectional current
- Manufacturers place a current density limit for metal to guarantee small resistance increase after ~10 years operation
- TSMC 0.18 μm
 - 1mA/ μm (metal wires 0.4 μm thick)
 - 0.28 mA/via