

Computer Architecture: A Constructive Approach

Multi-cycle SMIPS Implementations


Joel Emer
Computer Science & Artificial Intelligence Lab.
Massachusetts Institute of Technology

March 5, 2012

<http://csg.csail.mit.edu/6.S078>

L8-1

Harvard-Style Datapath for MIPS old way

 

March 5, 2012

<http://csg.csail.mit.edu/6.S078>

L8-2

old way

Hardwired Control Table

Opcode	ExtSel	BSrc	OpSel	MemW	RegW	WBSrc	RegDst	PCSrc
ALU	*	Reg	Func	no	yes	ALU	rd	pc+4
ALUi	sExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
ALUiu	uExt ₁₆	Imm	Op	no	yes	ALU	rt	pc+4
LW	sExt ₁₆	Imm	+	no	yes	Mem	rt	pc+4
SW	sExt ₁₆	Imm	+	yes	no	*	*	pc+4
BEQZ _{Z=0}	sExt ₁₆	*	0?	no	no	*	*	br
BEQZ _{Z=1}	sExt ₁₆	*	0?	no	no	*	*	pc+4
J	*	*	*	no	no	*	*	jabs
JAL	*	*	*	no	yes	PC	R31	jabs
JR	*	*	*	no	no	*	*	rind
JALR	*	*	*	no	yes	PC	R31	rind

Bsrc = Reg / Imm

RegDst = rt / rd / R31

WBSrc = ALU / Mem / PC

PCSrc = pc+4 / br / rind / jabs


March 5, 2012

<http://csg.csail.mit.edu/6.S078>

L8-3

new way

Single-Cycle SMIPS

 

Datapath and control were derived automatically from a high-level rule-based description

March 5, 2012

<http://csg.csail.mit.edu/6.S078>

L8-4

Single-Cycle SMIPS *code structure*

```


module mkProc(Proc);
  Reg#(Addr) pc <- mkRegU;
  RFile      rf <- mkRFile;
  Memory     mem <- mkTwoPortedMemory;
  let iMem = mem.iport ; let dMem = mem.dport;

  rule doProc;
    let inst = iMem(MemReq{op:Ld, addr:pc, data:?});
    let dInst = decode(inst);
    Data rVal1 = rf.rd1(dInst.rSrc1);
    Data rVal2 = rf.rd2(dInst.rSrc2);
    let eInst = exec(dInst, rVal1, rVal2, pc);


```

update rf, pc and dMem

 Decoding Instructions: input-output types



Reading Registers

 


March 5, 2012

<http://csg.csail.mit.edu/6.S078>

L8-7

Executing Instructions

 

March 5, 2012

<http://csg.csail.mit.edu/6.S078>

L8-8

Branch Address Calculation

```
function Addr brAddrCalc(Address pc, Data val,  
                          IType iType, Data imm);  
  let targetAddr = case (iType)  
    J, Jal   : {pc[31:28], imm[27:0]};  
    Jr, Jalr  : val;  
    default  : pc + imm;  
  endcase;  
  return targetAddr;  
endfunction
```

Some Useful Functions

```
function Bool memType (IType i)  
  return (i==Ld || i == St);  
endfunction  
  
function Bool regWriteType (IType i)  
  return (i==Alu || i==Ld || i==Jal || i==Jalr);  
endfunction  
  
function Bool controlType (IType i)  
  return (i==J || i==Jr || i==Jal || i==Jalr || i==Br);  
endfunction
```

Execute Function

```
function ExecInst exec(DecodedInst dInst, Data rVal1,
                      Data rVal2, Addr pc);
    ExecInst einst = ?;

    Data aluVal2 = (dInst.immValid)? dInst.imm : rVal2
    let aluRes = alu(rVal1, aluVal2, dInst.aluFunc);
    let brAddr = brAddrCal(pc, rVal1, dInst.iType,
                          dInst.imm);

    einst.iType = dInst.iType;
    einst.addr = (memType(dInst.iType)? aluRes : brAddr);
    einst.data = dInst.iType==St ? rVal2 : aluRes;
    einst.brTaken = aluBr(rVal1, aluVal2, dInst.brComp);
    einst.rDst = dInst.rDst;
    return einst;
endfunction
```

Single-Cycle SMIPS *atomic state updates*


```
if(memType(eInst.iType))
    eInst.data <- dMem(MemReq{
        op: eInst.iType==Ld ? Ld : St,
        addr: eInst.addr,
        data: eInst.data});

if(regWriteType(eInst.iType))
    rf.wr(eInst.rDst, eInst.data);

pc <= eInst.brTaken ? eInst.addr : pc + 4;

endrule
endmodule
```

Single-Cycle SMIPS: Clock Speed

 


$$t_{\text{Clock}} > t_M + t_{\text{DEC}} + t_{\text{RF}} + t_{\text{ALU}} + t_M + t_{\text{WB}}$$

We can improve the clock speed if we execute each instruction in two clock cycles

$$t_{\text{Clock}} > \max \{ t_M, (t_{\text{DEC}} + t_{\text{RF}} + t_{\text{ALU}} + t_M + t_{\text{WB}}) \}$$

Two-Cycle SMIPS

 

Introduce register "ir" to hold a fetched instruction and register "stage" to remember which stage (fetch/execute) we are in

ir: The instruction register

- ◆ You may recall from our earlier discussion of pipelining that when we take multiple cycles to perform some operation (e.g., IFFT), there is a possibility that intermediate registers do not contain any meaningful data in some cycles
- ◆ It is straight forward to convert ir into a pipeline register
 - We can associate (Valid/Invalid) bit with ir
 - Equivalently, we can think of ir as a single-element FIFO

Additional Types

```
typedef struct {  
    Addr    pc;  
    Bit#(32) inst;  
} TypeFetch2Decode deriving (Bits, Eq);  
  
typedef enum {Fetch, Execute}  
    TypeStage deriving (Bits, Eq);
```


Two-Cycle SMIPS

```
module mkProc(Proc);
  Reg#(Addr) pc <- mkRegU;
  RFile      rf <- mkRFile;
  Memory     mem <- mkTwoPortedMemory;
  let iMem = mem.iport; let dMem = mem.dport;
  Reg#(TypeFetch2Decode) ir <- mkRegU;
  Reg#(TypeStage) stage <- mkReg(Fetch);

  rule doFetch (state==Fetch);
    let inst = iMem(MemReq{op:Ld, addr:pc, data:?});
    ir <= TypeFetch2Decode{pc: pc, inst: inst};
    stage <= Execute;
  endrule
endmodule
```

Two-Cycle SMIPS

```
rule doExecute(stage==Execute);
  let irpc = ir.pc;
  let inst = ir.inst;
  let dInst = decode(inst);
  Data rVal1 = rf.rd1(dInst.rSrc1);
  Data rVal2 = rf.rd2(dInst.rSrc2);
  let eInst = exec(dInst, rVal1, rVal2, irpc);
  if(memType(eInst.iType))
    eInst.data <- dMem(MemReq{
      op: eInst.iType==Ld ? Ld : St,
      addr: eInst.addr, data: eInst.data});
  if(regWriteType(eInst.iType))
    rf.wr(eInst.rDst, eInst.data);
  pc <= eInst.brTaken ? eInst.addr : pc + 4;
  stage <= Fetch;
endrule
endmodule
```


no change from
single-cycle

Princeton versus Harvard Architecture

- ◆ Harvard architecture uses different memories for instructions and data
 - needed for a single-cycle implementation
- ◆ Princeton architecture uses the same memory for instruction and data and thus, requires at least two cycles to execute Load/Store instructions

The two-cycle implementations of Princeton and Harvard architectures are almost the same

SMIPS Princeton Architecture

 

Two-Cycle SMIPS Princeton

```
module mkProc(Proc);
  Reg#(Addr) pc <- mkRegU;
  RFile      rf <- mkRFile;
  Memory     mem <- mkOnePortedMemory;
  let uMem = mem.port;


  Reg#(TypeFetch2Decode) ir <- mkRegU;
  Reg#(TypeStage)        stage <- mkReg(Fetch);

  rule doFetch (stage==Fetch);
    let inst <- uMem(MemReq{op:Ld, addr:pc, data:?});
    ir <= TypeFetch2Decode{pc: pc, inst: inst};
    stage <= Execute;
  endrule
endmodule
```

Two-Cycle SMIPS Princeton

```
rule doExecute(stage==Execute);
  let irpc = ir.pc;
  let inst = ir.inst;
  let dInst = decode(inst);
  Data rVal1 = rf.rd1(dInst.rSrc1);
  Data rVal2 = rf.rd2(dInst.rSrc2);
  let eInst = exec(dInst, rVal1, rVal2, irpc);
  if(memType(eInst.iType))
    eInst.data <- uMem(MemReq{
      op: eInst.iType==Ld ? Ld : St,
      addr: eInst.addr, data: eInst.data});
  if(regWriteType(eInst.iType))
    rf.wr(eInst.rDst, eInst.data);
  pc <= eInst.brTaken ? eInst.addr : pc + 4;
  stage <= Fetch;
endrule
endmodule
```

Two-Cycle SMIPS: *Analysis*

 

In any given clock cycle, lots of unused hardware!

next lecture: Pipelining to increase the throughput