

Constructive Computer Architecture

Combinational circuits

Arvind
Computer Science & Artificial Intelligence Lab.
Massachusetts Institute of Technology

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-1

Contributors to the course material

- ◆ Arvind, Rishiyur S. Nikhil, Joel Emer, Muralidaran Vijayaraghavan
- ◆ Staff and students in 6.375 (Spring 2013), 6.S195 (Fall 2012, 2013), 6.S078 (Spring 2012)
 - Andy Wright, Asif Khan, Richard Ruhler, Sang Woo Jun, Abhinav Agarwal, Myron King, Kermin Fleming, Ming Liu, Li-Shiuan Peh
- ◆ External
 - Prof Amey Karkare & students at IIT Kanpur
 - Prof Jihong Kim & students at Seoul Nation University
 - Prof Derek Chiou, University of Texas at Austin
 - Prof Yoav Etsion & students at Technion

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-2


Content

- ◆ Design of a combinational ALU starting with primitive gates And, Or and Not
- ◆ Combinational circuits as acyclic wiring diagrams of primitive gates
- ◆ Introduction to BSV
 - Intro to types – enum, typedefs, numeric types, int#(32) vs integer, bool vs bit#(1), vectors
 - Simple operations: concatenation, conditionals, loops
 - Functions
 - Static elaboration and a structural interpretation of the textual code

Combinational circuits are acyclic interconnections of gates

- ◆ And, Or, Not
- ◆ Nand, Nor, Xor
- ◆ ...

Arithmetic-Logic Unit (ALU)

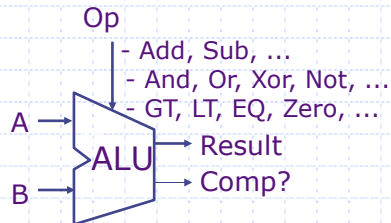

ALU performs all the arithmetic and logical functions

Each individual function can be described as a combinational circuit

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>


L01-5

Full Adder: A one-bit adder

```
function fa(a, b, c_in);  
    s = (a ^ b) ^ c_in;  
    c_out = (a & b) | (c_in & (a ^ b));  
    return {c_out, s};  
endfunction
```

Structural code – only specifies interconnection between boxes

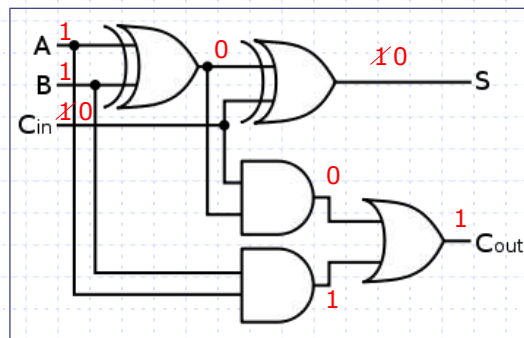Not quite correct – needs type annotations



December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-6

Full Adder: A one-bit adder

corrected


```
function Bit#(2) fa(Bit#(1) a, Bit#(1) b,
                    Bit#(1) c_in);
  Bit#(1) s = (a ^ b) ^ c_in;
  Bit#(1) c_out = (a & b) | (c_in & (a ^ b));
  return {c_out, s};
endfunction
```

"Bit#(1) a" type
declaration says that
a is one bit wide

{c_out, s} represents
bit concatenation

How big is {c_out, s}?

2 bits

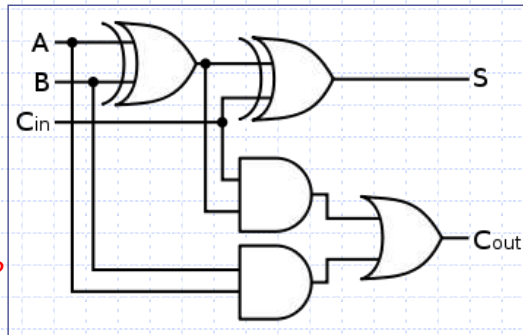

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-7

Types

◆ A type is a grouping of values:

- Integer: 1, 2, 3, ...
- Bool: True, False
- Bit: 0, 1
- A pair of Integers: Tuple2#(Integer, Integer)
- A function **fname** from Integers to Integers:

```
function Integer fname (Integer arg)
```

◆ Every expression and variable in a BSV program
has a type; sometimes it is specified explicitly
and sometimes it is deduced by the compiler

◆ Thus we say an expression has a type or belongs
to a type

The type of each expression is unique

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-8

Parameterized types:

- ◆ A type declaration itself can be parameterized by other types
- ◆ Parameters are indicated by using the syntax '#'
 - For example `Bit#(n)` represents `n` bits and can be instantiated by specifying a value of `n`
`Bit#(1)`, `Bit#(32)`, `Bit#(8)`, ...

Type synonyms

```
typedef bit [7:0] Byte;
```

```
typedef Bit#(8) Byte;
```

The same

```
typedef Bit#(32) Word;
```

```
typedef Tuple2#(a,a) Pair#(type a);
```

```
typedef Int#(n) MyInt#(type n);
```

```
typedef Int#(n) MyInt#(numeric type n);
```

The same

Type declaration versus deduction

- ◆ The programmer writes down types of some expressions in a program and the compiler deduces the types of the rest of expressions
- ◆ If the type deduction cannot be performed or the type declarations are inconsistent then the compiler complains

```
function Bit#(2) fa(Bit#(1) a, Bit#(1) b,  
                    Bit#(1) c_in);  
    Bit#(1) s = (a ^ b) ^ c_in;  
    Bit#(2) c_out = (a & b) | (c_in & (a ^ b));  
    return {c_out, s};  
endfunction
```

type error


Type checking prevents lots of silly mistakes

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-11

2-bit Ripple-Carry Adder

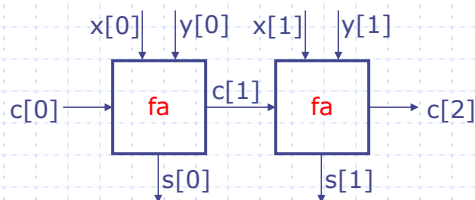

fa can be used as a black-box long as we understand its type signature

```
function Bit#(3) add(Bit#(2) x, Bit#(2) y,  
                    Bit#(1) c0);  
    Bit#(2) s = 0;    Bit#(3) c=0; c[0] = c0;  
    let cs0 = fa(x[0], y[0], c[0]);  
    c[1] = cs0[1];    s[0] = cs0[0];  
    let cs1 = fa(x[1], y[1], c[1]);  
    c[2] = cs1[1];    s[1] = cs1[0];  
    return {c[2], s};  
endfunction
```

The "let" syntax avoids having to write down types explicitly

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-12

"let" syntax

- ◆ The "let" syntax: avoids having to write down types explicitly


- `let cs0 = fa(x[0], y[0], c[0]);`
- `Bits#(2) cs0 = fa(x[0], y[0], c[0]);`

The same


Selecting a wire: $x[i]$

assume x is 4 bits wide



- ◆ Constant Selector: e.g., $x[2]$

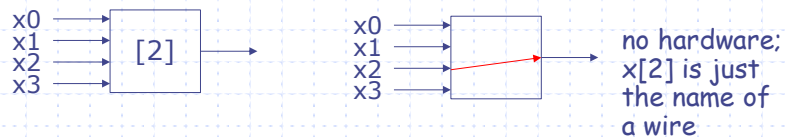

- ◆ Dynamic selector: $x[i]$

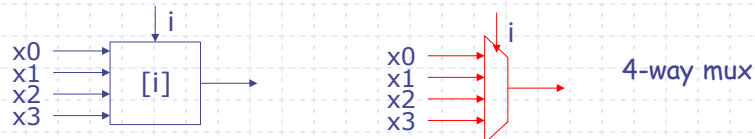

A 2-way multiplexer

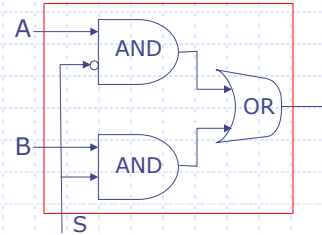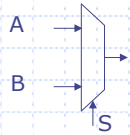

$(s==0) ? A : B$

Gate-level implementation

Conditional expressions are also synthesized using muxes


December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-15

A 4-way multiplexer
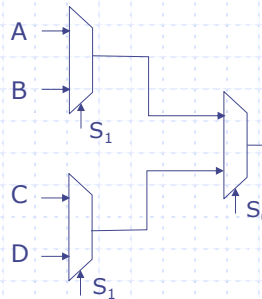
```
case {s1,s0} matches
  0: A;
  1: B;
  2: C;
  3: D;
endcase
```



December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-16

An w-bit Ripple-Carry Adder


```

function Bit#(w+1) addN(Bit#(w) x, Bit#(w) y,
                        Bit#(1) c0);
    Bit#(w) s; Bit#(w+1) c=0; c[0] = c0;
    for(Integer i=0; i<w; i=i+1)
    begin
        let cs = fa(x[i],y[i],c[i]);
        c[i+1] = cs[1]; s[i] = cs[0];
    end
    return {c[w],s};
endfunction

```

Not quite correct

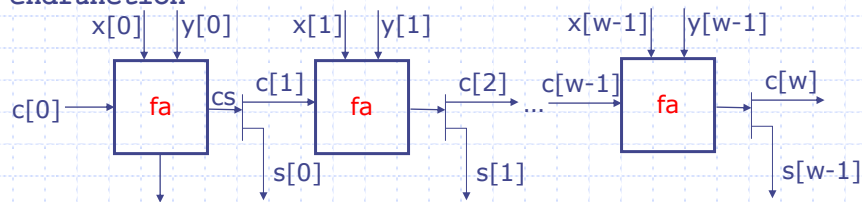Unfold the loop to get the wiring diagram



December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-17

Instantiating the parametric Adder

```

function Bit#(w+1) addN(Bit#(w) x, Bit#(w) y,
                        Bit#(1) c0);

```

Define add32, add3 ... using addN

```

// concrete instances of addN!
function Bit#(33) add32(Bit#(32) x, Bit#(32) y,
                        Bit#(1) c0) = addN(x,y,c0);

function Bit#(4) add3(Bit#(3) x, Bit#(3) y,
                        Bit#(1) c0) = addN(x,y,c0);

```

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-18

valueOf(w) versus w

- ◆ Each expression has a type and a value and these come from two entirely disjoint worlds
- ◆ w in $\text{Bit}\#(w)$ resides in the types world
- ◆ Sometimes we need to use values from the types world into actual computation. The function `valueOf` allows us to do that
 - Thus
 - $i < w$ is not type correct
 - $i < \text{valueOf}(w)$ is type correct

TAdd#(w, 1) versus w+1

- ◆ Sometimes we need to perform operations in the types world that are very similar to the operations in the value world
 - Examples: Add, Mul, Log
- ◆ We define a few special operators in the types world for such operations
 - Examples: $\text{TAdd}\#(m, n)$, $\text{TMul}\#(m, n)$, ...

A w-bit Ripple-Carry Adder

corrected

```
function Bit#(TAdd#(w,1)) addN(Bit#(w) x, Bit#(w) y,
                                Bit#(1) c0);
  Bit#(w) s; Bit#(TAdd#(w,1)) c; c[0] = c0;
  let valw = valueOf(w);
  for(Integer i=0; i<valw; i=i+1)
  begin
    let cs = fa(x[i],y[i],c[i]);
    c[i+1] = cs[1]; s[i] = cs[0];
  end
  return {c[valw],s};
endfunction
```

types world
equivalent of w+1

Lifting a type
into the value
world

Structural interpretation of a loop – unfold it to generate an acyclic graph

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-21

Static Elaboration phase

- ◆ When BSV programs are compiled, first type checking is done and then the compiler gets rid of many constructs which have no direct hardware meaning, like Integers, loops

```
for(Integer i=0; i<valw; i=i+1) begin
  let cs = fa(x[i],y[i],c[i]);
  c[i+1] = cs[1]; s[i] = cs[0];
end
```

```
cs0 = fa(x[0], y[0], c[0]); c[1]=cs0[1]; s[0]=cs0[0];
cs1 = fa(x[1], y[1], c[1]); c[2]=cs1[1]; s[1]=cs1[0];
...
csw = fa(x[valw-1], y[valw-1], c[valw-1]);
c[valw] = csw[1]; s[valw-1] = csw[0];
```

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-22


Integer **versus** Int# (32)

- ◆ In mathematics integers are unbounded but in computer systems integers always have a fixed size
- ◆ BSV allows us to express both types of integers, though unbounded integers are used only as a programming convenience

```
for(Integer i=0; i<valw; i=i+1)
  begin
    let cs = fa(x[i],y[i],c[i]);
    c[i+1] = cs[1]; s[i] = cs[0];
  end
```

Shift operators

Logical right shift by 2

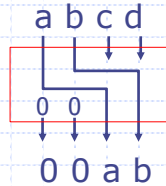


- ◆ Fixed size shift operation is cheap in hardware – just wire the circuit appropriately
- ◆ Rotate, sign-extended shifts – all are equally easy

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-25

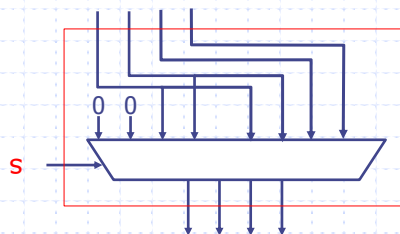Conditional operation: shift versus no-shift



- ◆ We need a mux to select the appropriate wires: if **s** is one the mux will select the wires on the left otherwise it would select wires on the right

```
(s==0) ? {a, b, c, d} : {0, 0, a, b};
```


December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-26

Logical right shift by n

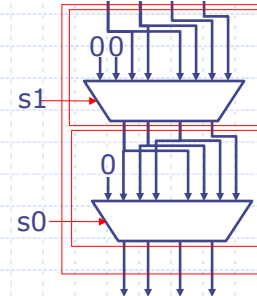- ◆ Shift n can be broken down in $\log n$ steps of fixed-length shifts of size 1, 2, 4, ...
 - Shift 3 can be performed by doing a shift 2 and shift 1
- ◆ We need a mux to omit a particular size shift
- ◆ Shift circuit can be expressed as $\log n$ nested conditional expressions



December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-27

A digression on types

- ◆ Suppose we have a variable c whose values can represent three different colors
 - We can declare the type of c to be `Bit#(2)` and say that 00 represents Red, 01 Blue and 10 Green
- ◆ A better way is to create a new type called `Color` as follows:

```
typedef enum {Red, Blue, Green}
Color deriving(Bits, Eq);
```

Types prevent us from mixing bits that represent color from raw bits

The compiler will automatically assign some bit representation to the three colors and also provide a function to test if the two colors are equal. If you do not use "deriving" then you will have to specify the representation and equality

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-28

Enumerated types

```
typedef enum {Red, Blue, Green}
Color deriving(Bits, Eq);

typedef enum {Eq, Neq, Le, Lt, Ge, Gt, AT, NT}
BrFunc deriving(Bits, Eq);

typedef enum {Add, Sub, And, Or, Xor, Nor, Slt, Sltu,
LShift, RShift, Sra}
AluFunc deriving(Bits, Eq);
```

Each enumerated type defines a new type

Combinational ALU

```
function Data alu(Data a, Data b, AluFunc func);
  Data res = case (func)
    Add    : (a + b);
    Sub    : (a - b);
    And    : (a & b);
    Or     : (a | b);
    Xor    : (a ^ b);
    Nor    : ~(a | b);
    Slt    : zeroExtend( pack( signedLT(a, b) ) );
    Sltu   : zeroExtend( pack( a < b ) );
    LShift : (a << b[4:0]);
    RShift : (a >> b[4:0]);
    Sra    : signedShiftRight(a, b[4:0]);
  endcase;
  return res;
endfunction
```

Given an implementation of the primitive operations like addN, Shift, etc. the ALU can be implemented simply by introducing a mux controlled by op to select the appropriate circuit

Comparison operators


```
function Bool aluBr(Data a, Data b, BrFunc brFunc);  
    Bool brTaken = case (brFunc)  
        Eq  : (a == b);  
        Neq : (a != b);  
        Le  : signedLE(a, 0);  
        Lt  : signedLT(a, 0);  
        Ge  : signedGE(a, 0);  
        Gt  : signedGT(a, 0);  
        AT  : True;  
        NT  : False;  
    endcase;  
    return brTaken;  
endfunction
```

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-31

ALU including Comparison operators

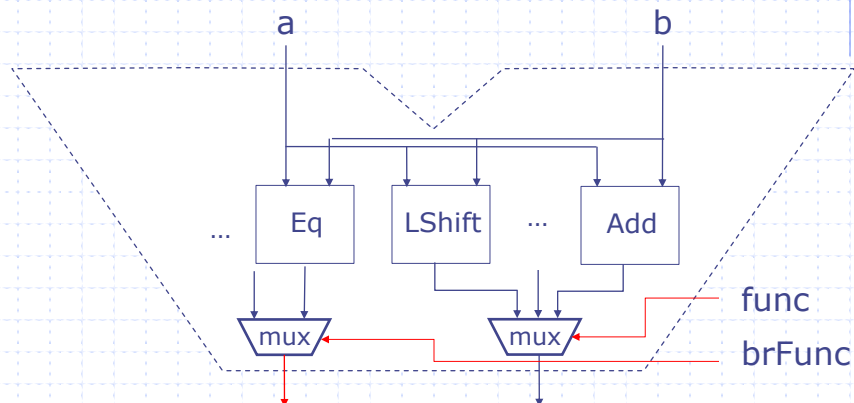

December 30, 2013

<http://csg.csail.mit.edu/6.s195/CDAC>

L01-32