

Instruction Pipelining: Hazard Resolution, Timing Constraints

Daniel Sanchez

Computer Science and Artificial Intelligence Laboratory
M.I.T.

Resolving Data Hazards

Strategy 1: *Wait for the result to be available by freezing earlier pipeline stages → stall*

Strategy 2: *Route data as soon as possible after it is calculated to the earlier pipeline stage → bypass*

Strategy 3: *Speculate on the dependence*
Two cases:

Guessed correctly → no special action required
Guessed incorrectly → kill and restart


Resolving Data Hazards (1)

Strategy 1:

*Wait for the result to be available by freezing earlier pipeline stages → **stall** (interlocks)*


Resolving Data Hazards by Stalling

Stall Condition

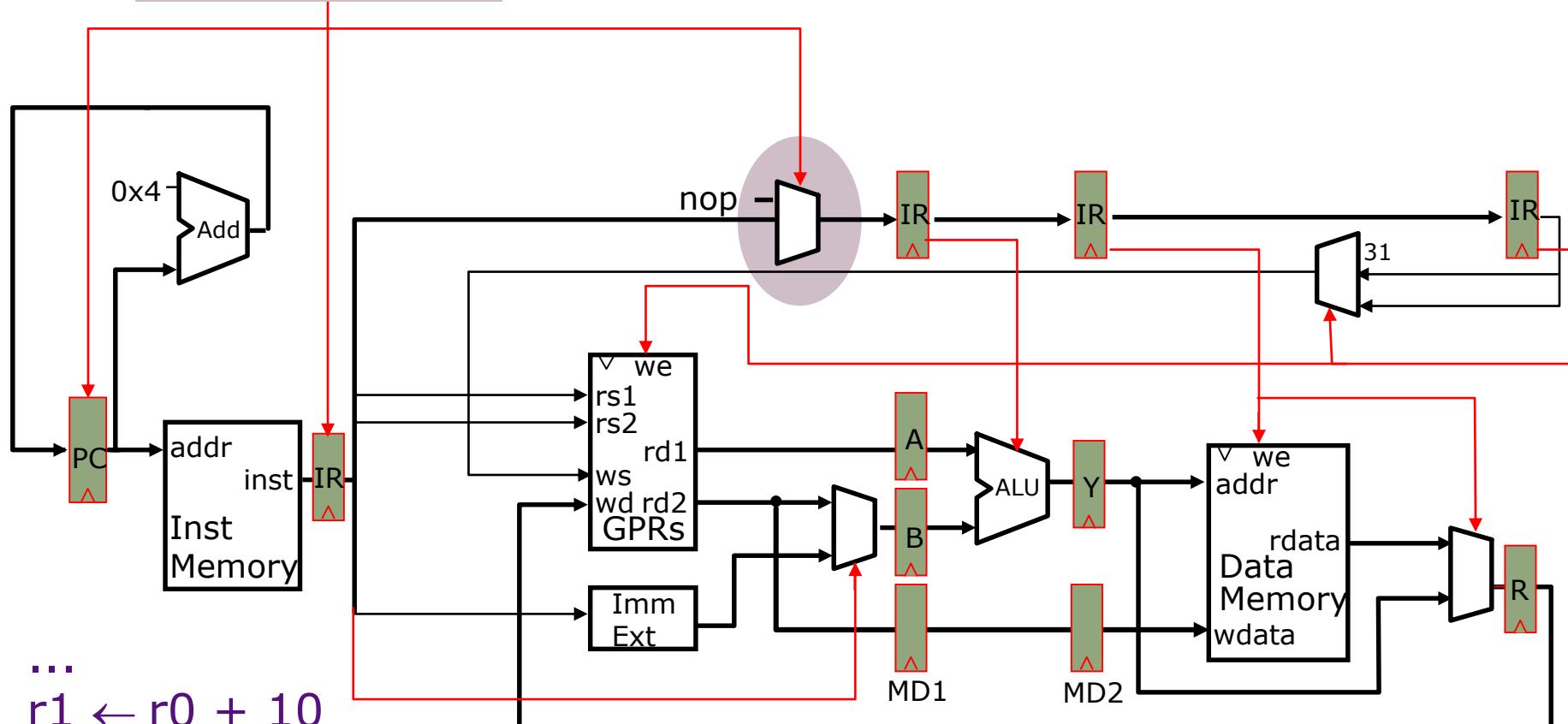

How do we know when to stall?


Stall Control Logic

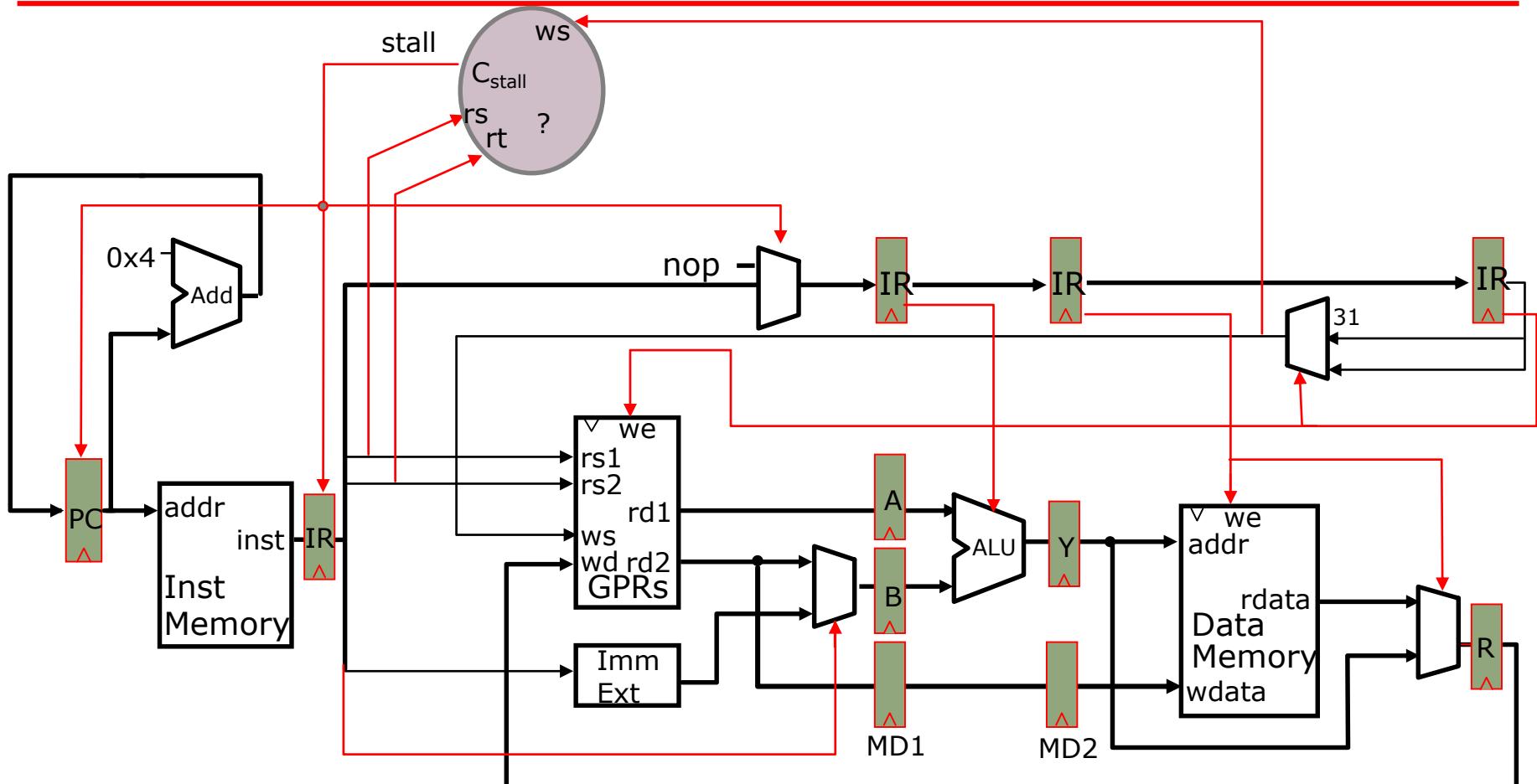

Compare the *source registers* of the instruction in the decode stage with the *destination register* of the *uncommitted instructions*.

Stall Control Logic

ignoring jumps & branches

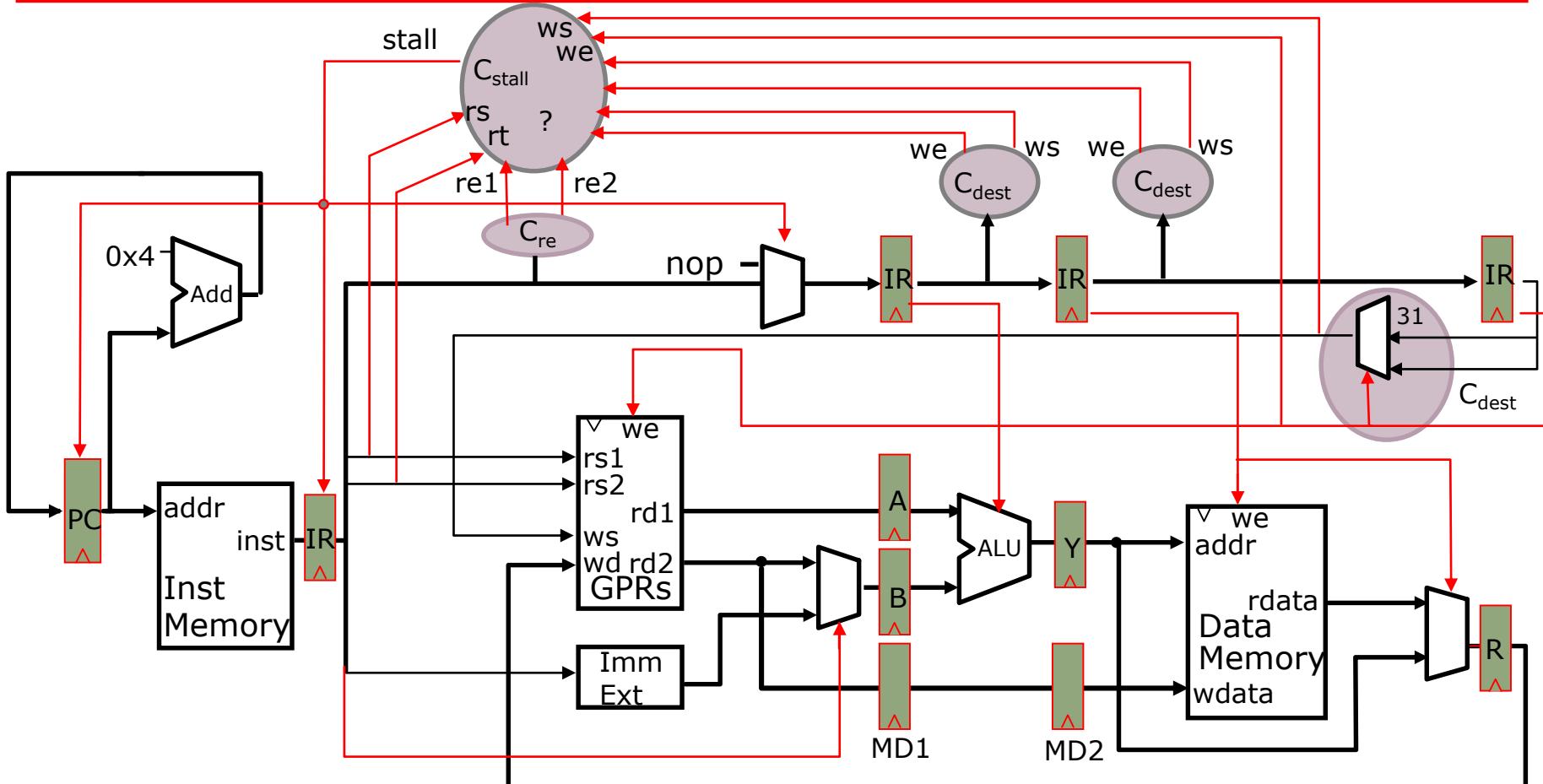

Should we always stall if the rs field matches some rd?
not every instruction writes a register \Rightarrow we
not every instruction reads a register \Rightarrow re

Source & Destination Registers

R-type:



I-type:



J-type:



		<i>source(s)</i>	<i>destination</i>
ALU	$rd \leftarrow (rs) \text{ func } (rt)$	rs, rt	rd
ALUi	$rt \leftarrow (rs) \text{ op imm}$	rs	rt
LW	$rt \leftarrow M [(rs) + \text{imm}]$	rs	rt
SW	$M [(rs) + \text{imm}] \leftarrow (rt)$	rs, rt	
BZ	$cond (rs)$ <i>true:</i> $PC \leftarrow (PC) + \text{imm}$ <i>false:</i> $PC \leftarrow (PC) + 4$	rs rs	
J	$PC \leftarrow (PC) + \text{imm}$		
JAL	$r31 \leftarrow (PC), PC \leftarrow (PC) + \text{imm}$		31
JR	$PC \leftarrow (rs)$	rs	
JALR	$r31 \leftarrow (PC), PC \leftarrow (rs)$	rs	31

Deriving the Stall Signal

C_{dest}

$ws = Case$ opcode	
ALU	$\Rightarrow rd$
ALUi, LW	$\Rightarrow rt$
JAL, JALR	$\Rightarrow R31$

$we = Case$ opcode

ALU, ALUi, LW	$\Rightarrow (ws \neq 0)$
JAL, JALR	$\Rightarrow on$
...	$\Rightarrow off$

C_{re}

$re1 = Case$ opcode	
ALU, ALUi,	$\Rightarrow on$
LW, SW, BZ,	
JR, JALR	
J, JAL	$\Rightarrow off$

$re2 = Case$ opcode

ALU, SW	$\Rightarrow on$
...	$\Rightarrow off$

C_{stall}


$$\begin{aligned} stall = & ((rs_D == ws_E) \cdot we_E + \\ & (rs_D == ws_M) \cdot we_M + \\ & (rs_D == ws_W) \cdot we_W) \cdot re1_D + \\ & ((rt_D == ws_E) \cdot we_E + \\ & (rt_D == ws_M) \cdot we_M + \\ & (rt_D == ws_W) \cdot we_W) \cdot re2_D \end{aligned}$$

This is not
the full story !

Hazards due to Loads & Stores

Stall Condition

What if
 $(r1)+7 = (r3)+5$?

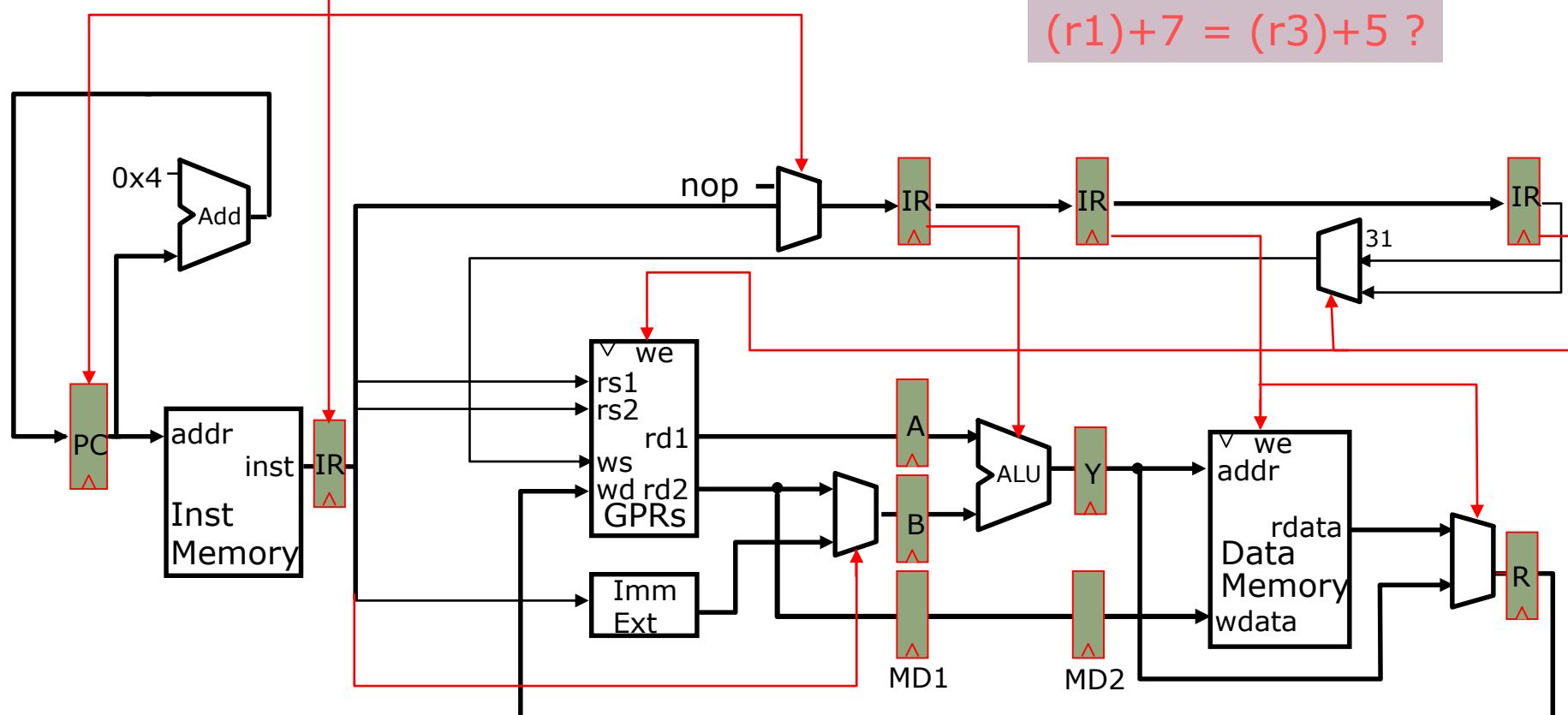

$M[(r1)+7] \leftarrow (r2)$
 $r4 \leftarrow M[(r3)+5]$

*Is there any possible data hazard
in this instruction sequence?*

Load & Store Hazards

```
...  
M[(r1)+7] ← (r2)  
r4 ← M[(r3)+5]  
...
```

$(r1)+7 = (r3)+5 \Rightarrow \text{data hazard}$

However, the hazard is avoided because *our memory system completes writes in one cycle!*

Load/Store hazards are sometimes resolved in the pipeline and sometimes in the memory system itself.

More on this later in the course.

Resolving Data Hazards (2)

Strategy 2:

Route data as soon as possible after it is calculated to the earlier pipeline stage → *bypass*

Bypassing

	<i>time</i>	t0	t1	t2	t3	t4	t5	t6	t7	...
(I ₁)	$r1 \leftarrow r0 + 10$	IF ₁	ID ₁	EX ₁	MA ₁	WB ₁				
(I ₂)	$r4 \leftarrow r1 + 17$		IF ₂	ID ₂	ID ₂	ID ₂	ID ₂	EX ₂	MA ₂	WB ₂
(I ₃)				IF ₃	IF ₃	IF ₃	IF ₃	ID ₃	EX ₃	MA ₃
(I ₄)								IF ₄	ID ₄	EX ₄
(I ₅)								IF ₅	ID ₅	


Each *stall* or *kill* introduces a bubble $\Rightarrow CPI > 1$

When is data actually available? **At Execute**

	<i>time</i>	t0	t1	t2	t3	t4	t5	t6	t7	...
(I ₁)	$r1 \leftarrow r0 + 10$	IF ₁	ID ₁	EX ₁	MA ₁	WB ₁				
(I ₂)	$r4 \leftarrow r1 + 17$		IF ₂	ID ₂	EX ₂	MA ₂	WB ₂			
(I ₃)				IF ₃	ID ₃	EX ₃	MA ₃	WB ₃		
(I ₄)					IF ₄	ID ₄	EX ₄	MA ₄	WB ₄	
(I ₅)						IF ₅	ID ₅	EX ₅	MA ₅	WB ₅

A new datapath, i.e., a *bypass*, can get the data from the output of the ALU to its input

Adding a Bypass

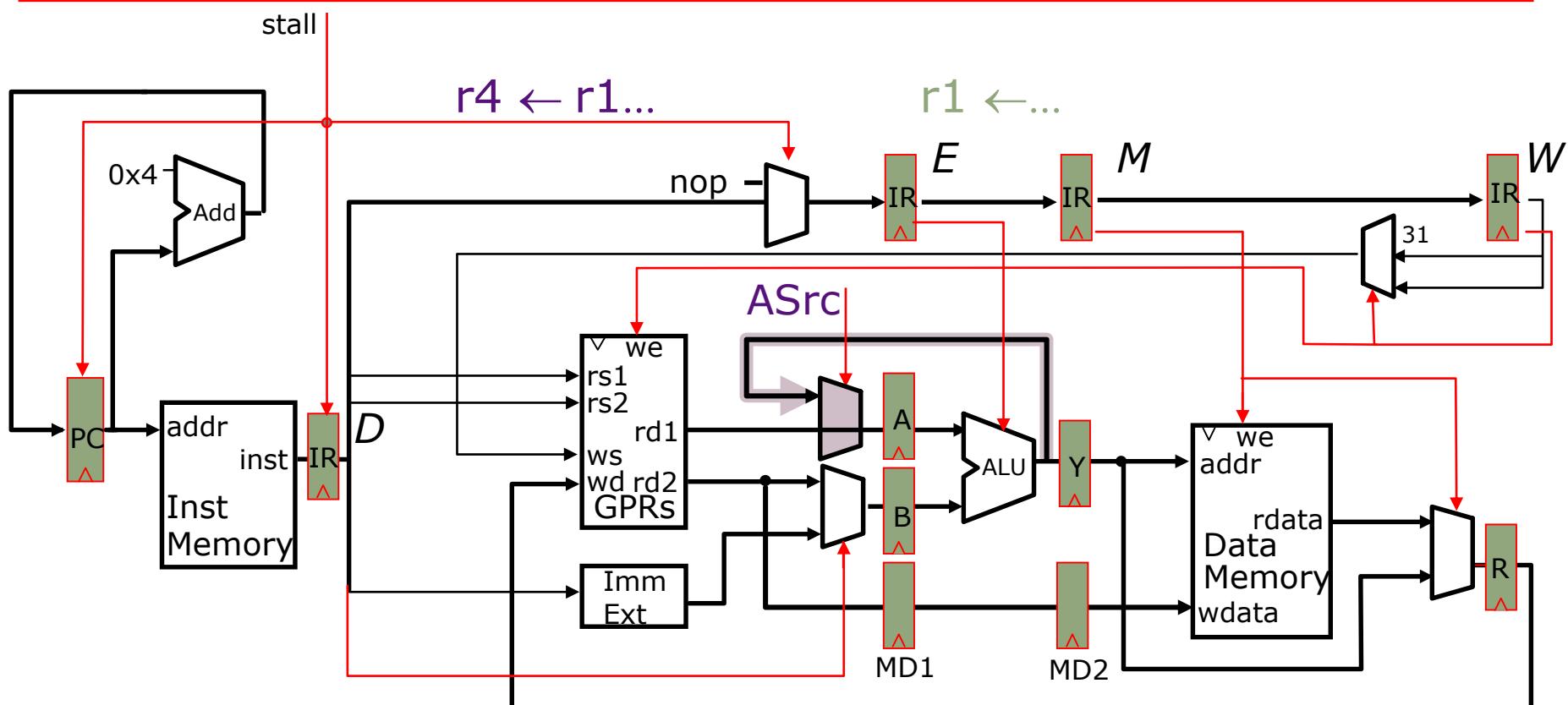

When does *this* bypass help?

(I₁) ...
(I₂) r1 ← r0 + 10
 r4 ← r1 + 17 yes

r1 ← M[r0 + 10]
r4 ← r1 + 17 no

JAL 500
r4 ← r31 + 17 no

The Bypass Signal

Deriving it from the Stall Signal

$$\begin{aligned} \text{stall} = & ((\cancel{\text{rs}_D == \text{ws}_E}) \cdot \text{we}_E + (\text{rs}_D == \text{ws}_M) \cdot \text{we}_M + (\text{rs}_D == \text{ws}_W) \cdot \text{we}_W) \cdot \text{re1}_D \\ & + ((\text{rt}_D == \text{ws}_E) \cdot \text{we}_E + (\text{rt}_D == \text{ws}_M) \cdot \text{we}_M + (\text{rt}_D == \text{ws}_W) \cdot \text{we}_W) \cdot \text{re2}_D \end{aligned}$$

$\text{ws} = \text{Case opcode}$

ALU	$\Rightarrow \text{rd}$
ALUi, LW	$\Rightarrow \text{rt}$
JAL, JALR	$\Rightarrow \text{R31}$

$\text{we} = \text{Case opcode}$

ALU, ALUi, LW	$\Rightarrow (\text{ws} \neq 0)$
JAL, JALR	$\Rightarrow \text{on}$
	$\Rightarrow \text{off}$

$$\text{ASrc} = (\text{rs}_D == \text{ws}_E) \cdot \text{we}_E \cdot \text{re1}_D$$

Is this correct?

No, because only ALU and ALUi instructions can benefit from this bypass

How might we address this?

Split we_E into two components: we-bypass, we-stall

Bypass and Stall Signals

Split we_E into two components: we-bypass, we-stall


$we\text{-bypass}_E = \begin{cases} \text{Case } opcode_E \\ \text{ALU, ALUi} & \Rightarrow (ws \neq 0) \\ \dots & \Rightarrow \text{off} \end{cases}$

$we\text{-stall}_E = \begin{cases} \text{Case } opcode_E \\ LW & \Rightarrow (ws \neq 0) \\ JAL, JALR & \Rightarrow \text{on} \\ \dots & \Rightarrow \text{off} \end{cases}$

$$ASrc = (rs_D == ws_E) \cdot we\text{-bypass}_E \cdot re1_D$$

$$\begin{aligned} stall = & ((rs_D == ws_E) \cdot we\text{-stall}_E + \\ & (rs_D == ws_M) \cdot we_M + (rs_D == ws_W) \cdot we_W) \cdot re1_D \\ & + ((rt_D == ws_E) \cdot we_E + (rt_D == ws_M) \cdot we_M + (rt_D == ws_W) \cdot we_W) \cdot re2_D \end{aligned}$$

Fully Bypassed Datapath

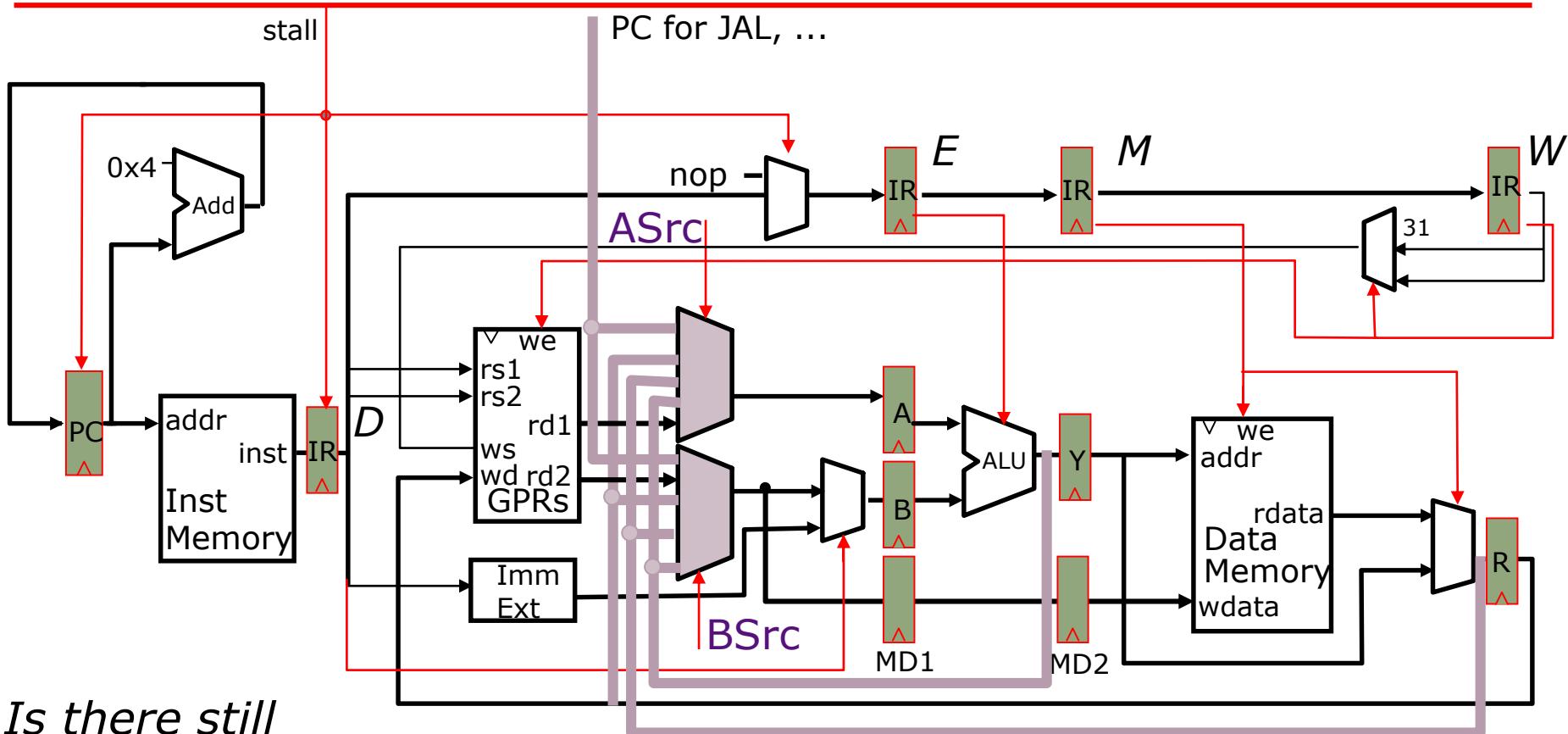

*Is there still
a need for the
stall signal?*

$$\begin{aligned} \text{stall} = & (rs_D == ws_E) \cdot (opcode_E == LW_E) \cdot (ws_E \neq 0) \cdot re1_D \\ & + (rt_D == ws_E) \cdot (opcode_E == LW_E) \cdot (ws_E \neq 0) \cdot re2_D \end{aligned}$$

Resolving Data Hazards (3)

Strategy 3:

Speculate on the dependence. Two cases:

Guessed correctly → no special action required

Guessed incorrectly → kill and restart

Instruction to Instruction Dependence

- What do we need to calculate next PC?
 - For Jumps
 - Opcode, offset, and PC
 - For Jump Register
 - Opcode and register value
 - For Conditional Branches
 - Opcode, offset, PC, and register (for condition)
 - For all others
 - Opcode and PC
- In what stage do we know these?
 - PC → Fetch
 - Opcode, offset → Decode (or Fetch?)
 - Register value → Decode
 - Branch condition ($(rs) == 0$) → Execute (or Decode?)

NextPC Calculation Bubbles

	time									
	t0	t1	t2	t3	t4	t5	t6	t7	...	
(I ₁)	r1 ← (r0) + 10	IF ₁	ID ₁	EX ₁	MA ₁	WB ₁				
(I ₂)	r3 ← (r2) + 17		IF ₂	IF ₂	ID ₂	EX ₂	MA ₂	WB ₂		
(I ₃)				IF ₃	IF ₃	ID ₃	EX ₃	MA ₃	WB ₃	
(I ₄)					IF ₄	IF ₄	ID ₄	EX ₄	MA ₄	WB ₄


	time									
	t0	t1	t2	t3	t4	t5	t6	t7	...	
Resource Usage	IF	I ₁	nop	I ₂	nop	I ₃	nop	I ₄		
	ID		I ₁	nop	I ₂	nop	I ₃	nop	I ₄	
	EX			I ₁	nop	I ₂	nop	I ₃	nop	I ₄
	MA				I ₁	nop	I ₂	nop	I ₃	nop
	WB					I ₁	nop	I ₂	nop	I ₄

nop \Rightarrow *pipeline bubble*

What's a good guess for next PC?

PC+4

Speculate NextPC is PC+4

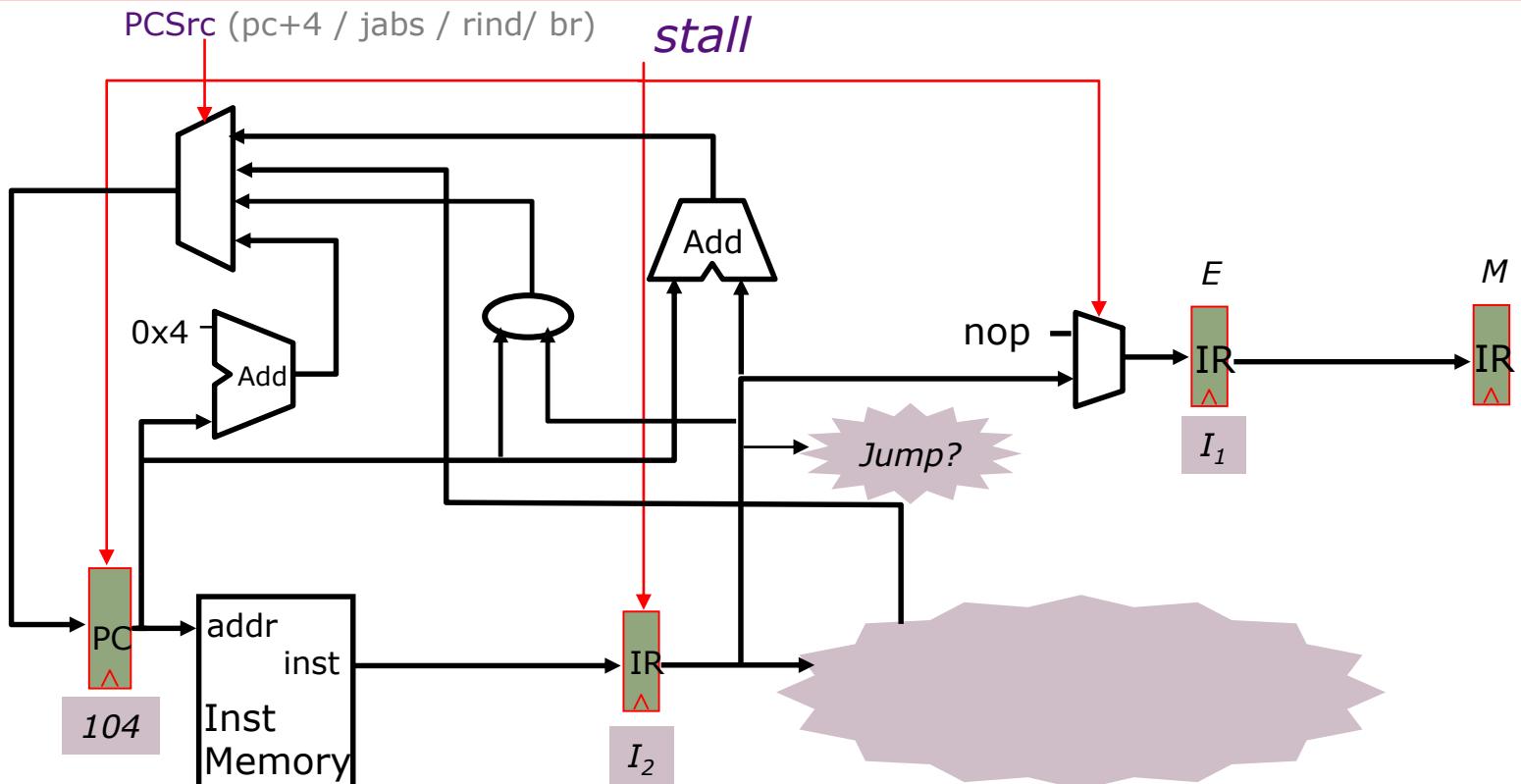


I_1	096	ADD	
I_2	100	J	200
I_3	104	ADD	<i>kill</i>
I_4	304	ADD	

What happens on mis-speculation,
i.e., when next instruction is not PC+4?

How?

Pipelining Jumps

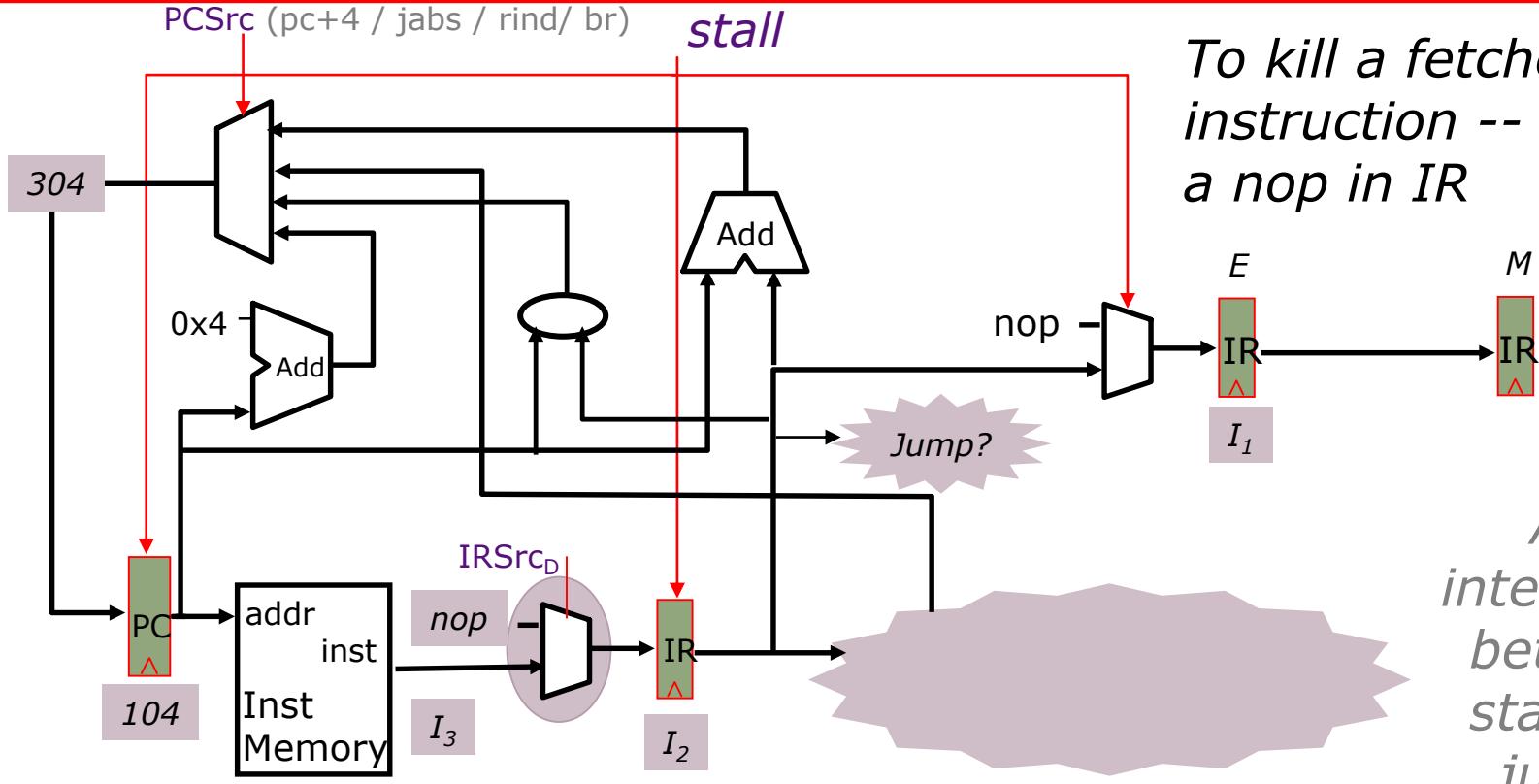

To kill a fetched instruction -- Insert a nop in IR

Any interaction between stall and jump?

I_1	096	ADD	
I_2	100	J	200
I_3	104	ADD	<i>kill</i>
I_4	304	ADD	

$IRSrc_D = \begin{cases} \text{Case opcode}_D \\ J, JAL \\ \dots \end{cases} \Rightarrow \begin{cases} \text{nop} \\ \text{IM} \end{cases}$


Jump Pipeline Diagrams

	time								
	t0	t1	t2	t3	t4	t5	t6	t7
(I ₁) 096: ADD	IF ₁	ID ₁	EX ₁	MA ₁	WB ₁				
(I ₂) 100: J 200		IF ₂	ID ₂	EX ₂	MA ₂	WB ₂			
(I ₃) 104: ADD		IF ₃	nop	nop	nop	nop			
(I ₄) 304: ADD			IF ₄	ID ₄	EX ₄	MA ₄	WB ₄		

Resource Usage	time								
	t0	t1	t2	t3	t4	t5	t6	t7	
	IF	I ₁	I ₂	I ₃	I ₄	I ₅			
	ID		I ₁	I ₂	nop	I ₄	I ₅		
	EX			I ₁	I ₂	nop	I ₄	I ₅	
	MA				I ₁	I ₂	nop	I ₄	I ₅
	WB					I ₁	I ₂	nop	I ₄

nop \Rightarrow *pipeline bubble*


Pipelining Conditional Branches

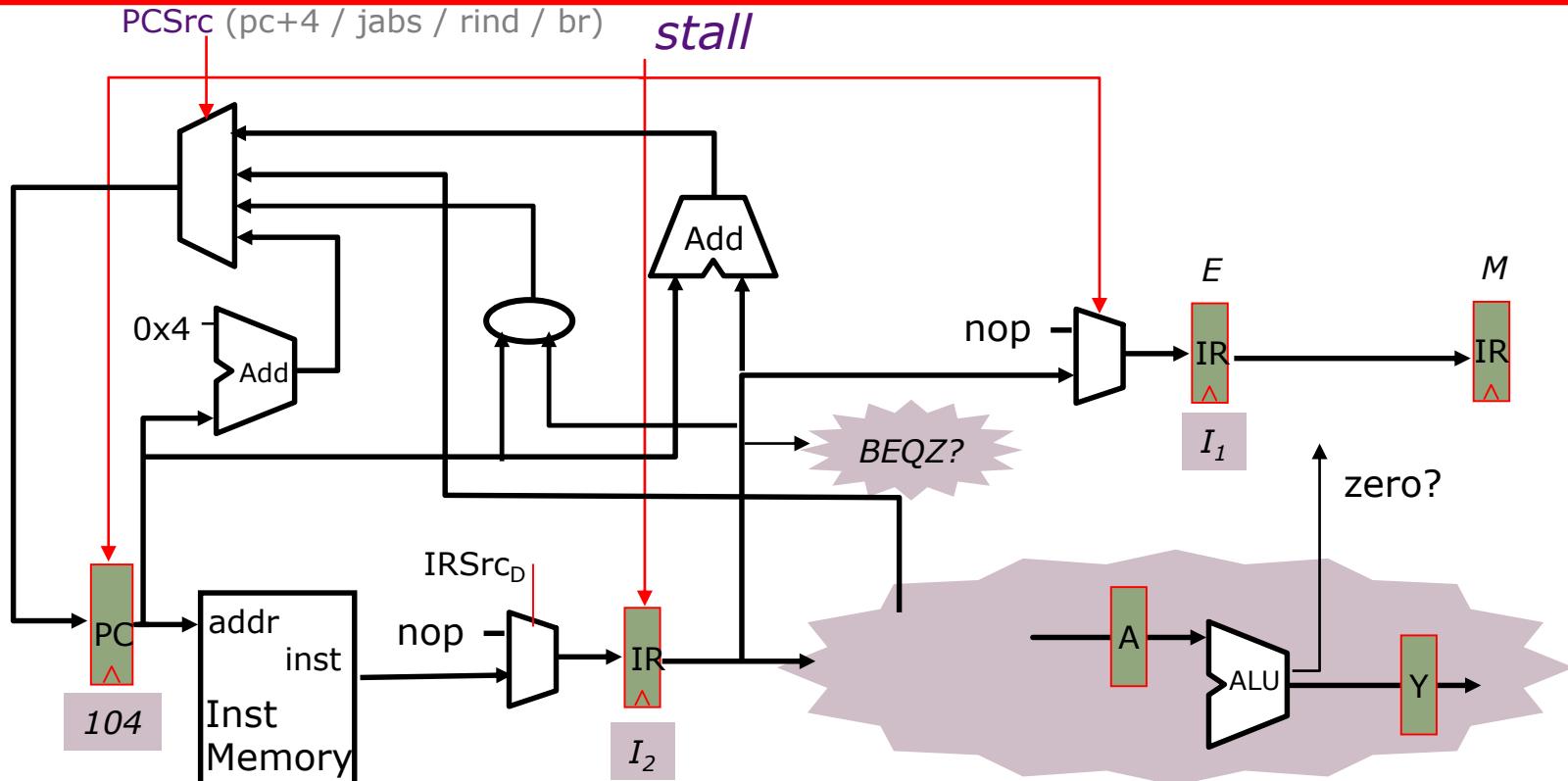

I_1	096	ADD
I_2	100	BEQZ r1 200
I_3	104	ADD
I_4	304	ADD

Branch condition is not known until the execute stage
what action should be taken in the decode stage?

Pipelining Conditional Branches

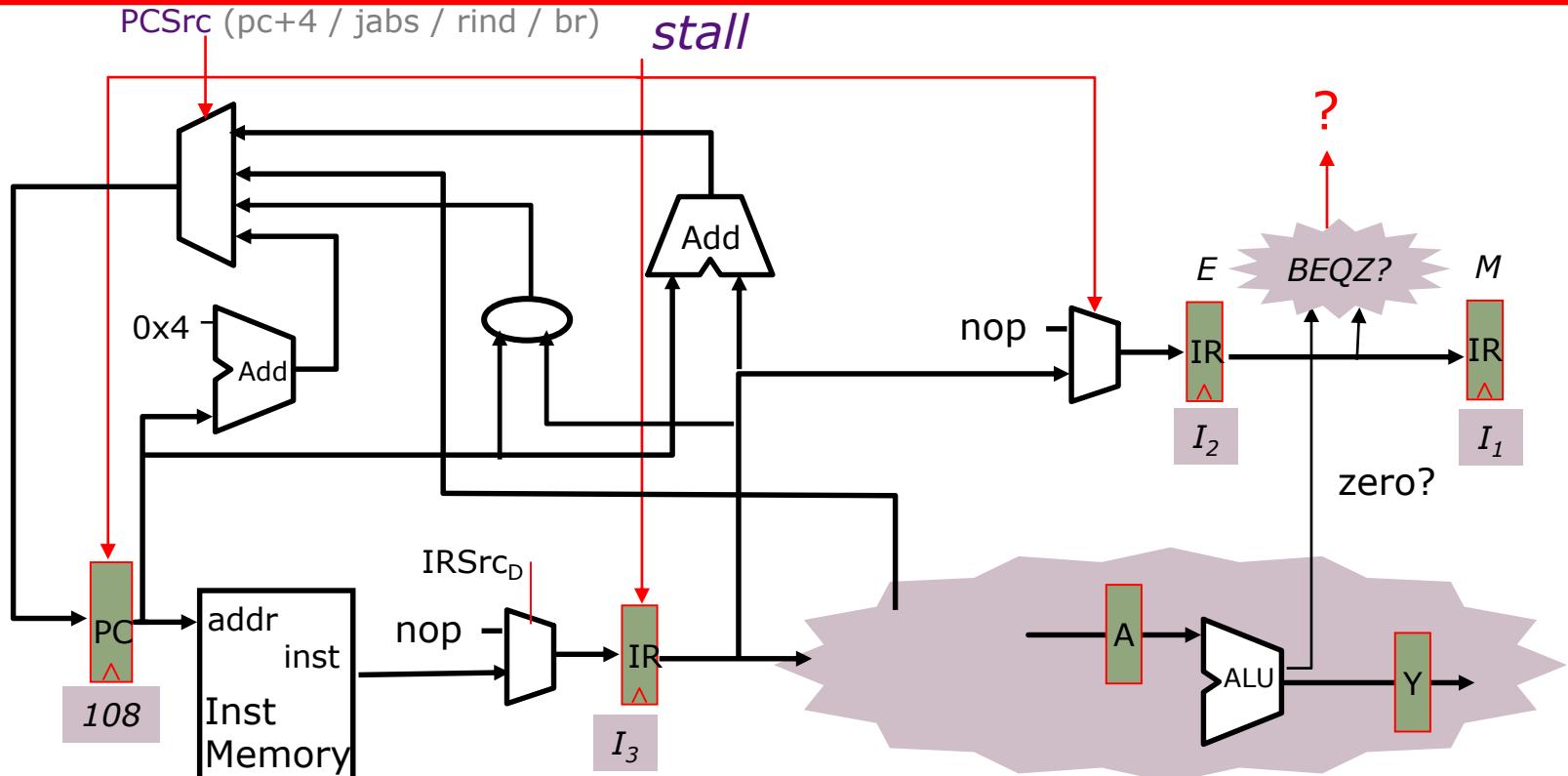


If the branch is taken

- kill the two following instructions
 - the instruction at the decode stage is not valid
- \Rightarrow *stall signal is not valid*

I ₁	096	ADD
I ₂	100	BEQZ r1 200
I ₃	104	ADD
I ₄	304	ADD

Pipelining Conditional Branches

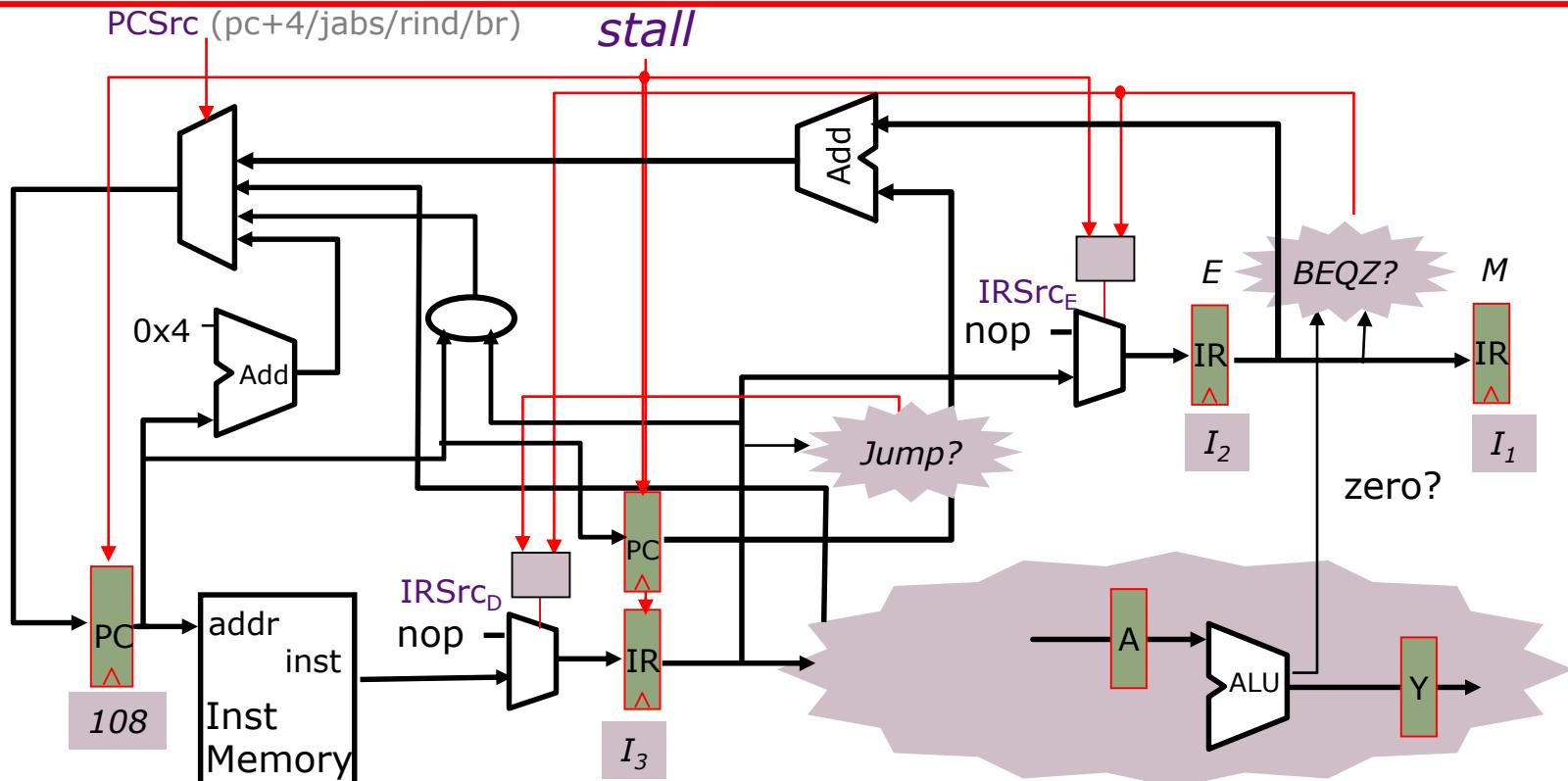

If the branch is taken

- kill the two following instructions
 - the instruction at the decode stage is not valid
- \Rightarrow **stall signal is not valid**

I_1	096	ADD
I_2	100	BEQZ r1 200
I_3	104	ADD
I_4	304	ADD

New Stall Signal

```
stall = ( ((rsD==wsE)·weE + (rsD==wsM)·weM + (rsD==wsW)·weW)·re1D
          + ((rtD==wsE)·weE + (rtD==wsM)·weM + (rtD==wsW)·weW)·re2D
      ) · !((opcodeE==BEQZ)·z + (opcodeE==BNEZ)·!z)
```

Don't stall if the branch is taken. Why?

Instruction at the decode stage is invalid

Control Equations for PC and IR Muxes

$\text{IRSrc}_D = \text{Case opcode}_E$

$\text{BEQZ}\cdot z, \text{BNEZ}\cdot !z \Rightarrow \text{nop}$

...

\Rightarrow

Case opcode_D

$J, \text{JAL}, \text{JR}, \text{JALR} \Rightarrow \text{nop}$

...

$\Rightarrow \text{IM}$

Give priority to the older instruction, i.e., execute stage instruction over decode stage instruction

$\text{IRSrc}_E = \text{Case opcode}_E$

$\text{BEQZ}\cdot z, \text{BNEZ}\cdot !z \Rightarrow \text{nop}$

...

$\Rightarrow \text{stall}\cdot \text{nop} + \text{!stall}\cdot \text{IR}_D$

$\text{PCSsrc} = \text{Case opcode}_E$

$\text{BEQZ}\cdot z, \text{BNEZ}\cdot !z \Rightarrow \text{br}$

...

\Rightarrow

Case opcode_D

$J, \text{JAL} \Rightarrow \text{jabs}$

$\text{JR}, \text{JALR} \Rightarrow \text{rind}$

... $\Rightarrow \text{pc+4}$

pc+4 is a speculative guess

$\text{nop} \Rightarrow \text{Kill}$

$\text{br/jabs/rind} \Rightarrow \text{Restart}$

$\text{pc+4} \Rightarrow \text{Speculate}$

Branch Pipeline Diagrams (resolved in execute stage)


	time									
	t0	t1	t2	t3	t4	t5	t6	t7	...	
(I ₁) 096: ADD	IF ₁	ID ₁	EX ₁	MA ₁	WB ₁					
(I ₂) 100: BEQZ 200		IF ₂	ID ₂	EX ₂	MA ₂	WB ₂				
(I ₃) 104: ADD			IF ₃	ID ₃	nop	nop	nop			
(I ₄) 108:				IF ₄	nop	nop	nop	nop		
(I ₅) 304: ADD					IF ₅	ID ₅	EX ₅	MA ₅	WB ₅	

Resource Usage	time									
	t0	t1	t2	t3	t4	t5	t6	t7	...	
	IF	I ₁	I ₂	I ₃	I ₄	I ₅				
	ID		I ₁	I ₂	I ₃	nop	I ₅			
	EX			I ₁	I ₂	nop	nop	I ₅		
	MA				I ₁	I ₂	nop	nop	I ₅	
	WB					I ₁	I ₂	nop	nop	I ₅

nop \Rightarrow *pipeline bubble*

Reducing Branch Penalty (resolve in decode stage)

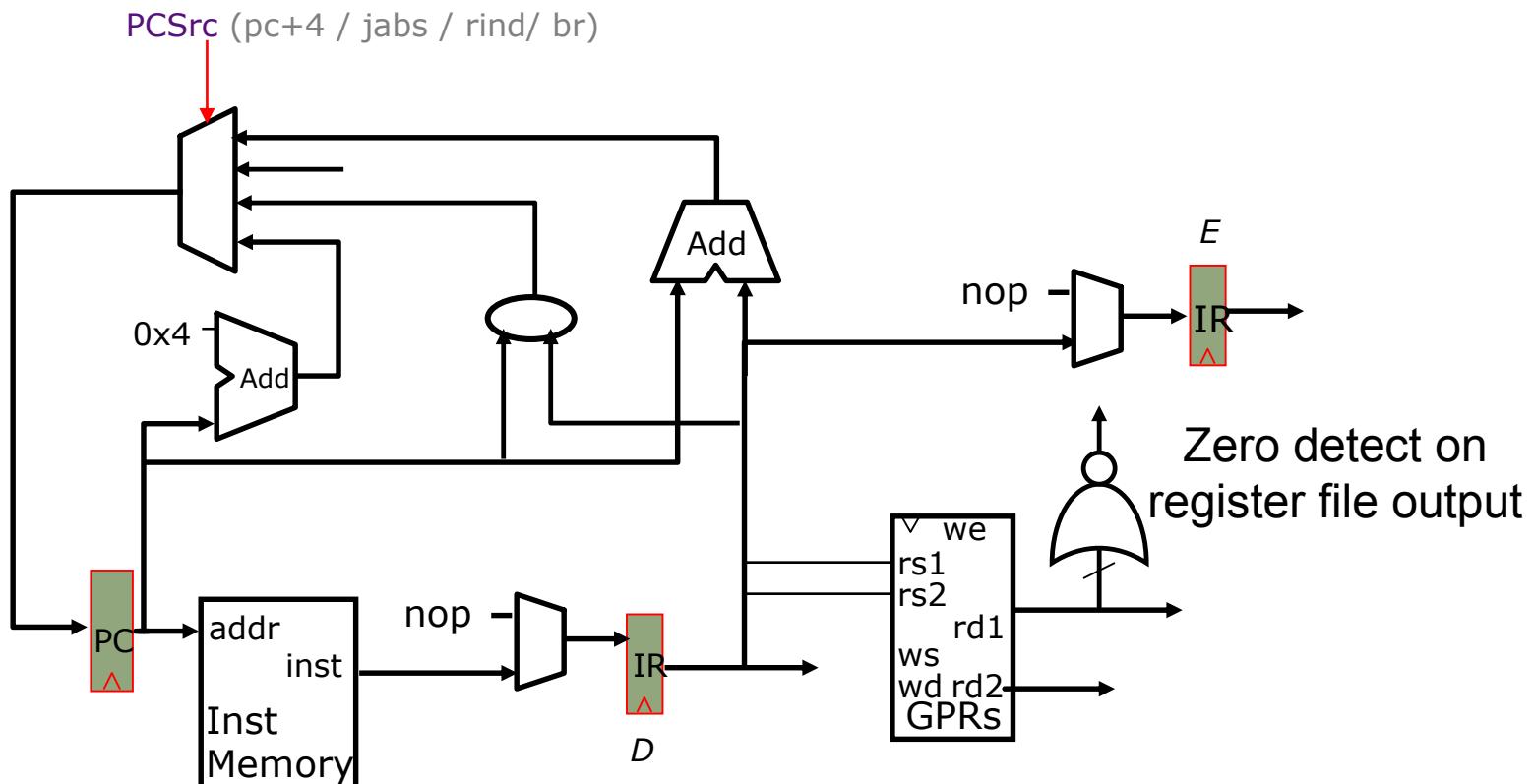- One pipeline bubble can be removed if an extra comparator is used in the Decode stage



Pipeline diagram now same as for jumps

Branch Delay Slots (expose control hazard to software)

- Change the ISA semantics so that the instruction that follows a jump or branch is always executed
 - gives compiler the flexibility to put in a useful instruction where normally a pipeline bubble would have resulted.

I ₁	096	ADD	
I ₂	100	BEQZ r1 200	<i>Delay slot instruction</i>
I ₃	104	ADD	<i>executed regardless of branch outcome</i>
I ₄	304	ADD	

- Other techniques include branch prediction, which can dramatically reduce the branch penalty... *to come later*

Why an instruction may not be dispatched every cycle (CPI>1)

- Full bypassing may be too expensive to implement
 - Typically all frequently used paths are provided
 - Some infrequently used bypass paths may increase cycle time and counteract the benefit of reducing CPI
- Loads have two cycle latency
 - Instruction after load cannot use load result
 - MIPS-I ISA defined *load delay slots*, a software-visible pipeline hazard (compiler schedules independent instruction or inserts NOP to avoid hazard). Removed in MIPS-II.
- Conditional branches may cause bubbles
 - Kill following instruction(s) if no delay slots

Machines with software-visible delay slots may execute significant number of NOP instructions inserted by the compiler.

Next lecture: Superscalar & Scoreboarded Pipelines